

ECE 203


Circuits I

Solving circuit problems

Lecture 3-3

Circuits with Series/Parallel Resistors

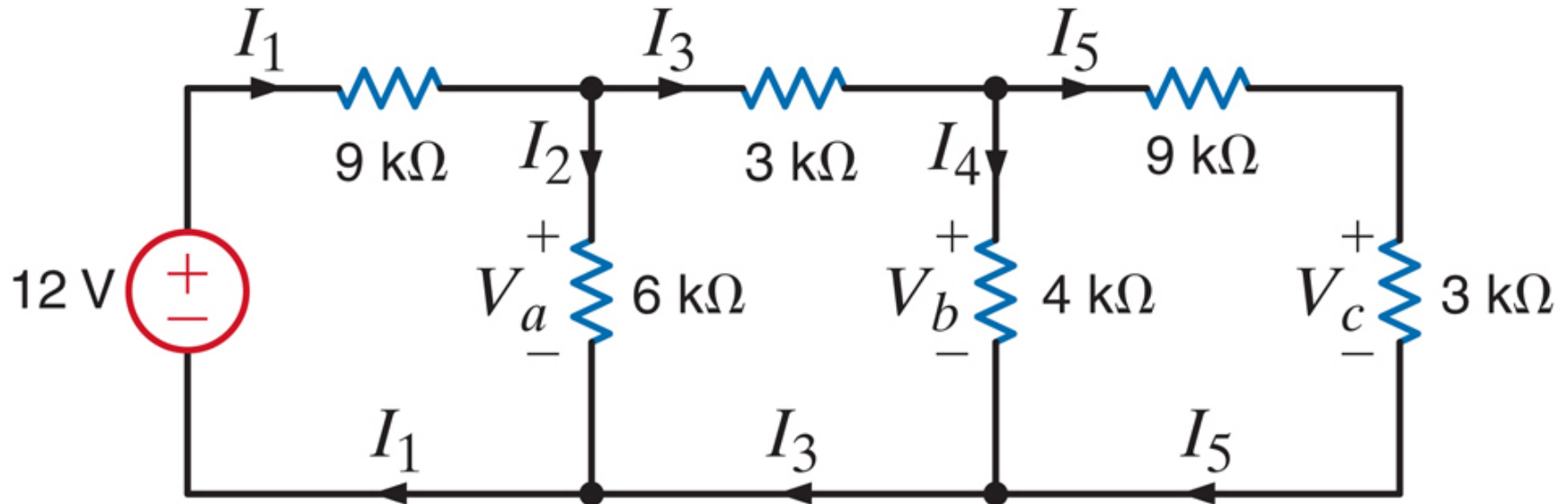Find all currents (I_1 thru I_5) and all voltages (V_a thru V_c) in this circuit:




We now have enough knowledge to solve a wide range of circuit problems.

This lecture will be very short- I'll introduce another technique, then I will do a series of examples.

Ultimate goal is to be able to solve for the voltage and current anywhere in a circuit.

Solution #1

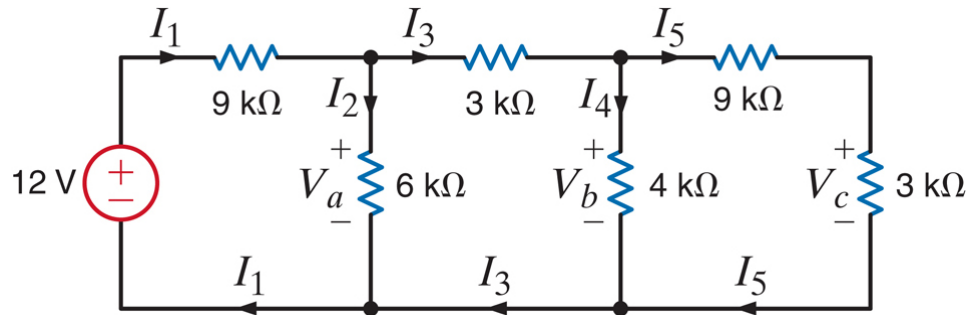

$$V_b = 4kI_4$$

$$I_4 = \frac{\frac{3}{2}}{4k}$$


$$= \frac{3}{8} \text{ mA}$$

$$I_5 = \frac{4k}{4k + (9k + 3k)} I_3$$

$$= \frac{1}{8} \text{ mA}$$

$$V_c = I_5(3k)$$

$$= \frac{3}{8} \text{ V}$$

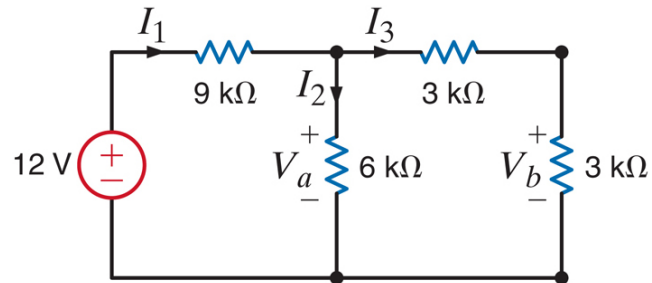

$$I_2 = \frac{3}{6k}$$

$$= \frac{1}{2} \text{ mA}$$


$$I_1 = I_2 + I_3$$

$$1 \times 10^{-3} = \frac{1}{2} \times 10^{-3} + I_3$$

$$I_3 = \frac{1}{2} \text{ mA}$$

$$V_b = 3kI_3$$

$$= \frac{3}{2} \text{ V}$$

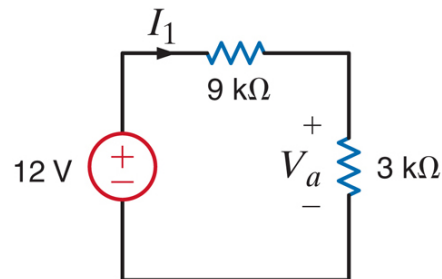

$$V_a = I_1(3k)$$

$$= 3 \text{ V}$$

$$I_1(9k + 3k) = 12$$

$$I_1 = 1 \text{ mA}$$