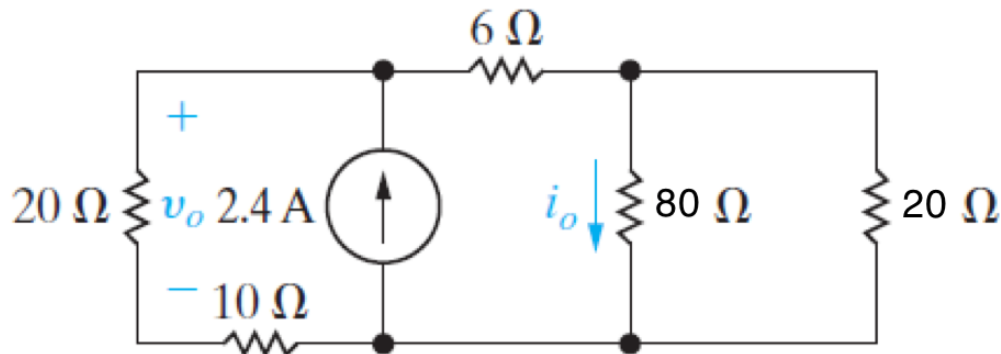


**Question 1** [10]


For the current-divider circuit shown here calculate:



- (i)  $i_o$  and  $v_o$ ,
- (ii) the power dissipated in the 6 Ω resistor,
- (iii) the power delivered by the current source.

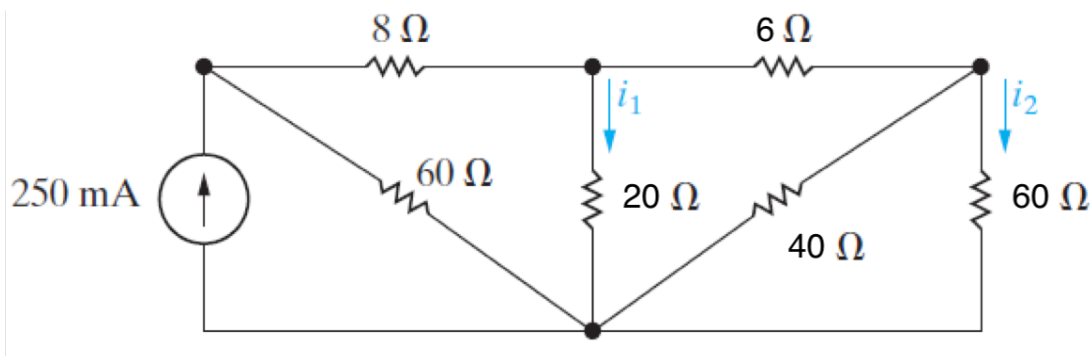
**Question 2** [10]

For the circuit shown, calculate  $i_1$  and  $i_2$  using current-division.




**Question 3 [10]**


Use a  $\Delta$ -to- $Y$  transformation to find the voltages  $v_1$  and  $v_2$  in the circuit below.

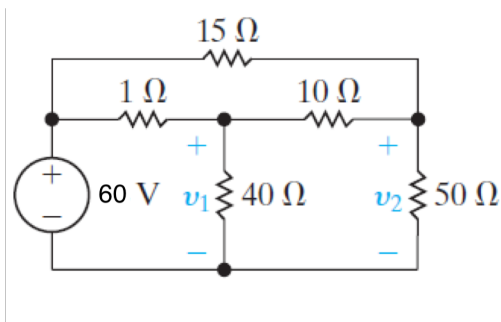**Question 4 [10]**

Use a  $Y$ -to- $\Delta$  transformation to find the equivalent resistance  $R_{ab}$ .

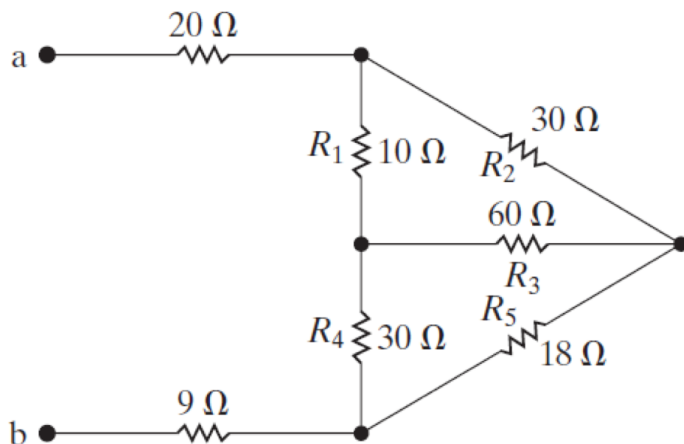**Question 5 [10]**

For the circuit circuit shown:

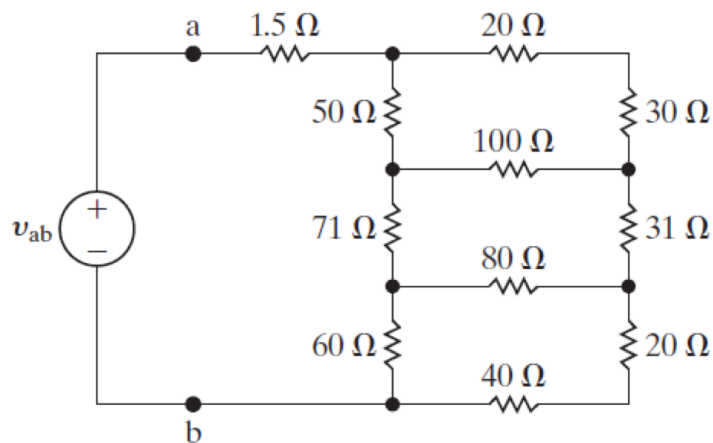

(a) Find the resistance seen by the ideal voltage source.

(b) If  $v_{ab} = 250$  V, how much power is dissipated in the  $31 \Omega$  resistor?