

**ECE 203**


**Circuits I**

## **2<sup>nd</sup> Order Transient Circuits**

**Lecture 11-2**

# Example 1

Find  $v(t)$  in this circuit:

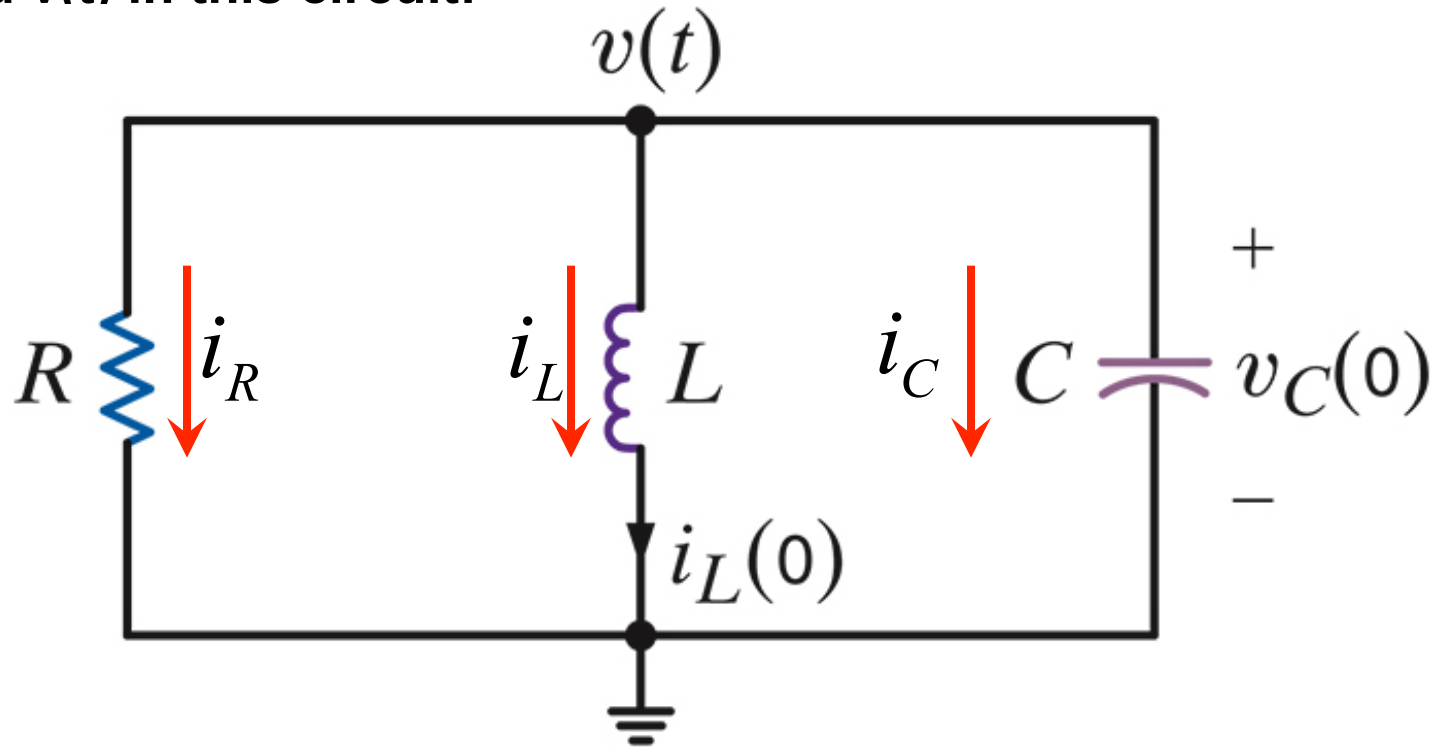

Initial Conditions:

$$R = 2\Omega, L = 5H, C = \frac{1}{5}F$$

$$i_L(0) = -1A, v_C(0) = 4V$$

# Example 1: Detailed Analysis

$$i_R + i_L + i_C = 0$$

$$\frac{v}{R} + \frac{1}{L} \int_0^t v(x) dx + i_L(0) + C \frac{dv}{dt} = 0$$

STEP 1  
MODEL

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

CHARACTERISTIC EQUATION

$$s^2 + 2.5s + 1 = 0$$

$$\Rightarrow \omega_o = 1; \zeta = 1.25$$

STEP 2


$$s = \frac{-2.5 \pm \sqrt{(2.5)^2 - 4}}{2} = \frac{-2.5 \pm 1.5}{2}$$

STEP 3  
ROOTS

$$v(t) = K_1 e^{-2t} + K_2 e^{-0.5t}$$

STEP 4  
FORM OF  
SOLUTION

STEP 5: FIND CONSTANTS

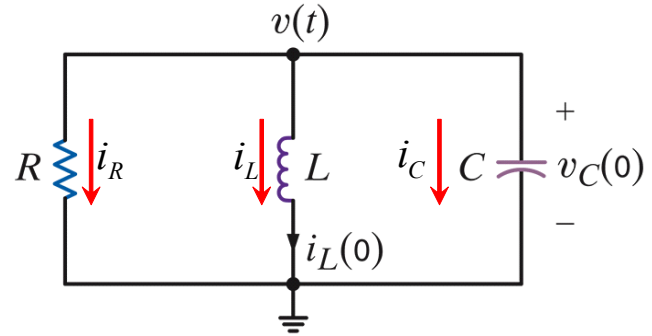

To determine the constants we need

$$v(0+); \frac{dv}{dt}(0+)$$

IF NOT GIVEN FIND  $v_C(0), i_L(0)$

$$v(0+) = v_C(0+) = v_C(0) = 4V$$

KCL AT  $t = 0+$

$$\frac{v_C(0+)}{R} + i_L(0+) + C \frac{dv}{dt}(0+) = 0$$


$$\frac{dv}{dt}(0+) = -\frac{4}{2(1/5)} - \frac{(-1)}{(1/5)} = -5$$

$$\left. \begin{array}{l} K_1 + K_2 = 4 \\ -2K_1 - 0.5K_2 = -5 \end{array} \right\} \Rightarrow K_1 = 2; K_2 = 2$$

$$v(t) = 2e^{-2t} + 2e^{-0.5t}; t > 0$$


ANALYZE  
CIRCUIT AT  
 $t=0+$

# Example 1: Waveform

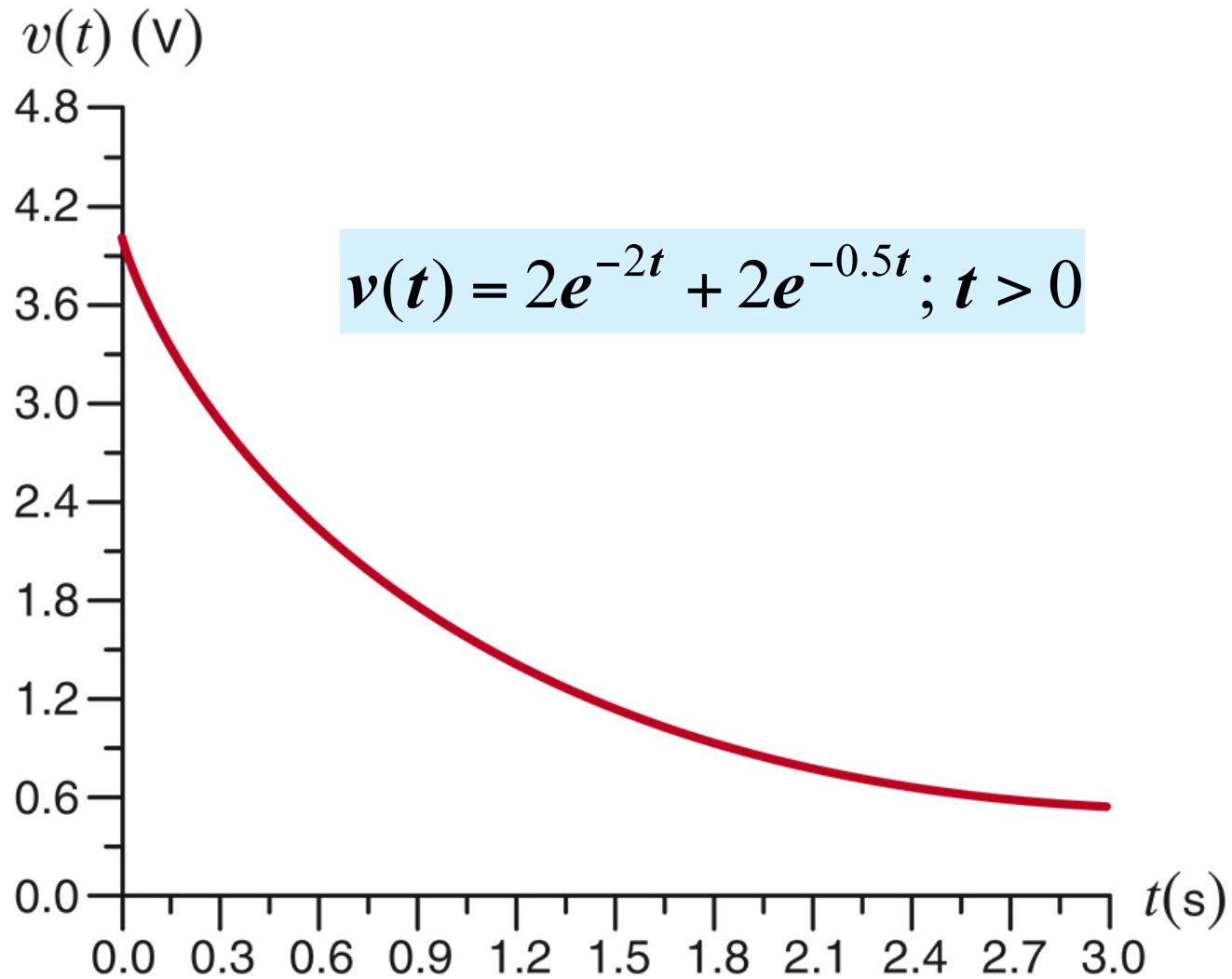

## Example 2

Find  $v_C(t)$  in this circuit:

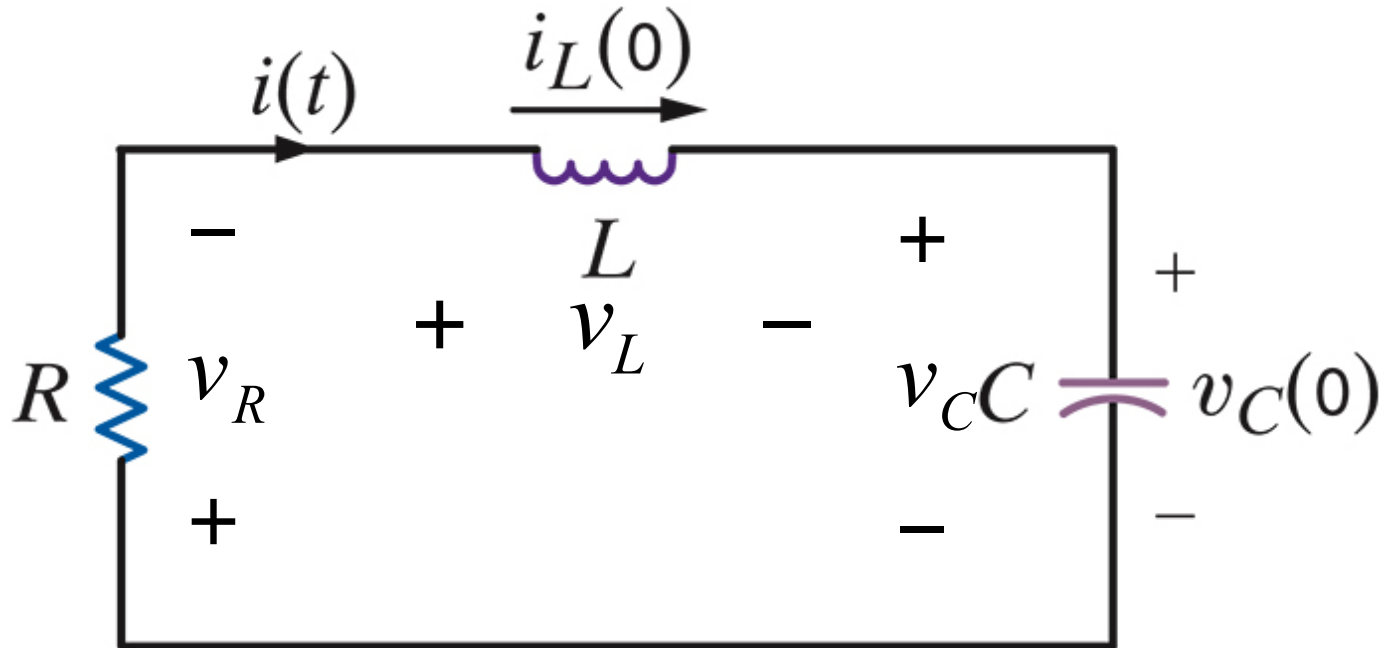

Initial Conditions:

$$R = 6\Omega, L = 1H, C = 0.04F$$


$$i_L(0) = 4A; v_C(0) = -4V$$

# Example 2: Detailed Analysis

$$v_R + v_L + v_C = 0$$

$$Ri(t) + L \frac{di}{dt}(t) + \frac{1}{C} \int_0^t i(x) dx + v_C(0) = 0$$

**STEP 1  
MODEL**

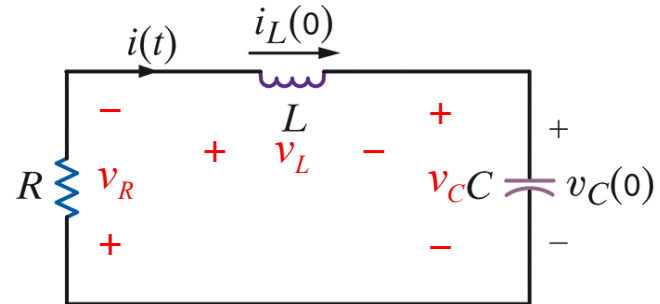

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt}(t) + \frac{1}{LC} i(t) = 0$$

$$\frac{d^2 i}{dt^2} + 6 \frac{di}{dt}(t) + 25i(t) = 0$$

$$\text{Ch. Eq.: } s^2 + 6s + 25 = 0$$

**STEP 2**

$$\omega_o^2 = 25 \Rightarrow \omega_o = 5$$

$$2\zeta\omega_o = 6 \Rightarrow \zeta = 0.6$$

**STEP 3  
ROOTS**

$$\text{roots: } s = \frac{-6 \pm \sqrt{36 - 100}}{2} = -3 \pm j4$$

$$i(t) = e^{-3t} (A_1 \cos 4t + A_2 \sin 4t)$$

**STEP 4  
FORM OF  
SOLUTION**

**STEP 5: FIND CONSTANTS**

$$i(0) = i_L(0) = 4A \Rightarrow A_1 = 4$$

$$\text{TO COMPUTE } \frac{di}{dt}(0+) \quad v_L(t) = L \frac{di}{dt}(t)$$

$$L \frac{di}{dt}(0) = -Ri(0) - v_C(0) \\ \Rightarrow \frac{di}{dt}(0+) = -20$$

**ANALYZE  
CIRCUIT AT  
t=0+**

$$\frac{di}{dt}(t) = -3i(t) + e^{-3t} (-4A_1 \sin 4t + 4A_2 \cos 4t)$$


$$@t = 0: -20 = -3 \times (4) + 4A_2 \Rightarrow A_2 = -2$$

$$i(t) = e^{-3t} (4 \cos 4t - 2 \sin 4t) [A]; t > 0$$

$$v_C(t) = -Ri(t) - L \frac{di}{dt}(t) = v_C(0) + \frac{1}{C} \int_0^t i(x) dx$$


$$v_C(t) = e^{-3t} (-4 \cos 4t + 22 \sin 4t) [V]; t > 0$$

## Example 2: Waveform

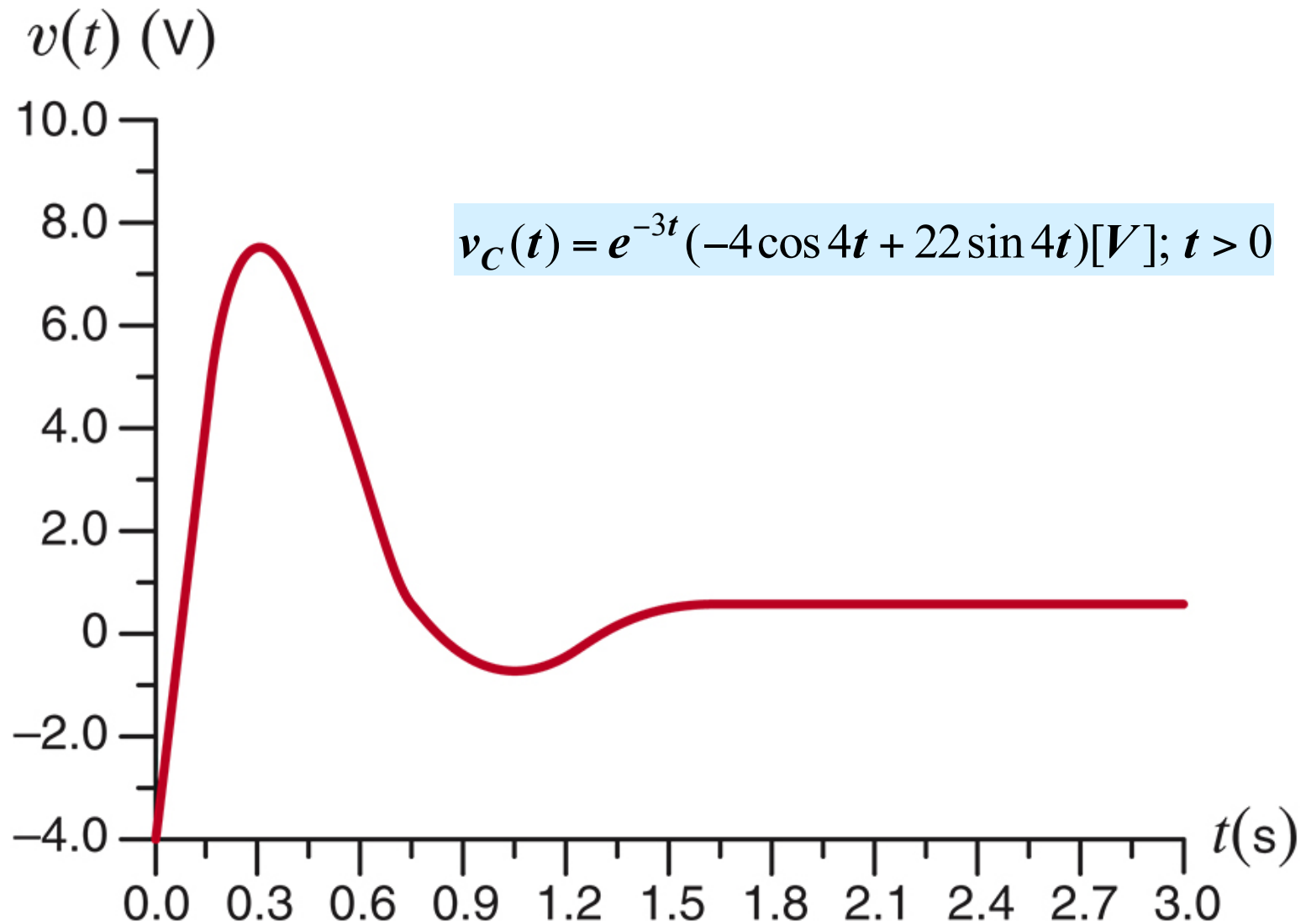

## Example 3

Find  $v(t)$  in this circuit:

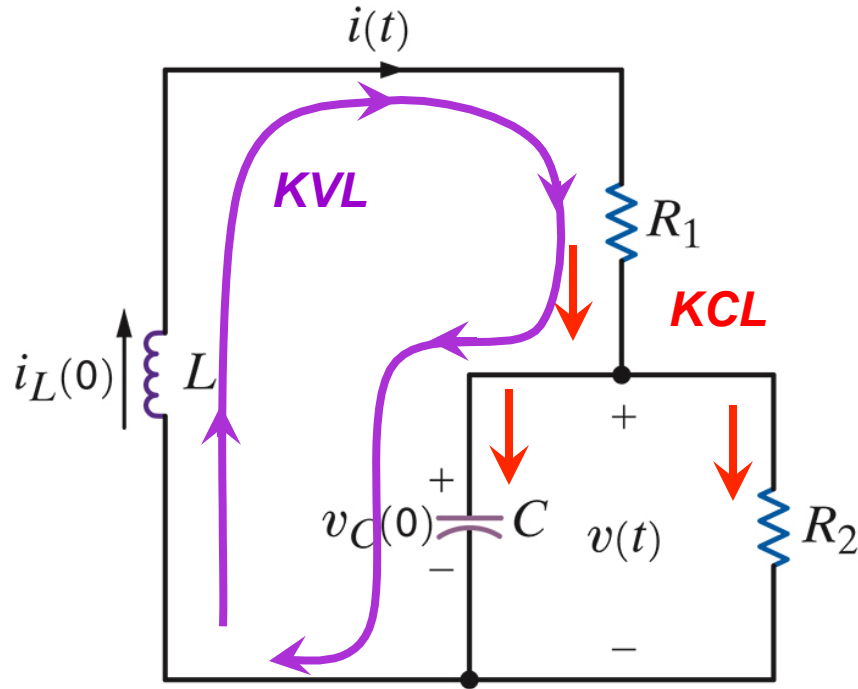

Initial Conditions:

$$R_1 = 10\Omega, R_2 = 8\Omega, C = 1F, L = 2H$$

$$v_C(0) = 1V, i_L(0) = 0.5A$$



# Example 3: Detailed Analysis

$$L \frac{di}{dt}(t) + R_1 i(t) + v(t) = 0 \quad i(t) = \frac{v(t)}{R_2} + C \frac{dv}{dt}(t)$$

$$L \left( \frac{1}{R_2} \frac{dv}{dt}(t) + C \frac{d^2 v}{dt^2} \right) + R_1 \left( \frac{v(t)}{R_2} + C \frac{dv}{dt}(t) \right) + v(t) = 0$$

$$\frac{d^2 v}{dt^2}(t) + \left( \frac{1}{R_2 C} + \frac{R_1}{L} \right) \frac{dv}{dt}(t) + \frac{R_1 + R_2}{R_2 L C} v(t) = 0$$

$$\frac{d^2 v}{dt^2}(t) + 6 \frac{dv}{dt}(t) + 9v(t) = 0$$

**STEP 1  
MODEL**

$$\text{Ch. Eq.: } s^2 + 6s + 9 = 0$$

**STEP 2**

$$\omega_o = 3, 2\zeta\omega_o = 6 \Rightarrow \zeta = 1$$


$$\text{Ch. Eq.: } s^2 + 6s + 9 = 0 = (s + 3)^2$$

**STEP 3  
ROOTS**

$$v(t) = e^{-3t} (B_1 + B_2 t)$$

**STEP 4  
FORM OF  
SOLUTION**

**STEP 5: FIND CONSTANTS**

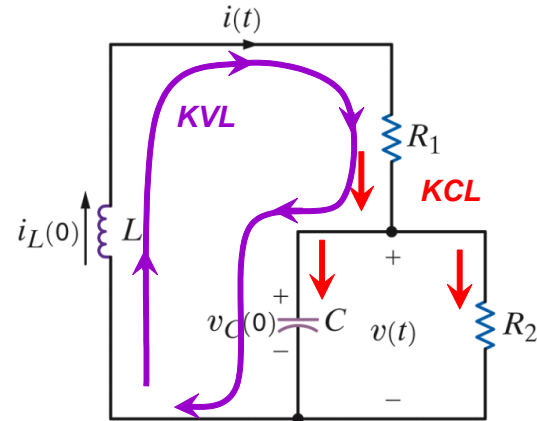

$$v(0+) = v_C(0+) = 1V$$

**ANALYZE  
CIRCUIT AT  
t=0+**

KCL AT  $t = 0 +$


$$i(0) = i_L(0) = \frac{v(0)}{R_2} + C \frac{dv}{dt}(0) \Rightarrow \frac{dv}{dt}(0) = 3$$

$$v(0) = 1 = B_1$$

$$\frac{dv}{dt}(0) = -3v(0) + B_2 = 3 \Rightarrow B_2 = 6$$

$$v(t) = e^{-3t} (1 + 6t); \quad t > 0$$



## Example 3: Waveform

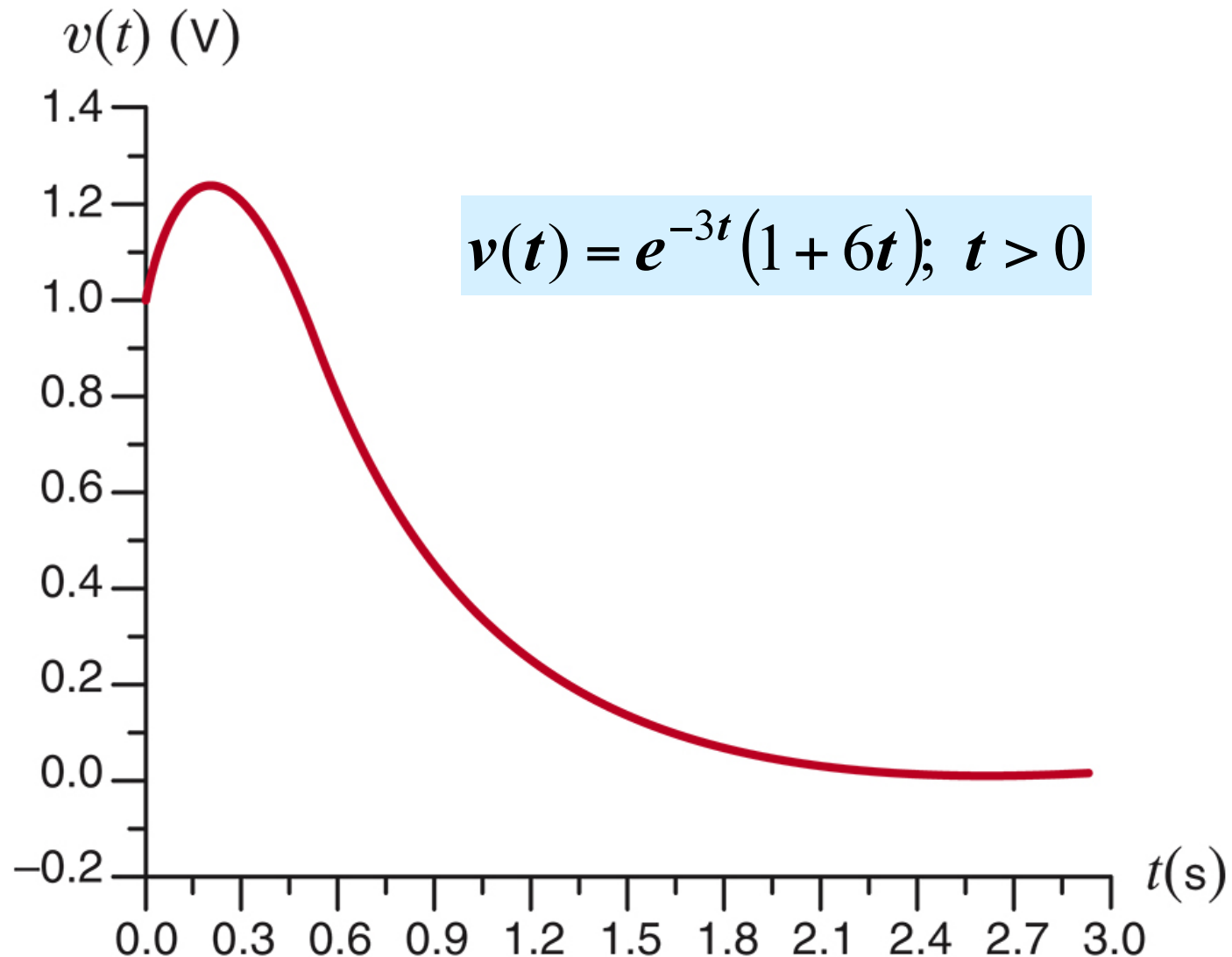
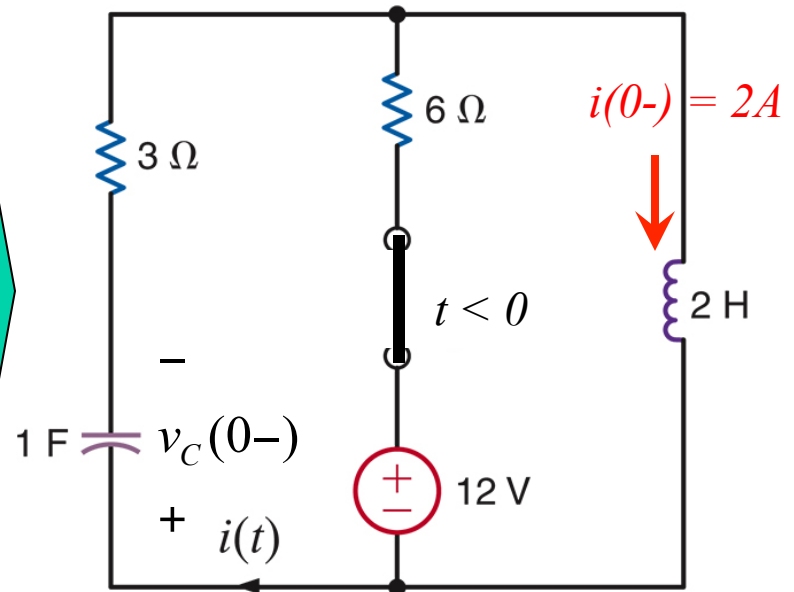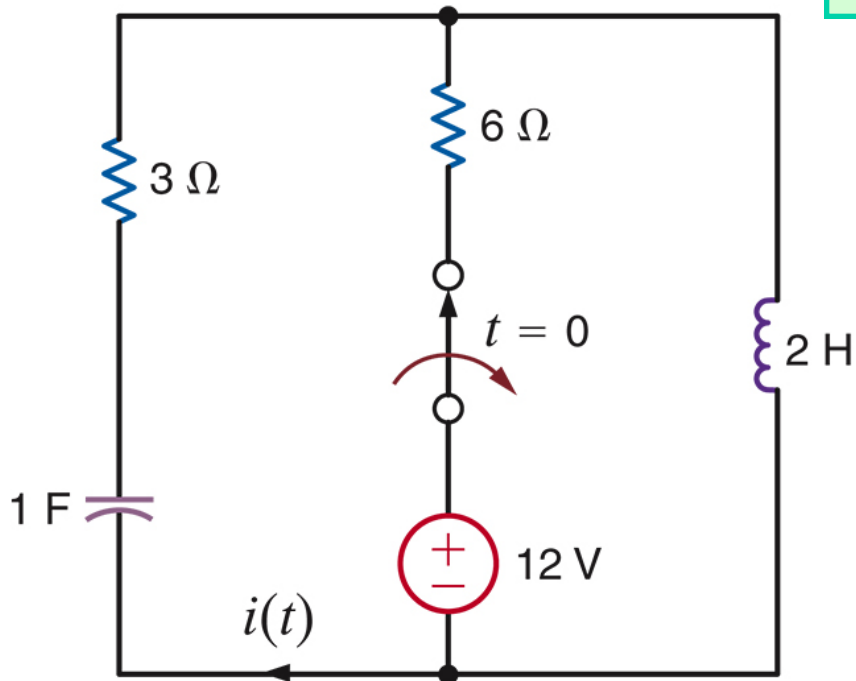
# Example 4

Find  $i(t)$  in this circuit:

To find initial conditions use steady state analysis for  $t < 0$



**Initial Conditions:**

$$v_C(0) = 0\text{ V} , \quad i_L(0) = 2\text{ A}$$

# Example 4: Detailed Analysis

Once the switch opens the circuit is RLC series

$$3i(t) + 2\frac{di}{dt}(t) + v_C(0) + \int_0^t i(x)dx = 0$$

STEP 1  
MODEL

$$\frac{d^2i}{dt^2}(t) + \frac{3}{2}\frac{di}{dt}(t) + \frac{1}{2}i(t) = 0$$

STEP 2

$$\text{Ch.Eq.: } s^2 + 1.5s + 0.5 = 0$$

$$\text{roots: } s = -1, -0.5$$

STEP 3  
ROOTS


$$i(t) = K_1 e^{-t} + K_2 e^{-\frac{t}{2}}; t > 0$$

STEP 4  
FORM OF  
SOLUTION

STEP 5: FIND CONSTANTS

$$i(0+) = 2A$$

$$v_C(0) = 0V$$

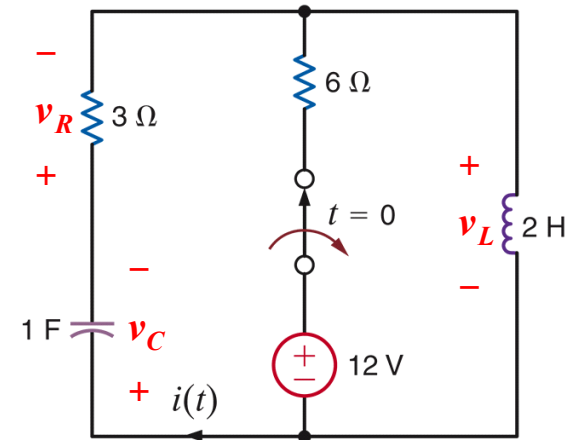

ANALYZE  
CIRCUIT AT  
 $t=0+$

$$v_C = C \frac{di}{dt} \Rightarrow \frac{di}{dt}(0+) = 0$$

$$2 = K_1 + K_2$$

$$0 = -K_1 - \frac{1}{2}K_2$$

$$i(t) = -2e^{-t} + 4e^{-\frac{t}{2}}; t > 0$$