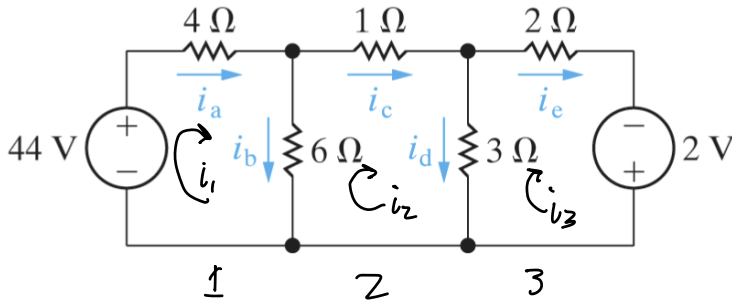


4.32 Solve Problem 4.12 using the mesh-current method.

Figure P4.12



Using Matrix to solve

$$\begin{bmatrix} 10 & -6 & 0 & | & -44 \\ -6 & 10 & -3 & | & 0 \\ 0 & -3 & 5 & | & -2 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = -8 \\ i_2 = -6 \\ i_3 = -4 \end{matrix}$$

a) $\begin{matrix} i_a = 8A & i_b = i_a - i_c = 2A \\ i_c = 6A & i_d = i_c - i_e = 2A \\ i_e = 4A \end{matrix}$

for loop 1:

$$+44V + 4i_1 + 6(i_1 - i_2) = 0$$

$$10i_1 - 6i_2 + 44 = 0$$

loop 2:

$$1(i_2) + 6(i_2 - i_1) + 3(i_2 - i_3) = 0$$

$$-6i_1 + 10i_2 - 3i_3 = 0$$

loop 3:

$$2V + 2(i_3) + 3(i_3 - i_2) = 0$$


$$-3i_2 + 5i_3 = -2$$

$$P_1 = -44(8) = -352W$$

$$P_3 = -2(4) = -8W$$

b) The total power is $-360W$

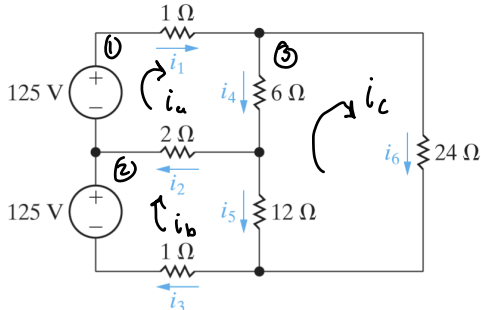4.33 Solve Problem 4.14 using the mesh-current method.



Solving w/matrix:

$$\begin{bmatrix} 9 & -2 & -6 & | & 125 \\ -2 & 15 & -12 & | & 125 \\ -6 & -12 & 42 & | & 0 \end{bmatrix} \Rightarrow \begin{matrix} i_a = 23.76A \\ i_b = 18.43A \\ i_c = 8.66A \end{matrix}$$

$$\begin{matrix} i_1 = 23.76A & i_2 = i_a - i_b = 5.33A \\ i_3 = 18.43A & i_4 = i_a - i_c = 15.1A \\ i_5 = 8.66A & i_6 = i_b - i_c = 9.77A \end{matrix}$$

loop 1: $1(i_a) + 6(i_a - i_b) + 2(i_a - i_b) - 125 = 0$

$$9i_a - 2i_b - 6i_c = 125$$


loop 2: $1(i_b) + 12(i_b - i_c) + 2(i_b - i_a) - 125 = 0$

$$-2i_a + 15i_b - 12i_c = 125$$

loop 3: $24i_c + 6(i_c - i_a) + 12(i_c - i_b) = 0$

$$-6i_a - 12i_b + 42i_c = 0$$

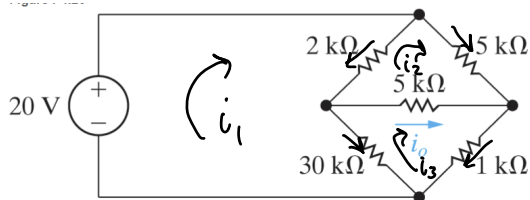4.35 Solve [Problem 4.26](#) using the mesh-current method.



Solving using matrix

$$\begin{bmatrix} 32k & -2k & -30k & 20 \\ -2k & 12k & -5k & 0 \\ -30k & -5k & 36k & 0 \end{bmatrix} \Rightarrow \begin{aligned} i_1 &= 0.0055A \\ i_2 &= 0.003A \\ i_3 &= 0.005A \end{aligned}$$

$$i_o = i_3 - i_2 = 0.005A$$

$$i_o = 2mA$$

$$\text{loop 1: } -20V + 2k(i_1 - i_2) + 30k(i_1 - i_3) = 0$$

$$32ki_1 - 2ki_2 - 30ki_3 = 20$$

$$\text{loop 2: } 2k(i_2 - i_1) + 5ki_2 + 5k(i_2 - i_3) = 0$$


$$-2ki_1 + 12ki_2 - 5ki_3 = 0$$

$$\text{loop 3: } 30k(i_3 - i_1) + 5k(i_3 - i_2) + 1ki_3 = 0$$

$$-30ki_1 - 5ki_2 + 36ki_3 = 0$$

4.36 [PSPICE MULTISIM](#)

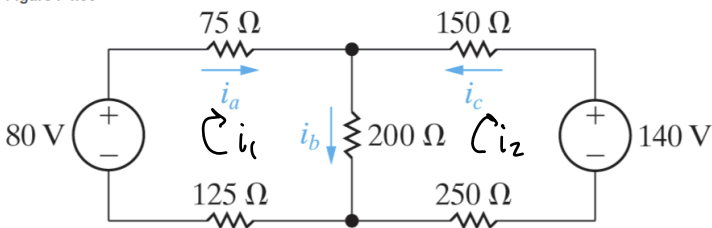- a) Use the mesh-current method to find the branch currents i_a , i_b , and i_c in the circuit in [Fig. P4.36](#).
b) Repeat (a) if the polarity of the 140 V source is reversed.



Solving @ w/ matrix

$$\begin{bmatrix} 400 & -200 & 80 \\ -200 & 600 & -140 \end{bmatrix} \Rightarrow \begin{aligned} i_1 &= 0.1A \\ i_2 &= -0.2A \end{aligned}$$

$$\text{A) } \begin{cases} i_a = 0.1A \\ i_b = (i_1 - i_2) = 0.3A \\ i_c = 0.2A \end{cases}$$

w/ reversed polarity

$$\begin{bmatrix} 400 & -200 & 80 \\ -200 & 600 & 140 \end{bmatrix} \begin{aligned} i_1 &= 0.38 \\ i_2 &= 0.36 \end{aligned}$$

$$\text{b) } \begin{cases} i_a = 0.38A \\ i_b = i_1 - i_2 = 0.02A \\ i_c = -0.36A \end{cases}$$

loop 1:

$$-80V + 75i_1 + 200(i_1 - i_2) + 125i_1 = 0$$


$$400i_1 - 200i_2 = 80$$

loop 2:

$$140V + 150i_2 + 250i_2 + 200(i_2 - i_1) = 0$$

$$-200i_1 + 600i_2 = -140$$

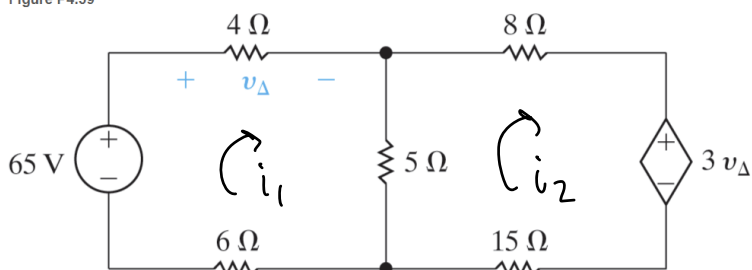4.39 PSPICE MULTISIM Use the mesh-current method to find the power dissipated in the $15\ \Omega$ resistor in the circuit in Fig. P4.39.



Solving w/ matrix

$$\begin{bmatrix} 15 & -5 & 65 \\ 7 & 28 & 0 \end{bmatrix} \begin{matrix} i_1 = 4 \\ i_2 = -1 \end{matrix}$$

$$V_{\Delta} = 4(4) = 16$$

$$P_{15} = (-1)^2(15) = 15\text{ W}$$

loop 1

$$-65 + 4i_1 + 6i_1 + 5(i_1 - i_2) = 0$$


$$15i_1 - 5i_2 = 65$$

loop 2

$$3(4i_1) + 8i_2 + 15i_2 + 5(i_2 - i_1) = 0$$

$$7i_1 + 28i_2 = 0$$

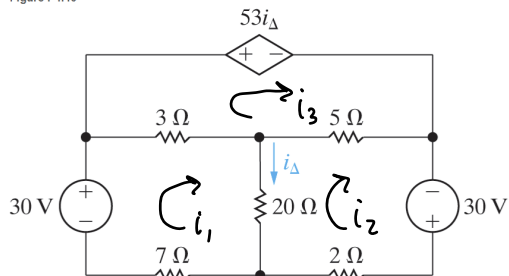4.40 PSPICE MULTISIM Use the mesh-current method to find the power developed in the dependent voltage source in the circuit in Fig. P4.40.



$$i_{\Delta} = (i_1 - i_2)$$

loop 1: $3(i_1 - i_3) + 20(i_1 - i_2) + 7i_1 = 30$

loop 2: $30i_1 - 20i_2 - 3i_3 = 30$
 $5(i_2 - i_3) + 20(i_2 - i_1) + 2i_2 = 30$

loop 3: $-20i_1 + 27i_2 - 5i_3 = 30$
 $53(i_1 - i_2) + 3(i_3 - i_1) + 5(i_3 - i_2) = 0$

$$50i_1 - 58i_2 + 8i_3 = 0$$

$$\begin{bmatrix} 30 & -20 & -3 & 30 \\ -20 & 27 & -5 & 30 \\ 50 & -58 & 8 & 0 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = 52\text{ A} \\ i_2 = 60\text{ A} \\ i_3 = 110\text{ A} \end{matrix}$$


$$P = 53(i_1 - i_2)i_3 = -46640\text{ W}$$

$$P = 46640\text{ W}$$

4.45

- a) Use the mesh-current method to find how much power the 5 A current source delivers to the circuit in Fig. P4.45.
- b) Find the total power delivered to the circuit.
- c) Check your calculations by showing that the total power developed in the circuit equals the total power dissipated.

Figure P4.45

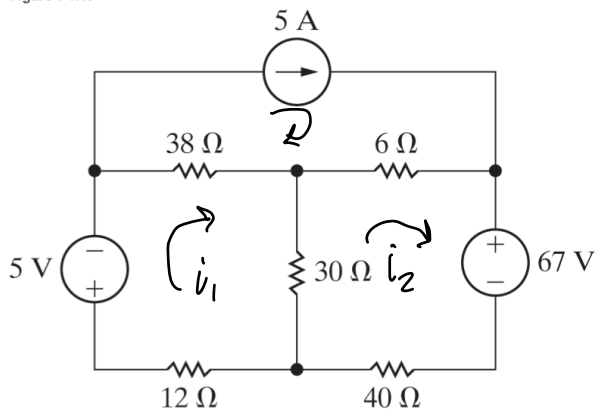

$$V = 38(2.5 - 5) + 6(0.5 - 5) = -122V$$

$$P = IV = (-122)(5) = -610W$$

$$P = 610W$$

loop 1:

$$5V + 38(i_1 - 5) + 30(i_1 - i_2) + 12i_1 = 0$$

$$80i_1 - 30i_2 = 185$$

loop 2:


$$67V + 6(i_2 - 5) + 30(i_2 - i_1) + 40i_2 = 0$$

$$-30i_1 + 76i_2 = -37$$

$$\begin{bmatrix} 80 & -30 & 185 \\ -30 & 76 & -37 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = 2.5A \\ i_2 = 0.5A \end{matrix}$$

4.53

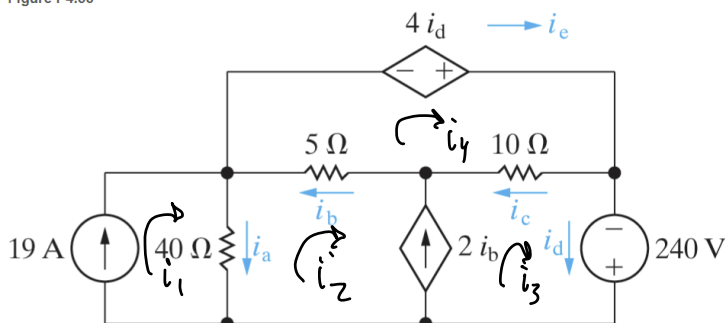- a) Find the branch currents $i_a - i_e$ for the circuit shown in Fig. P4.53.
- b) Check your answers by showing that the total power generated equals the total power dissipated.



$$\begin{bmatrix} 1 & 1 & -2 & 0 \\ 45 & 10 & -15 & 1000 \\ -5 & -14 & 15 & 10 \end{bmatrix} \Rightarrow \begin{matrix} i_2 = 26A \\ i_3 = 10A \\ i_4 = 18A \end{matrix}$$

$$i_a = i_1 - i_2 = -7A$$

$$i_b = i_4 - i_2 = -8A$$

$$i_c = i_4 - i_3 = 8A$$

$$i_d = i_3 = 10A$$

$$i_e = i_4 = 18A$$

$$i_1 = 19A$$

$$i_3 - i_2 = 2i_b \quad i_b = i_4 - i_2$$

$$i_3 - i_2 = 2i_4 - 2i_2$$

$$i_2 + i_3 - 2i_4 = 0$$

loop 2 + 3

$$40(i_2 - i_1) + 5(i_2 - i_4) + 10(i_3 - i_4) - 240 = 0$$

$$45i_2 + 10i_3 - 15i_4 = 240 + 40i_1 = 1000$$

loop 4

$$-4i_3 + 10(i_4 - i_3) + 5(i_4 - i_2) = 0$$

$$-5i_2 - 14i_3 + 15i_4 = 0$$