

Question 1 [1]

If the voltage (v) and current (i) through a circuit element are given by:

$$v(t) = e^{-t/2}$$


$$i(t) = e^{-t/2},$$

what is the total energy delivered to the element?

- (a) 0 J
- (b) 1 J
- (c) $\frac{1}{4}$ J
- (d) ∞

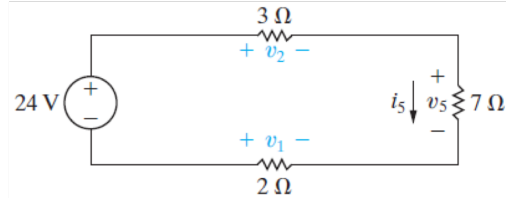Question 2 [1]


Compute the power delivered to the circuit shown below.



- (a) 48 W
- (b) 12 W
- (c) 288 W
- (d) 6 W

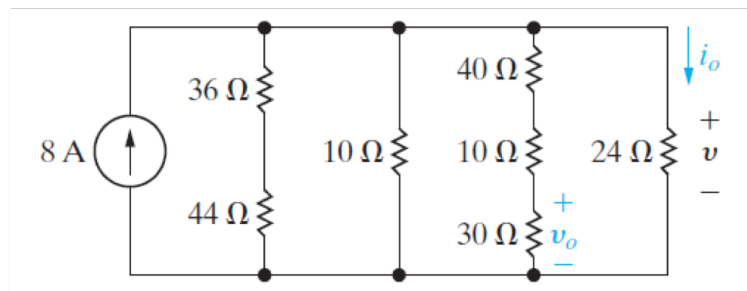Question 3 [1]


Find the equivalent resistance for the circuit shown below.



- (a) 6 Ω
- (b) 18 Ω
- (c) 24 Ω
- (d) 44 Ω

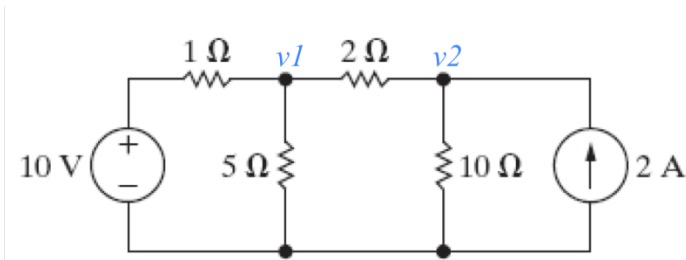Question 4 [1]


For the following circuit find the sum of the voltages v_1 and v_2 .



- (a) 10 V
- (b) 9 V
- (c) 20 V
- (d) 5 V

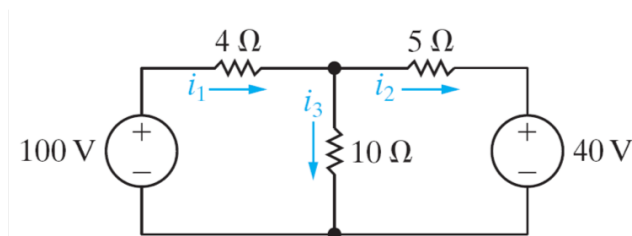Question 5 [1]


What is the value of i_3 in the circuit shown below?



- (a) 10 A
- (b) 4 A
- (c) 14 A
- (d) 6 A

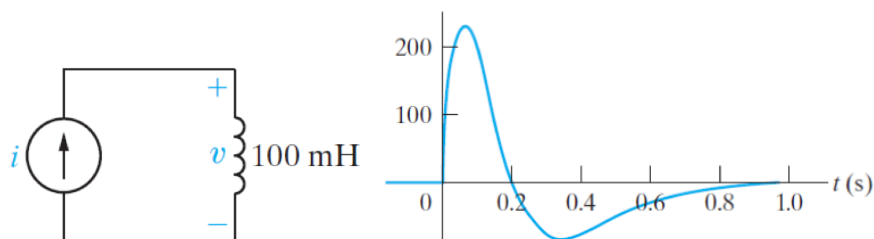Question 6 [1]

For $t > 0$, the current source generates a current, $i = 10te^{-5t}$ A, in the circuit shown below.




What does the corresponding graph show?

- (a) Power
- (b) Energy
- (c) Current
- (d) Voltage

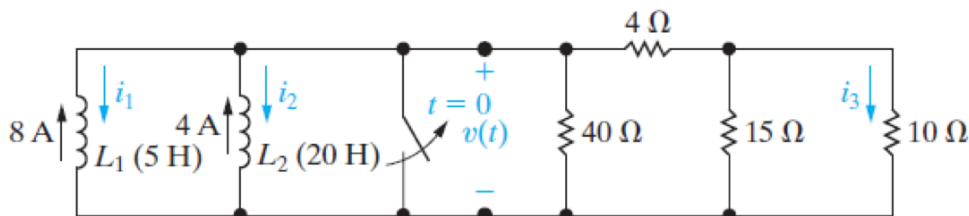Question 7 [1]

What is the value of the time constant for the RL circuit shown below?



- (a) 0.590 s
- (b) 3.125 s
- (c) 0.500 s
- (d) 0.333 s

Question 8 [1]

Consider a parallel RLC circuit. If, $R = 150\ \Omega$, $L = 50\ \text{mH}$, and $C = 0.2\ \mu\text{F}$, is the circuit:

- (a) Critically Damped
- (b) Overdamped
- (c) Underdamped

Question 9 [1]

Consider a parallel RLC circuit. If, $R = 250\ \Omega$, $L = 50\ \text{mH}$, and $C = 0.2\ \mu\text{F}$, is the circuit:

- (a) Critically Damped
- (b) Overdamped
- (c) Underdamped

Question 10 [1]

Consider a parallel RLC circuit. If, $R = 350\ \Omega$, $L = 50\ \text{mH}$, and $C = 0.2\ \mu\text{F}$, is the circuit:

- (a) Critically Damped
- (b) Overdamped
- (c) Underdamped