


ENGR 2910-101: Circuit Analysis

Homework 9: 03/18/20


Instructor: Leo Silbert

Due: 03/25/20

Question 1 [10]

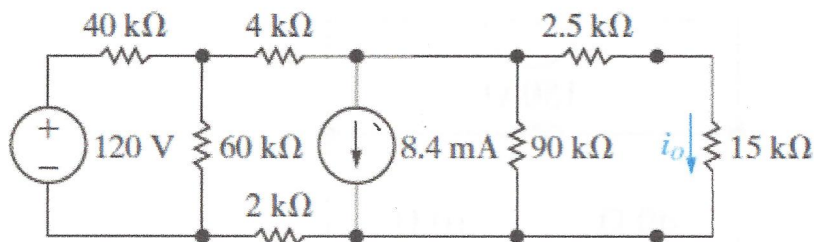

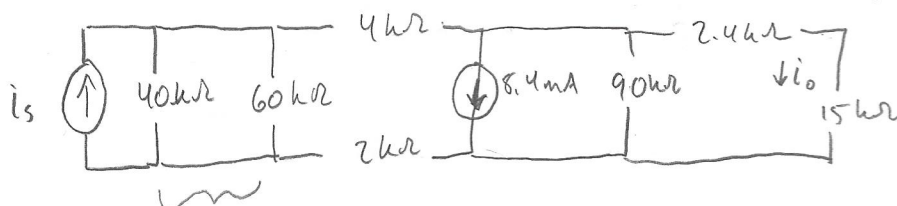
- (i) Using several source transformations find the value of the current flowing through the 15 kΩ resistor. [Hint: start on the left side of the circuit and work your way right.]
- (ii) Now that you know this current, work backwards through the original circuit and calculate the following: the voltage drop across the 90 kΩ and the current flowing through that branch; the current flowing through the 4 kΩ resistor, the voltage drop across the 60 kΩ resistor; and the current flowing in the left-hand part of the circuit.



$$i_1 = \frac{120}{40k} = 3mA$$


$$R_1 = \frac{40k \cdot 60k}{100} = 24k\Omega$$

$$V_1 = (3mA)(24k) = 72V$$

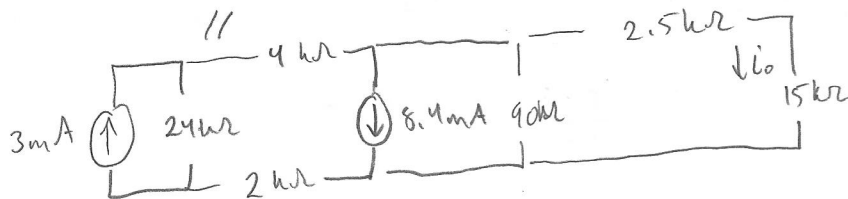



$$R_2 = 24k + 4k + 2k = 30k\Omega$$

$$i_2 = \frac{72}{30} = 2.4mA$$

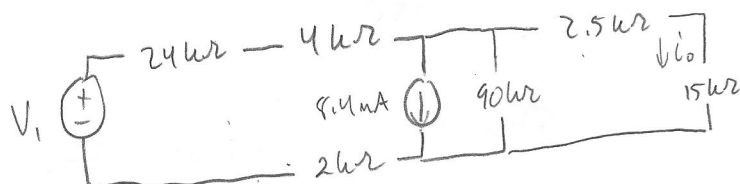


$$R_3 = 30k \parallel 90k = \frac{30k \cdot 90k}{120k} = 22.5k\Omega$$
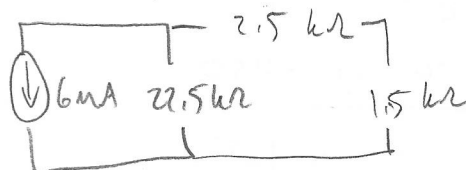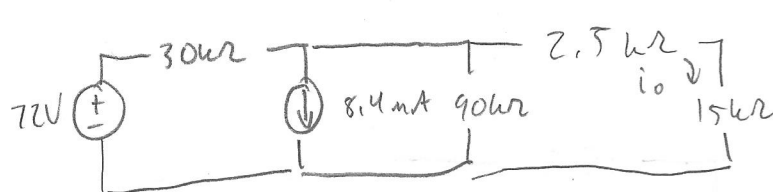
$$i_3 = 8.4mA - i_2 = 8.4mA - 2.4mA = 6mA$$



$$V_3 = (6mA)(22.5k) = 135V$$

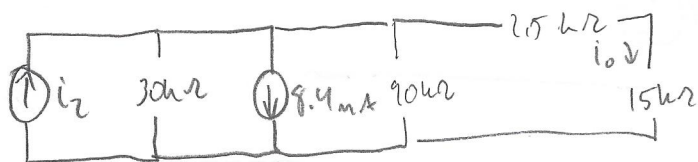
$$i_o = -\frac{V_3}{22.5k + 2.5k + 15k} = -\frac{135}{40k} = -3.375mA$$





Question 2 [10]

Find the Thévenin equivalent for the following circuit. [Hint: start off by making a source transformation then apply the mesh-current method.]

$$V = 3(150) = 450V$$

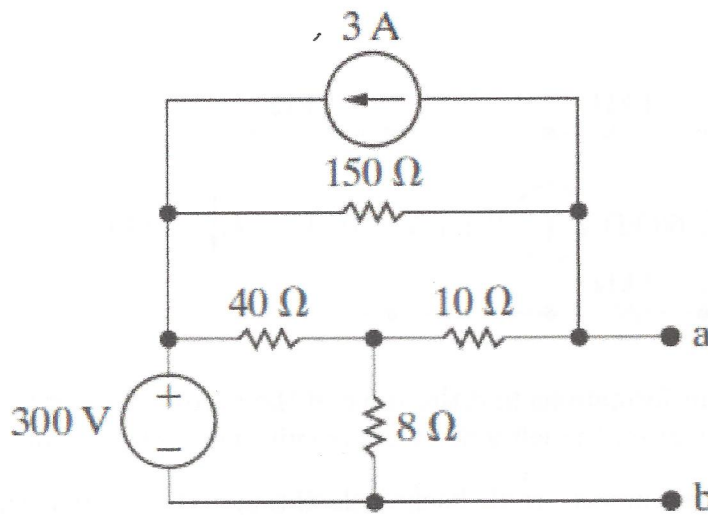
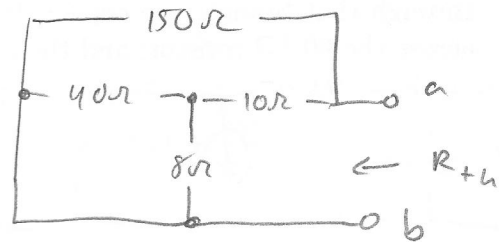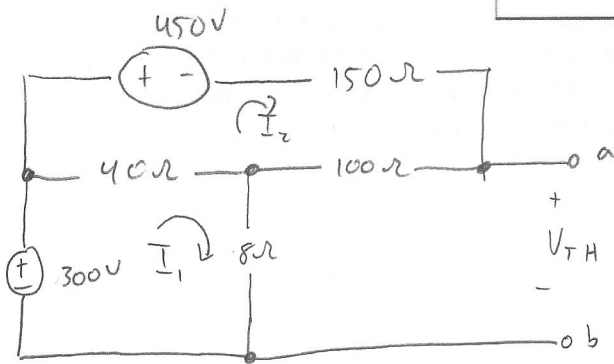
$$\begin{aligned} V_{TH} &= 10I_2 + 8I_1 \\ &= 10(-1.2) + 8(5.25) \\ &= 42 - 12 = 30V \end{aligned}$$




$$R_{TH} = [(40 \parallel 8) + 10] \parallel 150$$

$$= \left(\frac{40 \times 8}{48} + 10 \right) \parallel 150$$

$$= \frac{50}{3} \parallel 150$$
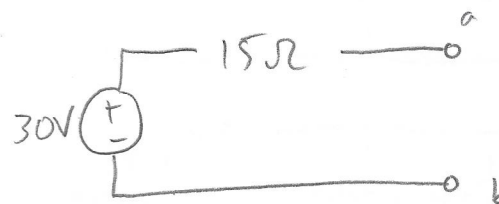
$$= \frac{\frac{50}{3} * 150}{\frac{50}{3} + 150} = 15\Omega = R_{TH}$$



Mesh current eqns.

$$-300 + 40(I_1 - I_2) + 8I_1 = 0$$

$$48I_1 - 40I_2 = 300$$

$$450 + 150(I_2) + 10(I_2) + 40(I_2 - I_1) = 0$$

$$-40I_1 + 200I_2 = -450$$

$$240I_1 - 200I_2 = 1500$$

$$-40I_1 + 200I_2 = -450$$

$$200I_1 = 1050$$

$$I_1 = 5.25A$$

$$I_2 = \frac{48I_1 - 300}{40} = -1.2A$$

Question 3 [10]

Find the Norton equivalent for the following circuit. [Hint: apply the node-voltage and mesh-current methods.]

$$i_{\Delta} = \frac{280 - V_1}{2000}$$

$$V_2 = 0V$$

KCL node 1

$$\frac{V_1 - 280}{2000} + \frac{V_1}{2000} + \frac{V_1 - V_2}{2000} = 280V - 0.2i_{\Delta}$$

$$\left(\frac{1}{2000} + \frac{1}{2000} + \frac{1}{2000}\right)V_1 - \frac{280}{2000} - \frac{V_2}{2000} = -0.2i_{\Delta}$$

$$\frac{3V_1 - 280 - V_2}{2000} = -0.2i_{\Delta}$$


$$3V_1 - 280 - V_2 = -400i_{\Delta}$$

$$3V_1 - 280 - V_2^0 = -400\left(\frac{280 - V_1}{2000}\right)$$

$$3V_1 - 280 = -56 + 0.2V_1$$

$$2.8V_1 = 224$$

$$V_1 = 80V$$

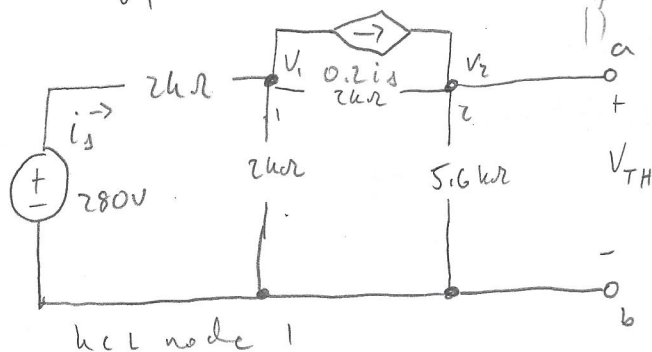

$$\frac{V_1 - 280}{2000} + \frac{V_1}{2000} + \frac{V_1 - V_2}{2000} = 0.2(i_{\Delta})$$

$$\left(\frac{1}{2000} + \frac{1}{2000} + \frac{1}{2000}\right)V_1 - \frac{V_2}{2000} - \frac{280}{2000} = 0.2i_{\Delta}$$

$$\frac{3V_1 - V_2 - 280}{2000} = -0.2i_{\Delta}$$

Homework 9

$$3V_1 - V_2 - 280 = -400\left(\frac{280 - V_1}{2000}\right)$$

$$3V_1 - V_2 - 280 = -56 + 0.2V_1$$

$$\begin{aligned} i_{\Delta} &= \frac{280 - V_1}{2000} \\ &= \frac{280 - 80}{2000} \\ &= 0.1A \end{aligned}$$

KCL node 2

$$i_{sc} = 0.2i_{\Delta} + \frac{V_1 - V_2}{2000} + \frac{V_2}{5600}$$

$$i_{sc} = 0.2(0.1) + \frac{80 - 0}{2000} + \frac{0/0}{5600}$$

$$i_{sc} = 0.06A$$

KCL node 2

$$\frac{V_2}{5600} + \frac{V_2 - V_1}{2000} = 0.2i_{\Delta}$$

$$-\frac{V_1}{2000} + \left(\frac{1}{5600} + \frac{1}{2000}\right)V_2 = 0.2i_{\Delta}$$

$$-\frac{14V_1}{28000} + \left(\frac{5+14}{28000}\right)V_2 = 0.2i_{\Delta}$$

$$-14V_1 + 19V_2 = 5600\left(\frac{280 - V_1}{2000}\right)$$

$$-14V_1 + 19V_2 = 784 - 2.8V_1$$

$$-11.2V_1 + 19V_2 = 784$$

$$-11.2\left(\frac{224 + V_2}{2.8}\right) + 19V_2 = 784$$

$$-896 - 4V_2 + 19V_2 = 784$$

$$V_2 = 112V$$

$$V_{TH} = 112V$$

Question 4 [10]

Use the test source method to find the Thévenin resistance. [Hint: use the node-voltage method.]

$$i_{\Delta} = \frac{V_3 - V_1}{150}$$

$$V_2 = 250 i_{\Delta}$$

$$V_2 = 250 \left(\frac{V_3 - V_1}{150} \right)$$

$$V_2 = \frac{250 V_3 - 250 V_1}{150}$$

KCL node 1

$$\frac{V_1}{100} + \frac{V_1 - V_2}{200} + \frac{V_1 - V_3}{150} = 0$$

$$\frac{6V_1 + 3V_1 - 3V_2 + 4V_1 - 4V_3}{600} = 0$$

$$13V_1 - 3V_2 - 4V_3 = 0$$

$$13V_1 - 3 \left(\frac{250}{150} V_3 - \frac{250}{150} V_1 \right) - 4V_3 = 0$$


$$13V_1 - 5V_3 + 5V_1 - 4V_3 = 0$$

$$18V_1 - 9V_3 = 0$$

$$V_1 = \frac{V_3}{2}$$

$$R_{TH} = \frac{V_3}{1A} = \frac{150V}{1A} = 150\Omega$$

$$V_{TH} = 0V$$

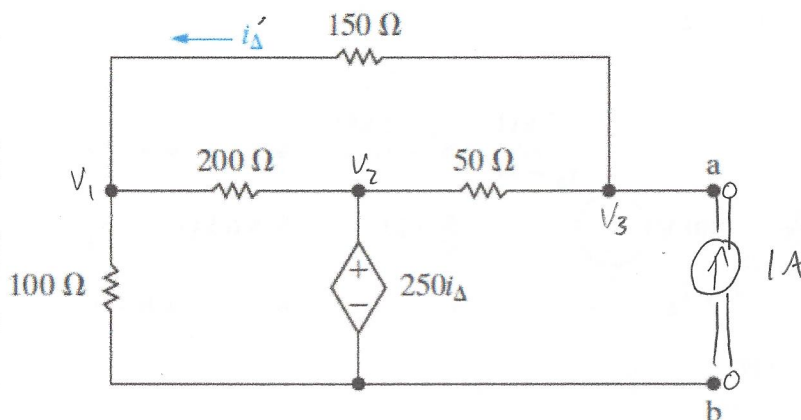

KCL node 3

$$\frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{150} = 1$$

$$\frac{3V_3 - 3V_2 + V_3 - V_1}{150} = 1$$

$$-V_1 - 3V_2 + 4V_3 = 150$$

$$-V_1 - 3 \left(\frac{250}{150} V_3 - \frac{250}{150} V_1 \right) + 4V_3 = 150$$


$$-V_1 - 5V_3 + 5V_1 + 4V_3 = 150$$

$$4V_1 - V_3 = 150$$

$$4 \left(\frac{V_3}{2} \right) - V_3 = 150$$



$$2V_3 - V_3 = 150$$

$$V_3 = 150V$$

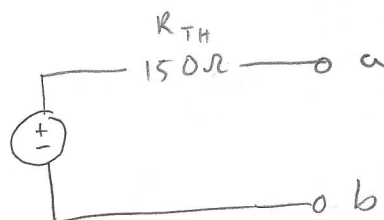

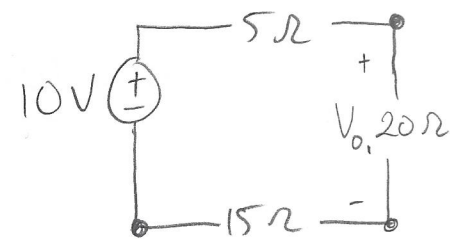
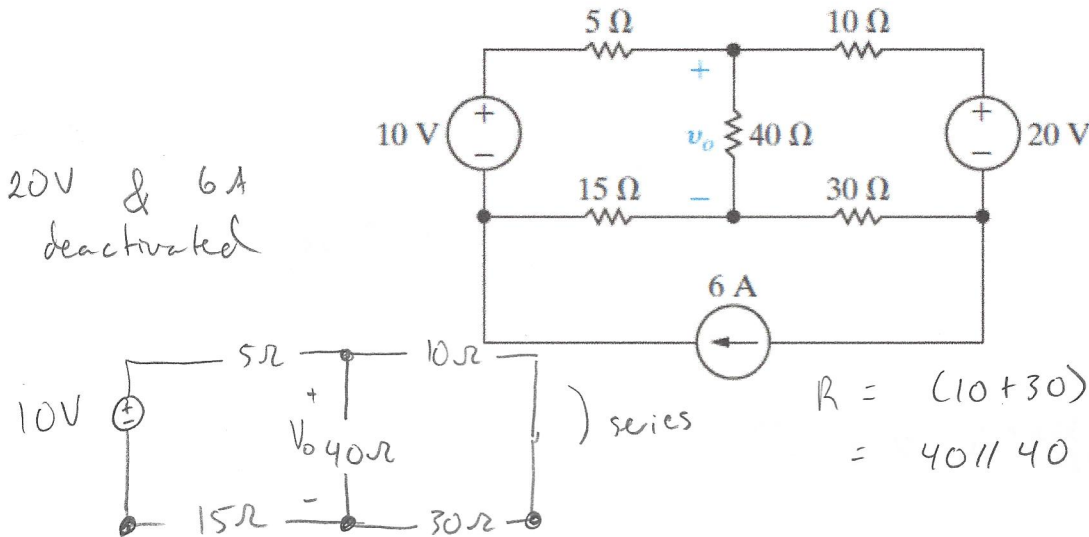
Question 5 [10]

Use the principle of superposition to find the voltage v_o . [Hint: when you analyze the current source, apply the node voltage method choosing the reference node as the node below the $40\ \Omega$ resistor.]




$$V_{o1} = \frac{20}{20+15+5} \times 10 = \frac{20}{40} \times 10 = 5V$$
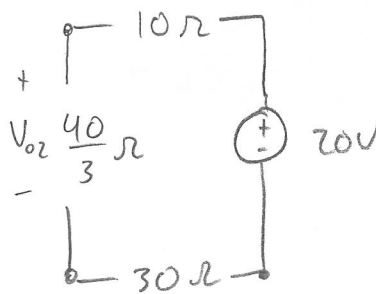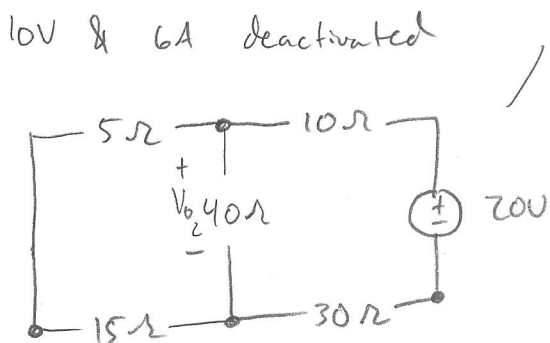
$$R = (5+15) \parallel 40 = 20 \parallel 40 = \frac{20 \times 40}{60} = \frac{40}{3} \Omega$$


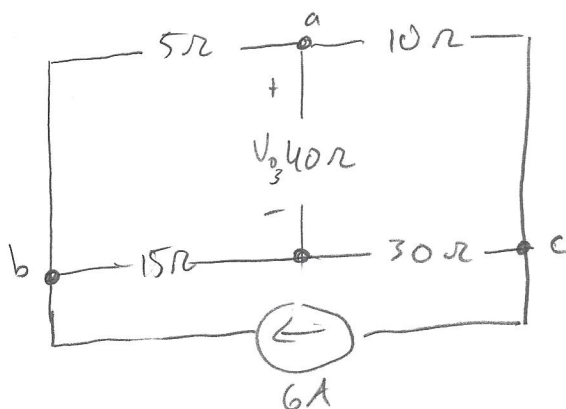
$$V_{o2} = \frac{\frac{40}{3}}{\frac{40}{3} + 30 + 10} \times 20 = \frac{40}{160} \times 20 = 5V$$



KCL a

$$\frac{V_{o3}}{40} + \frac{V_{o3} - V_c}{10} + \frac{V_{o3} - V_b}{5} = 0$$

$$V_{o3} + 4V_{o3} - 4V_c + 8V_{o3} - 8V_b = 0$$

$$13V_{o3} - 8V_b - 4V_c = 0$$

KCL b

$$\frac{V_b - V_{03}}{5} + \frac{V_b}{15} - 6 = 0$$

$$\frac{3V_b - 3V_{03} + V_b - 90}{15} = 0$$

$$-3V_{03} + 4V_b = 90$$

$$V_b = \frac{90 + 3V_{03}}{4}$$

sub eqns in

$$13V_{03} - 8\left(\frac{90 + 3V_{03}}{4}\right) - 4\left(\frac{-180 + 3V_{03}}{4}\right) = 0$$

$$13V_{03} - 180 - 6V_{03} + 180 - 3V_{03} = 0$$

$$4V_{03} = 0$$

$$V_{03} = 0V$$

KCL c

$$\frac{V_c - V_{03}}{10} + \frac{V_c}{30} + 6 = 0$$

$$\frac{3V_c - 3V_{03}}{30} + \frac{V_c}{30} + 6 = 0$$

$$-3V_{03} + 4V_c = -180$$

$$V_c = \frac{-180 + 3V_{03}}{4}$$

$$V_o = V_{01} + V_{02} + V_{03} = 5 + 5 + 0 = \underline{10V}$$

Q 3 continued

$$R_N = \frac{V_{TH}}{i_{sc}} = \frac{112V}{0.06A} = 1866.7\Omega$$

