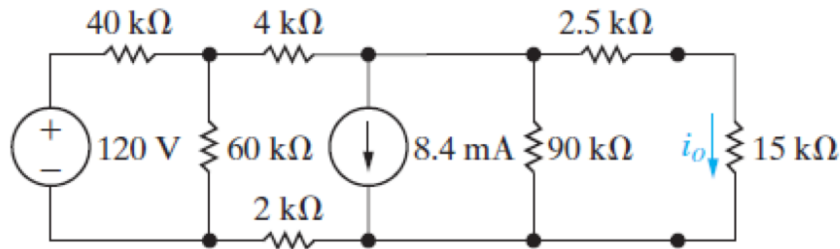



**Question 1** [10]

- (i) Using several source transformations find the value of the current flowing through the 15 kΩ resistor. [Hint: start on the left side of the circuit and work your way right.]
- (ii) Now that you know this current, work backwards through the original circuit and calculate the following: the voltage drop across the 90 kΩ and the current flowing through that branch; the current flowing through the 4 kΩ resistor, the voltage drop across the 60 kΩ resistor; and the current flowing in the left-hand part of the circuit.

---

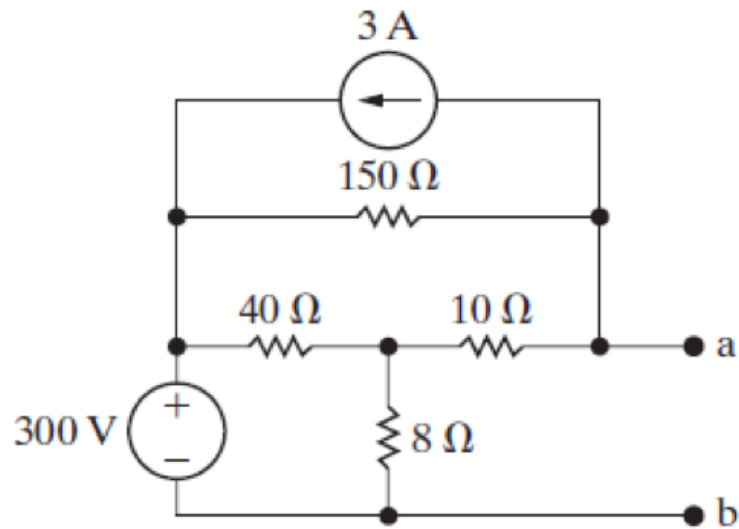**Question 2** [10]


Find the Thévenin equivalent for the following circuit. [Hint: start off by making a source transformation then apply the mesh-current method.]



---

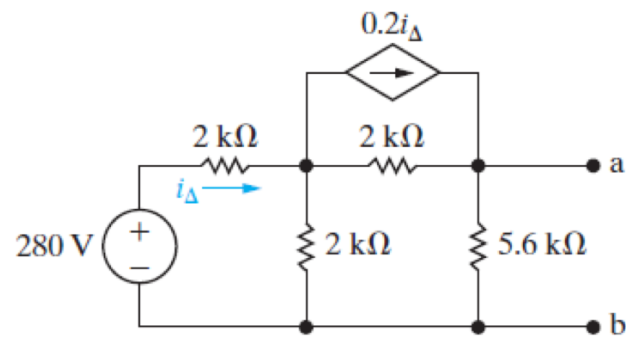**Question 3** [10]


Find the Norton equivalent for the following circuit. [Hint: apply the node-voltage and mesh-current methods.]



---

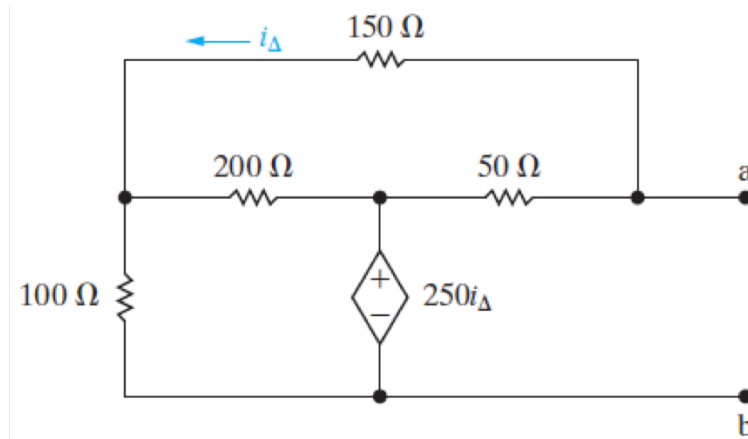**Question 4** [10]

Use the test source method to find the Thévenin resistance. [Hint: use the node-voltage method.]



---

**Question 5** [10]

Use the principle of superposition to find the voltage  $v_o$ . [Hint: when you analyze the current source, apply the node voltage method choosing the reference node as the node below the  $40\ \Omega$  resistor.]

