

ENGR 2910-101: Circuit Analysis


Homework 2:

Instructor: Brian Rashap

Due: See Brightspace

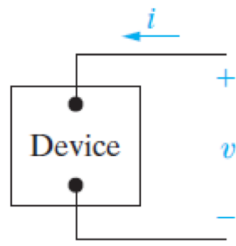Question 1 [4]

The terminal voltage and terminal current were measured (b) on the device (a) shown. Construct a circuit model for the device consisting of a single resistor. Provide a graph (either hand-drawn or software generated) showing how you determine the value of the resistor.




(a)

| i (mA) | v (V) |
|----------|---------|
| -10 | -120 |
| -5 | -60 |
| 5 | 60 |
| 10 | 120 |
| 15 | 180 |

(b)

Question 2 [4]

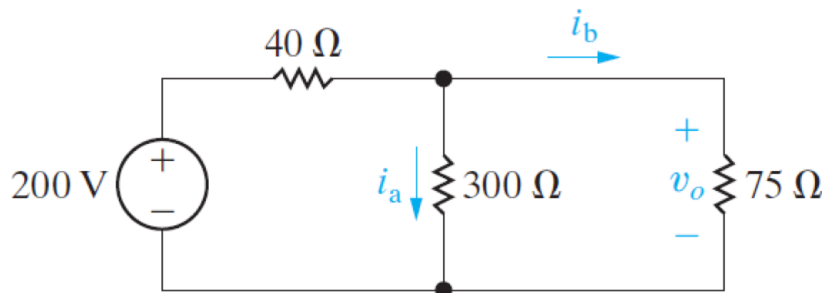


For the circuit shown, find:

- The value of i_a .
- The value of i_b .
- The value of v_o .
- the power dissipated in each resistor.
- the power delivered by the 200V source.

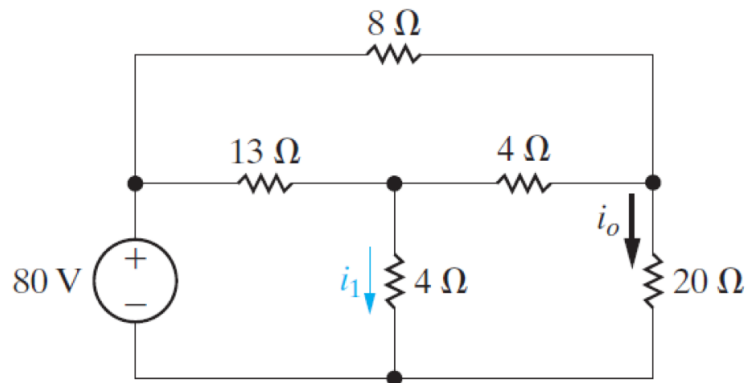Question 3 [4]


In the circuit below, the current $i_o = 2\text{ A}$.



- (a) Find i_1 .
- (b) Find the power dissipated in each resistor.
- (c) Verify that the total power dissipated in the circuit equals the power provided by the voltage source.

Question 4 [4]

The variable resistor R is adjusted until $i_o = 10\text{ mA}$. Find the value of R .

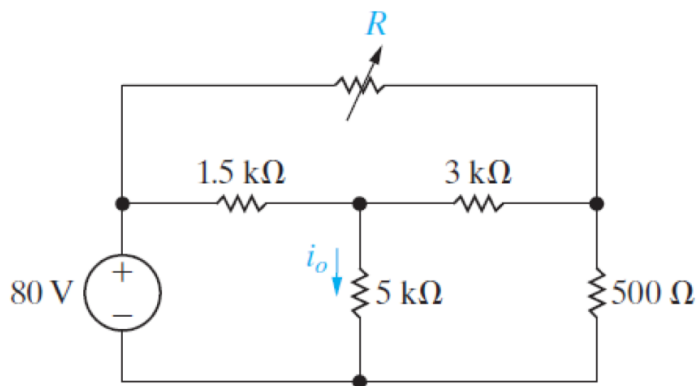**Question 5** [4]

Find v_o and the total power supplied in the circuit.

