

ECE 203
Exam 2

Name Ethan Rahhap

Please also put your name on the back of the last page of the exam.


Open notes. No computers or other internet-connected devices. You must show your work on each problem in order to get credit for your answer, even if you can do the work in your head. You must show sufficient work to demonstrate that you know how to solve the problem- guesses will not get credit.

ANSWERS (fill in your answers here)

- | | |
|-------------|--------------|
| 1. <u>A</u> | 6. <u>D</u> |
| 2. <u>C</u> | 7. <u>C</u> |
| 3. <u>D</u> | 8. <u>B</u> |
| 4. <u>B</u> | 9. <u>A</u> |
| 5. <u>C</u> | 10. <u>D</u> |

1. For the Op-amp circuit shown, find v_o .

- (A) 3 V B) -2 V C) 1 V D) -3 V

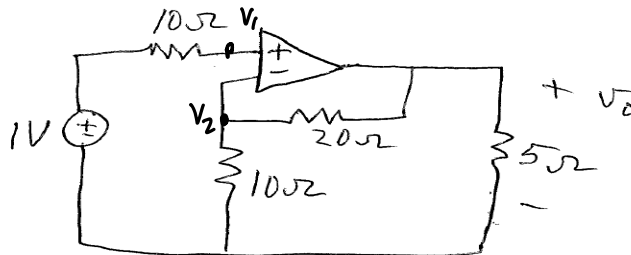

$$\frac{v_2 - v_o}{20} + \frac{v_2}{10} = 0$$

$$30v_2 - 10v_o = 0$$

$$\textcircled{1} \rightarrow v_o = 3v_2$$


$$v_2 = v_1 = 1V \textcircled{2}$$

$$\therefore v_o = 3v_2 = 3(1V)$$

$$v_o = 3V$$



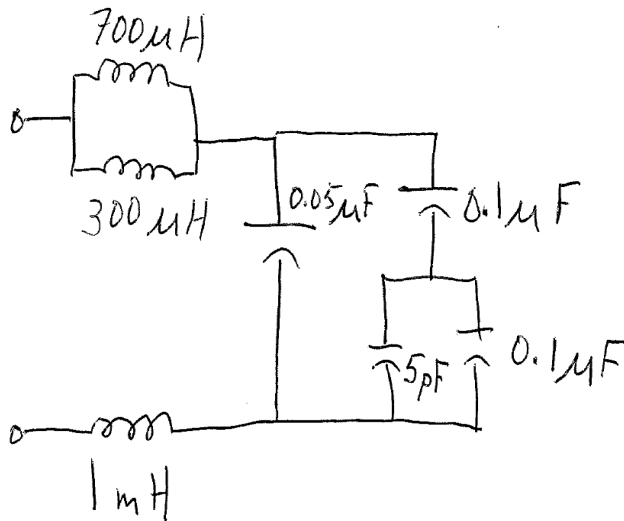2. Which of the following is the equivalent of the capacitor network shown below.




$$5 \text{ pF} \parallel 0.1 \mu\text{F} = (5 \times 10^{-12}) + (0.1 \times 10^{-6})$$

$$= 1.00005 \times 10^{-7}$$

$$700 \mu\text{H} \parallel 300 \mu\text{H} \Rightarrow \frac{1}{L_{eq}} = \frac{1}{700 \mu\text{H}} + \frac{1}{300 \mu\text{H}}$$





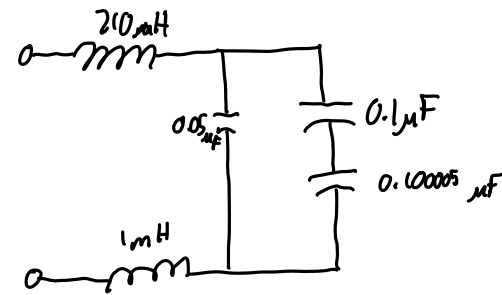
$$\frac{1}{L_{eq}} = \frac{1}{476.19} \Rightarrow L_{eq} = 210 \mu\text{H}$$



$$\frac{1}{C_{eq}} = \frac{1}{0.1 \mu\text{F}} + \frac{1}{0.1 \mu\text{F}}$$


$$C_{eq} = 5 \times 10^{-8} \text{ F}$$
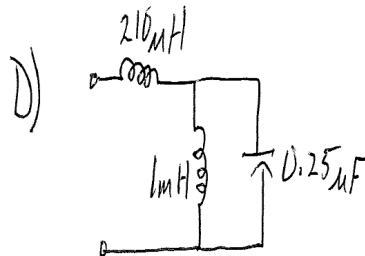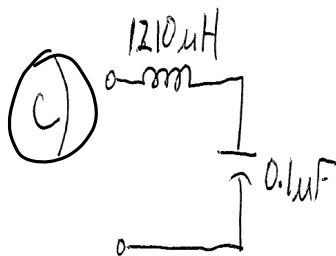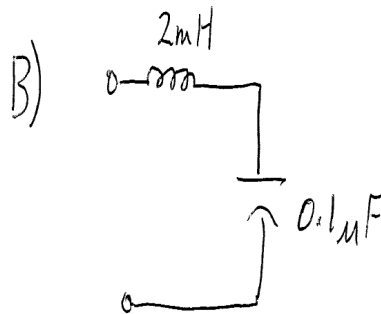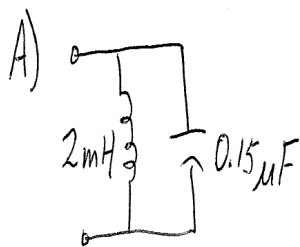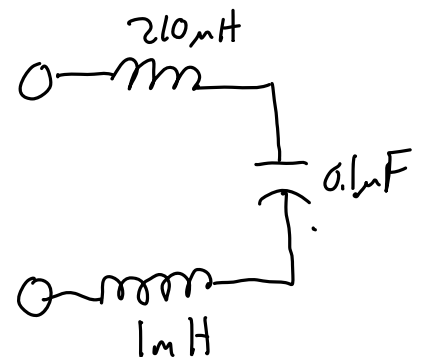
$$5 \times 10^{-8} \text{ F} \parallel 0.05 \mu\text{F} = 0.1 \mu\text{F}$$



3. Find the energy stored in the inductor.

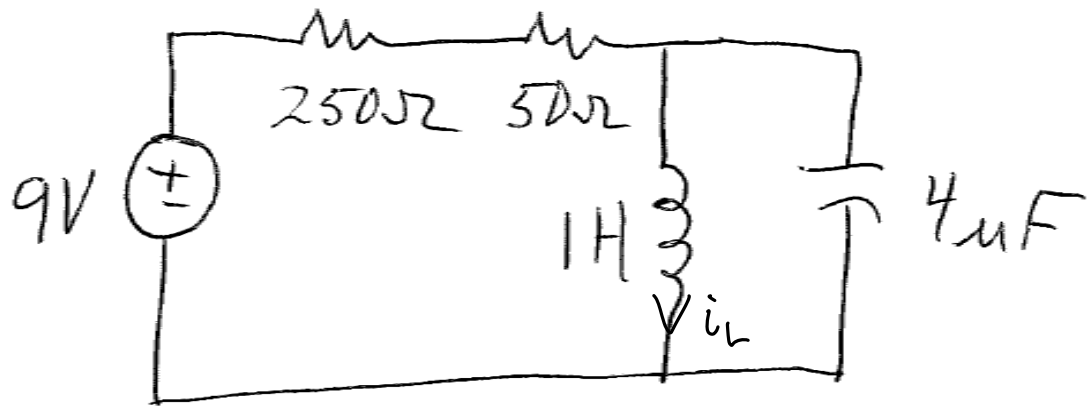- A) 0.65 mJ B) 40.5 J C) 0.16 mJ D) 0.45 mJ



$$i_L = \frac{9V}{(250 + 50\Omega)} = 0.03A$$


$$\text{Energy} = \frac{1}{2} L i^2$$

$$E = \frac{1}{2} (1H) (0.03)^2$$

$$E = \frac{0.9 \times 10^{-3}}{2} = 0.00045J$$




$$E = 0.45mJ$$

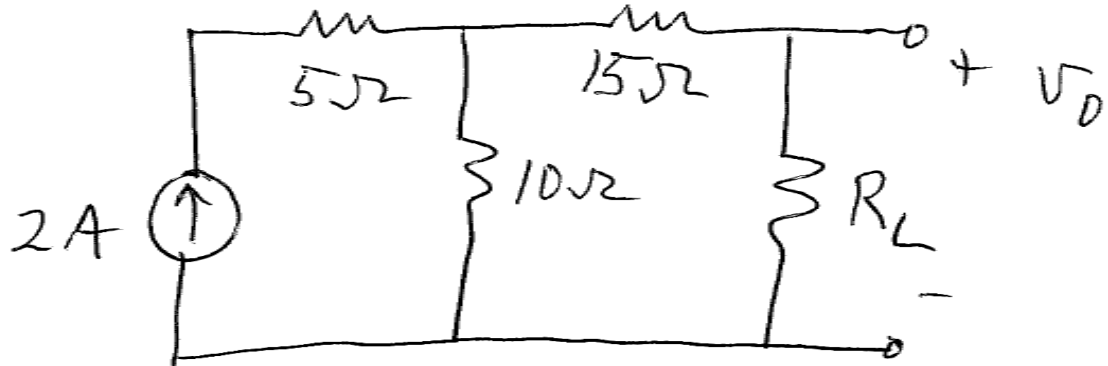Problems 4 and 5 refer to the following circuit. You would like to use Thévenin's theorem to find the voltage V_o (the voltage across the load resistor, R_L) in this circuit.



4. Find the Thévenin voltage (also known as the open-circuit voltage). Do this by removing the load resistor.


A) 40 V **B) 20 V** C) 30 V D) 12 V

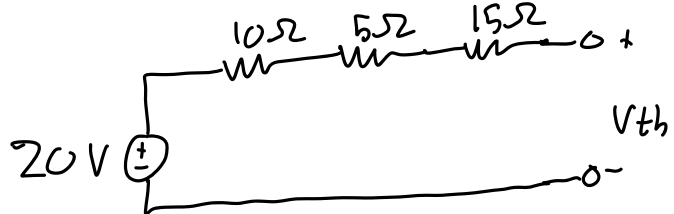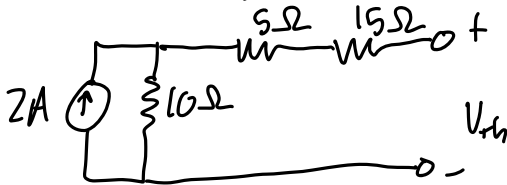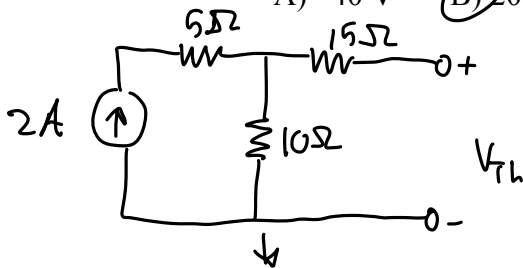

5. Find the Thévenin resistance. You will also need to remove the load resistor.

A) 3.33 Ω B) 6 Ω **C) 25 Ω** D) 10 Ω


Short circuit source

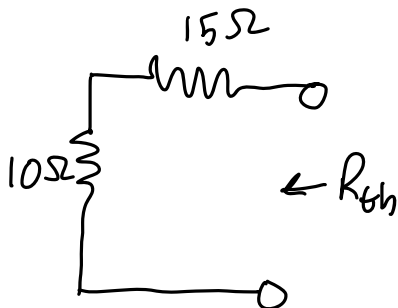

$$R_{th} = 15\Omega + 10\Omega = 25\Omega$$



6. Find the value of R_L for maximum power transfer to the load.

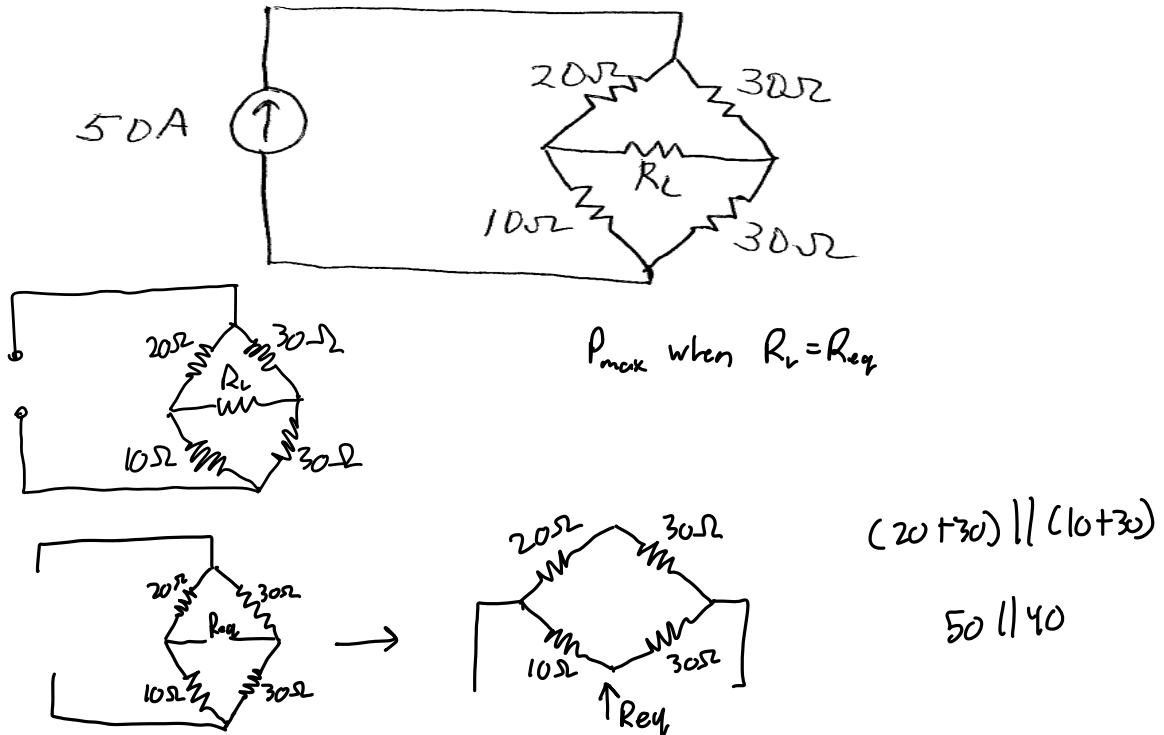- A) $20 \parallel 10 + 15 \Omega$ B) $30 \parallel 60 \Omega$ C) $20 \parallel 30 + 40 \Omega$ D) $50 \parallel 40 \Omega$



7. You would like to use superposition to find the value for v_o . For the first step in the process, you are going to calculate v_o' for the voltage source only. v_o' is:

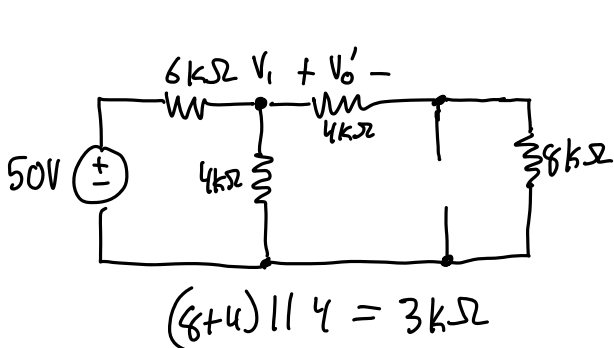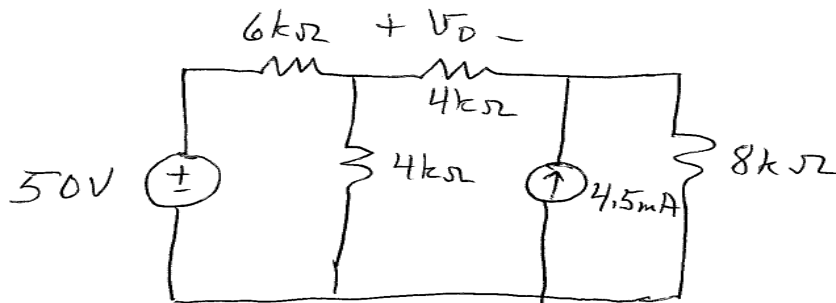- A) 12.5 V B) 2.22 V C) 5.56 V D) 7.78 V




$$V_i = 50V \left(\frac{3k\Omega}{3k\Omega + 6k\Omega} \right) = 16.67V$$

$$V_o' = V_i \left(\frac{4k\Omega}{(4+8)k\Omega} \right) = \frac{16.67}{3}$$

$$V_o' = 5.56V$$

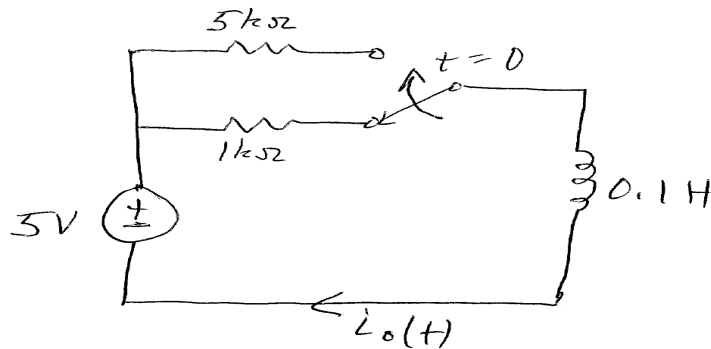Problems 8, 9, and 10 refer to the following first order circuit.




8. Find the current thru the inductor at $t = 0^+$.

- A) 1 mA **B) 5 mA** C) 6 mA D) 0 mA

@ $t = 0^+$


$$i_L(0^-) = \frac{5V}{1k\Omega} = 5mA$$

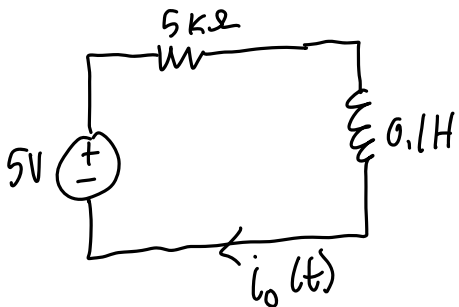

$$i_L(0^-) = i_L(0^+) = 5mA$$

9. What is the time constant for the circuit after the switch is thrown?

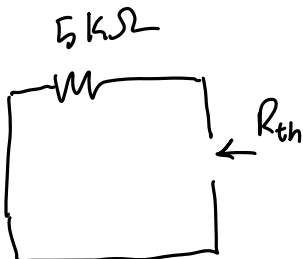- (A) 20 μs** B) 120 μs C) 17 μs D) 100 μs




$$\tau = \frac{L}{R}$$

$$R = R_{th} = 5k\Omega, L = 0.1H$$

$$\tau = \frac{0.1H}{5 \times 10^3 \Omega}$$

$$\tau = 2 \times 10^{-5} = 20\mu s$$

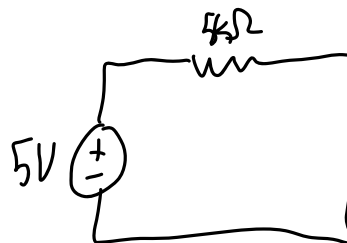10. Which of the following waveforms for $i_o(t)$ is correct?



$$I_s, t \rightarrow \infty \quad i(\infty) = \frac{V}{R} = 1$$

