


## ENGR 2910-101: Circuit Analysis

Homework 9: 03/18/20

Instructor: Leo Silbert

Due: 03/25/20

## Question 1 [10]

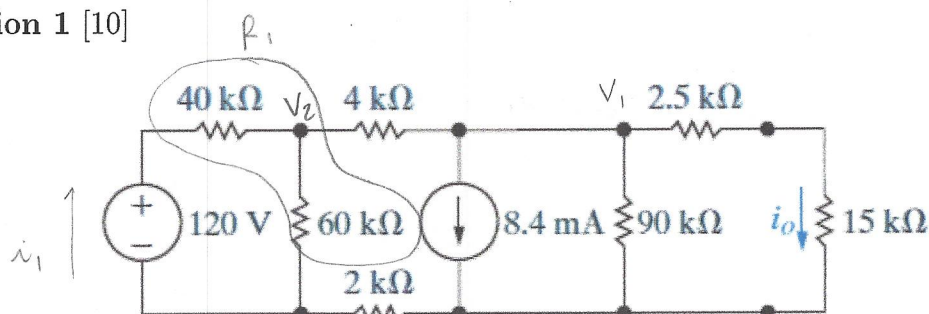


- (i) Using several source transformations find the value of the current flowing through the 15 kΩ resistor. [Hint: start on the left side of the circuit and work your way right.]
- (ii) Now that you know this current, work backwards through the original circuit and calculate the following: the voltage drop across the 90 kΩ and the current flowing through that branch; the current flowing through the 4 kΩ resistor, the voltage drop across the 60 kΩ resistor; and the current flowing in the left-hand part of the circuit.

i.

$$i_1 = \frac{120V}{40k\Omega} = 3mA \quad ; \quad R_1 = \frac{(40k\Omega)(60k\Omega)}{(40+60)k\Omega} = \frac{2400}{100} = 24k\Omega$$


→ in parallel

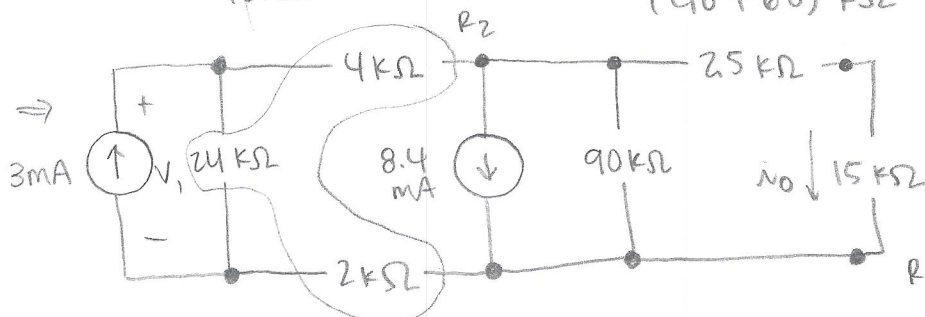

$$V_1 = (3mA)(24k\Omega) = 72V \text{ volts}$$

→ in series
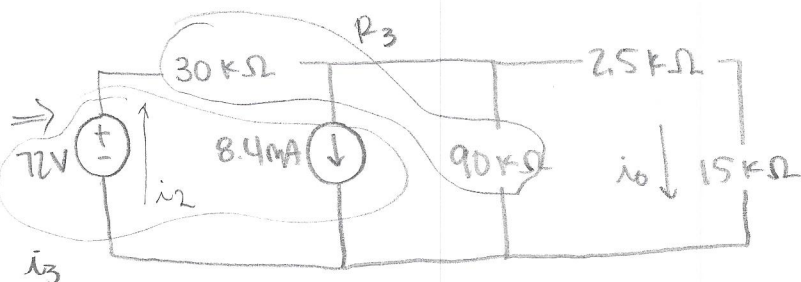
$$R_2 = (24 + 4 + 2)k\Omega = 30k\Omega$$




$$i_2 = \frac{72V}{30k\Omega} = 2.4mA$$

→ in parallel


$$R_3 = \frac{(30k\Omega)(90k\Omega)}{(30+90)k\Omega} = \frac{2700}{120} = 22.5k\Omega$$
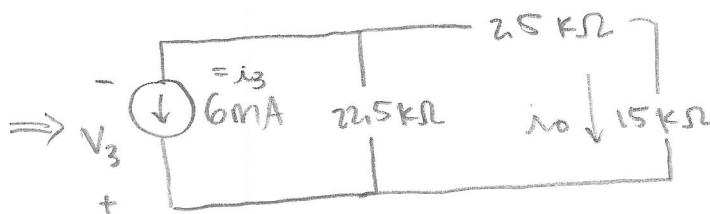
$$i_3 = (8.4mA) - i_2 = (8.4 - 2.4)mA = 6mA$$



$$V_3 = (6mA)(22.5k\Omega) = 135V \text{ volts}$$
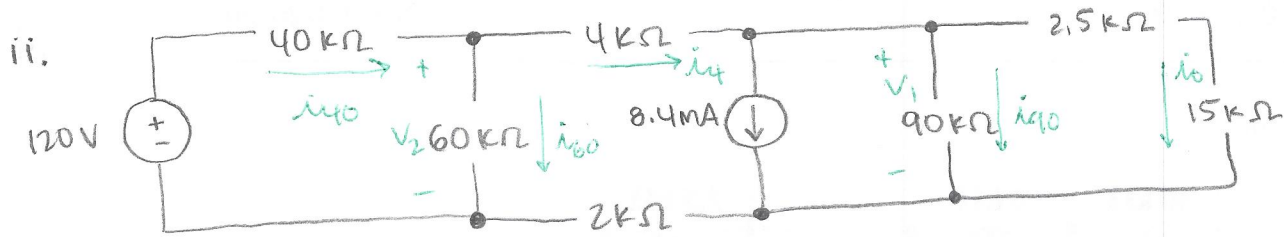
$$\Rightarrow i_o = \frac{-V_3}{(22.5 + 2.5 + 15) \text{ k}\Omega} = \frac{-135 \text{ V}}{40 \text{ k}\Omega} = \boxed{-3.375 \text{ mA} = i_o}$$



$$V_1 = (-3.375 \text{ mA})(2.5 + 15) \text{ k}\Omega \Rightarrow i_{90} = \frac{V_1}{90 \text{ k}\Omega} = \frac{-59.06 \text{ V}}{90 \text{ k}\Omega} = -0.656 \text{ mA}$$

$$= -59.06 \text{ Volts}$$

$$i_4 = (8.4 + i_{90} - 3.375) \text{ mA}$$

$$= 4.369 \text{ mA}$$

$$V_2 = i_4 (4 + 2) \text{ k}\Omega + V_1$$

$$= (4.369 \text{ mA})(6 \text{ k}\Omega) + (-59.06 \text{ V}) =$$


$$= -32.846 \text{ Volts}$$

$$i_{60} = \frac{V_2}{60 \text{ k}\Omega} = \frac{-32.846 \text{ V}}{60 \text{ k}\Omega} = -0.547 \text{ mA}$$


$$i_{40} = i_{60} + i_4 = (-0.547 + 4.369) \text{ mA} = 3.822 \text{ mA}$$
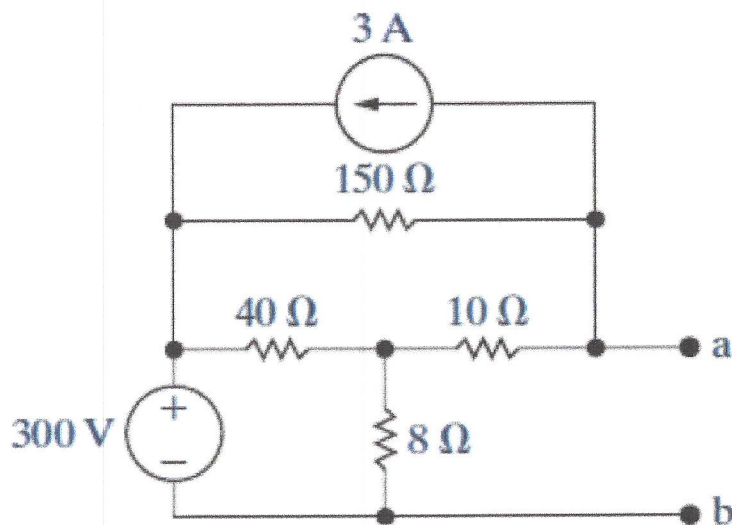
## Question 2 [10]

Find the Thévenin equivalent for the following circuit. [Hint: start off by making a source transformation then apply the mesh-current method.]



$$V_1 = (3A)(150\Omega) = 450V$$

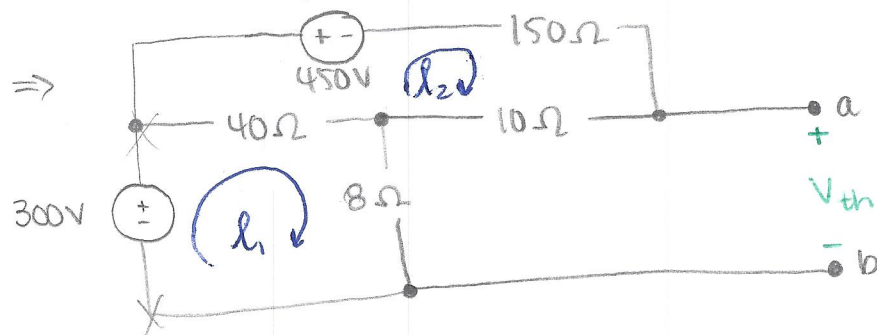

mesh-current  $i_1$ :  $-300 + 40(i_1 - i_2) + 8(i_1) = 0$

$$\Rightarrow 40i_1 - 40i_2 + 8i_1 = 300$$

$$\Rightarrow 48i_1 - 40i_2 = 300 \dots \text{eq 1}$$

mesh-current  $i_2$ :  $450 + (150)(i_2) + (10)(i_2) + 40(i_2 - i_1) = 0$

$$\Rightarrow 150i_2 + 10i_2 + 40i_2 - 40i_1 = -450$$

$$\Rightarrow -40i_1 + 200i_2 = -450 \dots \text{eq 2}$$


through solving matrix on calculator:

$$\begin{bmatrix} 48 & -40 & 300 \\ -40 & 200 & -450 \end{bmatrix} \Rightarrow \begin{matrix} i_1 = 5.25A \\ i_2 = -1.2A \end{matrix} \Rightarrow V_{TH} = 10i_2 + 8i_1 = 10(-1.2A) + 8(5.25A)$$

$$V_{TH} = 30 \text{ Volts}$$


$$\begin{aligned}
 R_{TH} &= (40 \parallel 8) + 10 \parallel 150 \\
 &= \left( \frac{40 \cdot 8}{48} + 10 \right) \parallel 150 \\
 &= (16.67) \parallel 150 \\
 &= \frac{(16.67)(150)}{150 + 16.67} \\
 &= 15.002 \, \Omega \\
 \Rightarrow R_{TH} &= 15 \, \Omega
 \end{aligned}$$

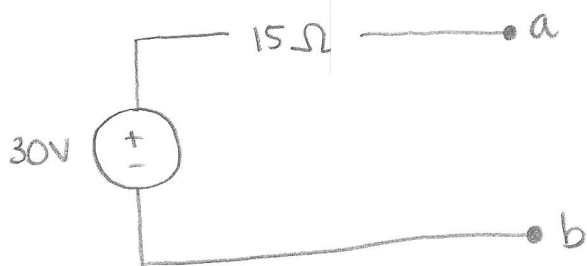$\Rightarrow$  Thevenin Equivalent Circuit :


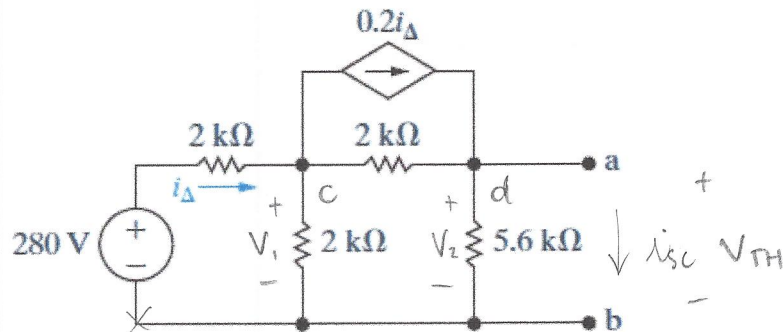
## Question 3 [10]

Find the Norton equivalent for the following circuit. [Hint: apply the node-voltage and mesh-current methods.]



$$i_{\Delta} = \frac{280 - V_1}{2000 \Omega} \Rightarrow V_2 = 0 \text{ because } a \text{ and } b \text{ is short circuited}$$

$$\text{KVL node } c: \frac{V_1 - 280}{2000 \Omega} + \frac{V_1}{2000} + \frac{V_1 - V_2}{2000} = -0.2 i_{\Delta}$$

$$\Rightarrow \frac{V_1}{2000} - \frac{280}{2000} + \frac{V_1}{2000} + \frac{V_1}{2000} - \frac{V_2}{2000} = -0.2 i_{\Delta}$$

$$\Rightarrow \frac{3V_1}{2000} - \frac{V_2}{2000} - \frac{280}{2000} = -\frac{400 i_{\Delta}}{2000}$$

$$\Rightarrow 3V_1 - V_2 - 280 = -400 i_{\Delta}$$

$$\Rightarrow 3V_1 - 0 - 280 = -400 \left( \frac{280 - V_1}{2000} \right)$$

$$\Rightarrow 3V_1 - 280 = \frac{-112000}{2000} + \frac{400V_1}{2000} \Rightarrow 2.8V_1 = 224 \Rightarrow V_1 = 80 \text{ Volts}$$

$$i_{\Delta} = \frac{280 - (80)}{2000} = \frac{200}{2000} = 0.1 \text{ A}$$

$$\text{KVL node } d: 0.2 i_{\Delta} + \frac{V_1 - V_2}{2000} + \frac{V_2}{5600} = i_{sc}$$

$$\Rightarrow i_{sc} = (0.2)(0.1) + \frac{80 - 0}{2000} + \frac{0}{5600}$$

$$\text{Homework 9} = 0.06 \text{ A} = i_{sc}$$

$$i_{\Delta} = \frac{280 - V_1}{2000}$$

FVI node c to find  $V_{TH}$   $\therefore$  calculate norton equivalent resistance:

starting from work on previous page:

$$3V_1 - V_2 - 280 = -400i_{\Delta}$$

$$\Rightarrow 3V_1 - V_2 - 280 = -400 \left( \frac{280 - V_1}{2000} \right)$$

$$\Rightarrow 2.8V_1 = 224 + V_2$$

$$\Rightarrow V_1 = \frac{224 + V_2}{2.8}$$

FVI node d:

$$\frac{V_2}{5600} + \frac{V_2 - V_1}{2000} = 0.2i_{\Delta}$$

$$\Rightarrow \frac{V_2 \cdot 5}{5600 \cdot 5} + \frac{V_2 \cdot 14}{2000 \cdot 14} - \frac{V_1 \cdot 14}{2000 \cdot 14} = 0.2i_{\Delta} \Rightarrow \frac{5V_2 + 14V_2}{28000} - \frac{14V_1}{28000} = 0.2i_{\Delta}$$

$$\Rightarrow -14V_1 + 19V_2 = 5600i_{\Delta}$$

$$\Rightarrow -14V_1 + 19V_2 = 5600 \left( \frac{280 - V_1}{2000} \right) \Rightarrow -14V_1 + 19V_2 = \frac{1568000}{2000} - \frac{5600V_1}{2000}$$


$$\Rightarrow -11.2V_1 + 19V_2 = 784$$

$$\Rightarrow -11.2 \left( \frac{224 + V_2}{2.8} \right) + 19V_2 = 784 \Rightarrow \frac{-2508.8}{2.8} - \frac{11.2V_2}{2.8} + 19V_2 = 784$$

$$\Rightarrow -896 - 4V_2 + 19V_2 = 784 \Rightarrow 15V_2 = 970 \Rightarrow V_2 = 112 \text{ volts} = V_{TH}$$

$$R_N = \frac{V_{TH}}{i_{sc}} = \frac{112V}{0.06A} = 1866.67 \Omega$$

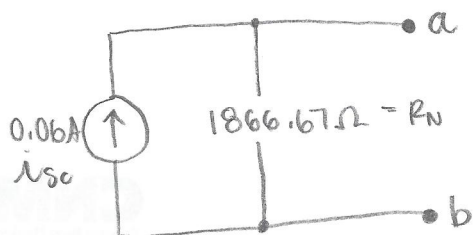
Norton  
Equivalent  
circuit  $\Rightarrow$





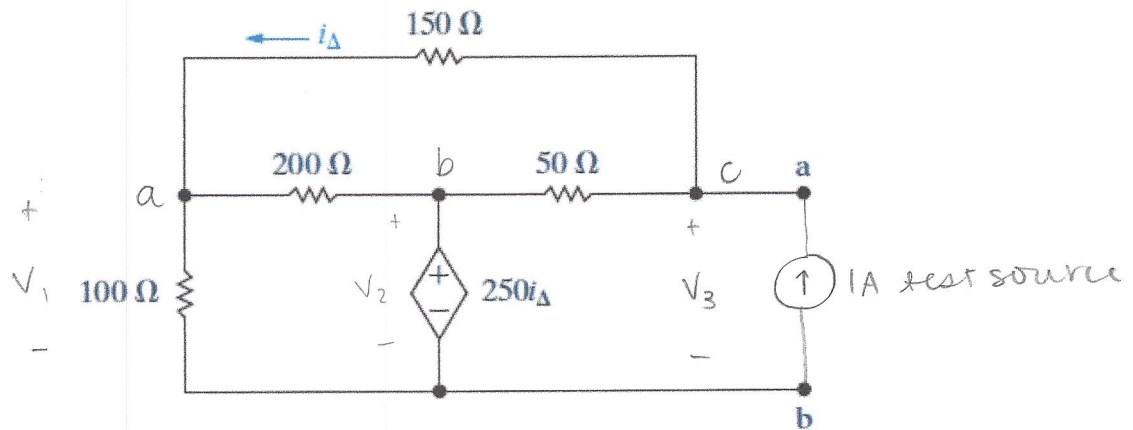Question 4 [10]

Use the test source method to find the Thévenin resistance. [Hint: use the node-voltage method.]



$$i_{\Delta} = \frac{V_3 - V_1}{150\Omega} \quad \left\{ \begin{array}{l} V_2 = 250i_{\Delta} = 250 \left( \frac{V_3 - V_1}{150} \right) = 1.67V_3 - 1.67V_1 = V_2 \end{array} \right.$$

$$\text{KCL node a: } \frac{V_1}{100} + \frac{V_1 - V_2}{200} + \frac{V_1 - V_3}{150} = 0$$

$$\Rightarrow \frac{6V_1}{600} + \frac{3V_1 - 3V_2}{600} + \frac{4V_1 - 4V_3}{600} = 0$$

$$\Rightarrow 6V_1 + 3V_1 - 3V_2 + 4V_1 - 4V_3 = 0$$

$$\Rightarrow 13V_1 - 3V_2 - 4V_3 = 0$$

$$\Rightarrow 13V_1 - 3(1.67V_3 - 1.67V_1) - 4V_3 = 0$$

$$\Rightarrow 13V_1 - 5.01V_3 + 5.01V_1 - 4V_3 = 0$$

$$\Rightarrow 18.01V_1 - 9.01V_3 = 0$$

$$V_1 = 0.5V_3$$

$$\text{KCL node c: } \frac{V_3 - V_2}{50} + \frac{V_3 - V_1}{150} = 1$$

$$\Rightarrow \frac{3V_3 - 3V_2}{150} + \frac{V_3 - V_1}{150} = 1$$

$$\Rightarrow 4V_3 - 3V_2 - V_1 = 150$$

$$\Rightarrow 4V_3 - 3(1.67V_3 - 1.67V_1) - V_1 = 150$$

$$\Rightarrow 4V_3 - 5.01V_3 + 5.01V_1 - V_1 = 150$$

$$\Rightarrow -1.01V_3 + 4.01V_1 = 150$$


$$\Rightarrow 4.01(0.5V_3) - 1.01V_3 = 150$$

$$\Rightarrow 2V_3 - 1.01V_3 = 150$$

$$\Rightarrow V_3 = 150 \text{ Volts}$$


$$R_{TH} = \frac{V_3}{1A} = \frac{150V}{1A} = 150\Omega$$

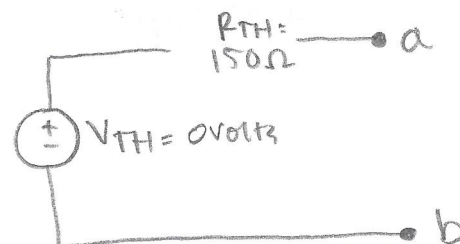$V_{TH} = 0$  volts because of no existing independent source.



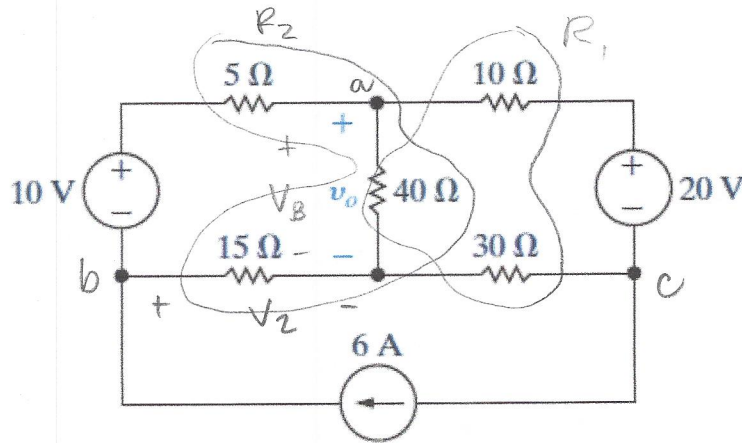**Question 5 [10]**

Use the principle of superposition to find the voltage  $v_o$ . [Hint: when you analyze the current source, apply the node voltage method choosing the reference node as the node below the  $40\ \Omega$  resistor.]



$$R_1 = (30 + 10) \parallel 40 = 40 \parallel 40 = \frac{(40)(40)}{40 + 40} = \frac{1600}{80} = 20\ \Omega$$

$$\Rightarrow \begin{array}{c} 5\ \Omega \\ | \\ 10V \\ | \\ 15\ \Omega \end{array} \quad \begin{array}{c} + \\ V_\phi \\ - \end{array} \quad 20\ \Omega \Rightarrow V_\phi = \left( \frac{20}{20 + 15 + 5} \right) (10V) = 5\text{volts}$$

$$R_2 = (5 + 15) \parallel 40 = 20 \parallel 40 = \frac{(20)(40)}{40 + 20} = \frac{800}{60} = 13.3\ \Omega$$

$$\Rightarrow \begin{array}{c} + \\ V_a \\ - \end{array} \quad \begin{array}{c} 10\ \Omega \\ | \\ 13.3\ \Omega \\ | \\ 30\ \Omega \end{array} \quad \begin{array}{c} + \\ 20V \\ - \end{array} \Rightarrow V_a = \left( \frac{13.3}{13.3 + 10 + 30} \right) (20V) = 4.99V = 5\text{volts}$$

$$\text{KCL node a: } \frac{V_B}{40} + \frac{V_B - V_1}{10} + \frac{V_B - V_2}{5} = 0$$

$$\Rightarrow \frac{V_B}{40} + \frac{4V_B - 4V_1}{40} + \frac{8V_B - 8V_2}{40} = 0$$

$$\Rightarrow 13V_B - 4V_1 - 8V_2 = 0$$

$$\text{KCL node b: } \frac{V_2 - V_B}{5} + \frac{V_2}{15} - 6 = 0$$

$$\Rightarrow \frac{3V_2 - 3V_B}{15} + \frac{V_2}{15} = 6$$

$$\Rightarrow -3V_B + 4V_2 = 90$$

$$\Rightarrow V_2 = \frac{90 + 3V_B}{4}$$



$$\text{KCL node c: } \frac{V_1 - V_B}{10} + \frac{V_1}{30} + 6 = 0$$

$$\Rightarrow \frac{3V_1 - 3V_B}{30} + \frac{V_1}{30} = -6$$

$$\Rightarrow 4V_1 - 3V_B = -180$$

$$\Rightarrow V_1 = \frac{-180 + 3V_B}{4}$$

$$\Rightarrow 13V_B - 4V_1 - 8V_2 = 0$$

$$\Rightarrow 13V_B - 4\left(\frac{-180 + 3V_B}{4}\right) - 8\left(\frac{90 + 3V_B}{4}\right) = 0$$

$$\Rightarrow 13V_B + \frac{720}{4} - \frac{12V_B}{4} - \frac{720}{4} - \frac{24V_B}{4} = 0$$

$$\Rightarrow 13V_B - 3V_B - 6V_B = 0$$

$$\Rightarrow 4V_B = 0$$

$$\Rightarrow V_B = 0 \text{ volts}$$

Principle of superposition:

$$V_0 = V_\phi + V_\alpha + V_\beta$$

$$= (5 + 5 + 0) \text{ volts}$$

$$\Rightarrow \boxed{V_0 = 10 \text{ volts}}$$