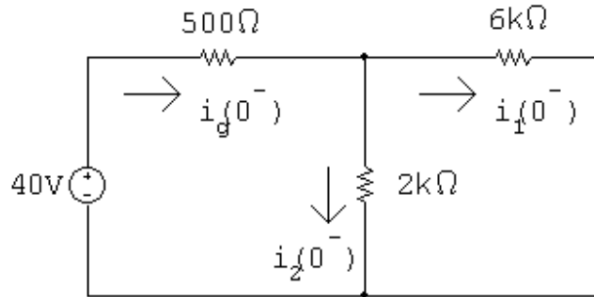


P 7.1 [a]  $t < 0$ :



$$2\text{ k}\Omega \parallel 6\text{ k}\Omega = 1.5\text{ k}\Omega.$$

Find the current from the voltage source by combining the resistors in series and parallel and using Ohm's law:

$$i_g(0^-) = \frac{40}{(1500 + 500)} = 20\text{ mA}.$$

Find the branch currents using current division:

$$i_1(0^-) = \frac{2000}{8000}(0.02) = 5\text{ mA};$$

$$i_2(0^-) = \frac{6000}{8000}(0.02) = 15\text{ mA}.$$

[b] The current in an inductor is continuous. Therefore,

$$i_1(0^+) = i_1(0^-) = 5\text{ mA};$$

$$i_2(0^+) = -i_1(0^+) = -5\text{ mA}. \quad (\text{when switch is open})$$

$$[c] \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3}}{8 \times 10^3} = 5 \times 10^{-5}\text{ s}; \quad \frac{1}{\tau} = 20,000;$$


$$i_1(t) = i_1(0^+)e^{-t/\tau} = 5e^{-20,000t}\text{ mA}, \quad t \geq 0.$$

$$[d] \quad i_2(t) = -i_1(t) \quad \text{when } t \geq 0^+;$$

$$\therefore i_2(t) = -5e^{-20,000t}\text{ mA}, \quad t \geq 0^+.$$


[e] The current in a resistor can change instantaneously. The switching operation forces  $i_2(0^-)$  to equal 15 mA and  $i_2(0^+) = -5\text{ mA}$ .

P 7.5  $t < 0$ :

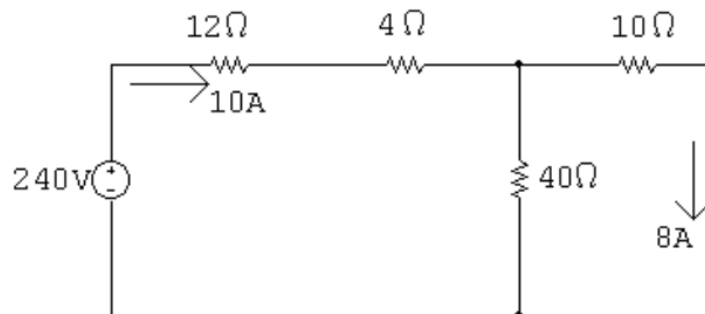

$$i_L(0^+) = 8 \text{ A.}$$

$t > 0$ :

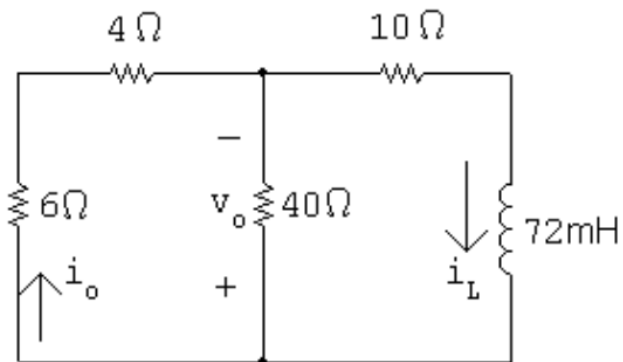

$$R_e = \frac{(10)(40)}{50} + 10 = 18 \Omega;$$


$$\tau = \frac{L}{R_e} = \frac{0.072}{18} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250;$$

$$\therefore i_L = 8e^{-250t} \text{ A.}$$


$$\therefore v_o = -10i_L - 0.072 \frac{di_L}{dt} = -80e^{-250t} + 144e^{-250t}$$

$$= 64e^{-250t} \text{ A} \quad t \geq 0^+.$$

P 7.15 [a]  $t < 0$ :

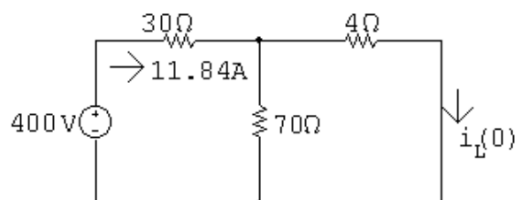

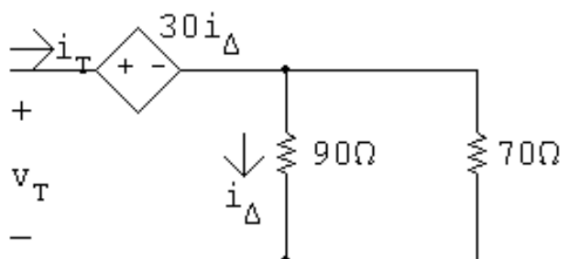
$$i_L(0^-) = i_L(0^+) = \frac{70}{70 + 4}(11.84) = 11.2 \text{ A.}$$



$$i_{\Delta} = \frac{70}{160}i_T = 0.4375i_T;$$

$$v_T = 30i_{\Delta} + i_T \frac{(90)(70)}{160} = 30(0.4375)i_T + \frac{(90)(70)}{160}i_T = 52.5i_T;$$
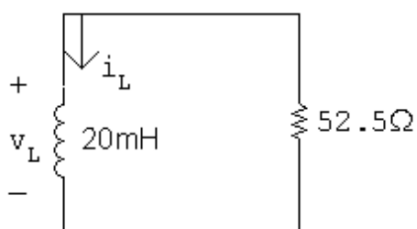
$$\frac{v_T}{i_T} = R_{Th} = 52.5 \Omega.$$




$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{52.5} = \therefore \frac{1}{\tau} = 2625;$$

$$i_L = 11.2e^{-2625t} \text{ A,} \quad t \geq 0.$$

[b]  $v_L = L \frac{di_L}{dt} = 20 \times 10^{-3}(-2625)(11.2e^{-2625t}) = -588e^{-2625t} \text{ V,} \quad t \geq 0^+.$


[c]

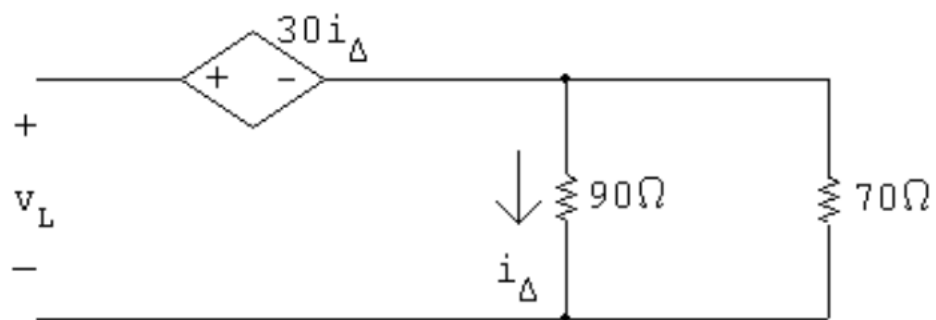

$$v_L = 30i_\Delta + 90i_\Delta = 120i_\Delta;$$


$$i_\Delta = \frac{v_L}{120} = -4.9e^{-2625t} \text{ A} \quad t \geq 0^+.$$

P 7.18 [a]  $t < 0$ :

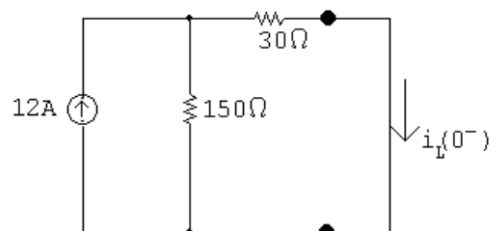

$$i_L(0^-) = \frac{150}{180}(12) = 10 \text{ A.}$$

$t \geq 0$ ;

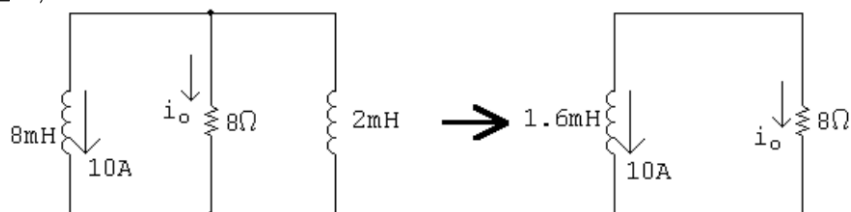

$$\tau = \frac{1.6 \times 10^{-3}}{8} = 200 \times 10^{-6}; \quad 1/\tau = 5000;$$

$$i_o = -10e^{-5000t} \text{ A} \quad t \geq 0.$$

[b]  $w_{\text{del}} = \frac{1}{2}(1.6 \times 10^{-3})(10)^2 = 80 \text{ mJ.}$

[c]  $0.95w_{\text{del}} = 76 \text{ mJ};$

$$\therefore 76 \times 10^{-3} = \int_0^{t_o} 8(100e^{-10,000t}) dt;$$

$$\therefore 76 \times 10^{-3} = -80 \times 10^{-3} e^{-10,000t} \Big|_0^{t_o} = 80 \times 10^{-3} (1 - e^{-10,000t_o});$$

$$\therefore e^{-10,000t_o} = 0.05 \quad \text{so} \quad t_o = 299.57 \mu\text{s};$$

$$\therefore \frac{t_o}{\tau} = \frac{299.57 \times 10^{-6}}{200 \times 10^{-6}} = 1.498 \quad \text{so} \quad t_o \approx 1.498\tau.$$

P 7.22 [a] Calculate the initial voltage drop across the capacitor:

$$v(0) = (2.7\text{ k}\|3.3\text{ k})(40\text{ mA}) = (1485)(40 \times 10^{-3}) = 59.4\text{ V}.$$

The equivalent resistance seen by the capacitor is


$$R_e = 3\text{ k}\|(2.4\text{ k} + 3.6\text{ k}) = 3\text{ k}\|6\text{ k} = 2\text{ k}\Omega;$$

$$\tau = R_e C = (2000)(0.5 \times 10^{-6}) = 1000\text{ }\mu\text{s}; \quad \frac{1}{\tau} = 1000;$$

$$v = v(0)e^{-t/\tau} = 59.4e^{-1000t}\text{ V} \quad t \geq 0.$$


$$[\text{b}] \quad i = \frac{v}{2.4\text{ k} + 3.6\text{ k}} = 9.9e^{-1000t}\text{ mA}, \quad t \geq 0^+.$$

P 7.25 [a]  $t < 0$ :

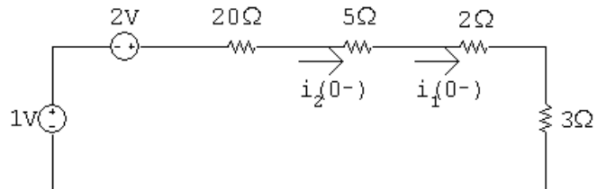

$$i_1(0^-) = i_2(0^-) = \frac{3}{30} = 100 \text{ mA}.$$

[b]  $t > 0$ :

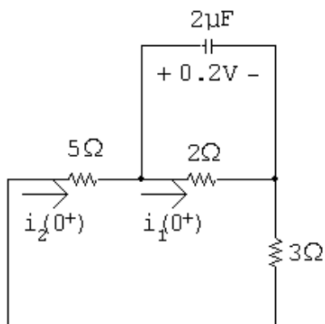

$$i_1(0^+) = \frac{0.2}{2} = 100 \text{ mA};$$

$$i_2(0^+) = \frac{-0.2}{8} = -25 \text{ mA}.$$

[c] Capacitor voltage cannot change instantaneously, therefore,

$$i_1(0^-) = i_1(0^+) = 100 \text{ mA}.$$

[d] Switching can cause an instantaneous change in the current in a resistive branch. In this circuit

$$i_2(0^-) = 100 \text{ mA} \quad \text{and} \quad i_2(0^+) = 25 \text{ mA}.$$

[e]  $v_c = 0.2e^{-t/\tau} \text{ V}, \quad t \geq 0;$


$$\tau = R_e C = 1.6(2 \times 10^{-6}) = 3.2 \mu\text{s}; \quad \frac{1}{\tau} = 312,500;$$

$$v_c = 0.2e^{-312,000t} \text{ V}, \quad t \geq 0;$$

$$i_1 = \frac{v_c}{2} = 0.1e^{-312,000t} \text{ A}, \quad t \geq 0.$$

$$[\text{f}] \quad i_2 = \frac{-v_c}{8} = -25e^{-312,000t} \text{ mA}, \quad t \geq 0^+.$$

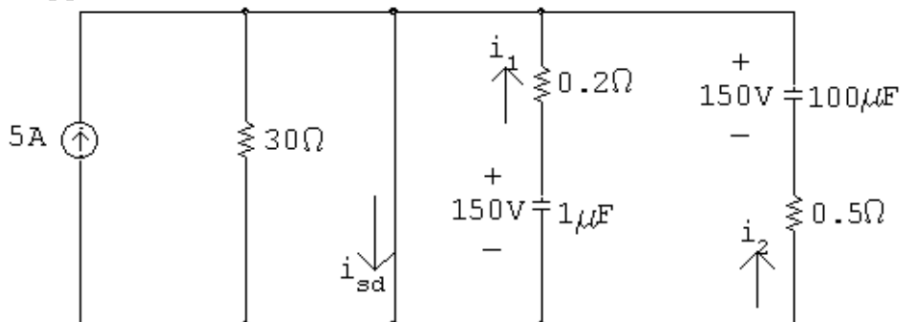P 7.34 [a] At  $t = 0^-$  the voltage on each capacitor will be  $150 \text{ V}(5 \times 30)$ , positive at the upper terminal. Hence at  $t \geq 0^+$  we have



$$\therefore i_{sd}(0^+) = 5 + \frac{150}{0.2} + \frac{150}{0.5} = 1055 \text{ A.}$$

At  $t = \infty$ , both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 5 \text{ A.}$$

[b]  $i_{sd}(t) = 5 + i_1(t) + i_2(t);$

$$\tau_1 = 0.2(10^{-6}) = 0.2 \mu\text{s};$$

$$\tau_2 = 0.5(100 \times 10^{-6}) = 50 \mu\text{s};$$


$$\therefore i_1(t) = 750e^{-5 \times 10^6 t} \text{ A}, \quad t \geq 0^+;$$

$$i_2(t) = 300e^{-20,000 t} \text{ A}, \quad t \geq 0;$$

$$\therefore i_{sd} = 5 + 750e^{-5 \times 10^6 t} + 300e^{-20,000 t} \text{ A}, \quad t \geq 0^+.$$




P 7.38 [a]  $t < 0$ :

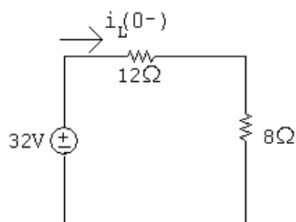

$$i_L(0^-) = \frac{32}{20} = 1.6 \text{ A.}$$

$t > 0$ :

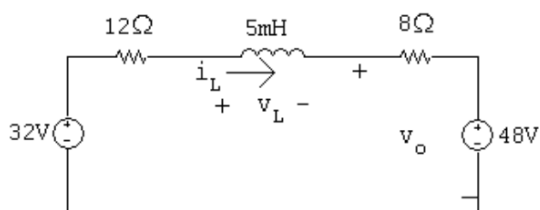

$$i_L(\infty) = \frac{32 - 48}{12 + 8} = -0.8 \text{ A;}$$

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{12 + 8} = 250 \mu\text{s;} \quad \frac{1}{\tau} = 4000;$$

$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -0.8 + (1.6 + 0.8)e^{-4000t} = -0.8 + 2.4e^{-4000t} \text{ A,} \quad t \geq 0.$$


$$v_o = 8i_L + 48 = 8(-0.8 + 2.4e^{-4000t}) + 48 = 41.6 + 19.2e^{-4000t} \text{ V,} \quad t \geq 0.$$

[b]  $v_L = L \frac{di_L}{dt} = 5 \times 10^{-3}(-4000)[2.4e^{-4000t}] = -48e^{-4000t} \text{ V,} \quad t \geq 0^+$

$$v_L(0^+) = -48 \text{ V.}$$

From part (a)  $v_o(0^+) = 0 \text{ V.}$

Check: at  $t = 0^+$  the circuit is:

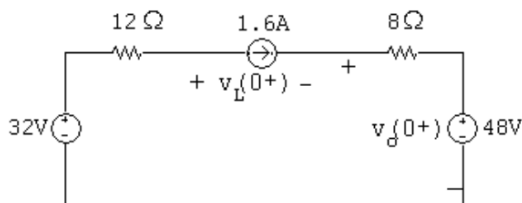

$$v_o(0^+) = 48 + (8 \Omega)(1.6 \text{ A}) = 60.8 \text{ V;} \quad v_L(0^+) + v_o(0^+) = 12(-1.6) + 32;$$

$$\therefore v_L(0^+) = -19.2 + 32 - 60.8 = -48 \text{ V.}$$