

**Question 1 [2]**

Draw out a completed circuit with a voltage source and three resistors in series.

**Question 2 [4]**

Draw out a completed circuit with a voltage source and three resistors in parallel.

**Question 3 [2]**

Choose one: The equivalent resistance of a circuit with resistors in series is larger/smaller than the individual resistors that make up the circuit.

**Question 4 [2]**

Choose one: The equivalent resistance of a circuit with resistors in parallel is larger/smaller than the individual resistors that make up the circuit.