
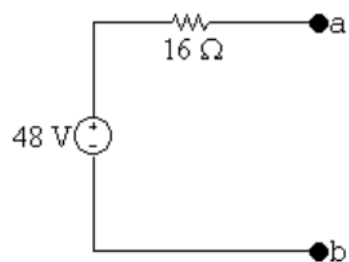


P 4.64 $v_{\text{Th}} = \frac{40}{50}(60) = 48 \text{ V};$
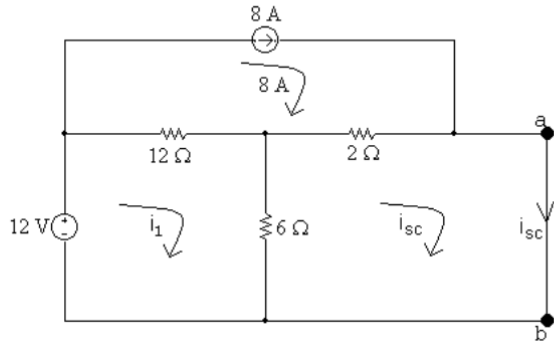
$$R_{\text{Th}} = 8 + 10 \parallel 40 = 16 \, \Omega.$$



P 4.66




$$-12 + 12(i_1 - 8) + 6(i_1 - i_{sc}) = 0;$$


$$2(i_{sc} - 8) + 6(i_{sc} - i_1) = 0.$$

Solving, $i_{sc} = 8.67 \text{ A};$
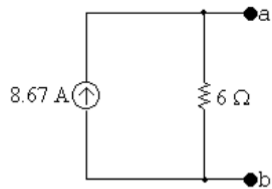
$$R_{Th} = 2 + 12 \parallel 6 = 6 \Omega.$$



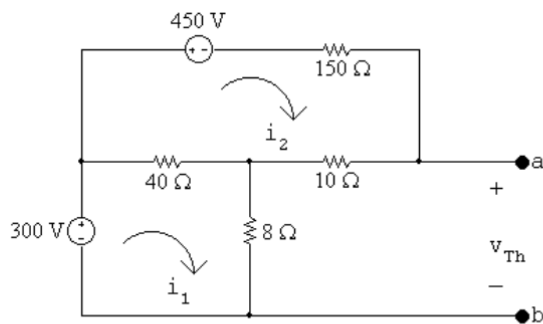P 4.67 After making a source transformation the circuit becomes




$$-300 + 40(i_1 - i_2) + 8i_1 = 0;$$

$$450 + 150i_2 + 10i_2 + 40(i_2 - i_1) = 0.$$




$$\therefore i_1 = 5.25 \text{ A and } i_2 = -1.2 \text{ A}.$$

$$v_{\text{Th}} = 10i_2 + 8i_1 = 30 \text{ V};$$

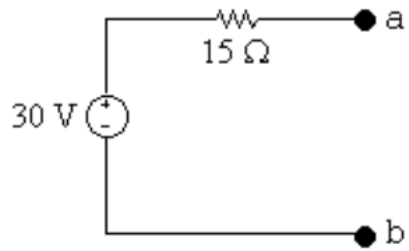
$$R_{\text{Th}} = (40 \parallel 8 + 10) \parallel 150 = 15 \, \Omega.$$



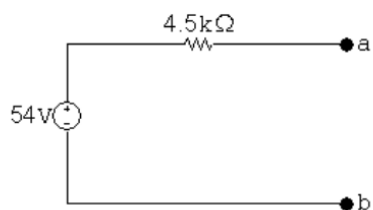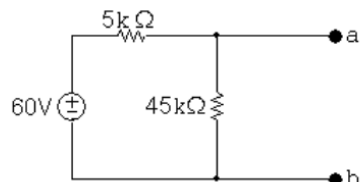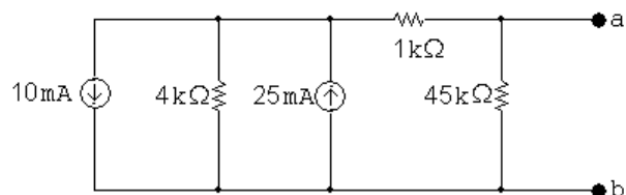P 4.72 [a] First, find the Thévenin equivalent with respect to a,b using a succession of source transformations.



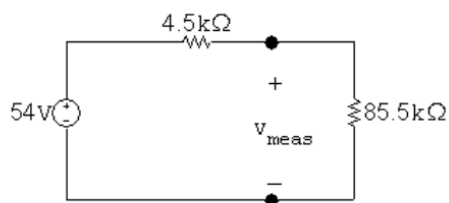
$$\therefore v_{\text{Th}} = 54 \text{ V} \quad R_{\text{Th}} = 4.5 \text{ k}\Omega.$$



$$v_{\text{meas}} = \frac{54}{90}(85.5) = 51.3 \text{ V}.$$

$$\text{[b] \%error} = \left(\frac{51.3 - 54}{54} \right) \times 100 = -5\%.$$

P 4.75

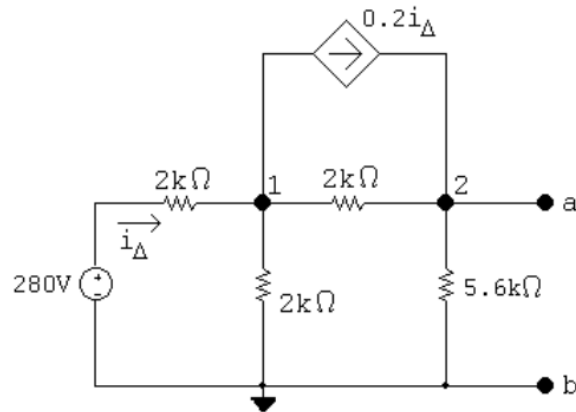

The node voltage equations and dependant source equation are:

$$\frac{v_1 - 280}{2000} + \frac{v_1}{2000} + \frac{v_1 - v_2}{2000} + 0.2i_{\Delta} = 0;$$

$$\frac{v_2 - v_1}{2000} + \frac{v_2}{5600} - 0.2i_{\Delta} = 0;$$

$$i_{\Delta} = \frac{280 - v_1}{2000}.$$

In standard form:


$$v_1 \left(\frac{1}{2000} + \frac{1}{2000} + \frac{1}{2000} \right) + v_2 \left(-\frac{1}{2000} \right) + i_{\Delta}(0.2) = \frac{280}{2000};$$

$$v_1 \left(-\frac{1}{2000} \right) + v_2 \left(\frac{1}{2000} + \frac{1}{5600} \right) + i_{\Delta}(-0.2) = 0;$$

$$v_1 \left(\frac{1}{2000} \right) + v_2(0) + i_{\Delta}(1) = \frac{280}{2000}.$$

Solving, $v_1 = 120 \text{ V}; \quad v_2 = 112 \text{ V}; \quad i_{\Delta} = 0.08 \text{ A}$

$$V_{Th} = v_2 = 112 \text{ V}.$$

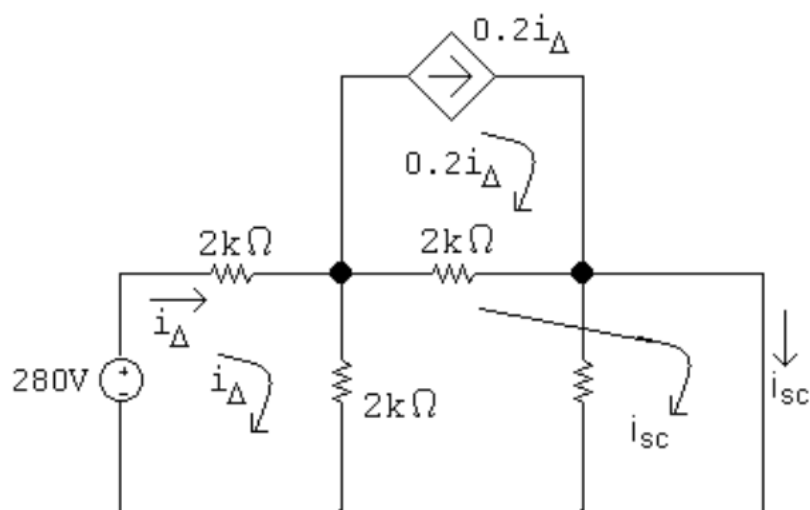

The mesh current equations are:

$$-280 + 2000i_{\Delta} + 2000(i_{\Delta} - i_{sc}) = 0;$$

$$2000(i_{sc} - 0.2i_{\Delta}) + 2000(i_{sc} - i_{\Delta}) = 0.$$


Put these equations in standard form:

$$i_{\Delta}(4000) + i_{sc}(-2000) = 280;$$


$$i_{\Delta}(-2400) + i_{sc}(4000) = 0.$$

Solving, $i_{\Delta} = 0.1 \text{ A}$; $i_{sc} = 0.06 \text{ A}$;
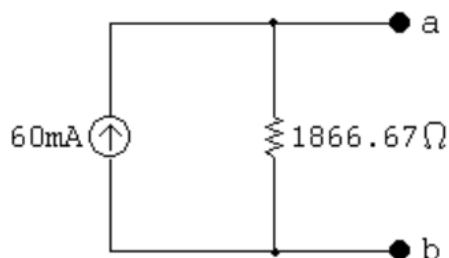
$$R_{Th} = \frac{112}{0.06} = 1866.67 \Omega.$$



P 4.78 [a] Open circuit:

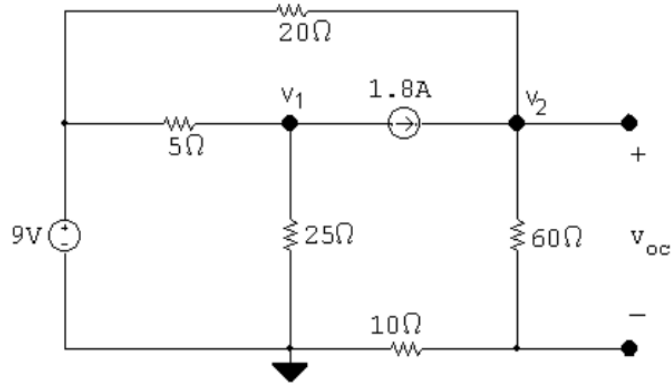


$$\frac{v_2 - 9}{20} + \frac{v_2}{70} - 1.8 = 0;$$

$$v_2 = 35 \text{ V};$$

$$v_{\text{Th}} = \frac{60}{70}v_2 = 30 \text{ V}.$$

Short circuit:

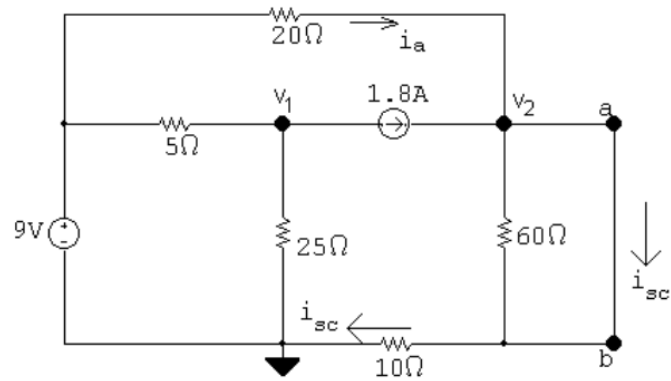

$$\frac{v_2 - 9}{20} + \frac{v_2}{10} - 1.8 = 0;$$


$$\therefore v_2 = 15 \text{ V}.$$

$$i_a = \frac{9 - 15}{20} = -0.3 \text{ A};$$

$$i_{\text{sc}} = 1.8 - 0.3 = 1.5 \text{ A};$$


$$R_{\text{Th}} = \frac{30}{1.5} = 20 \Omega.$$

[b]

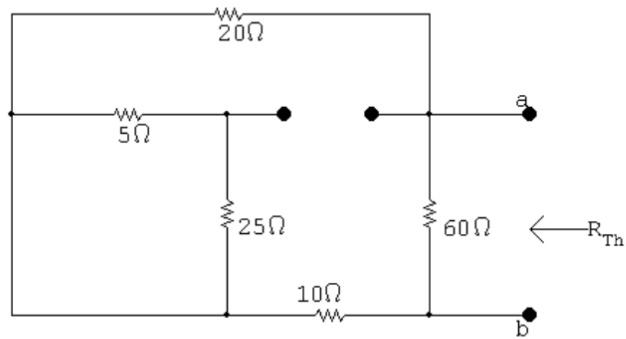

$$R_{Th} = (20 + 10) \parallel 60 = 20 \, \Omega \text{ (CHECKS).}$$

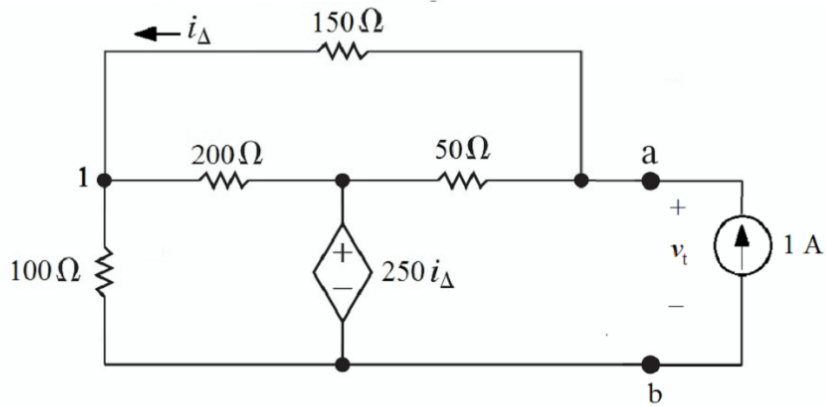P 4.79 $V_{Th} = 0$, since circuit contains no independent sources.



$$\frac{v_1}{100} + \frac{v_1 - 250i_\Delta}{200} + \frac{v_1 - v_t}{150} = 0;$$

$$\frac{v_t - v_1}{150} + \frac{v_t - 250i_\Delta}{50} - 1 = 0;$$

$$i_\Delta = \frac{v_t - v_1}{150}.$$


In standard form:

$$v_1 \left(\frac{1}{100} + \frac{1}{200} + \frac{1}{150} \right) + v_t \left(-\frac{1}{150} \right) + i_\Delta \left(-\frac{250}{200} \right) = 0;$$

$$v_1 \left(-\frac{1}{150} \right) + v_t \left(\frac{1}{150} + \frac{1}{50} \right) + i_\Delta \left(-\frac{250}{50} \right) = 1;$$

$$v_1 \left(-\frac{1}{150} \right) + v_t \left(\frac{1}{150} \right) + i_\Delta (-1) = 0.$$


P 4.82 [a]

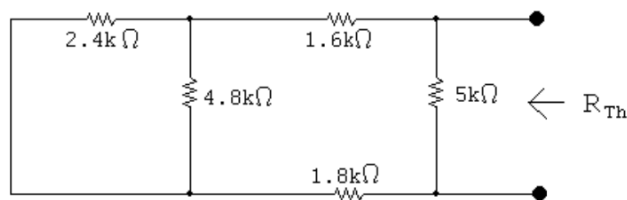

$$R_{Th} = 5000 \parallel (1600 + 2400 \parallel 4800 + 1800) = 2.5 \text{ k}\Omega;$$

$$R_o = R_{Th} = 2.5 \text{ k}\Omega.$$

[b]

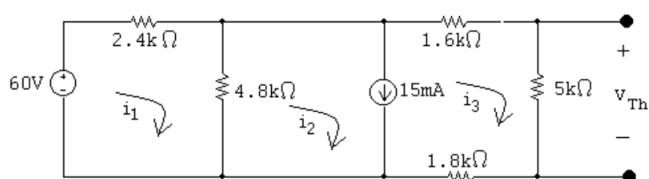

$$7200i_1 - 4800i_2 = 60;$$


$$-4800i_1 + 4800i_2 + 8400i_3 = 0;$$

$$i_2 - i_3 = 0.015.$$

Solving,

$$i_1 = 19.4 \text{ mA}; \quad i_2 = 16.6 \text{ mA}; \quad i_3 = 1.6 \text{ mA};$$

$$v_{oc} = 5000i_3 = 8 \text{ V}.$$

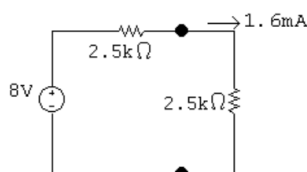

$$p_{\max} = (1.6 \times 10^{-3})^2 (2500) = 6.4 \text{ mW}.$$

[c] The resistor closest to $2.5 \text{ k}\Omega$ from Appendix H has a value of $2.7 \text{ k}\Omega$. Use voltage division to find the voltage drop across this load resistor, and use the voltage to find the power delivered to it:


$$v_{2.7k} = \frac{2700}{2700 + 2500}(8) = 4.154 \text{ V};$$

$$p_{2.7k} = \frac{(4.154)^2}{2700} = 6.391 \text{ mW}.$$

The percent error between the maximum power and the power delivered to the best resistor from Appendix H is

$$\% \text{ error} = \left(\frac{6.391}{6.4} - 1 \right) (100) = -0.1\%.$$

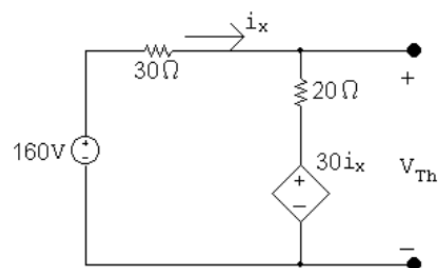
P 4.87 We begin by finding the Thévenin equivalent with respect to R_o . After making a couple of source transformations the circuit simplifies to



$$i_{\Delta} = \frac{160 - 30i_{\Delta}}{50}; \quad i_{\Delta} = 2 \text{ A};$$

$$V_{Th} = 20i_{\Delta} + 30i_{\Delta} = 50i_{\Delta} = 100 \text{ V}.$$

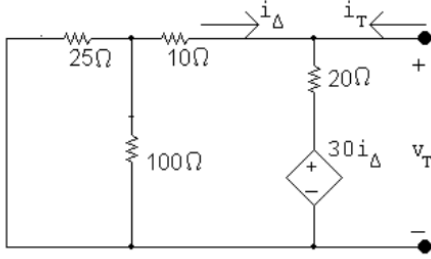Using the test-source method to find the Thévenin resistance gives




$$i_T = \frac{v_T}{30} + \frac{v_T - 30(-v_T/30)}{20};$$

$$\frac{i_T}{v_T} = \frac{1}{30} + \frac{1}{10} = \frac{4}{30} = \frac{2}{15};$$

$$R_{Th} = \frac{v_T}{i_T} = \frac{15}{2} = 7.5 \Omega.$$

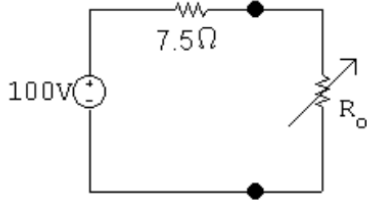Thus our problem is reduced to analyzing the circuit shown below:



$$p = \left(\frac{100}{7.5 + R_o} \right)^2 R_o = 250;$$

$$\frac{10^4}{R_o^2 + 15R_o + 56.25} R_o = 250;$$

$$\frac{10^4 R_o}{250} = R_o^2 + 15R_o + 56.25;$$

$$40R_o = R_o^2 + 15R_o + 56.25;$$

$$R_o^2 - 25R_o + 56.25 = 0;$$

$$R_o = 12.5 \pm \sqrt{156.25 - 56.25} = 12.5 \pm 10;$$

$$R_o = 22.5 \Omega;$$

$$R_o = 2.5 \Omega.$$

