

ECE 203

Circuits I

Kirchoff's Laws

Lecture 2-2

Some Definitions

- 1) **Node**- A point of connection between any two or more circuit elements
- 2) **Loop**- A closed path through a circuit, but only traversing any given node once
- 3) **Branch**- a part of a circuit containing one circuit element

Go to example 2-2.1

Kirchoff's Current Law

The sum of all currents entering a node equals zero.

Basically a statement of conservation of charge.

So, put another way, whatever current enters a node also has to leave the node.

Kirchoff's Current Law = KCL

- A very powerful analytic tool for studying circuits
- For some examples, go to [Example 2-2.2](#)

Kirchoff's Voltage Law = KVL

- The sum of the voltages around any loop is zero
- A manifestation of energy conservation
- For some examples for to Example 2-2.3

Voltage Notation

Some examples of how voltages are denoted in circuit diagrams







