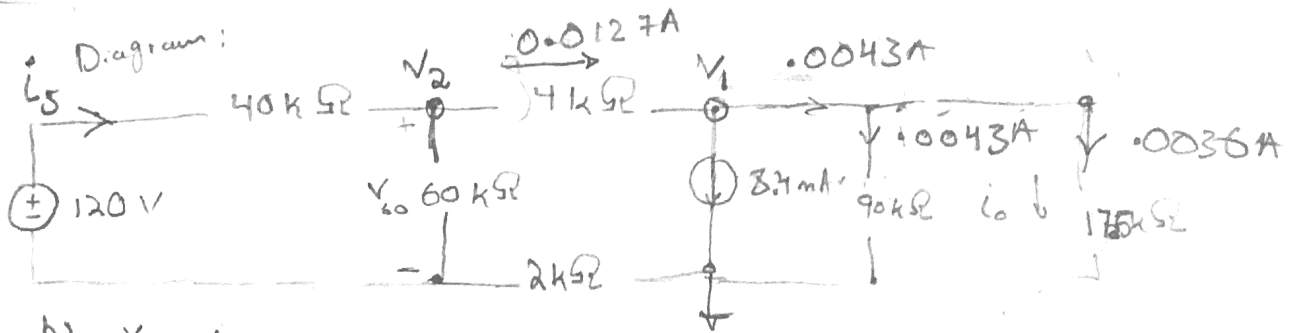


# Problem # 1

Abdul Popal






H.W. 9

Given :





Find: a)  $i_0$  b)  $V_1$ ,  $i_{90}$ ,  $i_4$ ,  $V_2$ ,  $i_s$

Solution: a)

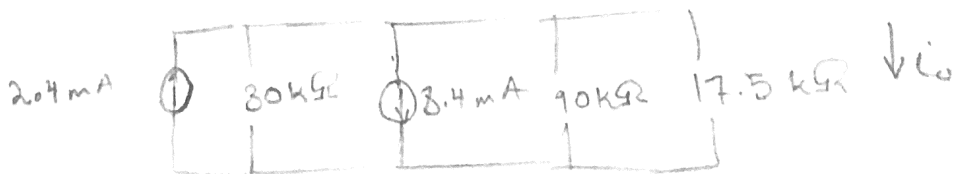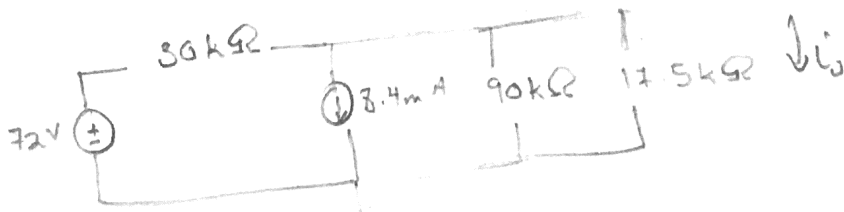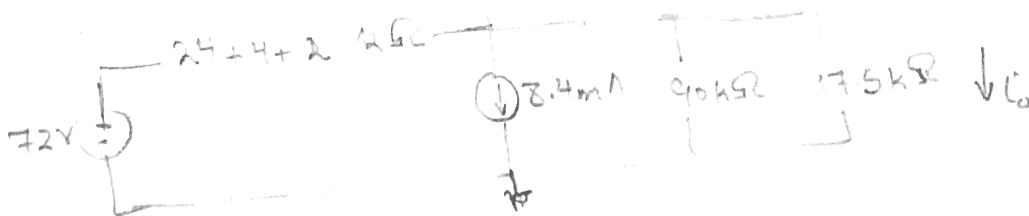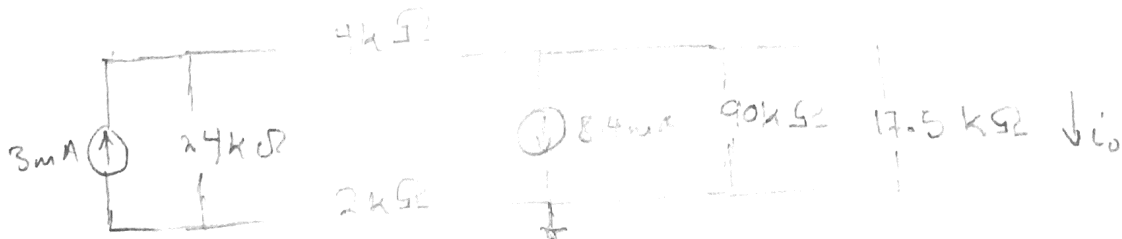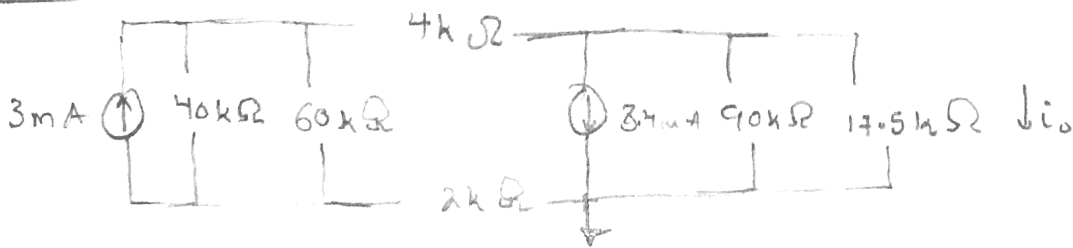

\* voltages are the same across branches

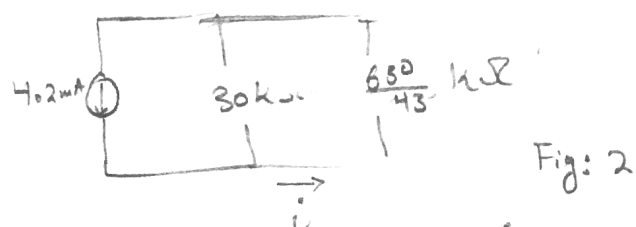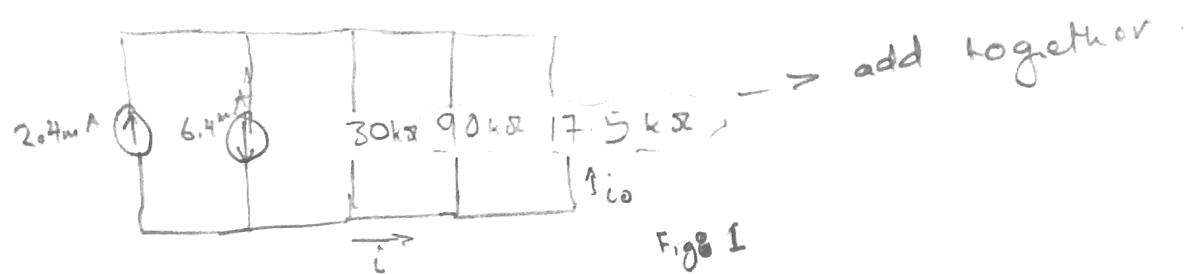

\* using current division:

$$i = \frac{9.84375}{\frac{630}{43}} (4.2 \times 10^{-3} \text{ A}) = 0.0043 \text{ A} \quad \text{using Fig 2.}$$

$$i_o = \frac{630/43}{17.5} (0.0043 \text{ A}) = \underline{\underline{0.0036 \text{ A}}} \quad \text{using Fig 1.}$$

$$b) V_1 = V_{90} = V_{17.5} = 17.5 \text{ k}\Omega (0.0036 \text{ A}) = \underline{\underline{63 \text{ V}}}$$

$$i_{90} = i - i_o = (0.0043 - 0.0036) \text{ A}$$

$$i_{90} = \underline{\underline{0.7 \text{ mA}}}$$

Using Initial Diagram:

$$-i_4 + 0.0043 \text{ A} + 0.0036 \text{ A} = 0$$

$$i_4 = \underline{\underline{0.0127 \text{ A}}}$$

$$\text{Node 2: } \frac{-(120 - V_2)}{40 \text{ k}\Omega} + 0.0127 \text{ A} + \frac{V_2}{60 \text{ k}\Omega} = 0$$

$$\frac{V_2 - 120}{40 \text{ k}\Omega} + \frac{V_2}{60 \text{ k}\Omega} = -0.0127$$

$$60,000(V_2 - 120) + 40,000 V_2 = -0.0127$$

$$60,000 V_2 - 60,000(120) + 40,000 V_2 = -0.0127$$

$$V_2 (100,000) = 60,000(120) - 0.0127$$


$$V_2 = \underline{\underline{72 \text{ V}}} = V_{60}$$

$$\text{KCL(2): } -i_8 + 0.0127 \text{ A} + 0.0012 \text{ A} = 0$$

$$i_8 = 0.0139 \text{ A} \text{ or } \underline{\underline{13.9 \text{ mA}}}$$


## Problem # 2

Given:

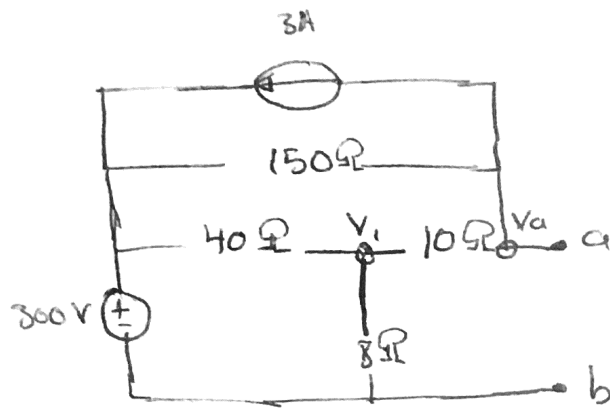

Find:  $R_{TH}$ ,  $V_{TH}$

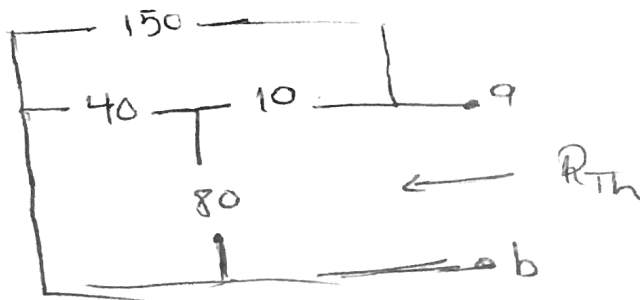Solution: ○ open circuit for current.  
○ short circuit for voltage.



$$\begin{aligned} R_{TH} &= 150 \parallel \{ 10 + (40 \parallel 3) \} \\ &= 150 \parallel \left\{ \frac{50}{3} \right\} \\ &= \underline{\underline{15 \Omega}} \end{aligned}$$

Node(1);  $\frac{V_1 - 300}{40} + \frac{V_1 - V_a}{10} + \frac{V_1}{3} = 0 \quad \dots (1)$

$$50 V_1 - 20 V_a = 1500$$


$3A + \frac{V_a - 300}{150} + \frac{V_a - V_1}{10} = 0 \quad \dots (2)$

$$-15 V_1 + 16 V_a = -150$$

Using Matrices:  $V_1 = 42V$   
 $V_a = 30V$

$$\begin{aligned} V_{TH} &= V_a - V_b \\ &= 30 - 0 = \underline{\underline{30V}} \end{aligned}$$

Problem #3  
(Given)

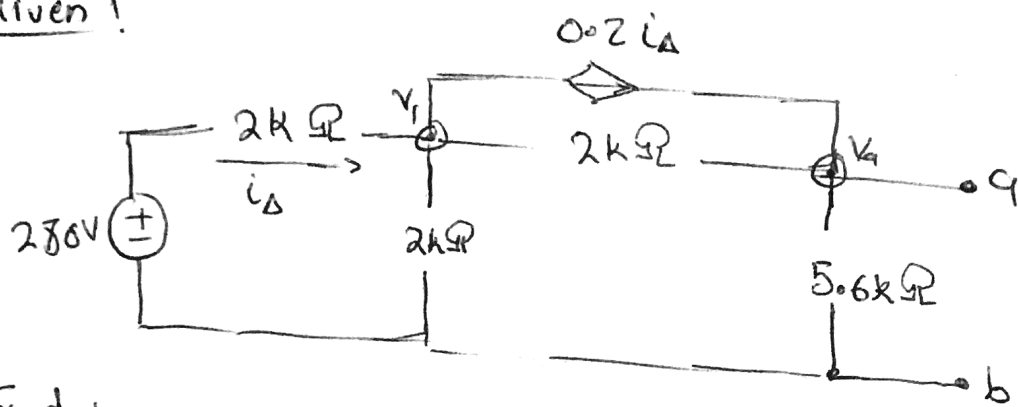

Find Norton equivalent for the following circuit.

Solution;

$$\frac{V_1 - 280}{2000} + \frac{V_1}{2000} + \frac{V_1 - V_a}{2000} + 0.2 i_\Delta = 0 \quad \dots (1)$$

$$3V_1 - V_a + 400 i_\Delta = 280 \quad \dots (1)$$

$$-0.2 i_\Delta + \frac{V_a - V_1}{2000} + \frac{V_a}{5600} = 0 \quad \dots (2)$$

$$-14V_1 + 19V_a - 5600 i_\Delta = 0 \quad \dots (2)$$


$$2000 i_\Delta = 280 - V_1 \quad \dots (3)$$

$$V_1 + 0V_a + 2000 i_\Delta = 280 \quad \dots (3)$$

using calculator :  $V_1 = 120V$ ,  $V_a = 112V$ ,  $i_\Delta = 0.08A$

$$V_{Th} = V_a - V_b = 112 - 0 = \underline{\underline{112V}}$$

Problem #3 cont.  $0.2 i_A$

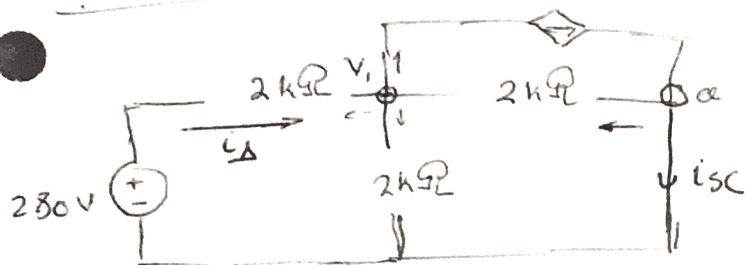

Node ( $V_1$ ):

$$\frac{V_1 - 280}{2000} + \frac{V_1}{2000} + 0.2 i_A + \frac{V_1}{2000} = 0$$

$$\frac{3V_1}{2000} = \frac{280}{2000} - 0.2 i_A \quad \dots (4)$$

$$i_A = \frac{V_1 - 280}{2000} \quad \dots (5) \text{ using } \text{Constraint} \cdot \text{KCL @ } \text{a}$$

$$V_1 = 80V, \quad i_A = 0.1A$$

$$-0.2 i_A - \frac{V_1}{2000} + i_{SC} = 0$$


$$i_{SC} = \frac{V_1}{2000} + 0.2 i_A \quad \dots (6)$$

$$i_{SC} = I_N = \underline{\underline{60mA}}$$

$$R_N = \frac{V_{TH}}{I_N} = \frac{112}{0.06} = \underline{\underline{1.867k\Omega}}$$

# Problem # 4

Given:

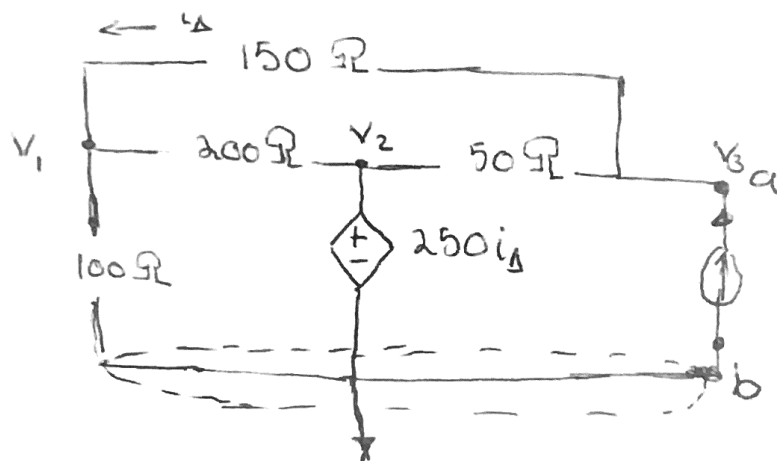

Find:  $R_{TH} = ?$

Solution: since no independent source is contained within the circuit therefore  $V_{TH} = 0$

→ To find  $R_{TH}$  we put a 1A independent source —

$$V_2 = 250 i_{\Delta} \quad \dots (1)$$

$$\frac{V_1}{100} + \frac{V_1 - 250 i_{\Delta}}{200} + \frac{V_1 - V_3}{150} = 0 \quad \dots (2)$$

$$18V_1 - 4V_3 - 750 i_{\Delta} = 0 \quad \dots (2)$$

$$\frac{V_3 - V_1}{150} + \frac{V_3 - V_2}{50} - 1 = 0 \quad \dots (3)$$

$$-V_1 + 4V_3 - 750 i_{\Delta} = 150 \quad \dots (3)$$

~~sub~~  $i_{\Delta} = \frac{V_3 - V_1}{150} \quad \dots (4) \quad \therefore \text{Sub (4) in (2), (3)}$


$$18V_1 - 9V_3 = 0 \rightarrow V_1 = \frac{V_3}{2}$$

$$4V_1 - V_3 = 150$$

$$V_3 = 150V \therefore R_{TH} = \frac{150V}{1A} = 150\Omega$$

# Problem # 5


Given

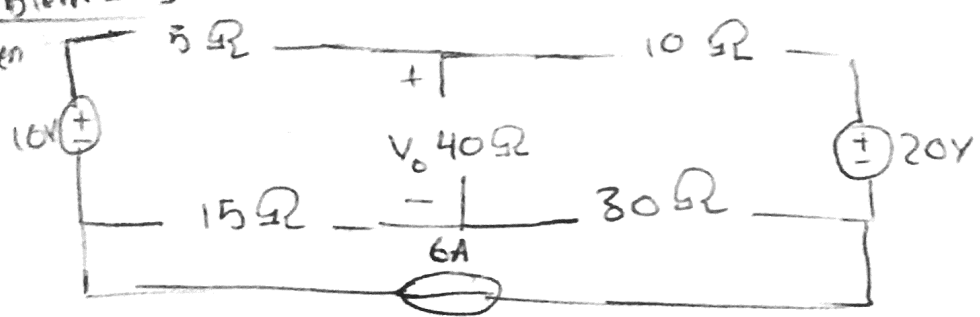

Find:  $V_o$  using principle of super position -

Solution :-

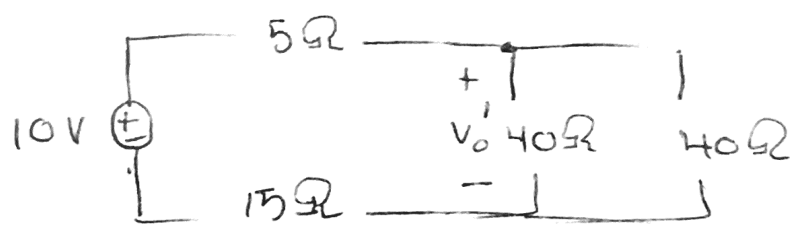
a) \* Deactivate 20V by short circuit and 6A source by open circuit




\* using voltage divider -

$$V_o' = \frac{40\Omega}{(20 + 5 + 15)\Omega} \times 10V = 5V$$

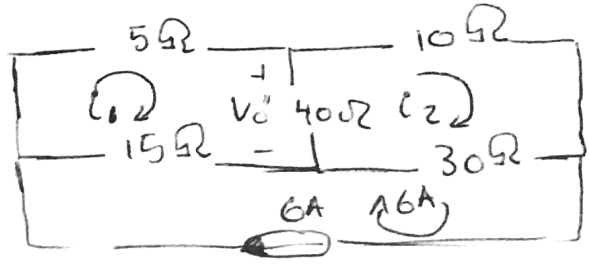b) \* Deactivate 20V source, 10V voltage source



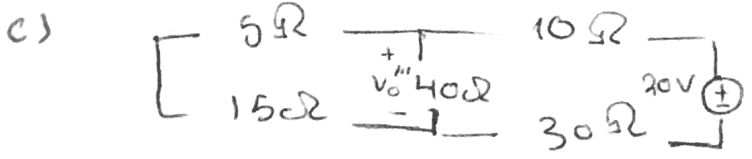mesh(1):  
 $60i_1 - 40i_2 = 90 \dots (1)$   
 mesh(2):  
 $-40i_1 + 80i_2 = 180 \dots (2)$   
 Eq (1) and (2):  $i_1 = 4.5A$   
 $i_2 = 4.5A$



therefore:  $V_o'' = 0$

$$V_o''' = \frac{20 \parallel 40}{(20 \parallel 40) + 40} (20V) = 5V$$

$$V_o = V_o' + V_o'' + V_o''' = 10V$$