

9.1 Consider the sinusoidal voltage

$$v(t) = 40 \cos(100\pi t + 60^\circ) \text{ V.}$$

- What is the maximum amplitude of the voltage?
- What is the frequency in hertz?
- What is the frequency in radians per second?
- What is the phase angle in radians?
- What is the phase angle in degrees?
- What is the period in milliseconds?
- What is the first time after  $t = 0$  that  $v = -40 \text{ V}$ ?
- The sinusoidal function is shifted  $10/3 \text{ ms}$  to the right along the time axis. What is the expression for  $v(t)$ ?
- What is the minimum number of milliseconds that the function must be shifted to the left if the expression for  $v(t)$  is  $40 \sin 100\pi t \text{ V}$ ?

a)  $\boxed{\text{Max amplitude: } 40 \text{ V}}$

b)  $2\pi f = 100\pi \Rightarrow \boxed{f = 50 \text{ Hz}}$

c)  $\boxed{\omega = 100\pi = 314.159 \text{ rad/s}}$

d)  $60 \times \frac{\pi}{180} = \boxed{1.05 \text{ rad} = \theta}$

e)  $\boxed{\theta = 60^\circ}$

f)  $\boxed{T = \frac{1}{f} = 20 \text{ ms}}$

g)  $\cos(\pi) = -1$

$$100\pi t + \frac{\pi}{3} = \pi$$

$$\boxed{t = 6.67 \text{ ms}}$$

h)  $v = 40 \cos\left[100\pi\left(t - \frac{0.01}{3}\right) + \frac{\pi}{3}\right]$

$$\boxed{v = 40 \cos[100\pi t] \text{ V}}$$

i)  $100\pi(t - t_0) + \frac{\pi}{3} = 100\pi t + \left(\frac{3\pi}{2}\right)$

$$100\pi t_0 = \frac{7\pi}{6}$$

$$\boxed{t_0 = 11.67 \text{ ms}}$$

9.5 A sinusoidal voltage is zero at  $t = (-2\pi/3) \text{ ms}$  and increasing at a rate of  $80,000 \text{ V/s}$ . The maximum amplitude of the voltage is  $80 \text{ V}$ .

- What is the frequency of  $v$  in radians per second?
- What is the expression for  $v$ ?

$$v(t) = 80 \cos(\omega t + \theta)$$

$$\frac{dv}{dt} = -80\omega \sin(\omega t + \theta)$$

$$80\omega = 80000$$

a)  $\boxed{\omega = 1000 \text{ rad/s}}$


b)  $f = \frac{\omega}{2\pi} = 159.16 \text{ Hz}, T = \frac{1}{159.16} = 6.28 \text{ ms}$

$$\frac{-2\pi/3}{6.28} = -0.334 \quad \theta = 120 - 90 = 30^\circ$$

$$\boxed{v(t) = 80 \cos(1000t + 30^\circ) \text{ V}}$$

9.8 Find the rms value of the half-wave rectified sinusoidal voltage shown in Fig. P9.8.

Figure P9.8

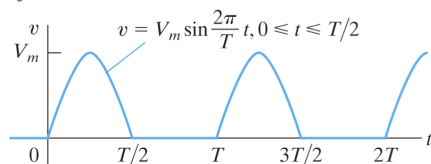

$$\int_0^{T/2} V_m^2 \sin^2\left(\frac{2\pi}{T}t\right) dt = \frac{V_m^2}{2} \int_0^{T/2} (1 - \cos\frac{4\pi}{T}t) dt$$

$$= \frac{V_m^2}{2} \left(\frac{T}{2}\right)$$

$$V_{rms} = \sqrt{\frac{1}{T} \cdot \frac{V_m^2 T}{4}} \Rightarrow \boxed{V_{rms} = \frac{V_m}{2}}$$

9.13 A 400 Hz sinusoidal voltage with a maximum amplitude of 100 V at  $t = 0$  is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 20 A.

- What is the frequency of the inductor current?
- If the phase angle of the voltage is zero, what is the phase angle of the current?
- What is the inductive reactance of the inductor?
- What is the inductance of the inductor in millihenrys?
- What is the impedance of the inductor?

$$c) \boxed{400 \text{ Hz}}$$

$$b) I = \frac{100}{j\omega L} \angle 0^\circ = \frac{100}{\omega L} \angle -90^\circ$$

$$\boxed{\theta = -90^\circ}$$

$$c) \frac{100}{\omega L} = 20 \quad \boxed{\omega L = 5 \Omega}$$

$$d) L = \frac{5}{2f\pi} = \frac{5}{800\pi}$$

$$\boxed{L = 1.99 \text{ mH}}$$

$$e) \boxed{Z_L = j\omega L = j 5 \Omega}$$


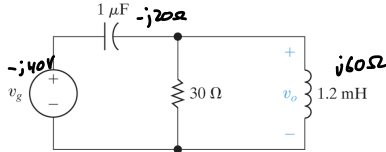
9.28  The circuit in Fig. P9.28 is operating in the sinusoidal steady state. Find the steady-state expression for  $v_o(t)$  if  $v_g = 40 \sin 50,000t$  V.

Figure P9.28



$$V_g = 40 \angle -90^\circ = -j40 \text{ V}$$

$$\frac{1}{j\omega L} = \frac{1}{j(10^5)(50 \times 10^{-3})} = -j20 \Omega$$

$$j\omega L = j(50 \times 10^3)(1.2 \times 10^{-3}) = j60 \Omega$$

$$Z_o = -j20 + 30 \parallel j60 = 24 - j8 \Omega$$

$$I_g = \frac{-j40}{24 - j8} = 0.5 - j1.5 \text{ A}$$


$$V_o = \frac{30 \angle j60}{30 + j60} (0.5 - j1.5) = 30 - j30$$

$$V_o = 42.43 \angle -45^\circ \text{ V}$$

$$\boxed{v_o(t) = 42.43 \cos(50,000t - 45^\circ) \text{ V}}$$

9.29  Find the steady-state expression for  $i_o(t)$  in the circuit in Fig. P9.29 if  $v_s = 100 \sin 50t$  mV.

Figure P9.29

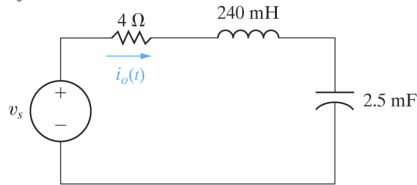

$$Z = 4 + j\omega L + \frac{1}{j\omega C}$$


$$= 4 + j50(0.24) - \frac{j}{50 \times 2.5 \times 10^{-3}}$$

$$= 5.66 \angle 45^\circ \Omega$$

$$I_o = \frac{V}{Z} = \frac{0.1 \angle -90^\circ}{5.66 \angle 45^\circ} = 17.67 \angle -135^\circ \text{ mA}$$

$$\boxed{i_o(t) = 17.67 \cos(50t - 135^\circ) \text{ mA}}$$

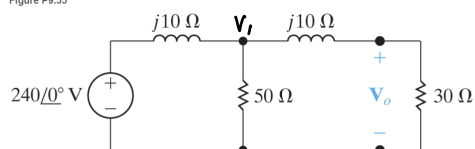9.55 Use the node-voltage method to find  $V_o$  in the circuit in Fig. P9.55.   
 Figure P9.55




$$\frac{V_1 - 240}{j10} + \frac{V_1}{50} + \frac{V_1}{30 + j10} = 0$$

$$(V_1 - 240)(50)(30 + j10) + V_1(j10)(30 + j10) + V_1(50)(j10) = 0$$

$$V_1 = 199.63 \angle -24.44^\circ \text{ V}$$

$$V_o = \frac{30}{30 + j10} V_1 = 188.43 \angle -42.68^\circ \text{ V}$$

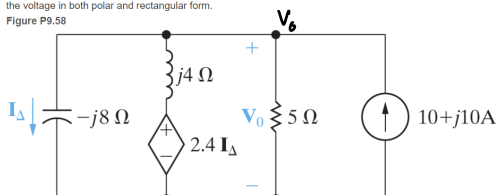9.58 Use the node-voltage method to find the phasor voltage  $V_o$  in the circuit shown in Fig. P9.58. Express the voltage in both polar and rectangular form.   
 Figure P9.58



$$\frac{V_o}{-j8} + \frac{V_o - 2.4 I_\Delta}{j4} + \frac{V_o}{5} - (10 + j10) = 0$$

$$\frac{V_o}{-j8} + \frac{V_o - 2.4 \left( \frac{V_o}{-j8} \right)}{j4} + \frac{V_o}{5} = 10 + j10$$


$$\frac{V_o}{-j8} + \frac{V_o - 0.3 j V_o}{j4} + \frac{V_o}{5} = 10 + j10$$

$$V_o \left[ -\frac{1}{j8} + \frac{1}{j4} - \frac{j0.3}{j4} + \frac{1}{5} \right] = 10 + j10$$

$$V_o = \frac{10 + j10}{0.125 - 0.125j} = 80j \text{ V}$$

$$V_o = 80 \angle 90^\circ \text{ V}$$

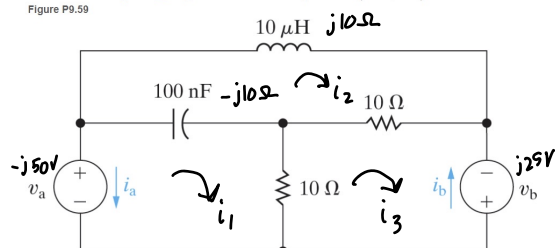9.59 **PSPICE MULTISIM** Use the mesh-current method to find the steady-state expression for the branch currents  $i_a$  and  $i_b$  in the circuit seen in Fig. P9.59 if  $v_a = 50 \sin 10^6 t \text{ V}$  and  $v_b = 25 \cos(10^6 t + 90^\circ) \text{ V}$ .   
 Figure P9.59



$$V_a = 50 \angle -90^\circ = -j50 \text{ V}$$

$$V_b = 25 \angle 90^\circ = j25 \text{ V}$$

$$\frac{1}{j\omega C} = \frac{-j}{(10^6)(0.1 \times 10^{-6})} = -j10 \Omega$$

$$j\omega L = j10^6(10 \times 10^{-6}) = j10 \Omega$$

$$(1) j10 i_1 + 10 i_2 - 10 i_3 = 0$$

$$(2) (10 - j10) i_1 + j10 i_2 - 10 i_3 = -j50$$

$$(3) -10 i_1 - 10 i_2 + 20 i_3 = j25$$

Solving for  $i_1$  and  $i_3$

$$i_1 = 0.5 - j1.5 \text{ A} \quad i_3 = -1 + j0.5 \text{ A}$$


$$i_a = -i_1 = -0.5 + j1.5 = 1.58 \angle 108.43^\circ$$

$$i_b = -i_3 = 1 - j0.5 = 1.12 \angle -26.57^\circ$$

$$i_a = 1.58 \cos(10^6 t + 108.43^\circ) \text{ A}$$

$$i_b = 1.12 \cos(10^6 t - 26.57^\circ) \text{ A}$$

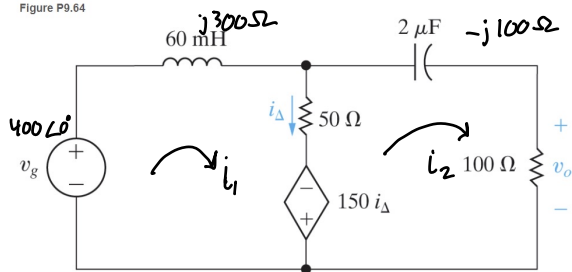9.64 PSpice MULTISIM Use the mesh-current method to find the steady-state expression for  $v_o$  in the circuit seen in Fig. P9.64. If  $v_g$  equals  $400 \cos 5000t$  V.  
Figure P9.64



$$-400 + (50 + j300)i_1 - 50i_2 - 150(i_1 - i_2) = 0$$

$$(150 - j100)i_2 - 50i_1 + 150(i_1 - i_2) = 0$$

Solving

$$i_1 = -0.8 + j.6 \text{ A} , i_2 = -1.6 + j0.8 \text{ A}$$

$$V_o = 100i_2 = -160 + j80 = 178.89 \angle 153.43^\circ$$

$$V_o = 178.89 \cos(5000t + 153.43^\circ) \text{ V}$$