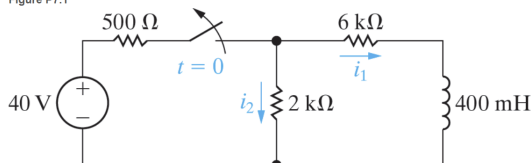


7.1 **PROBLEM** The switch in the circuit in Fig. P 7.1 has been closed for a long time before opening at  $t = 0$ .  
Figure P7.1



- Find  $i_1(0^-)$  and  $i_2(0^-)$ .
- Find  $i_1(0^+)$  and  $i_2(0^+)$ .
- Find  $i_1(t)$  for  $t \geq 0$ .
- Find  $i_2(t)$  for  $t \geq 0^+$ .
- Explain why  $i_2(0^-) \neq i_2(0^+)$ .

$$a) \begin{cases} i_1(0^-) = \frac{2k}{2k+6k} (20mA) = 5mA \\ i_2(0^-) = \frac{6k}{2k+6k} (20mA) = 15mA \end{cases}$$


$$b) \begin{cases} i_1(0^+) = i_1(0^-) = 5mA \\ i_2(0^+) = -i_1(0^+) = -5mA \end{cases}$$

$$c) \tau = \frac{L}{R} = \frac{400mH}{8k\Omega}$$

$$\tau = 5 \times 10^{-5} \text{ sec}$$

$$i_1(t) = 5e^{-\frac{t}{5 \times 10^{-5}}} \text{ mA}$$

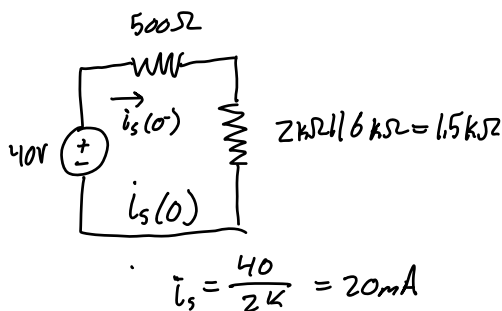
$$i_2(t) = 5e^{-\frac{t}{5 \times 10^{-5}}} \text{ mA}$$




$$d) \begin{cases} i_2(t) = -i_1(t) \\ i_2(t) = -5e^{-(20k)t} \text{ mA} \end{cases}$$

e) When the switch opens the current in the resistor changes instantly. before the switch opens  $i_2(0^-) = 15mA$  but after  $i_2(0^+) = -5mA$

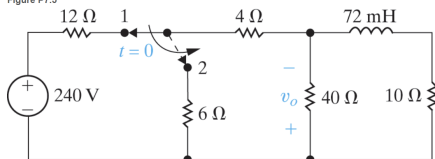7.5 **PROBLEM** The switch in the circuit in Fig. P 7.5 has been in position 1 for a long time. At  $t = 0$ , the switch moves instantaneously to position 2. Find  $v_o(t)$  for  $t \geq 0^+$ .  
Figure P7.5



for  $t < 0$

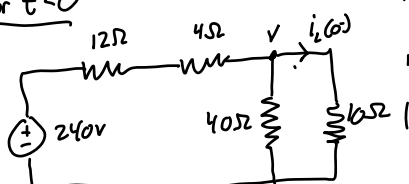


$$\frac{v-240}{16} + \frac{v}{40} + \frac{v}{10} = 0$$

$$v = 80V$$


$$i_2(0^+) = \frac{80}{10} = 8A$$

for  $t = 0$

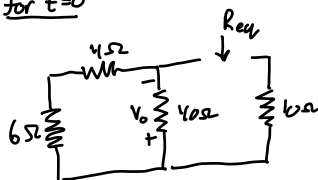

$$R_{eq} = (6+4) \parallel 40 + 10 = 18\Omega$$
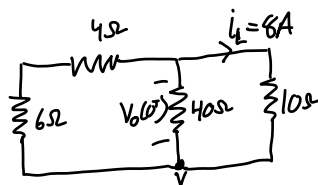
$$\tau = \frac{L}{R} = \frac{72mH}{18\Omega} = 4ms$$



KCL


$$\frac{V_o}{10} + \frac{V_o}{40} = 8A$$

$$V_o(0^+) = 64V$$


$$V_o = V_o(0^+) e^{-t/\tau}$$

$$V_o = 64 e^{-\frac{t}{4ms}} V$$

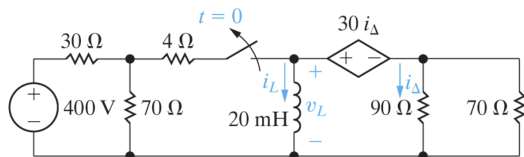7.15 The switch in Fig. P 7.15 has been closed for a long time before opening at  $t = 0$ . Find Figure P7.15



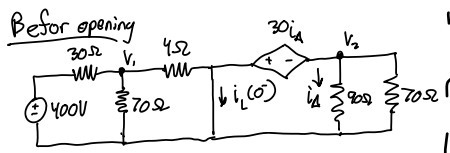- a)  $i_L(t)$ ,  $t \geq 0$ .  
b)  $v_L(t)$ ,  $t \geq 0^+$ .  
c)  $i_A(t)$ ,  $t \geq 0^+$ .



$$\frac{V_1 - 400}{30} + \frac{V_1}{70} + \frac{V_1}{4} = 0$$

$$14(V_1 - 400) + 6V_1 + 105V_1 = 0$$

$$125V_1 = 5600$$

$$V_1 = 44.8V$$


KVL

$$0 - 30i_A - 90i_A = 0$$

$$i_A = 0$$

$$a) \therefore i_L(t) = \frac{V_1}{4} = 11.2A$$

Switch open

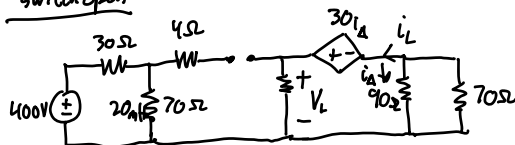

KVL

$$V_L - 30i_A - 90i_A = 0$$

$$V_L = 120i_A = L \frac{di_L}{dt} \quad \text{--- (1)}$$

$$i_L + i_A + \frac{90i_A}{70} = 0$$

$$i_A = \frac{-i_L}{2.78}$$

F(s) = 0

$$20 \times 10^{-3} s + 52.63 = 0$$

$$s = -2.6 \times 10^3$$

$$\therefore i_L = i_L(0^-) e^{-2.6 \times 10^3 t}$$

$$i_A(t) = \frac{-i_L(t)}{2.78} = \frac{11.2 \times e^{-2.6 \times 10^3 t}}{2.78}$$

$$c) \boxed{i_A(t) = -4.91 \times e^{-2.6 \times 10^3 t} A}$$

from (1)

$$20 \times 10^{-3} \frac{di_L}{dt} = 120 \frac{-i_L}{2.78}$$


$$(20 \times 10^{-3} + 52.63) i_A = 0$$

$$V_L(t) = L \frac{di_L(t)}{dt} = 20 \times 10^{-3} \frac{d}{dt} (11.2 \times e^{-2.6 \times 10^3 t})$$

$$V_L(t) = 20 \times 10^{-3} \times 11.2 \times e^{-2.6 \times 10^3 t} \times (-2.6 \times 10^3)$$


$$b) \boxed{V_L(t) = -582.4 e^{-2.6 \times 10^3 t} V}$$

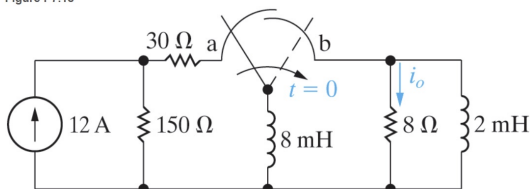7.18 PROBLEM In the circuit shown in Fig. P 7.18, the switch has been in position a for a long time. At  $t = 0$ , it moves instantaneously from a to b. Figure P7.18




- a) Find  $i_o(t)$  for  $t \geq 0$ .

before opening

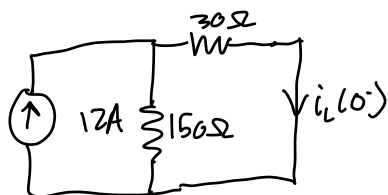

$$i_L(0^-) = \frac{150}{30+150} (12) = 10A$$

for  $t \geq 0$

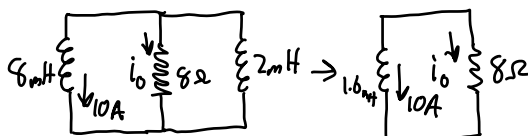


$$(8mH)L(2mH) = 1.6mH$$

$$\tau = \frac{L}{R} = \frac{1.6 \times 10^{-3}}{8} = 200 \times 10^{-6}$$

$$\frac{1}{\tau} = 5000$$

$$\boxed{i_o = -10 e^{-5000 t} A}$$

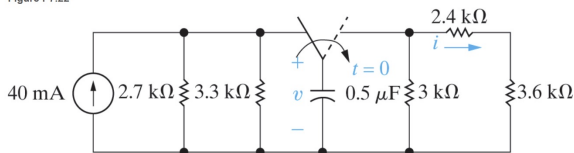7.22 The switch in the circuit in Fig. P 7.22 has been in the left position for a long time. At  $t = 0$  it moves to the right position and stays there.



- a) Write the expression for the capacitor voltage,  $v(t)$ , for  $t \geq 0$ .  
b) Write the expression for the current through the  $40 \text{ k}\Omega$  resistor,  $i(t)$ , for  $t \geq 0^+$ .

Initial voltage

$$V(0) = (40 \times 10^{-3}) (1.485 \times 10^3) = 59.4 \text{ V}$$

$$\frac{1}{R} = \frac{1}{2.7} + \frac{1}{3.3} = 1.485$$

Req for cap

$$R_{eq} = 3 \text{ k}\Omega \parallel (2.4 + 3.6) \text{ k}\Omega = 2 \text{ k}\Omega$$


$$\tau = R_{eq} C = (2 \times 10^3) (0.5 \times 10^{-6}) = 1.0 \text{ ns}$$

$$a) \boxed{V(t) = V_0 e^{-\frac{t}{\tau}} = 59.4 e^{-1000t} \text{ V}}$$


$$i(t) = \frac{V(t)}{R} = \frac{59.4 e^{-1000t}}{(2.4 + 3.6) \text{ k}}$$

$$b) \boxed{i(t) = 9.9 e^{-1000t} \text{ mA}}$$

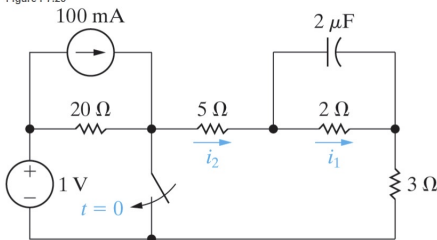
7.25 PSpice Multisim The switch in the circuit in Fig. P 7.25 is closed at  $t = 0$  after being open for a long time.



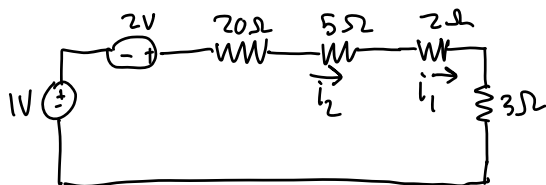- a) Find  $i_1(0^-)$  and  $i_2(0^-)$ .  
b) Find  $i_1(0^+)$  and  $i_2(0^+)$ .  
c) Explain why  $i_1(0^-) = i_1(0^+)$ .  
d) Explain why  $i_2(0^-) \neq i_2(0^+)$ .  
e) Find  $i_1(t)$  for  $t \geq 0$ .  
f) Find  $i_2(t)$  for  $t \geq 0^+$ .


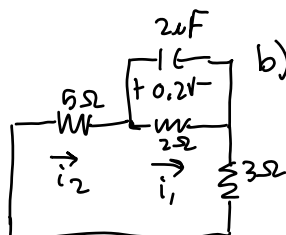
$$a) \boxed{i_1(0^-) = i_2(0^-) = \frac{V}{R} = \frac{3V}{30\Omega} = 100 \text{ mA}}$$



$$b) \boxed{i_1(0^+) = \frac{0.2}{2} = 100 \text{ mA}}$$

$$\boxed{i_2(0^+) = \frac{-0.2}{8} = -25 \text{ mA}}$$

c) Since capacitors do not change voltages instantly  $i_1(0^-) = i_1(0^+)$  for a certain amount of time

d) flipping a switch instantly changes the current running through a resistive path


$$\tau = R_{eq} C = 1.6 (2 \times 10^{-6}) = 3.2 \mu\text{s}$$

$$V_c = 0.2 e^{-\frac{t}{\tau}} = 0.2 e^{-312 \times 10^3 t} \text{ V}$$

$$e) \boxed{i_1 = \frac{V_c}{2} = 0.1 e^{-312 \times 10^3 t} \text{ A}}$$

$$f) \boxed{i_2 = \frac{-V_c}{8} = -25 e^{-312 \times 10^3 t} \text{ mA}}$$

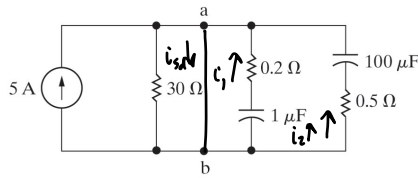7.34 PROBLEM MULTISIM After the circuit in Fig. P 7.34 has been in operation for a long time, a screwdriver is inadvertently connected across the terminals a, b. Assume the resistance of the screwdriver is negligible.  
Figure P 7.34



- a) Find the current in the screwdriver at  $t = 0^+$  and  $t = \infty$ .  
b) Derive the expression for the current in the screwdriver for  $t \geq 0^+$ .

$$V = (5 \text{ A})(30 \Omega) = 150 \text{ V}$$

$$a) \quad \begin{cases} i_{sd}(0^+) = 5 + \frac{150}{0.2} + \frac{150}{0.5} = 1.065 \times 10^3 \text{ mA} \\ i_{sd}(\infty) = 5 \text{ A} \end{cases}$$

$$i_{sd}(t) = 5 + i_1(t) + i_2(t)$$

$$\tau_1 = 0.2 (10^{-6}) = 0.2 \mu\text{s}$$


$$\tau_2 = 0.5 (100 \times 10^{-6}) = 50 \mu\text{s}$$

$$i_1 = \frac{150}{0.2} e^{-5 \times 10^6 t} = 750 e^{-5 \times 10^6 t} \text{ A}$$


$$i_2 = \frac{150}{0.5} e^{-20000 t} = 300 e^{-20000 t} \text{ A}$$

$$b) \quad i_{sd} = 5 + 750 e^{-5 \times 10^6 t} + 300 e^{-20000 t} \text{ A}$$

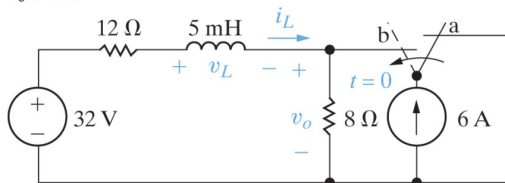7.38 PROBLEM MULTISIM The switch in the circuit shown in Fig. P 7.38 has been in position a for a long time before moving to position b at  $t = 0$ .  
Figure P 7.38



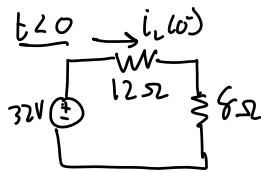
- a) Find the numerical expressions for  $i_L(t)$  and  $v_o(t)$  for  $t \geq 0$ .  
b) Find the numerical values of  $v_L(0^+)$  and  $v_o(0^+)$ .



$$i_L(0^-) = \frac{32}{20} = 1.6 \text{ A}$$

$$V_o = 8 i_L + 48$$

$t \geq 0$

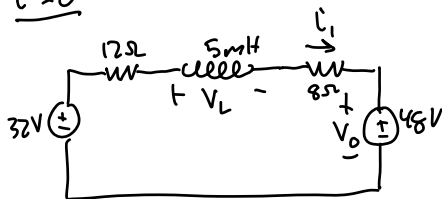

$$i_L(\infty) = \frac{32 - 48}{20} = -0.8 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{20} = 250 \mu\text{s}$$

$$i_L(t) = -0.8 + 1.6 e^{-4000 t} + 0.8 e^{-4000 t}$$

$$a.1) \quad i_L(t) = -0.8 + 2.4 e^{-4000 t} \text{ A}$$

$$V_o(t) = 8(-0.8 + 2.4 e^{-4000 t}) + 48$$

$$a.2) \quad V_o(t) = 41.6 + 19.2 e^{-4000 t} \text{ V}$$

$$V_L = L \frac{di_L}{dt} = (5 \times 10^{-3}) (-4 \times 10^3) (2.4 e^{-4000 t}) = -48 e^{-4000 t} \text{ V}$$

$$b.1) \quad V_L(0^+) = -48$$

$$V_o(0^+) = 48 + (8)(1.6)$$

$$b.2) \quad V_o(0^+) = 60.8 \text{ V}$$