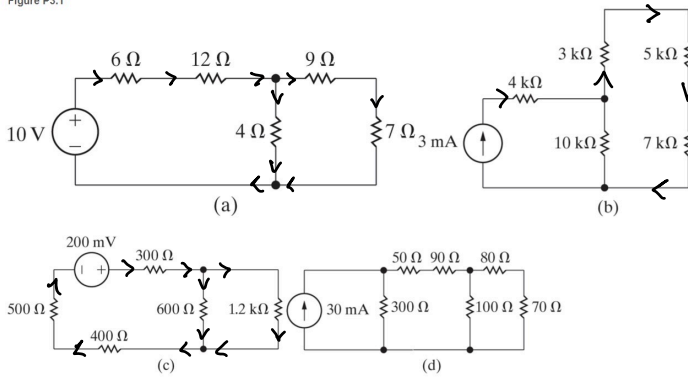



3.1 For each of the circuits shown in Fig. P 3.1, Figure P3.1



- a) identify the resistors connected in series,
b) simplify the circuit by replacing the series-connected resistors with equivalent resistors.


Circuit(b)

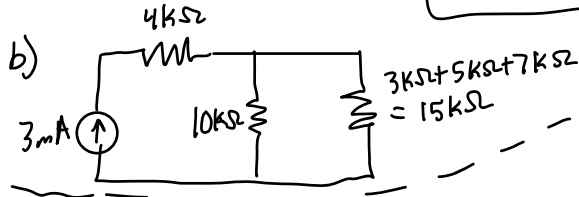a) The resistors in series are $3k\Omega, 5k\Omega, 7k\Omega$



Circuit(d): a) Resistors in parallel are:


$$\begin{array}{|l|} \hline 50\Omega, 90\Omega \\ \hline 80\Omega, 70\Omega \\ \hline \end{array}$$

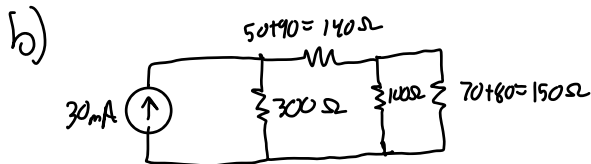

Circuit(c)

a) resistors in series


$$\begin{array}{|l|} \hline 6\Omega, 12\Omega \\ \hline 9\Omega, 7\Omega \\ \hline \end{array}$$

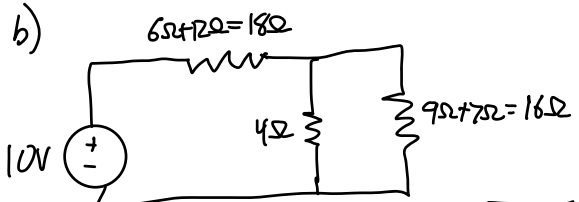




Circuit(c)

a) the resistors in series are:

$$300\Omega, 400\Omega, 500\Omega$$

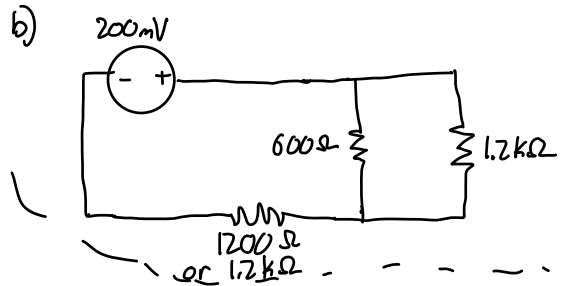

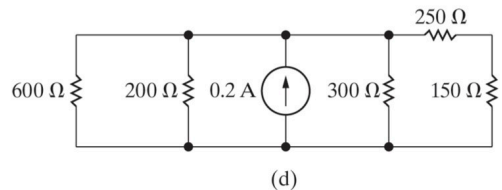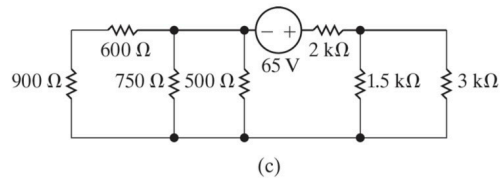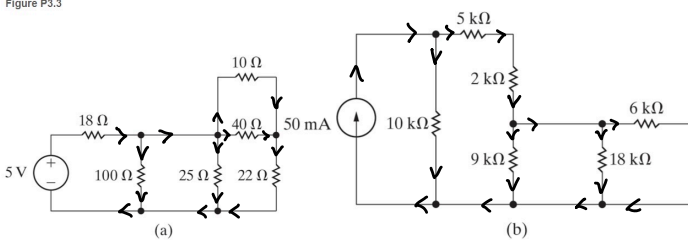3.3 For each of the circuits shown in Fig. P 3.3, Figure P3.3




- a) identify the resistors connected in parallel,
b) simplify the circuit by replacing the parallel-connected resistors with equivalent resistors.

$$R = \frac{R_1 R_2}{R_1 + R_2}, \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

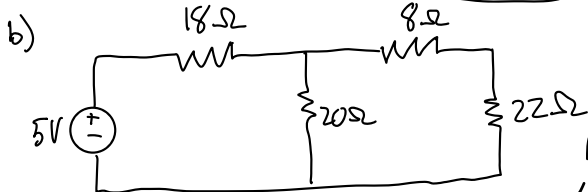3.3 cont

circuit (a) a) resistors in parallel: $\boxed{100\Omega, 25\Omega, 40\Omega, 10\Omega}$



$$R = \frac{2500}{125} = 20\Omega$$


$$R = \frac{400}{50} = 8\Omega$$

circuit (c) a) resistors in parallel

$$R = \frac{(1.5)(3)}{4.5} = 1k\Omega$$


$$R = 300\Omega$$
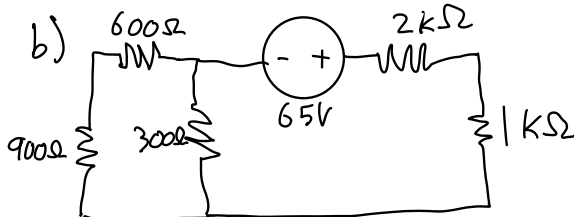
$$\boxed{1.5k\Omega, 3k\Omega, 500\Omega, 75\Omega}$$



circuit (b) a) the parallel resistors are:
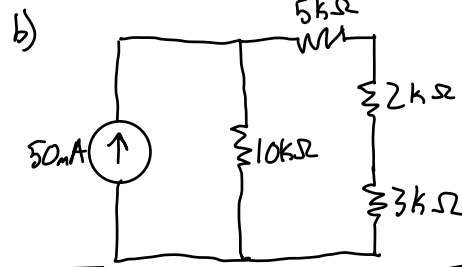
$$\boxed{9k\Omega, 18k\Omega, 6k\Omega}$$




$$\frac{1}{R} = \frac{1}{9} + \frac{1}{18} + \frac{1}{6}$$

$$\frac{1}{R} = \frac{2}{18} + \frac{1}{18} + \frac{3}{18} = \frac{1}{3}$$

$$R = 3$$

circuit (d) a) Resistors in parallel are:

$$\boxed{200\Omega, 600\Omega, 300}$$

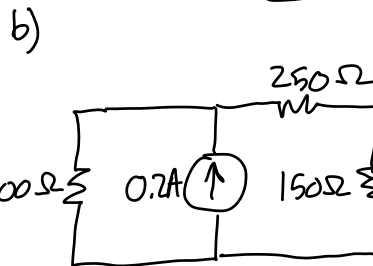


$$\frac{1}{R} = \frac{1}{200} + \frac{1}{600} + \frac{1}{300}$$

$$\frac{1}{R} = \frac{1}{100}$$

$$R = 100\Omega$$

3.5 PROBLEM Find the equivalent resistance R_{ab} for each of the circuits in Fig. P 3.5.


Figure P3.5

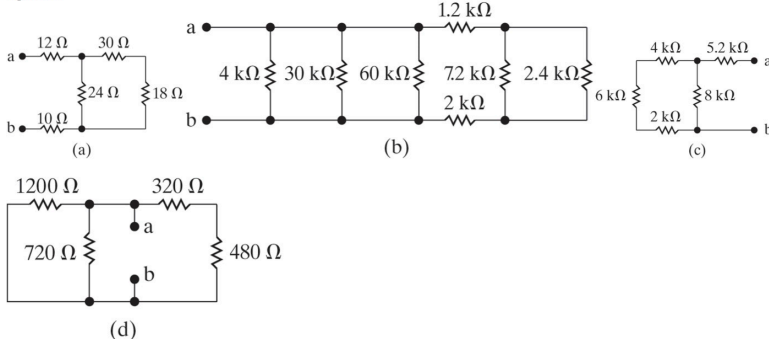

circuit (a)

$$R_{ab} = 12\Omega + 16\Omega + 10\Omega$$

$$\boxed{R_{ab} = 38\Omega}$$

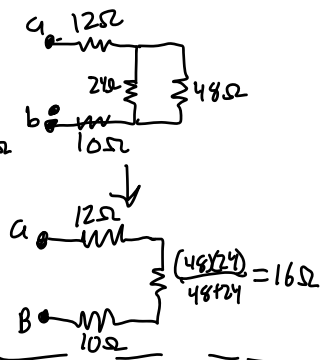

circuit b

$$\frac{(2.2)(2.4)}{2.2+2.4} = 1.8k\Omega$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{30} + \frac{1}{60}$$

$$\frac{1}{R} = \frac{15}{60} + \frac{2}{60} + \frac{1}{60}$$


$$R = 0.3k\Omega$$

$$\frac{1}{R_{ab}} = \frac{1}{4} + \frac{1}{30} + \frac{1}{60} + \frac{1}{5}$$

$$\frac{1}{R_{ab}} = \frac{15}{60} + \frac{2}{60} + \frac{1}{60} + \frac{12}{60}$$

$$\frac{1}{R_{ab}} = \frac{1}{2}$$

circuit (c)

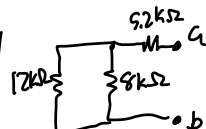

$$R_{ab} = \frac{(12)(8)}{20} + 5.2$$

$$\boxed{R_{ab} = 10k\Omega}$$

circuit d







$$R_{ab} = \frac{(450)(900)}{450+900}$$

$$\boxed{R_{ab} = 288\Omega}$$


3.7 PSPICE MULTISIM

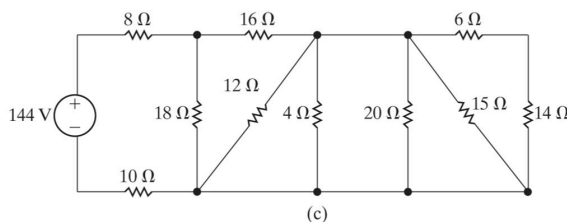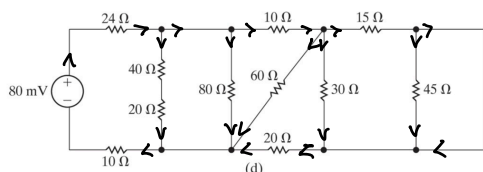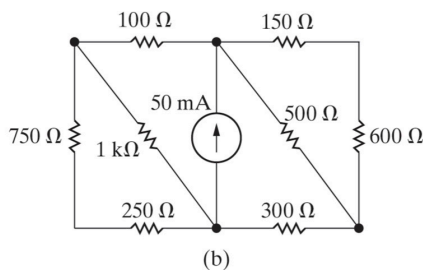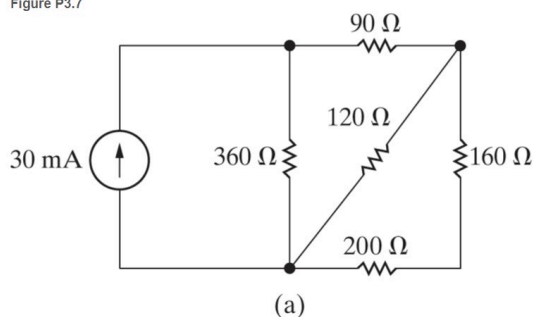a) In the circuits in Fig. P 3.7 (a)-(d), find the equivalent resistance seen by the source.
Figure P3.7



b) For each circuit find the power delivered by the source.

Circuit (a)


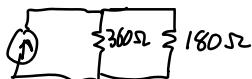


$$R = \frac{(360)(180)}{360 + 180} \Rightarrow R = 120 \Omega \quad a)$$

$$b) P = I^2 R \Rightarrow P = (30 \text{ mA})^2 120 \Omega$$

$$P = 108 \text{ mW}$$

Circuit (b)

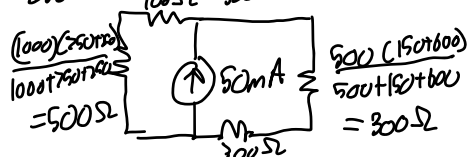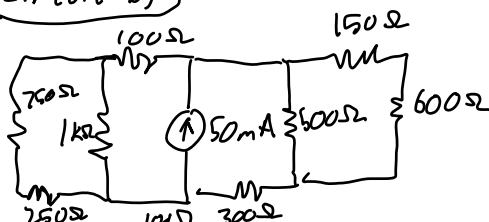


$$R = \frac{(300 + 300)(500 + 100)}{300 + 300 + 500 + 100}$$

$$R = 300 \Omega$$

$$P = I^2 R$$

$$P = (50 \text{ mA})^2 (300 \Omega)$$

$$P = 750 \text{ mW}$$

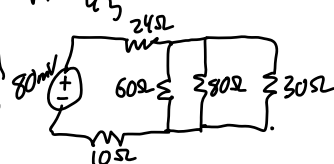

$$\frac{1}{R} = \frac{1}{60} + \frac{1}{80} + \frac{1}{30} = \frac{1}{16}$$



$$P = \frac{V^2}{R} = \frac{(80 \text{ mV})^2}{50 \Omega}$$



$$R = 50 \Omega$$

$$P = 128 \mu \text{W}$$

Circuit (c)

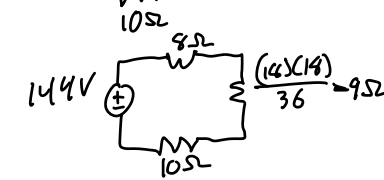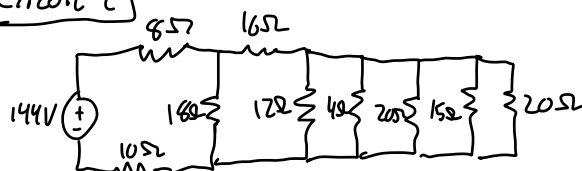

$$\frac{1}{R} = \frac{1}{12} + \frac{1}{4} + \frac{1}{20} + \frac{1}{15} + \frac{1}{20}$$

$$\frac{1}{R} = \frac{5}{60} + \frac{15}{60} + \frac{3}{60} + \frac{4}{60} + \frac{3}{60}$$

$$\frac{1}{R} = \frac{1}{2}$$


$$R = 8 + 9 + 10$$

$$R = 27 \Omega$$

$$P = \frac{V^2}{R} = \frac{144^2}{27}$$

$$P = 768 \text{ W}$$

Circuit (d)

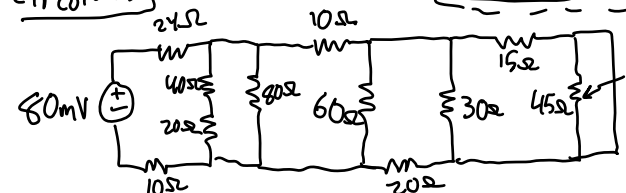

$$R = \frac{(20)(15)}{20 + 15} = 10 \Omega$$

$$R = \frac{(30)(60)}{30 + 60} = 20 \Omega$$

$$R = \frac{(300 + 300)(500 + 100)}{300 + 300 + 500 + 100}$$

$$R = 300 \Omega$$


$$P = I^2 R$$

$$P = (50 \text{ mA})^2 (300 \Omega)$$


$$P = 750 \text{ mW}$$

DESIGN
PROBLEM
3.13

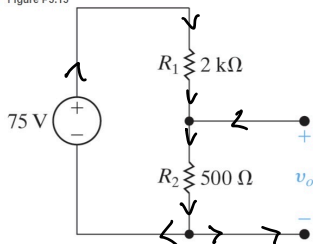- a) Calculate the no-load voltage v_o for the voltage-divider circuit shown in Fig. P3.13. Figure P3.13



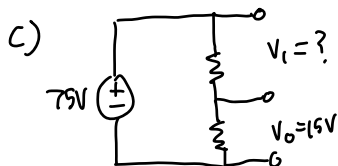- b) Calculate the power dissipated in R_1 and R_2 .
c) Assume that only 1 W resistors are available. The no-load voltage is to be the same as in (a). Specify the smallest ohmic values of R_1 and R_2 .



$$i_{R_1} = \frac{V_1}{R_1} = \frac{60}{R_1}$$

$$\left(\frac{60}{R_1}\right)^2 R_1 \leq 1 \text{ W}$$

$$\left(\frac{3600}{R_1^2}\right) R_1 \leq 1 \text{ W}$$

$$R_1 \geq 3600 \Omega$$

So smallest value is:

$$R_1 = 3600 \Omega$$

$$75 = (3600)(I) + R_2(I)$$

$$75 = (3600 + R_2)I$$

$$I = \frac{75}{3600 + R_2} \quad \text{--- (1)}$$

$$I = \frac{75 - 15}{R} = \frac{60}{3600} = \frac{1}{60} \text{ A} \quad \text{--- (2)}$$

$$a) \quad V_o = \frac{500}{500 + 2000} (75) = 15 \text{ V}$$

$$V_o = 15 \text{ V}$$

$$b) \quad P_1 = I^2 R_1 \quad P_2 = I^2 R_2$$

$$R_{eq} = 2500 \Omega \quad V = 75 \text{ V}$$

$$I = \frac{75}{2500} = 30 \text{ mA}$$

$$P_1 = (30 \text{ mA})^2 (2000) = 1.8 \text{ W}$$

$$P_2 = (30 \text{ mA})^2 (500) = 0.45 \text{ W}$$

$$\text{equat (1) + 2}$$




$$\frac{25}{3600 + R_2} = \frac{1}{60}$$

$$3600 + R_2 = 75 \times 60$$

$$R_2 = 900 \Omega$$

DESIGN
PROBLEM
3.16

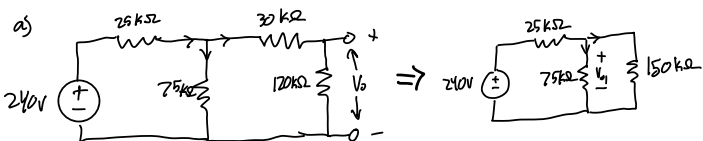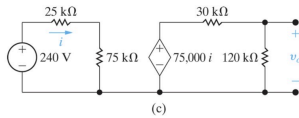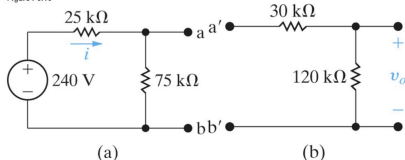- a) The voltage divider in Fig. P3.16(a) is loaded with the voltage divider shown in Fig. P3.16(b); that is, a is connected to a' and b is connected to b'. Find v_o . Figure P3.16



$$R = \frac{(50 \text{ k}\Omega)(75 \text{ k}\Omega)}{50 \text{ k}\Omega + 75 \text{ k}\Omega} = 50 \text{ k}\Omega$$

$$V_{o1} = 240 \times \frac{50 \text{ k}\Omega}{50 \text{ k}\Omega + 25 \text{ k}\Omega}$$

$$V_{o1} = 80 \times 2 = 160 \text{ V}$$

$$V_o = 160 \times \frac{120 \text{ k}\Omega}{120 \text{ k}\Omega + 30 \text{ k}\Omega} = 32 \times 4$$

$$V_o = 128 \text{ V}$$

- b) Now assume the voltage divider in Fig. P3.16(b) is connected to the voltage divider in Fig. P3.16(a) by means of a current-controlled voltage source as shown in Fig. P3.16(c). Find v_o .
c) What effect does adding the dependent-voltage source have on the operation of the voltage divider that is connected to the 240 V source?

$$b) \quad i = \frac{240 \text{ V}}{100 \text{ k}\Omega} = 2.4 \text{ mA}$$

$$75,000 (2.4 \times 10^{-3} \text{ A}) = 180 \text{ V}$$




$$V_o = 180 \text{ V} \times \frac{120 \text{ k}\Omega}{120 \text{ k}\Omega + 30 \text{ k}\Omega}$$

$$V_o = 144 \text{ V}$$

c) adding the dependent voltage source removes some of the load on the 75,000 Ω voltage divider, i.e. it would have the same voltage as in the left side of the circuit

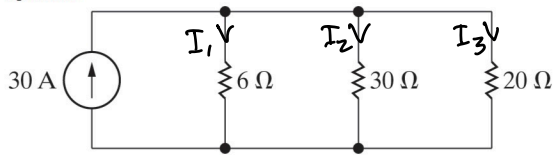3.20 PSPICE MULTISIM Find the power dissipated in the $30\ \Omega$ resistor in the current-divider circuit in Fig. P3.20.



$$I_2 = \left(\frac{R_{eq}}{30\ \Omega} \right) \times 30\text{ A} = \frac{4}{30} \times 30 = 4\text{ A}$$

$$P_2 = (I_2)^2 R_2 = (4\text{ A})^2 \times 30\ \Omega$$


$$\boxed{P_2 = 480\text{ W}}$$

$$R_{eq} = \frac{1}{\frac{1}{R_{eq}}} = \frac{1}{\frac{1}{6} + \frac{1}{30} + \frac{1}{20}}$$


$$\frac{1}{R_{eq}} = \frac{1}{4} \Rightarrow R_{eq} = 4$$

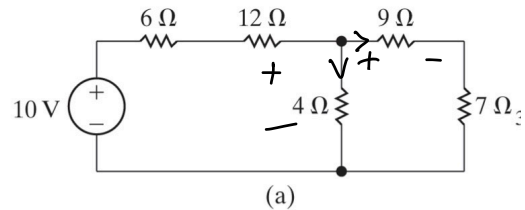3.23 Look at the circuit in Fig. P3.1(a).

- Use voltage division to find the voltage across the $4\ \Omega$ resistor, positive at the top.
- Use the result from part (a) and voltage division to find the voltage across the $9\ \Omega$ resistor, positive on the left.



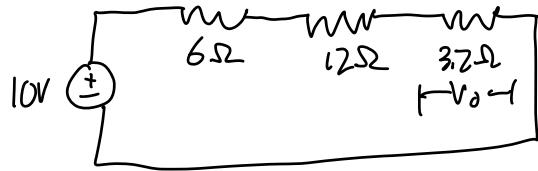
$$R = \frac{4(9+7)}{4+9+7} = 3.2\ \Omega$$



$$V_0 = 10\text{ V} \left[\frac{3.2}{3.2+6+12} \right]$$
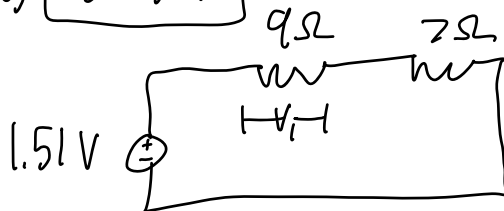
$$\text{a) } \boxed{V_0 = 1.51\text{ V}}$$



$$V_1 = 1.51\text{ V} \left[\frac{9}{9+7} \right]$$

$$\text{b) } \boxed{V_1 = 0.45\text{ V}}$$