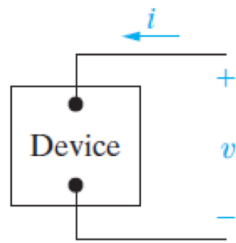


**Question 1** [10]


The terminal voltage and terminal current were measured (b) on the device (a) shown. Construct a circuit model for the device consisting of a single resistor. Provide a graph (either hand-drawn or software generated) showing how you determine the value of the resistor.



(a)

$i$ (mA)	$v$ (V)
-10	-120
-5	-60
5	60
10	120
15	180

(b)

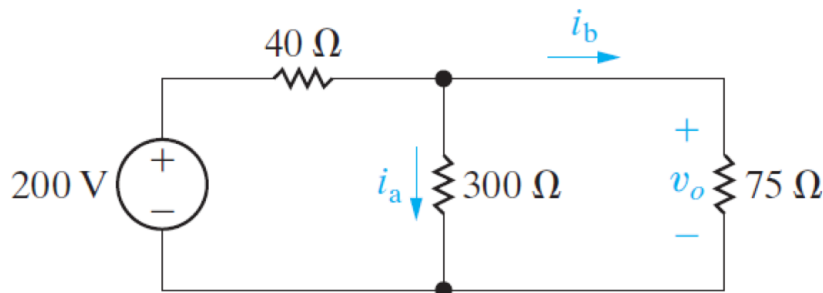**Question 2** [10]


For the circuit shown, find:

- (a) The value of  $i_a$ .
- (b) The value of  $i_b$ .
- (c) The value of  $v_o$ .
- (d) the power dissipated in each resistor.
- (e) the power delivered by the 200V source.

---

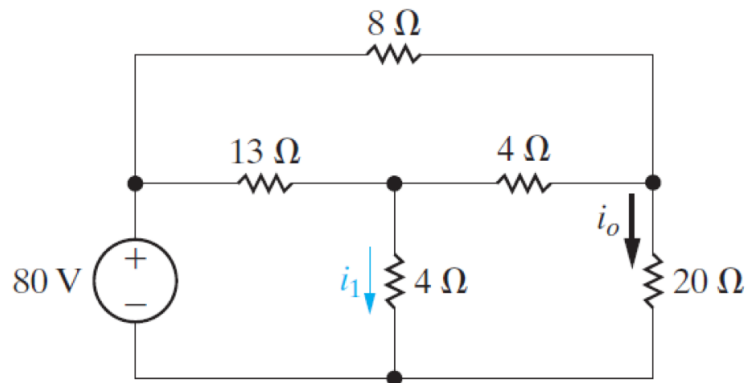**Question 3** [10]


In the circuit below, the current  $i_o = 2\text{ A}$ .



- (a) Find  $i_1$ .
- (b) Find the power dissipated in each resistor.
- (c) Verify that the total power dissipated in the circuit equals the power provided by the voltage source.

**Question 4** [10]

The variable resistor  $R$  is adjusted until  $i_o = 10\text{ mA}$ . Find the value of  $R$ .

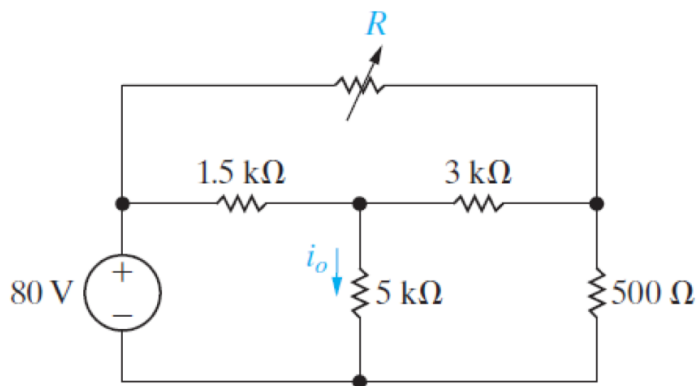**Question 5** [10]

Find  $v_o$  and the total power supplied in the circuit.

