
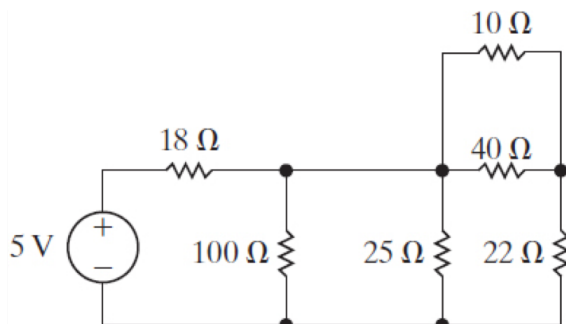


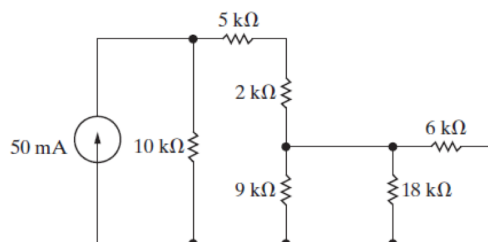**Question 1** [10]


For each of the circuits (a)-(d), find the equivalent resistance and the power delivered by the source.




(a)



(b)

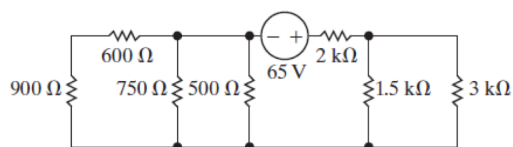


(c)

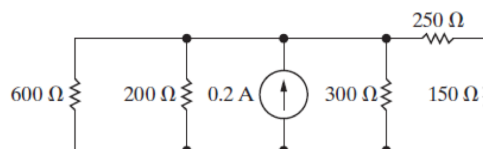

(d)

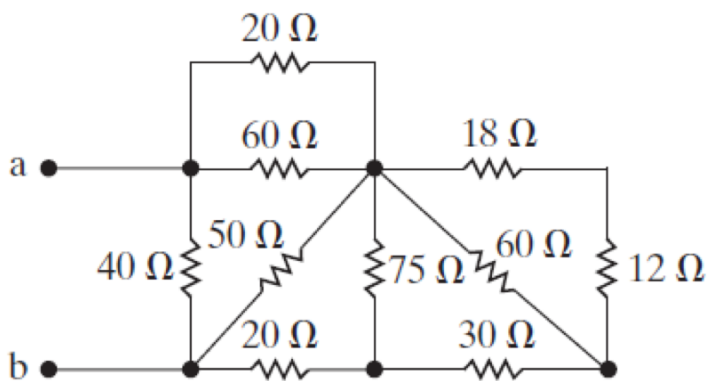
**Question 2** [10]

Find the equivalent resistance  $R_{ab}$  for the following circuit.




**Question 3** [10]

A battery of 45 V delivers 112 W of power to the circuit that contains 5 identical resistors ( $R_i=R$ ). What is the value of  $R$ ?

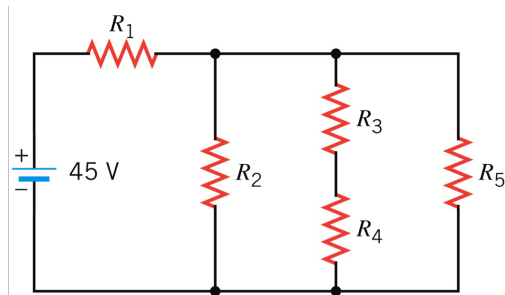**Question 4** [10]

For the voltage-divider circuit shown:

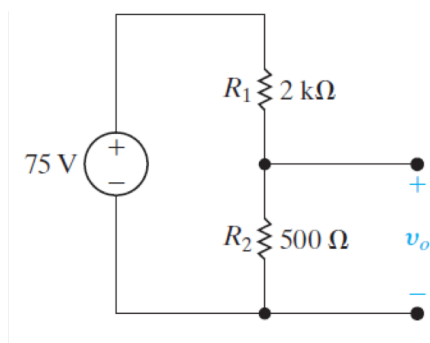

- Calculate the no-load voltage  $v_o$ .
- Calculate the power dissipated in  $R_1$  and  $R_2$ .
- If only 1 W resistors are available and that the no-load voltage is to be the same as in part (a), specify the smallest values of  $R_1$  and  $R_2$ .

**Question 5** [10]

Use a  $\Delta$ -to- $Y$  transformation to find the voltages  $v_1$  and  $v_2$  in the circuit below.

