

ECE 203

Circuits I

Loop Analysis

Lecture 4-2

Loop Analysis

- ❑ Loop analysis is similar to nodal analysis, but utilizes KVL**
- ❑ Also called mesh analysis**
- ❑ The variables are loop currents; we define loop currents throughout the circuit, and use KVL around each loop**
- ❑ Choice of loops is fairly open, but each branch of the circuit must be included; ultimately, need as many loops as there are unknown currents in the circuit**
- ❑ Once the loop currents are known, any circuit parameter can be calculated**


Step-by-step

- 1) Establish where each loop in the circuit is
- 2) Assign the current variable for each loop; for example, I_1 , I_2 , ...
- 3) Write the equations for KVL for each loop
- 4) Use Ohm's law to rewrite the loop equation in terms of currents and resistances (you should have the same number of equations as loops)

Step-by-step continued

- 5) Solve for the unknown currents (you have a few choices of how to do this—substitution, matrix, etc)
- 6) Use Ohm's law to solve for unknown voltages in the circuit


A Two-Loop Circuit

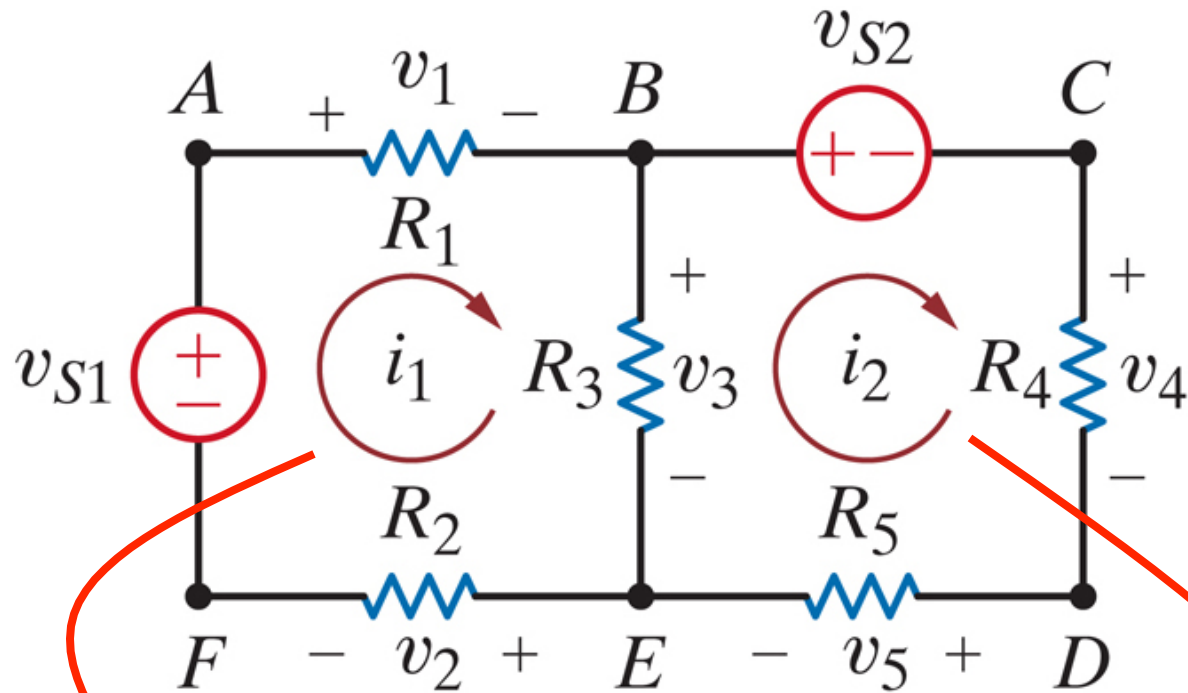

$$+v_1 + v_3 + v_2 - v_{S1} = 0$$

$$+v_{S2} + v_4 + v_5 - v_3 = 0$$

Two-loop circuit continued

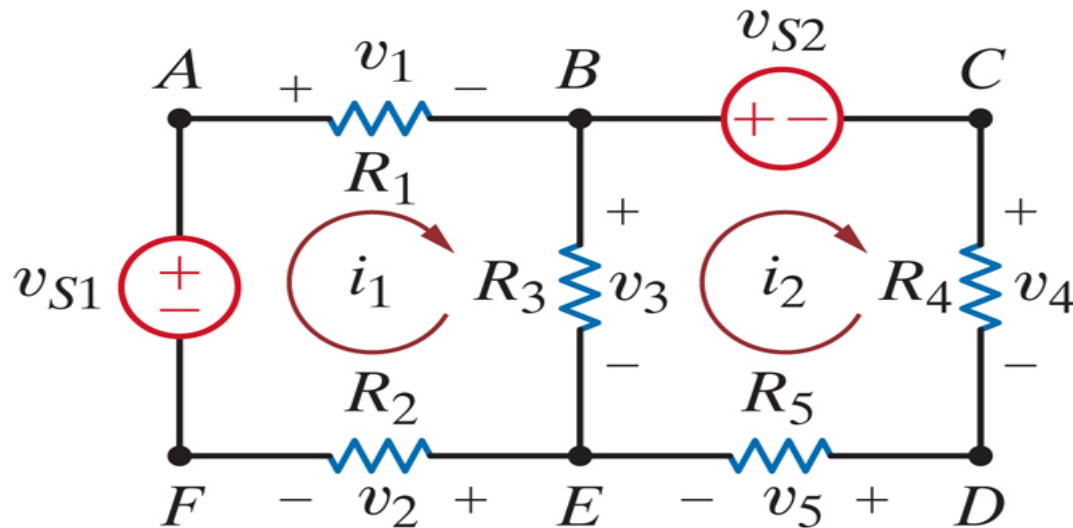

$$i_1 R_1 + (i_1 - i_2) R_3 + i_1 R_2 - v_{s1} = 0$$

$$v_{s2} + i_2 R_4 + i_2 R_5 - (i_1 - i_2) R_3 = 0$$



Matrix Representation

$$\left\{ \begin{array}{l} +v_1 + v_3 + v_2 - v_{S1} = 0 \\ +v_{S2} + v_4 + v_5 - v_3 = 0 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} i_1(R_1 + R_2 + R_3) - i_2(R_3) = v_{S1} \\ -i_1(R_3) + i_2(R_3 + R_4 + R_5) = -v_{S2} \end{array} \right.$$



$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 + R_5 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{S1} \\ -v_{S2} \end{bmatrix}$$

Loop Selection

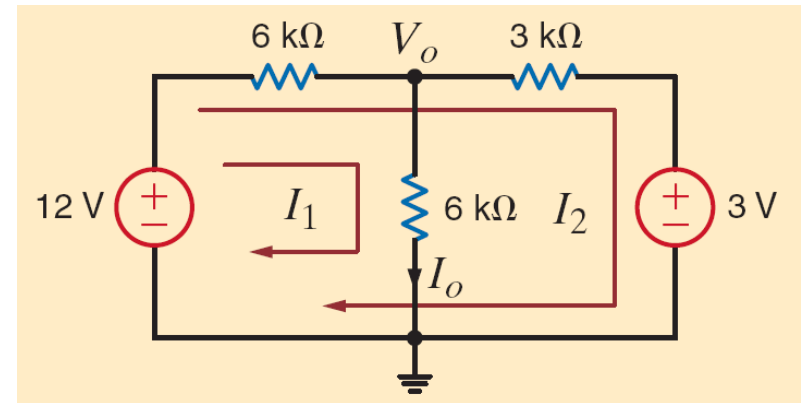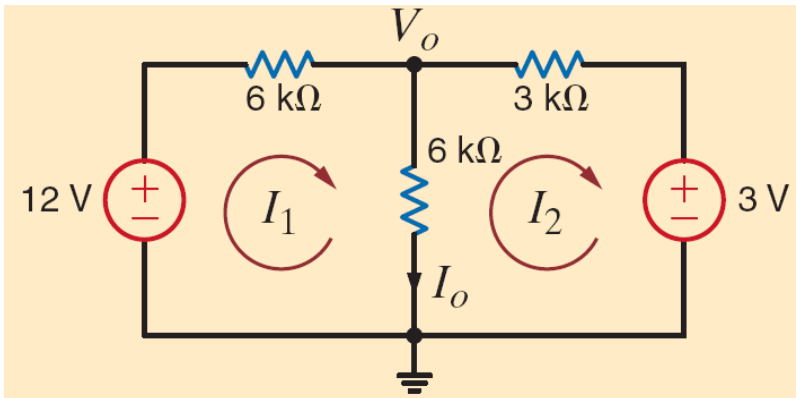


Can I choose I_1 and I_2 loops this way, instead?

$$-12 + 6k(I_1 + I_2) + 6kI_1 = 0$$

$$-12 + 6k(I_1 + I_2) + 3kI_2 + 3 = 0$$

$$\Rightarrow \begin{cases} I_1 = 0.75 \text{ mA} \\ I_2 = 0.5 \text{ mA} \end{cases}$$

Circuits with Current Sources

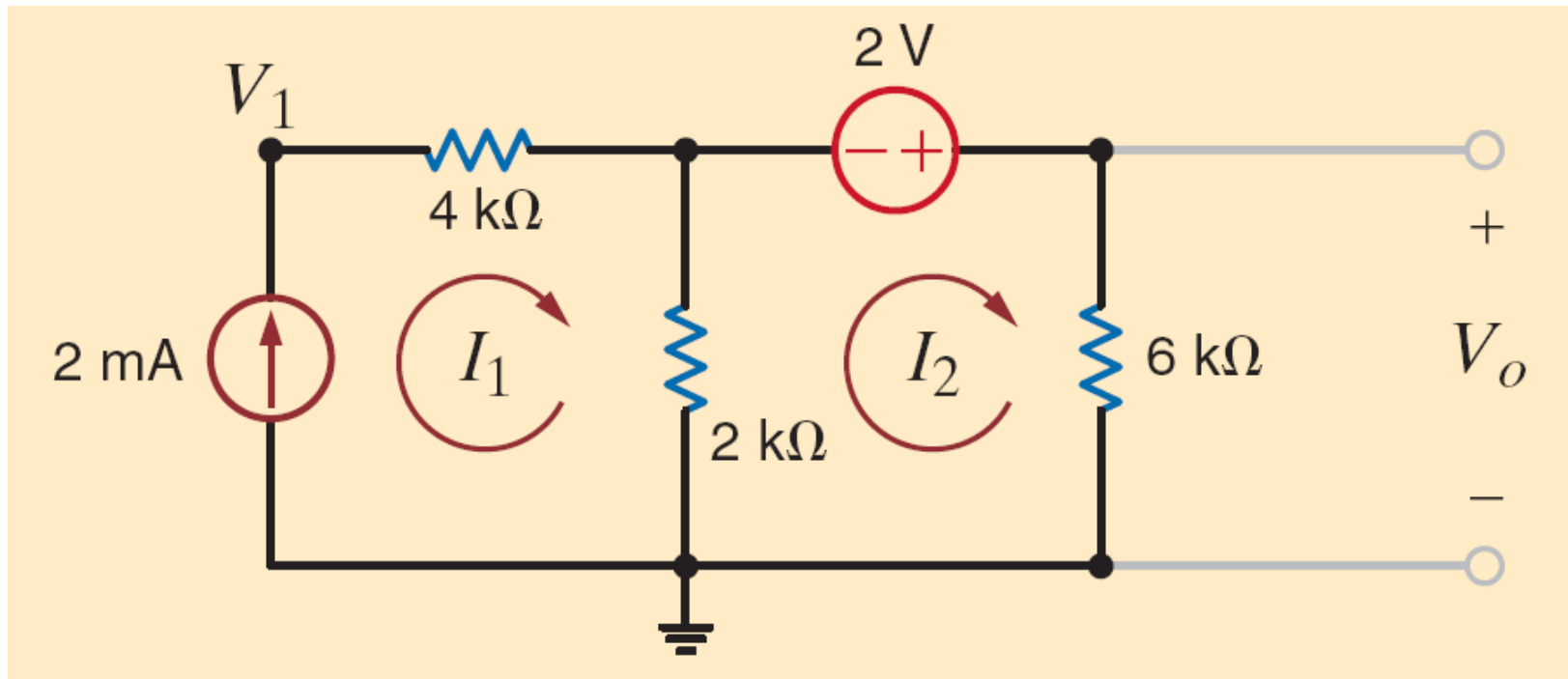

$$2\text{k}(I_2 - I_1) - 2 + 6\text{k}I_2 = 0$$

$$I_1 = 2 \times 10^{-3}$$

$$\Rightarrow \begin{cases} I_1 = 2.0\text{ mA} \\ I_2 = 0.8\text{ mA} \end{cases}$$