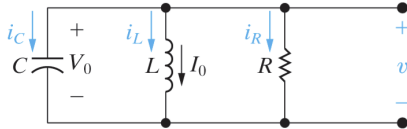


8.2 **PSPICE MULTISIM** The circuit elements in the circuit in Fig. 8.1 are  $R = 200 \Omega$ ,  $L = 50 \text{ mH}$ , and  $C = 0.2 \mu\text{F}$ . The initial inductor current is  $-45 \text{ mA}$  and the initial capacitor voltage is  $15 \text{ V}$ .

- Calculate the initial current in each branch of the circuit.
- Find  $v(t)$  for  $t \geq 0$ .
- Find  $i_L(t)$  for  $t \geq 0$ .

Figure 8.1 A circuit used to illustrate the natural response of a parallel RLC circuit.



a)

$$i_{R, \text{initial}} = \frac{15}{200} = 75 \text{ mA}$$

$$i_{L, \text{initial}} = -45 \text{ mA}$$

$$i_{C, \text{initial}} = -(-45) - 75 = -30 \text{ mA}$$

b)

$$s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$$

$$s^2 + \frac{s}{(200)(0.2 \times 10^{-6})} + \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 0$$

$$s^2 + 25000s + 10^8 = 0$$

$$s = \frac{-25000 \pm \sqrt{(25000)^2 - 4(1)(10^8)}}{2}$$

$$s = -12500 \pm 7500$$

$$s = -5000 \text{ or } s = -20000$$

$$v = A_1 e^{-5000t} + A_2 e^{-20000t}$$

①  $v(0) = A_1 + A_2 = 15 \text{ V}$

$$v' = -5000A_1 e^{-5000t} - 20000A_2 e^{-20000t}$$

$$v'(0) = -5000A_1 - 20000A_2$$

$$v'(0) = \frac{i_C(0)}{C} = \frac{-30 \times 10^{-3}}{0.2 \times 10^{-6}}$$

②  $-5000A_1 - 20000A_2 = -15 \times 10^4$

Solving eq ① + ②

$$A_1 = 10, A_2 = 5$$

$$\therefore v = 10e^{-5000t} + 5e^{-20000t} \text{ V}$$

c)  $i_L = -i_C - i_R$

$$\rightarrow i_R = 50e^{-5000t} + 25e^{-20000t} \text{ mA}$$

$$\rightarrow i_C = C \frac{dv}{dt}$$

$$i_C = -10e^{-5000t} - 20e^{-20000t} \text{ mA}$$

$$i_L = -40e^{-5000t} - 5e^{-20000t} \text{ mA}$$

8.3 **PSPICE MULTISIM** The resistance in Problem 8.2 is increased to  $250 \Omega$ . Find the expression for  $v(t)$  for  $t \geq 0$ .

$$\alpha = \frac{1}{2RC} = \frac{1}{2(250)(0.2 \times 10^{-6})}$$

$$\alpha = 10^4$$

$$\alpha^2 = 10^8 = \omega^2$$

$$v = A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$$

$$v = (A_1 t + A_2) e^{-\alpha t}$$

$$v = (75000t + 15) e^{-10000t} \text{ V}$$

$$i_C(0^+) = -i_L - i_R = 45 - \frac{15}{250} = -15 \text{ mA}$$

$$v(0) = A_2 = 15$$

$$v' = A_1 [t(-\alpha e^{-\alpha t}) + e^{-\alpha t}] - \alpha A_2 e^{-\alpha t}$$

$$v'(0) = A_1 - \alpha A_2 = \frac{i_C}{C} = \frac{-15 \times 10^{-3}}{0.2 \times 10^{-6}} = -75000$$

$$A_1 = (10^4)(15) - 75000 = 75000$$

8.4 The resistance in Problem 8.2 is increased to 312.5  $\Omega$ . Find the expression for  $v(t)$  for  $t \geq 0$ .

$$\alpha = \frac{1}{2RL} = \frac{1}{2(312.5)(0.2 \times 10^{-6})} = 8000$$

$$\omega^2 = 10^8$$

$$s = -8000 \pm \sqrt{8000^2 - 10^8}$$

$$s = -8000 \pm 6000j$$

$$v(t) = A_1 e^{-8000t} \cos(6000t) + A_2 e^{-8000t} \sin(6000t)$$

$$v(0) = A_1 = 15V$$

$$i_L = +45 - \frac{15}{312.5} = -3mA$$

$$v'(0) = -8000A_1 + 6000A_2 = \frac{-3 \times 10^{-3}}{0.2 \times 10^{-6}}$$

$$A_2 = \frac{-8000(15) - 15000}{6000}$$

$$A_2 = 17.5V$$


$$v(t) = 15e^{-8000t} \cos(6000t) + 17.5e^{-8000t} \sin(6000t) V$$

8.8 The natural voltage response of the circuit in Fig. 8.1 is

$$v(t) = 120e^{-400t} \cos 300t + 80e^{-400t} \sin 300t V,$$

when the capacitor is 250  $\mu F$ . Find (a)  $L$ ; (b)  $R$ ; (c)  $V_0$ ; (d)  $I_0$ ; and (e)  $i_L(t)$ .

Figure 8.1 A circuit used to illustrate the natural response of a parallel RLC circuit.

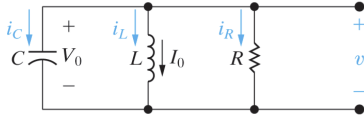

$$\alpha = 400 \quad \omega = 300$$

$$\omega_0^2 = \omega^2 + \alpha^2 = 25 \times 10^4$$

$$\omega_0^2 = \frac{1}{LC} = 25 \times 10^4$$

$$L = \frac{1}{(25 \times 10^4)(250 \times 10^{-6})}$$

$$a) \boxed{L = 16mH}$$

$$\frac{1}{2RC} = 400$$

$$R = \frac{1}{2(400)(250 \times 10^{-6})}$$

$$b) \boxed{R = 5\Omega}$$

$$c) \boxed{V_0 = V(0) = 120V}$$

$$I_0 = i_L(0)$$

$$i_L(0) = -i_R(0) - i_C(0)$$

$$i_L(0) = -\frac{120}{5} - [(250 \times 10^{-6})(-400(120) + 300(80))]$$

$$i_L(0) = -18A$$

$$d) \boxed{I_0 = -18A}$$


$$i_L(t) = -i_R(t) - i_C(t)$$

$$i_R(t) = \frac{v(t)}{5} = e^{-400t} (24 \cos 300t + 16 \sin 300t) A$$

$$i_C(t) = (250 \times 10^{-6}) v'(t) = e^{-400t} (-17 \sin 300t - 6 \cos 300t) A$$

$$e) \boxed{i_L(t) = e^{-400t} (-18 \cos 300t + \sin 300t) A}$$

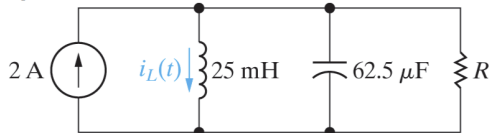8.32 PSpice MULTISIM Assume that at the instant the 2 A current source is applied to the circuit in Fig. P8.32, the initial current in the 25 mH inductor is 1 A, and the initial voltage on the capacitor is 50 V (positive at the upper terminal). Find the expression for  $i_L(t)$  for  $t \geq 0$  if  $R$  equals 12.5  $\Omega$ .  
Figure P8.32



$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(25 \times 10^{-3})(62.5 \times 10^{-6})} = 640000$$

$$\alpha^2 = \left(\frac{1}{2RC}\right)^2 = \left(\frac{1}{2(12.5)(62.5 \times 10^{-6})}\right)^2 = 409600$$

$$\omega_d = \sqrt{640000 - 409600} = \sqrt{230400}$$

$$\omega_d = 480 \text{ rad/s}$$

$$i = 2 \text{ A}$$

$$i_L = 2 + A_1 e^{-640t} \cos(480t) + A_2 e^{-640t} \sin(480t)$$

$$i_L(0) = 2 + A_1 = 1 \Rightarrow A_1 = -1$$

$$\frac{d}{dt} i_L(0) = -640A_1 + 480A_2 + \frac{d}{dt} i_L(0) = \frac{V}{L}$$

$$\therefore -640(-1) + 480A_2 = \frac{50}{25 \times 10^{-3}}$$

$$A_2 = 2.83$$

$$i_L(t) = 2 - e^{-640t} \cos(480t) + 2.83 e^{-640t} \sin(480t) \text{ A}$$

8.33 PSpice MULTISIM The resistance in the circuit in Fig. P8.32 is changed to 8  $\Omega$ . Find  $i_L(t)$  for  $t \geq 0$ .

$$\omega_o^2 = \frac{1}{LC} = 640000$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(8)(62.5 \times 10^{-6})} = 1000$$

$$s = -1000 \pm \sqrt{1000^2 - 640000}$$

$$s = -400, s = -1600$$

$$\therefore i_L = 2 + A_1 e^{-400t} + A_2 e^{-1600t}$$

$$i_L(0) = 2 + A_1 + A_2 = 1$$

$$A_1 + A_2 = -1$$

$$\frac{d}{dt} i_L = -400A_1 e^{-400t} - 1600A_2 e^{-1600t}$$

$$\frac{d}{dt} i_L(0) = -400A_1 - 1600A_2$$

$$\text{Since } \frac{d}{dt} i_L = \frac{V}{L}$$

$$-400A_1 - 1600A_2 = \frac{50}{25 \times 10^{-3}}$$

$$\text{Solving for } A_1 + A_2$$

$$A_1 = \frac{1}{3}, A_2 = -\frac{4}{3}$$

$$\therefore i_L(t) = 2 + \frac{1}{3} e^{-400t} - \frac{4}{3} e^{-1600t} \text{ A}$$

$$\omega_0^2 = 640000$$

$$\alpha = \frac{1}{2(10)(625 \times 10^{-6})} = 800$$

$$\alpha^2 = 640000$$

$$i_L = 2 + A_1 t e^{-800t} + A_2 e^{-800t}$$

$$i_L(0) = 2 + A_2 = 1$$

$$A_2 = -1$$

$$\frac{d}{dt} i_L = A_1 [-800 t e^{-800t} + e^{-800t}] - 800 e^{-800t} A_2$$

$$\frac{d}{dt} i_L(0) = A_1 - 800 A_2 = \frac{V}{L} = 2000$$

$$A_1 = 2000 - 800$$

$$A_1 = 1200$$

$$i_L(t) = 2 + 1200 t e^{-800t} - e^{-800t} \text{ A}$$