


ECE 203

Circuits I

Thévenin and Norton Theorems With Dependent Sources

Lecture 8-2

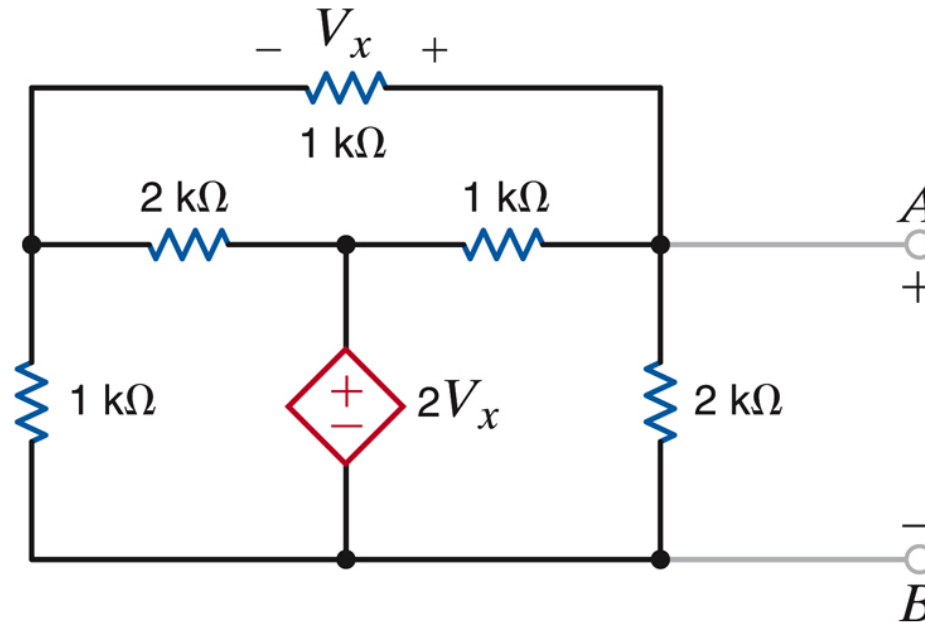What is the Thévenin equivalent of this circuit at AB terminal?




What is the value of V_{oc} ? $V_{oc} = 0V$

What is the value of I_{sc} ? $I_{sc} = 0A$

What is the value of R_{Th} ? $R_{Th} = V_{oc}/I_{sc} = 0/0 !$

How to find R_{Th} ?

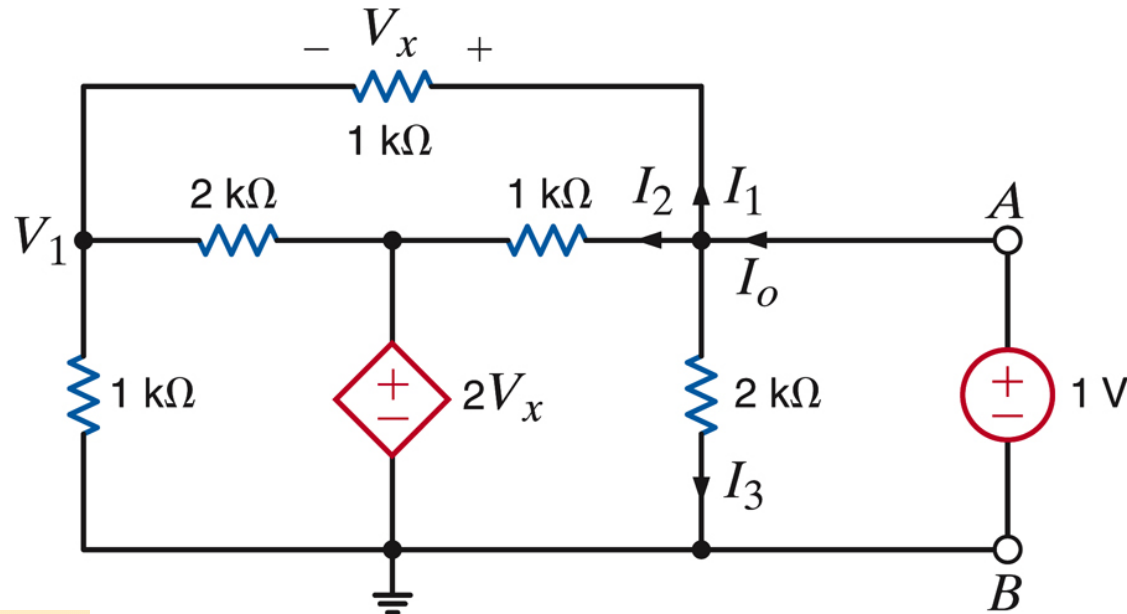
Connect a 1V voltage source at AB terminal and calculate the current flowing back into the circuit




$$\begin{cases} V_1 + V_x = 1 \\ \frac{V_1}{1k} + \frac{V_1 - 2V_x}{2k} + \frac{V_1 - 1}{1k} = 0 \end{cases} \Rightarrow I_o = I_1 + I_2 + I_3 = \frac{15}{14} \text{ mA} \Rightarrow R_{Th} = \frac{1}{I_o} = \frac{14}{15} \text{ k}\Omega$$

Note: In a circuit with a dependent source, you can't directly calculate the Thévenin resistance.

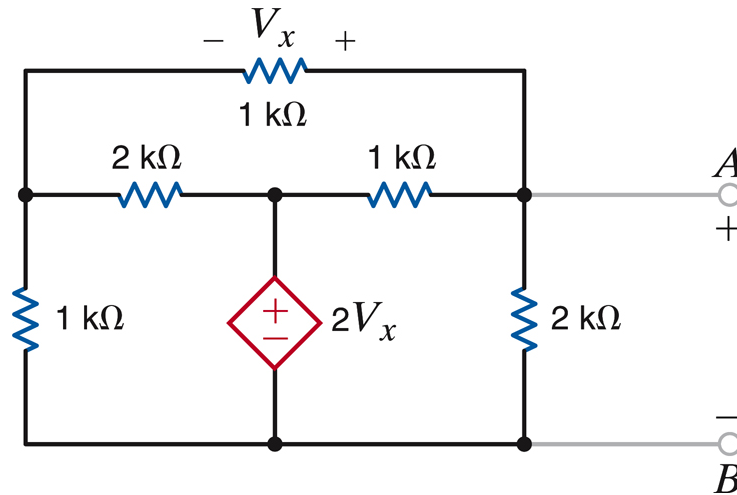
Thévenin's & Norton's Equivalent Currents



Thevenin

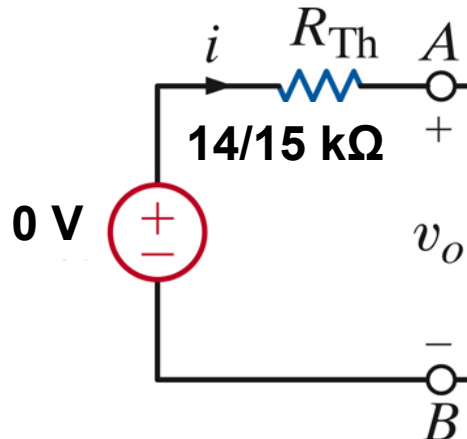


Norton

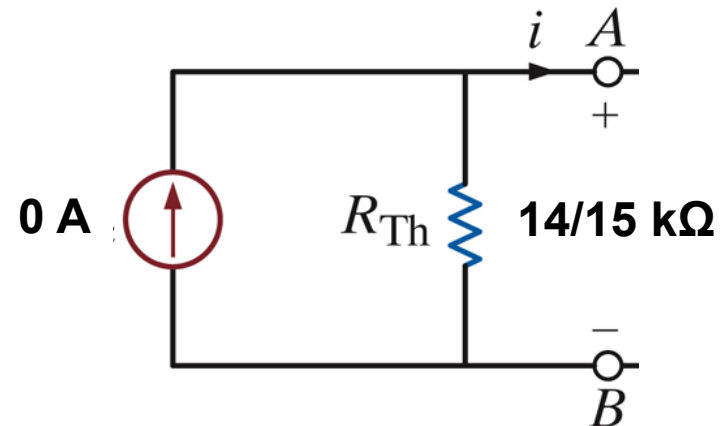

Yet Another Example:

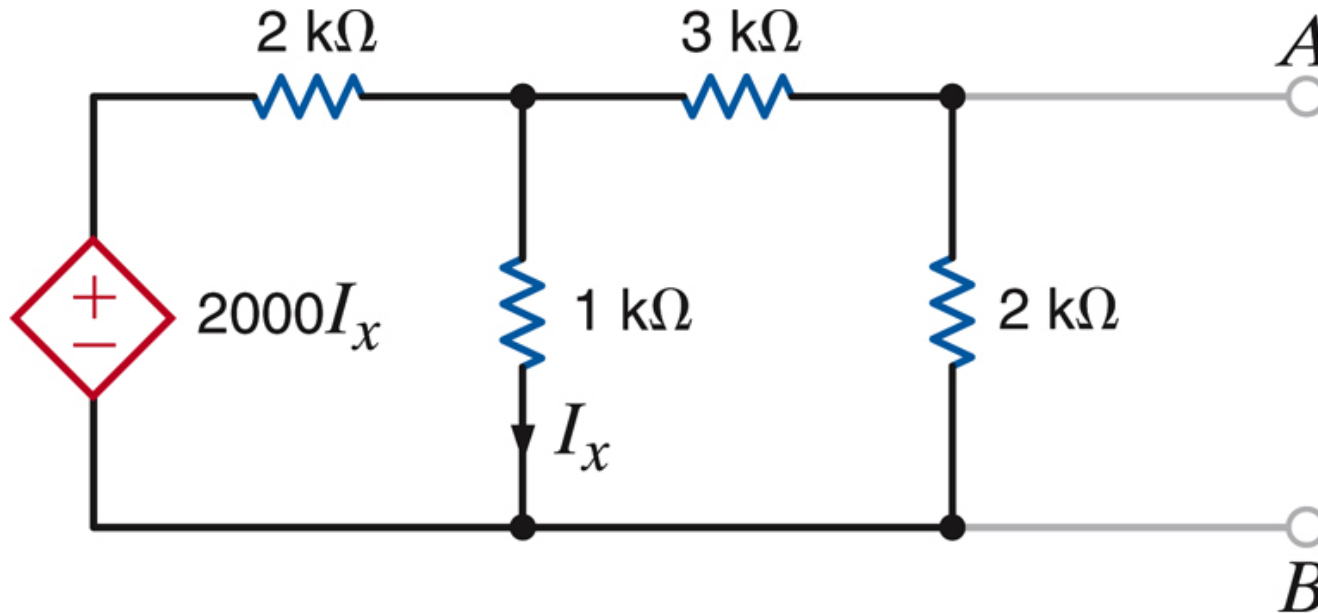What is the Thévenin equivalent of this circuit at AB terminal?




What is the value of V_{oc} ? $V_{oc} = 0V$

What is the value of I_{sc} ? $I_{sc} = 0A$


What is the value of R_{Th} ? $R_{Th} = V_{oc}/I_{sc} = 0/0 !$

How to find R_{Th} ?

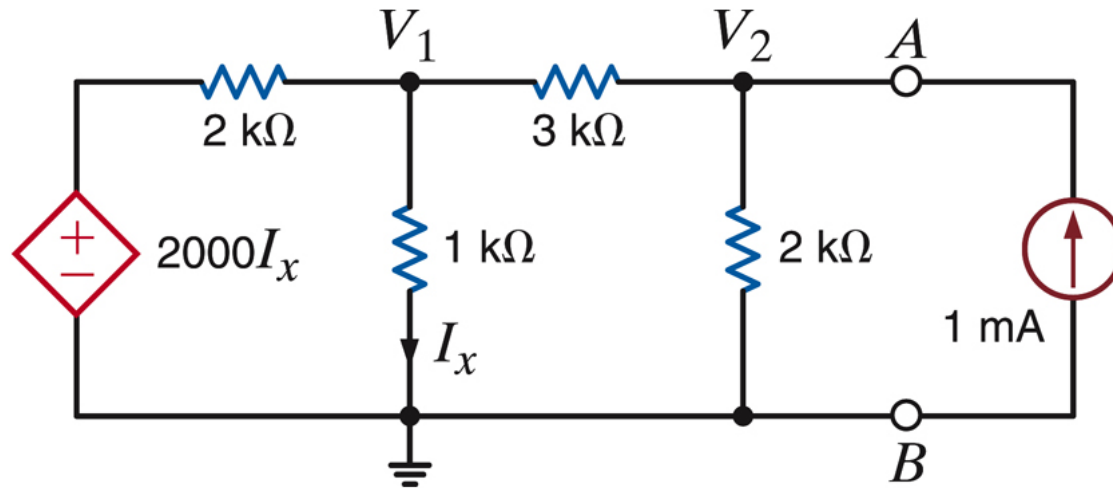
Connect a 1A (or 1mA) current source at AB terminal and measure the voltage


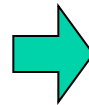
$$\begin{cases} \frac{V_1 - 2000I_x}{2\text{k}} + \frac{V_1}{1\text{k}} + \frac{V_1 - V_2}{3\text{k}} = 0 \\ \frac{V_2 - V_1}{3\text{k}} + \frac{V_2}{2\text{k}} = 1 \times 10^{-3} \end{cases}$$



$$V_2 = \frac{10}{7} \text{ V}$$

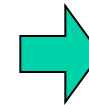

$$\begin{aligned} R_{Th} &= \frac{V_2}{1 \times 10^{-3}} \\ &= \frac{10}{7} \text{ k}\Omega \end{aligned}$$

Utility of Thévenin's & Norton's Theorems

- ❑ Thévenin's & Norton's theorems often permit us to break a large problem into several smaller problems.**
- ❑ They allow us to replace a network, no matter how large, at a pair of terminals with Thévenin or Norton equivalent circuit.**
- ❑ In fact, we could represent the entire US power grid at a pair of terminals with one of the equivalent circuits.**

Summary of how to apply Thévenin and Norton Theorems

- I. Circuits with all independent sources
 - 1) Break circuit at point of interest
 - 2) Calculate $V_{oc} = V_{Th}$; Or, calculate I_{sc}
 - 3) Short voltage sources and open current sources; calculate R_{Th}

Summary of how to apply Thévenin and Norton Theorems

II. Circuits with only dependent sources

- 1) Generally don't break the circuit anywhere; usually have an output we are interested in
- 2) Put test voltage (or current) at output
- 3) Calculate I_{in} (or V_{in}) due to test voltage
- 4) $R_{Th} = V_{test}/I_{in}$ or, $R_{Th} = V_{in}/I_{test}$; There is neither a voltage source nor a current source in the equivalent circuit

Note: Do not short (or open) dependent sources

Summary of how to apply Thévenin and Norton Theorems

III. Circuits with independent and dependent sources

- 1) Break circuit at point of interest
- 2) Calculate $V_{oc} = V_{Th}$
- 3) Calculate I_{sc}
- 4) $R_{Th} = V_{oc}/I_{sc}$

Note: Do not open (or short) dependent sources

Examples:

Go to examples 8-2.1 thru 8-2.3