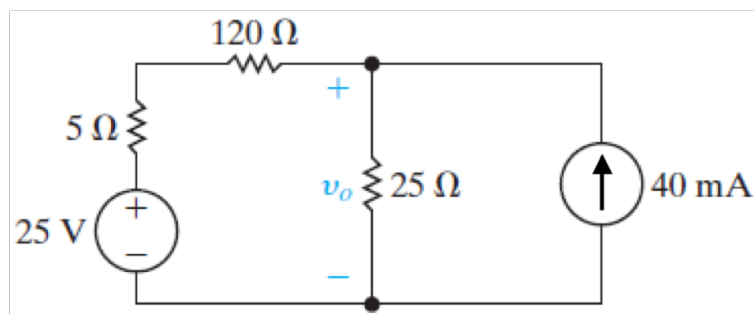



Question 1 [4]

Use the node-voltage method to find: v_o and the power developed in the voltage source.



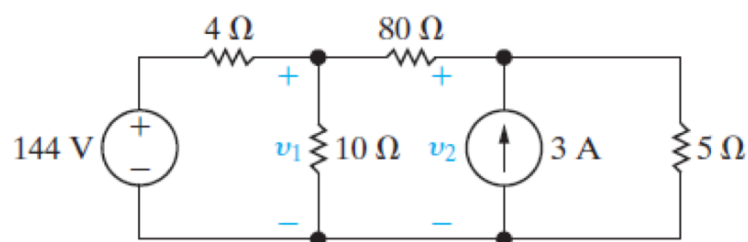
Question 2 [4]

Use the node-voltage method to find v_1 and v_2 in the circuit below.



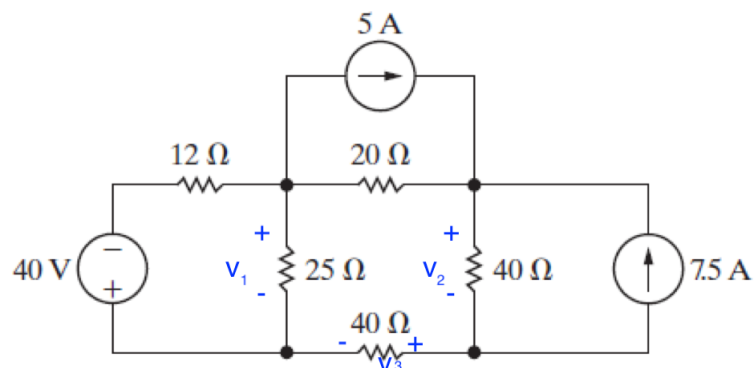
Question 3 [4]

Use the node-voltage method to find the voltages shown, v_1 , v_2 , and v_3 .



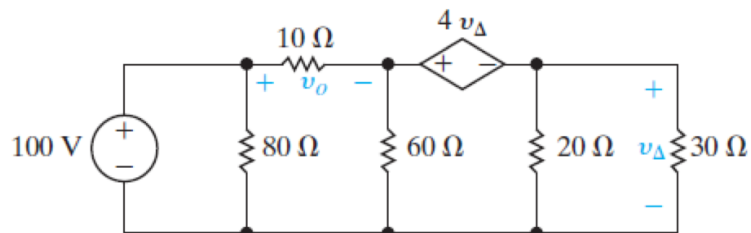
Question 4 [4]

Use the node-voltage method to find v_o in the circuit shown below.



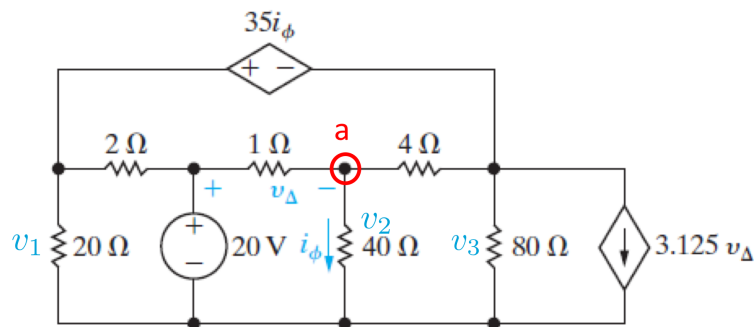Question 5 [4]

Use the node-voltage method to find: [Hints: identify the supernode and also use the node labeled **a**.]



- (a) the voltage across the $20\ \Omega$ resistor, v_1 ,
- (b) the voltage across the $40\ \Omega$ resistor, v_2 ,
- (c) the voltage across the $80\ \Omega$ resistor, v_3 ,
- (d) the controlling voltage, v_Δ ,
- (e) the controlling current, i_ϕ .