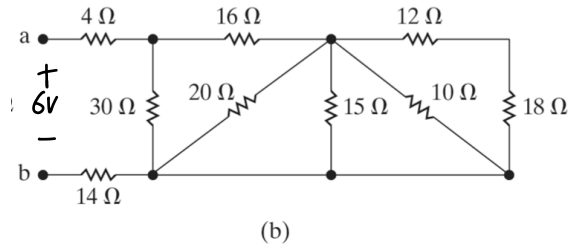


3.25 Attach a 6 V voltage source between the terminals a-b in Fig. P3.6 (b), with the positive terminal at the top.

- Use voltage division to find the voltage across the 4 Ω resistor, positive at the top.
- Use the result from part (a) to find the current in the 4 Ω resistor from left to right.
- Use the result from part (b) and current division to find the current in the 16 Ω resistor from left to right.
- Use the result from part (c) and current division to find the current in the 10 Ω resistor from top to bottom.
- Use the result from part (d) to find the voltage across the 10 Ω resistor, positive at the top.
- Use the result from part (e) and voltage division to find the voltage across the 18 Ω resistor, positive at the top.



$$a) \frac{4}{4+12+14} (6V) = 0.8V$$

$$V_{4\Omega} = 0.8V$$

$$b) V = IR \Rightarrow I = \frac{V}{R}$$

$$I = \frac{0.8V}{4\Omega} = 0.2A \quad \boxed{I = 0.2A}$$

$$c) R = 20\Omega$$

$$i = \frac{12}{20} (0.2) = 120mA$$

$$\boxed{i = 120mA}$$

$$d) \frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{15} + \frac{1}{10} + \frac{1}{30} = \frac{1}{4}$$

$$i = \frac{4}{10} (0.12) = 48mA \quad \boxed{i = 48mA}$$


$$e) V = iR \Rightarrow V = (48mA)(10\Omega)$$

$$V = 480mV$$

$$f) V = \frac{18}{30} (480mV) \quad \boxed{V = 288mV}$$

$$\frac{1}{R_{eq}} = \frac{1}{(12+18)} + \frac{1}{10} + \frac{1}{15} + \frac{1}{20} = \frac{1}{4}$$
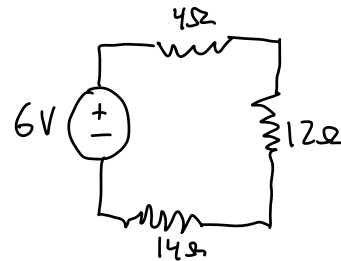
$$\frac{1}{R_{eq}} = \frac{1}{30} + \frac{1}{20} = \frac{1}{12} \quad R_{eq} = 12\Omega$$



$$a) \frac{1}{R} = \frac{1}{36} + \frac{1}{18} = \frac{1}{12} \quad R = 12\Omega$$

$$i = \frac{12\Omega}{36\Omega} (450mA) = 0.15A$$

$$\boxed{i = 150mA}$$

$$b) V = iR \quad V = (150mA)(36)$$

$$\boxed{V = 5.4V}$$

$$c) \frac{1}{R_{eq}} = \frac{1}{18} + \frac{1}{36} = \frac{1}{12}$$

$$V = \frac{12}{12+6} (5.4V) = 3.6V$$

$$\boxed{V = 3.6V}$$


$$(d)$$

$$V = \frac{10}{26+10} (3.6V) = 1V$$

$$\boxed{V = 1V}$$

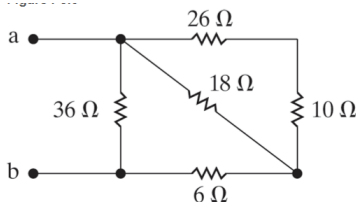3.27 Attach a 450 mA current source between the terminals a-b in Fig. P3.6 (a), with the current arrow pointing up.

- Use current division to find the current in the 36 Ω resistor from top to bottom.
- Use the result from part (a) to find the voltage across the 36 Ω resistor, positive at the top.
- Use the result from part (b) and voltage division to find the voltage across the 18 Ω resistor, positive at the top.
- Use the result from part (c) and voltage division to find the voltage across the 10 Ω resistor, positive at the top.




(a)

$$\frac{1}{R} = \frac{1}{18} + \frac{1}{36} = \frac{1}{12}$$

$$R_{eq} = 12\Omega$$

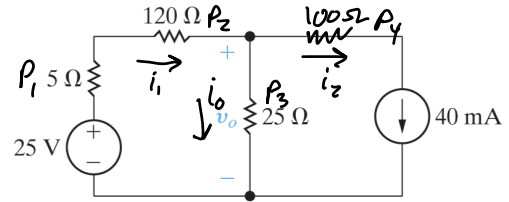4.8 **PSPICE MULTISIM** A 100 Ω resistor is connected in series with the 40 mA current source in the circuit in Fig. P4.6.

- Find v_o .
- Find the power developed by the 40 mA current source.
- Find the power developed by the 25 V voltage source.
- Verify that the total power developed equals the total power dissipated.
- What effect will any finite resistance connected in series with the 40 mA current source have on the value of v_o ?



a) Node Voltage Method

$$\frac{v_o - 25}{125} + \frac{v_o}{25} + 0.04 \text{ A} = 0$$

$$v_o - 25 + 5v_o + 5 = 0$$

$$v_o = \frac{20}{6} \Rightarrow v_o = 3.33 \text{ V}$$

b) voltage drops: $3.33 - (0.04)(100) = -0.667 \text{ V}$

$$p = Vi = (-0.667)(0.04) \Rightarrow p = 26.68 \text{ mW}$$

$$c) i = \frac{V}{R} = \frac{3.33 - 25}{125} = -173.36 \text{ mA}$$

$$P = (-173.36 \text{ mA})(25) \Rightarrow P = 4.33 \text{ W}$$

$$d) P_1 = (173.36)^2 (5) = 150.27 \text{ mW}$$

$$P_2 = (173.36)^2 (120) = 3.61 \text{ W}$$

$$P_3 = \frac{(3.33)^2}{25} = 443.56 \text{ mW}$$

$$P_4 = (0.04)^2 (100) = 160 \text{ mW}$$


$$P_{\text{dev}} = 4.33 + 0.02668 = 4.357 \text{ W}$$

$$P_{\text{dis}} = 0.15027 + 3.61 + 0.44356 + 0.16 = 4.36 \text{ W}$$

They are Equal

e) v_o is independent of any series connected to the 40 mA current source so there will not be any effect

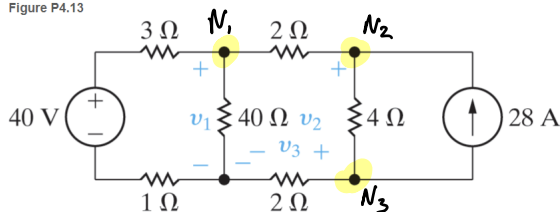4.13 **PSPICE MULTISIM** Use the node-voltage method to find v_1 , v_2 , and v_3 in the circuit in Fig. P4.13. How much power does the 16 V voltage source deliver to the circuit?



$$\underline{N_1} \quad \frac{v_1}{40} + \frac{v_1 - v_2}{2} + \frac{v_1 - 40}{4} = 0 \quad (1)$$

$$\underline{N_2} \quad \frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{4} - 28 = 0 \quad (2)$$

$$\underline{N_3} \quad 28 + \frac{v_2}{2} + \frac{v_3 - v_2}{4} = 0 \quad (3)$$

$$\underline{N_1}: v_1 + 20v_1 - 20v_2 + 10v_1 - 400 = 0$$

$$31v_1 - 20v_2 = 400 \quad (1)$$

$$\underline{N_2}: 2v_2 - 2v_1 + v_2 - v_3 - 112 = 0$$

$$-2v_1 + 3v_2 - v_3 = 112 \quad (2)$$

$$\underline{N_3}: -v_2 + 3v_3 = -112 \quad (3)$$

$$v_1 = \frac{400}{31} + \frac{20}{31} v_2$$

$$v_3 = \frac{v_2}{3} - \frac{112}{3}$$

sub eq 2

$$-2\left(\frac{400}{31} + \frac{20}{31}v_2\right) + 3v_2 - \left(\frac{v_2}{3} - \frac{112}{3}\right) = 112$$

$$-\frac{40}{31}v_2 + 3v_2 - \frac{v_2}{3} = 112 + \frac{800}{31} - \frac{112}{3}$$

$$v_2 = 73 \text{ V}$$

$$\underline{v_2 = 73 \text{ V}}$$

Eq 1

$$31v_1 - 20(73) = 400$$

$$\underline{v_1 = 60 \text{ V}}$$

Eq 3

$$-73 + 3v_3 = -112$$


$$\underline{v_3 = -13 \text{ V}}$$

4.21 PSPICE MULTISIM

a) Find the node voltages v_1 , v_2 , and v_3 in the circuit in Fig. P4.21.

b) Find the total power dissipated in the circuit.

Figure P4.21

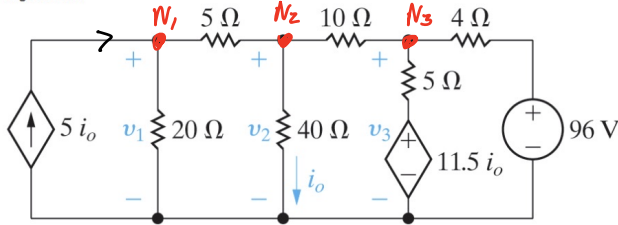

$$N_1: -\frac{v_2}{8} + \frac{v_1}{20} + \frac{v_1}{5} - \frac{v_2}{5} = 0$$

$$-5v_2 + 2v_1 + 8v_1 - 8v_2 = 0$$

$$10v_1 - 13v_2 = 0 \quad (1)$$

$$N_2: \frac{v_2}{40} + \frac{v_2}{5} - \frac{v_1}{5} + \frac{v_2}{10} - \frac{v_3}{10} = 0$$

$$v_2 + 8v_2 - 8v_1 + 4v_2 - 4v_3 = 0$$

$$-8v_1 + 13v_2 - 4v_3 = 0 \quad (2)$$

$$N_3: \frac{v_3}{10} - \frac{v_2}{10} + \frac{v_3}{5} - \frac{11.5}{5} \left(\frac{v_2}{40} \right) + \frac{v_3}{4} - 24 = 0$$

$$20v_3 - 20v_2 + 40v_3 - 11.5v_2 + 50v_3 - 4800 = 0$$

$$-31.5v_2 + 110v_3 = 4800 \quad (3)$$

$$N_1: -5i + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0$$

$$N_2: \frac{v_2}{40} + \frac{v_2 - v_1}{5} + \frac{v_2 - v_3}{10} = 0$$

$$N_3: \frac{v_3 - v_2}{10} + \frac{v_3 - 11.5i_o}{5} + \frac{v_3 - 96}{4} = 0$$

$$i_o = \frac{v_2}{40}$$

$$Eq 1: v_1 = \frac{13v_2}{10}$$

$$Eq 3: v_3 = \frac{4800}{110} + \frac{31.5}{110} v_2$$

$$Eq 2$$

$$-8 \left(\frac{13}{10} \right) v_2 + 13v_2 - 4 \left(\frac{4800}{110} + \frac{31.5}{110} v_2 \right) = 0$$

$$v_2 \left(-\frac{52}{5} + 13 - \frac{63}{55} \right) - \frac{192}{11} = 0$$

$$v_2 = 120V$$

$$Sub Eq 1: v_1 = \frac{13}{10} (120) = 156V$$


$$v_1 = 156V$$

$$Sub Eq 3: v_3 = \frac{4800}{110} + \frac{31.5}{110} (120)$$

$$v_3 = 78V$$

4.22 PSPICE MULTISIM Use the node-voltage method to find the value of v_o in the circuit in Fig. P4.22.

Figure P4.22

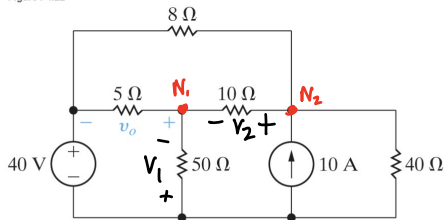

$$v_o + 40 - v_1 = 0$$

$$v_o = 50 - 40$$

$$v_o = 10V$$

$$N_1: \frac{v_1 - 40}{5} + \frac{v_1}{50} + \frac{v_1 - v_2}{10} = 0 \Rightarrow 10v_1 - 400 + v_1 + 5v_1 - 5v_2 = 16v_1 - 5v_2 - 400$$

$$N_2: \frac{v_2 - v_1}{10} + \frac{v_2}{40} - 10 + \frac{v_2 - 40}{8} = 0 \Rightarrow 4v_2 - 4v_1 + v_2 - 400 + 5v_2 - 200 = 0$$

$$-4v_1 + 10v_2 - 600 = 0$$

$$Eq 1 \Rightarrow v_1 = 25 + \frac{5}{16} v_2$$

$$Eq 2 \Rightarrow -4 \left(25 + \frac{5}{16} v_2 \right) + 10v_2 - 600 = 0$$

$$-100 - \frac{5}{4} v_2 + 10v_2 - 600 = 0$$

$$v_2 = \frac{700}{10 - \frac{5}{4}}$$

$$v_2 = 80V$$

$$Sub in Eq 1$$


$$v_1 = 25 + \frac{5}{16} (80)$$

$$v_1 = 50V$$

4.23 PSPICE MULTISIM

- a) Use the node-voltage method to find the branch currents i_1 , i_2 , and i_3 in the circuit in Fig. P4.23.
- b) ~~Check your solution for i_1 , i_2 , and i_3 by showing that the power dissipated in the circuit equals the power developed.~~

Figure P4.23

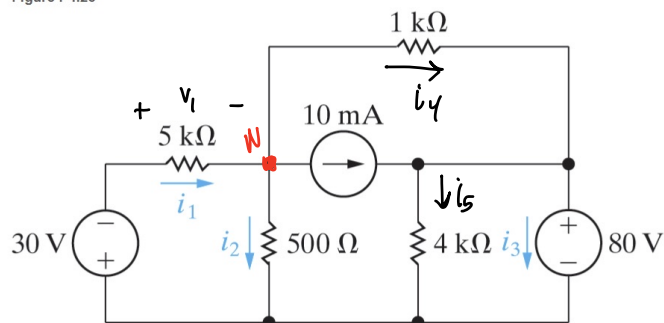

$$\underline{N} \quad \frac{v_1 - 30}{5000} + \frac{v_1}{500} + \frac{v_1 - 80}{1000} + 0.01 = 0$$

$$v_1 + 30 + 10v_1 + 5v_1 - 400 + 50 = 0$$

$$16v_1 = 320$$

$$v_1 = 20V$$

$$i_1 = \frac{-v_1 - 30}{5000} \Rightarrow i_1 = -0.01A \text{ or } i_1 = -10mA$$

$$i_2 = 0.04A \text{ or } 40mA$$

$$i_3 = 10mA - i_4 - i_5$$

$$i_4 = \frac{(80 - 20)}{1000} = 0.06A$$

$$i_5 = \frac{80}{4000} = 0.02A$$

$$i_3 = 0.01 - 0.06 - 0.02$$

$$i_3 = -0.07A \text{ or } -70mA$$