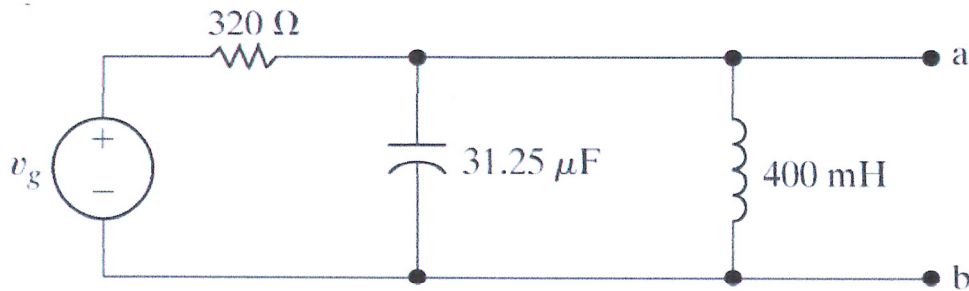


Question 1 [15]

The sinusoidal voltage source in the circuit below is developing a voltage equal to $50\sin(400t)V$.



- Find the Thevenin voltage with respect to terminals a,b. Express in both complex ($a + jb$) and Phasor form.
- Find the Thevenin impedance with respect to terminals a,b (in complex form).
- Draw the Thevenin equivalent circuit using a voltage source, resistor, capacitor and/or inductor.

a) $Z_R = 320$

$Z_L = j(400)(0.400) = j160$

$Z_C = \frac{1}{j(400)(31.25 \times 10^{-6})} = -j80$

VOLTAGE DIVIDER

$$V_{ab} = \frac{Z_C \parallel Z_L}{Z_R + (Z_C \parallel Z_L)} (-j50)$$

$$= \frac{-j160}{320 - j160} (-j50)$$

$$= \frac{-j}{2 - j} \left(\frac{2+j}{2+j} \right) (-j50)$$


$$= \frac{1-j^2}{5} (-j50)$$

$$V_{TH} = -20 - j10$$

$$= 22.4 \angle -153.43^\circ$$

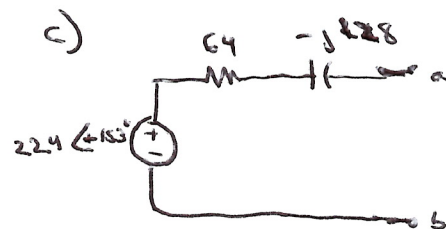b) $I_{sc} = \frac{-j50}{-j80} = \frac{1}{j6.4}$

$$Z_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{-20 - j10}{(1/j6.4)} = 64 - j128$$




$$Z_{TH} = 64 - j128$$

$$= 64 + \left(\frac{-j}{1/128} \right)$$

↑ ↑
R C

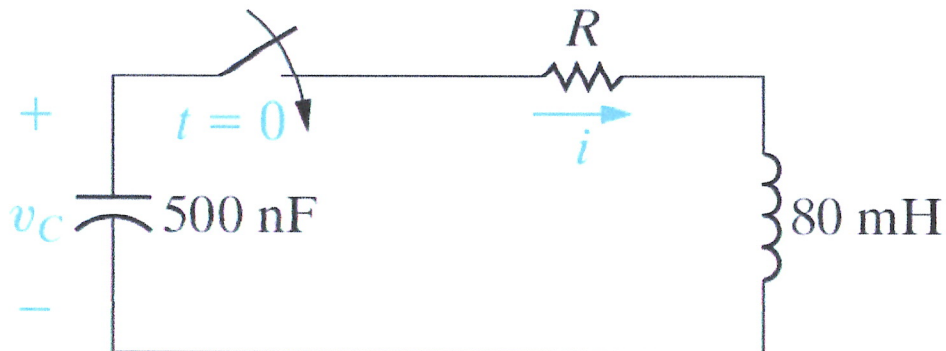Question 2 [15]

Find the value of R that makes the below circuit Critically Damped.



$$\omega_0^2 = \frac{1}{LC} = \frac{1}{(0.080)(500 \times 10^{-9})} = 25 \times 10^6$$


$$\alpha = \frac{R}{2L} = \omega_0 \text{ for critically damped}$$

$$R = 2(0.080)(5 \times 10^3)$$

$$\boxed{R = 800 \Omega}$$

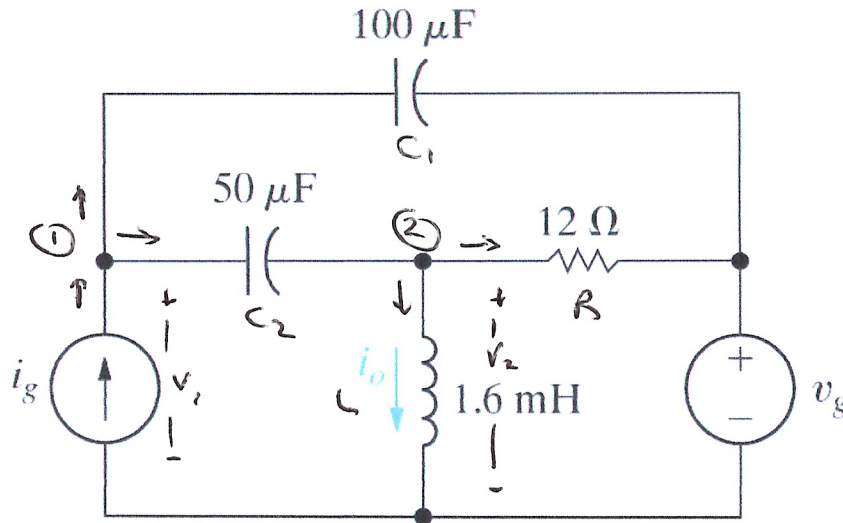Question 3 [15]

Use the Node-Voltage method to find the matrix representation of V_1 and V_2 if $i_g = 5 \cos(2500t)A$ and $v_g = 20 \cos(2500t + 90^\circ)V$. You do NOT need to solve for V_1 and V_2 , nor reduce the matrix to reduced row echelon form.



$$Z_R = 12$$

$$Z_L = j(2500)(0.0016) = j4$$

$$Z_{C1} = \frac{1}{j(2500)(100 \times 10^{-6})} = -j4$$

$$Z_{C2} = \frac{1}{j(2500)(50 \times 10^{-6})} = -j8$$

$$I_g = 5 \angle 0^\circ A = 5$$

$$V_g = 20 \angle 90^\circ V = j20$$

$$\textcircled{1} \quad 5 - \frac{V_1 - V_2}{-j8} - \frac{V_1 - j20}{-j4} = 0$$

$$5 + \frac{jV_1 - jV_2}{8} + \frac{jV_1 - 20}{4} = 0$$

$$j\frac{3}{8}V_1 - j\frac{1}{8}V_2 = 0$$



$$\textcircled{2} \quad \frac{V_1 - V_2}{-j8} - \frac{V_2}{j4} - \frac{V_2 - j20}{12} = 0$$

$$j\frac{1}{8}V_1 + \left(-\frac{1}{12} + j\frac{1}{8}\right)V_2 = -\frac{5}{3}j$$

$$\begin{bmatrix} j0.375 & -j0.125 & 0 \\ j0.125 & -0.83 + j0.125 & -j1.66 \end{bmatrix}$$

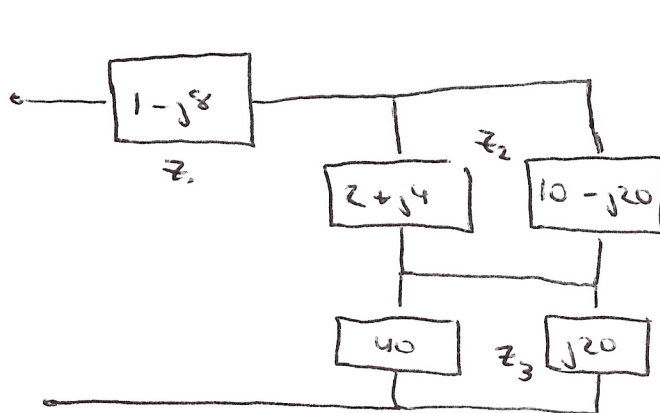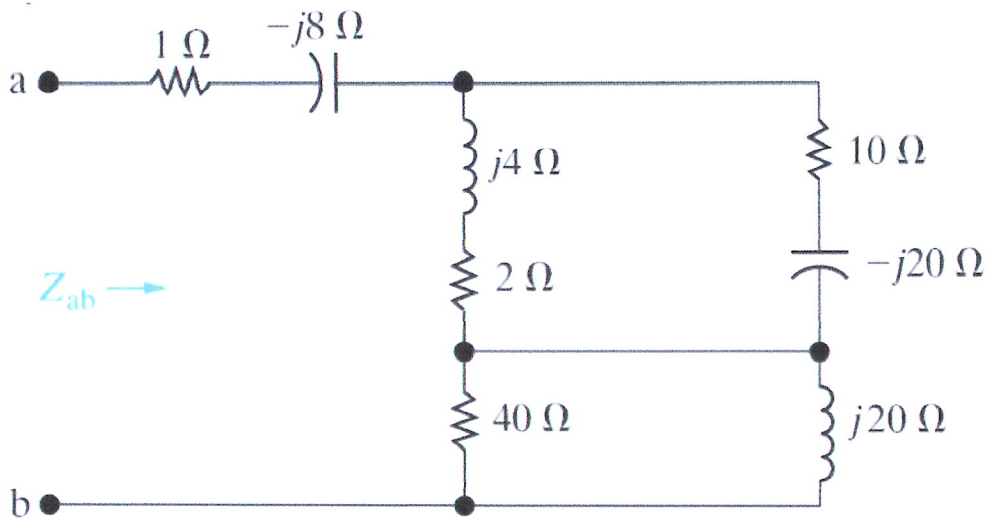Question 4 [15]


Find Z_{eq} (Z_{ab}) for the circuit below.



$$\begin{aligned}
 Z_{ab} &= Z_1 + Z_2 + Z_3 \\
 &= (1 - j8) + (3 + j4) + (8 + j16) \\
 &= 12 + j12 \Omega
 \end{aligned}$$

$$\begin{aligned}
 (2 + j4) \parallel (10 - j20) &\Rightarrow \frac{1}{Z_2} = \frac{1}{2 + j4} + \frac{1}{10 - j20} \\
 \Rightarrow \frac{1}{Z_2} &= \frac{2 - j4}{20} + \frac{1}{5} \left(\frac{2 + j4}{20} \right) \\
 &= \frac{2 - j4}{20} + \frac{2 + j4}{100} \\
 &= \frac{100}{2000} (12 - j16) = \frac{12 - j16}{200} \\
 Z_2 &= \frac{200}{12 - j16} = \frac{200}{400} (12 + j16) = 3 + j4 \\
 40 \parallel j20 &\Rightarrow \frac{1}{Z_3} = \frac{1}{40} + \frac{1}{j20} \\
 &= \frac{1}{j40} + \frac{2}{j40} \\
 &= \frac{2 + j}{j40} \\
 Z_3 &= \frac{j40}{2 + j} = \frac{j40(2 - j)}{(2 + j)(2 - j)} = \frac{j80 + 40}{5} \\
 &= \frac{40}{5} (1 + j2) \\
 &= 8 + j16
 \end{aligned}$$

Question 5 [20]

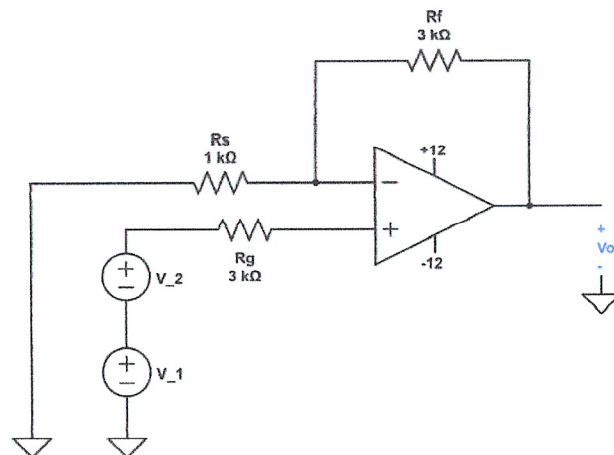

- What is the voltage at the inverting input (v_n) in terms of v_1 and v_2 .
- Using Kirchhoff's Current Law, what is the equation for currents at the inverting input node?
- Using KCL Equation from (b), derive the equation for v_o as a function of v_1 and v_2 . What is the gain of this op amp circuit?
- If $v_1 = 1V$ and $v_2 = 3 * \cos(\frac{\pi}{2}t)$, draw a graph of v_o vs time. Show at least two periods of the output.

a) IDEAL OP AMP

$$v_n = v_p = v_1 + v_2$$

b) IDEAL OP AMP

$$i_n = 0$$

$$\text{KCL: } \frac{v_o - v_n}{3k} - \frac{v_n}{1k} = 0 \Rightarrow \frac{v_o - (v_1 + v_2)}{3k} - \frac{(v_1 + v_2)}{1k} = 0$$

$$c) \Rightarrow v_o - v_n - 3v_n = 0$$

$$v_o = 4v_n = 4(v_1 + v_2)$$


GAIN 4

$$d) v_1 + v_2 = 1 + 3 \cos\left(\frac{\pi}{2}t\right)$$

$$\omega = 2\pi f \Rightarrow f = \frac{1}{4}$$


$$\text{period} = \frac{1}{f} = 4 \text{ seconds}$$

SATURATION AT $\pm 12V$

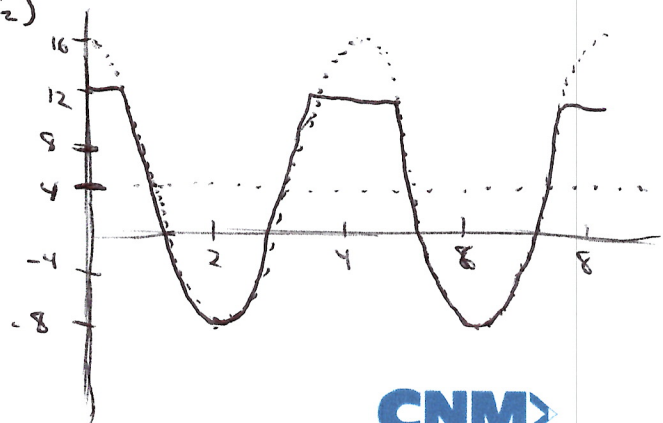


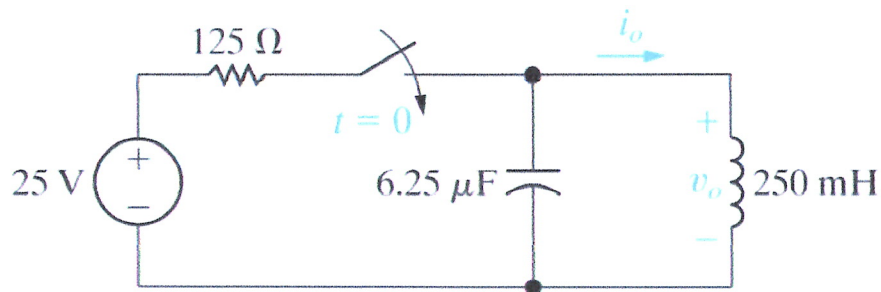Question 6 [20]

Assume there is no energy stored in the circuit below when the switch is closed at $t = 0$.



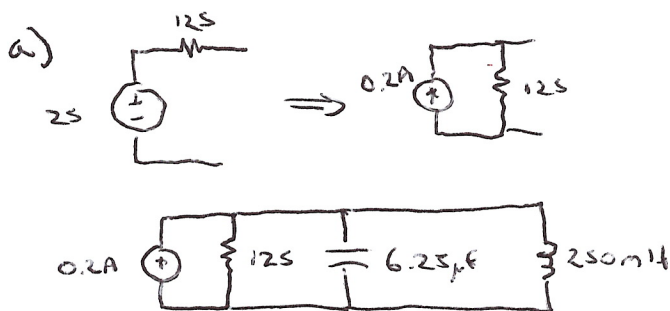- Using the Source Transformation, redraw the circuit as a parallel RLC circuit.
- Find $i_o(t)$ for $t \geq 0$.



$$b) \quad \alpha = \frac{1}{2RC} = 640 \quad \omega^2 = 40.96 \times 10^4 \quad \left. \vphantom{\alpha} \right\} \text{UNDER DAMPED}$$

$$\omega_o^2 = \frac{1}{LC} = 64 \times 10^4$$

$$\omega_d = \sqrt{800^2 - 640^2} = 480$$

$$I_s = 0.2 \text{ A}$$

$$i_o(t) = 0.2 + B_1' e^{-400t} \cos(480t) + B_2' e^{-400t} \sin(480t)$$

$$i_o(0) = 0.2 + B_1' \Rightarrow B_1' = -0.2$$

$$\frac{di_o}{dt}(0) = -\alpha B_1' + \omega_d B_2' = \frac{V_o}{L} \quad V_o = 0 \text{ V}$$

$$\Rightarrow -640(-0.2) + 480 B_2'$$

$$\Rightarrow B_2' = -0.267$$

$$i_o(t) = 0.2 - 0.2 e^{-400t} \cos(480t) + 0.267 e^{-400t} \sin(480t)$$

Extra Credit

Who was Max Salazar (either a factual or humorous answer will be accepted)?