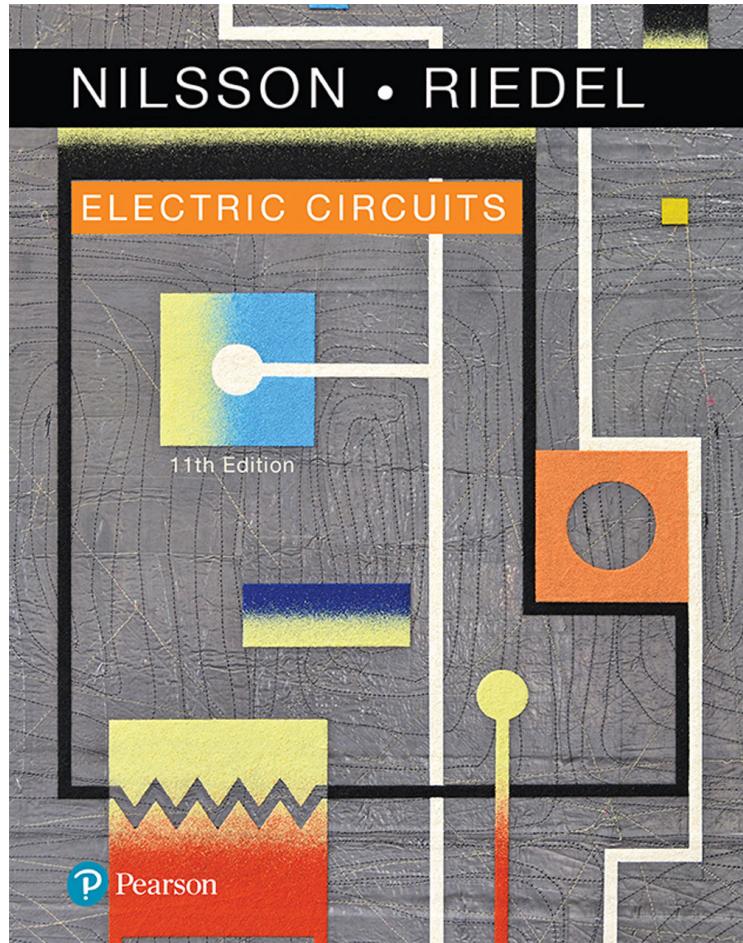


# Electric Circuits

Eleventh Edition



## Chapter 9

### Sinusoidal Steady-State Analysis

# Practical Perspective - A Household Distribution Circuit



Yulia Grigoryeva/Shutterstock



Björn Erlandsson /123RF




Tetra Images/Alamy Stock Photo

# Why Sinusoidal Source?

- The generation, transmission, distribution, and consumption of electrical energy occur under essentially sinusoidal steady-state conditions.
- An understanding of sinusoidal behavior makes it possible to predict the behavior of circuits with nonsinusoidal sources.
- Steady-state sinusoidal behavior often simplifies the design of electrical systems.

A Household  
Distribution  
Circuit

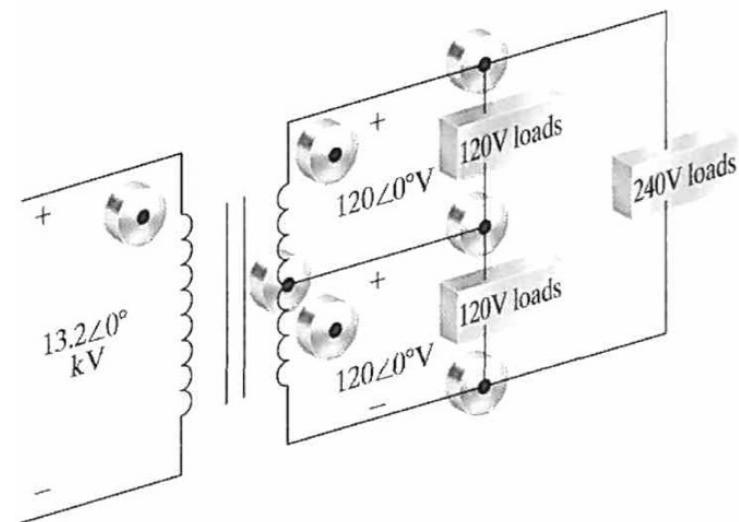

# Learning Objectives

- Sinusoidal Source & Response
- The Phasor
- Passive Circuits Elements in the Frequency Domain
- Kirchoff's Laws (Frequency Domain)
- Circuit Simplifications (Frequency Domain)
- Source Transformations (Frequency Domain)
- Node-Voltage & Mesh Current Methods (Freq. Domain)
- Transformers
- Phasor Diagrams

# 9.1 Sinusoidal Source

- We can generate emf's using rotating coils.
- This is the basis of power generation for the transmission of electricity and communications devices.
- Devices that generate the power are typically **sinusoidal**, time-varying sources - **Alternating Current (ac)** sources.
- **A sinusoidal voltage/current source** (independent or dependent) produces a voltage/current that varies sinusoidally with time.

$$v(t) = V_m \cos(\omega t + \phi)$$

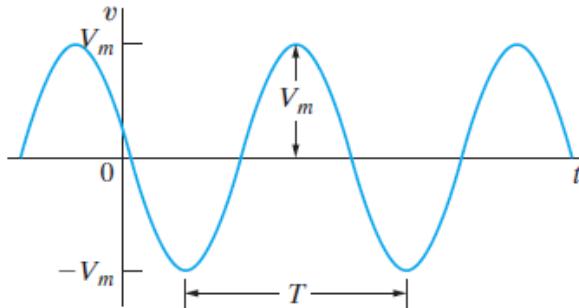


Figure 9.1: A sinusoidal voltage.

$V_m$ : Maximum amplitude

$\omega$ : Angular frequency

$\phi$ : Phase angle (radians/degrees)

$$\omega = 2\pi f = 2\pi/T$$

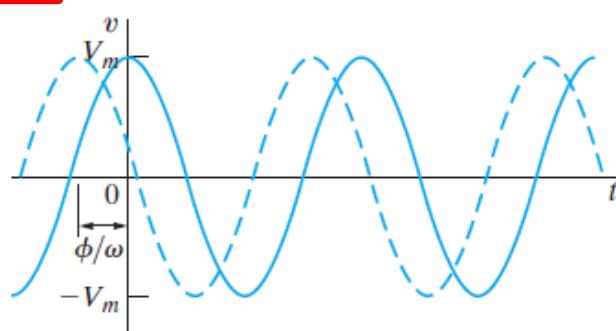


Figure 9.2: The sinusoidal voltage from Fig. 9.1 shifted to the right when  $\phi = 0$ .

$f$ : Frequency

$T$ : Period

# RMS Value

- Here in the USA electrical outlets provide a voltages of 120 V or 240 V at 60 Hz  
*(In other parts of the world: 220/240 V at 50Hz)*
- Because in ac circuits the voltage and current can both be positive and negative, it is convenient to define the **root mean square** (rms) voltage or current.
- The **rms** value of a periodic function is defined as the **square root** of the **mean value of the squared function**:

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$



$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} \quad \longrightarrow \quad \text{Power}$$

We can completely describe a specific sinusoidal signal if we know its *frequency*, *phase angle*, and *amplitude* (either the maximum or the rms value).

## 9.2 Sinusoidal Response

$$v_s = V_m \cos(\omega t + \phi)$$



$$L \frac{di}{dt} + Ri = V_m \cos(\omega t + \phi)$$




$$i = \boxed{\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t}} + \boxed{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)}$$

Transient component

Steady-state component

As "t → ∞"

Figure 9.5: An *RL* circuit excited by a sinusoidal voltage source.

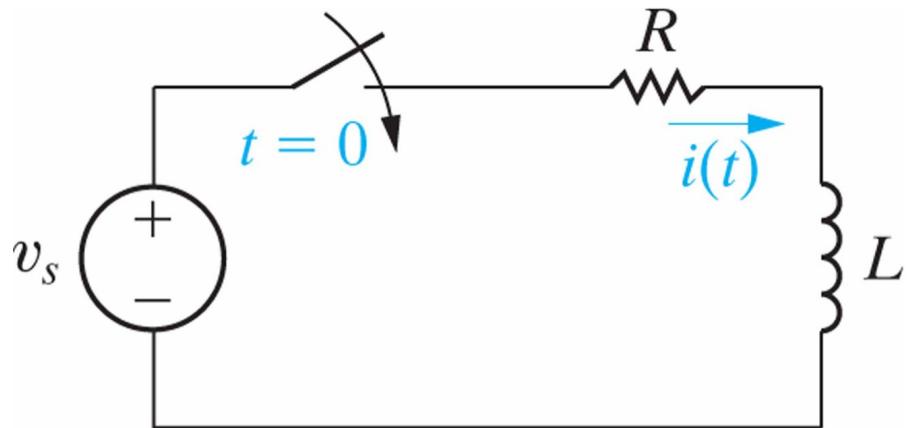

# Steady-State Solution

- The steady-state solution is a sinusoidal function.
- The frequency of the response signal is identical to the frequency of the source signal. *This condition is always true in a linear circuit when the circuit parameters, R, L, and C, are constant.*
- The maximum amplitude of the steady-state response, in general, differs from the maximum amplitude of the source. For the circuit discussed, the maximum amplitude of the response signal is  $V_m/\sqrt{R^2+\omega^2L^2}$ , and that of the signal source is  $V_m$ .
- The phase angle of the response signal, in general, differs from the phase angle of the source. For the circuit being discussed, the phase angle of the current is  $\phi - \theta$  and that of the voltage source is  $\phi$ .

Here we will develop an alternative method using vectors/complex numbers.

# 9.3 The Phasor

The **phasor** is a complex number that carries the **amplitude** and **phase angle** information of a sinusoidal function (see Appendix B).

## Complex Numbers Review


$$j = \sqrt{-1}$$

Rectangular and polar complex variables are related:

$$z = x + jy = |z|e^{j\theta}$$

real part

imaginary part

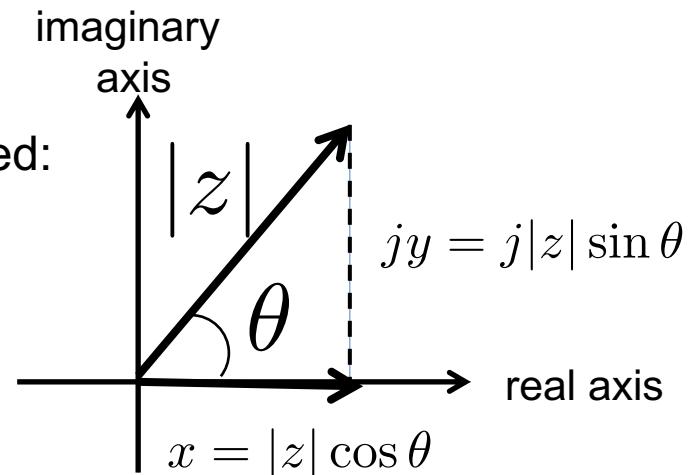


Amplitude:  $|z|^2 = zz^* = (x + jy)(x - jy) = x^2 + y^2$

Phase:  $\tan \theta = \frac{y}{x}$
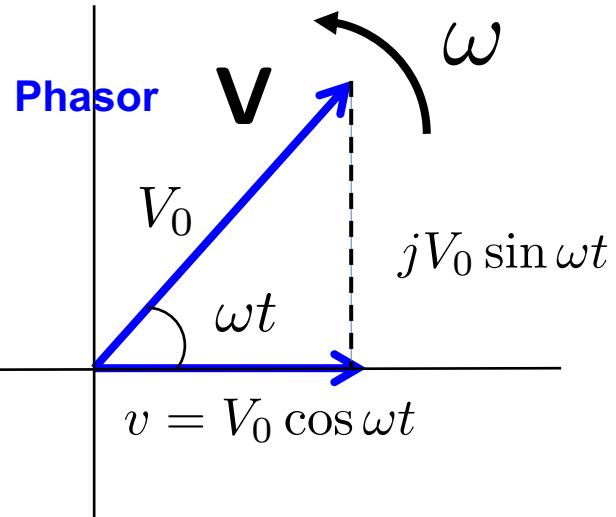
## Phasor Notation

- At any instant in time the voltage is described by its **amplitude** and **phase angle**.
- Instantaneous voltage given by projection onto **real (horizontal) axis**.
- We can combine this information into “one” complex number:



**Phasor**  $\mathbf{V} = V_0 \exp(j\omega t) = \underbrace{V_0 \cos \omega t}_{\text{real part}} + j \underbrace{V_0 \sin \omega t}_{\text{imag. part}}$

(use Euler's identity:  $e^{j\theta} = \cos \theta + j \sin \theta$  )

$$\implies v(t) = \Re(\mathbf{V}) = \Re[V_0 \exp(j\omega t)] = V_0 \cos \omega t$$

# Phasor & Inverse Phasor Transform

Phasor Transform & Angle Notation:

$$\mathbf{V} = V_m e^{j\phi} = \mathcal{P}\{V_m \cos(\omega t + \phi)\} \rightarrow \mathbf{V} = V_m \cos \phi + jV_m \sin \phi$$

$$1/\cancel{\phi^\circ} \equiv 1e^{j\phi}$$

Inverse Phasor Transform:

$$\mathcal{P}^{-1}\{V_m e^{j\phi}\} = \Re\{V_m e^{j\phi} e^{j\omega t}\}$$



$$\mathbf{V} = 100 \angle -26^\circ \rightarrow v = 100 \cos(\omega t - 26)$$

The **phasor transform** is useful in circuit analysis because it reduces the task of finding the maximum amplitude and phase angle of the steady-state sinusoidal response to the algebra of complex numbers.

# 9.4 PASSIVE CIRCUIT ELEMENTS IN THE FREQUENCY DOMAIN

- The transient component vanishes as  $t \rightarrow \infty$ , so *the steady-state component of the solution must also satisfy the differential equation governing the circuit.*
- In a linear circuit driven by sinusoidal sources, the steady-state response also is sinusoidal, and *the frequency of the sinusoidal response is the same as the frequency of the sinusoidal source.*
- Using the **phasor notation**, we can postulate that the steady-state solution is of the form  $R\{Ae^{j\beta}e^{j\omega t}\}$ , where  $A$  is the maximum amplitude of the response and  $\beta$  is the phase angle of the response.
- When we substitute the postulated steady-state solution into the differential equation, the exponential terms  $e^{j\omega t}$  cancel out, leaving the solution for  $A$  and  $\beta$  in the domain of complex numbers or **frequency domain**.

## The V-I Relationship for a Resistor

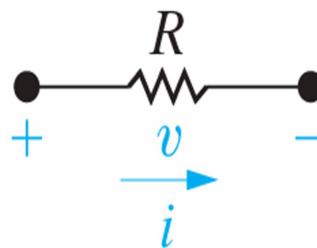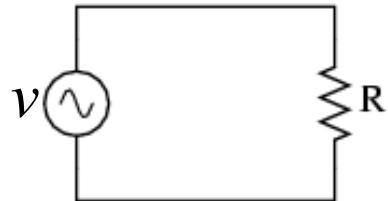

$$v = V_0 \cos \omega t$$




sinusoidal ac source with angular frequency  $\omega = 2\pi f$



$$\text{Ohm's Law} \quad v = iR$$

$$i = \frac{v}{R} = \frac{V_0}{R} \cos \omega t = I_0 \cos \omega t$$

current **IN phase** with voltage

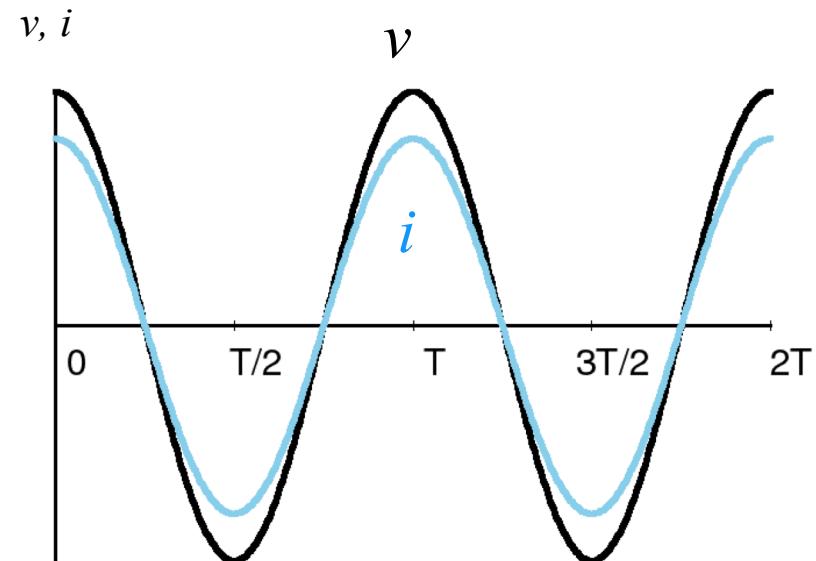

## The V-I Relationship for an Inductor

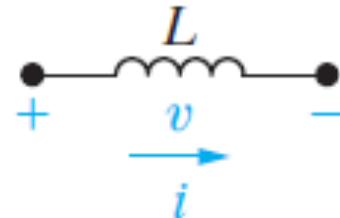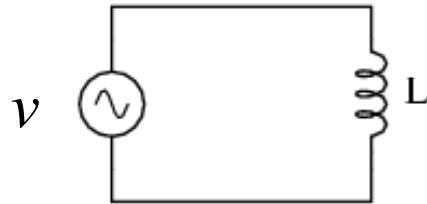


$$v = V_0 \cos \omega t$$

(integrate)

$$v = L \frac{di}{dt} \rightarrow i = \frac{V_0}{\omega L} \sin \omega t$$
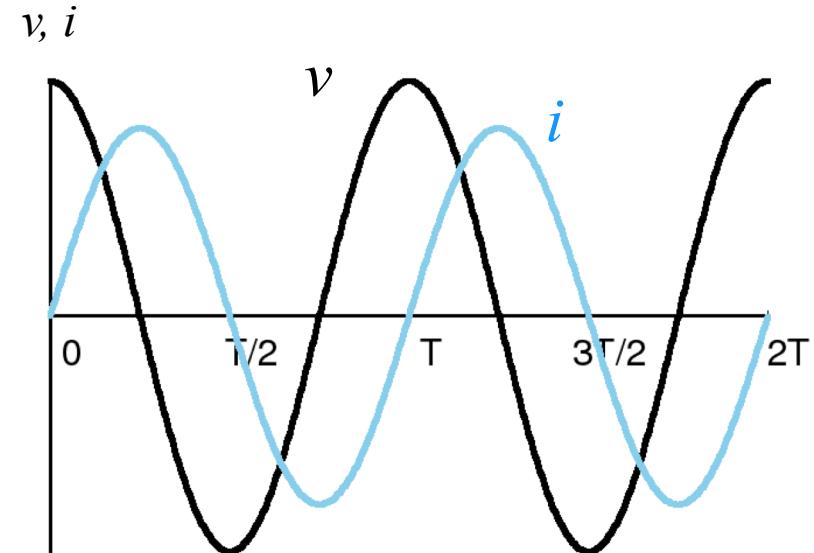
$$i = \frac{V_0}{\omega L} \cos \left( \omega t - \frac{\pi}{2} \right) = \frac{V_0}{X_L} \cos(\omega t - 90^\circ)$$





current **LAGS** voltage by  $90^\circ$

**inductive reactance**

$$\frac{V_0}{I_0} = \omega L = X_L$$

## The V-I Relationship for a Capacitor

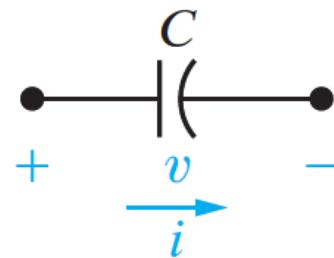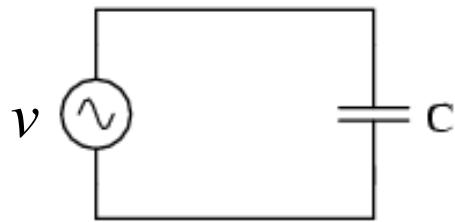

$$v = V_0 \cos \omega t$$

(differentiate)


$$v = \frac{q}{C} \rightarrow i = C \frac{dv}{dt} = -\omega C V_0 \sin \omega t$$

$$i = \omega C V_0 \cos \left( \omega t + \frac{\pi}{2} \right) = \frac{V_0}{X_C} \cos(\omega t + 90^\circ)$$

current **LEADS** voltage by  $90^\circ$

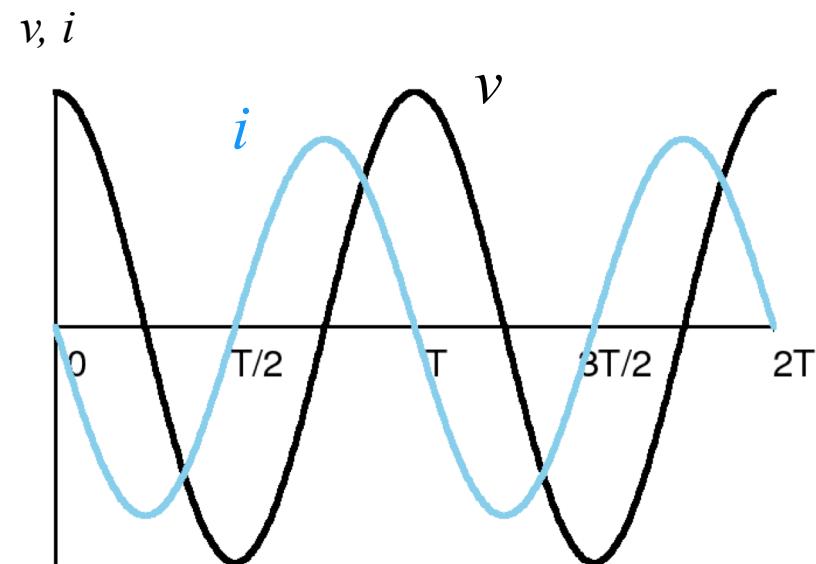**capacitive reactance**

$$\frac{V_0}{I_0} = \frac{1}{\omega C} = X_C$$



# Illustration

$$i_{ss}(t) = \Re \{ I_m e^{j\beta} e^{j\omega t} \}$$



$$\Re \{ j\omega L I_m e^{j\beta} e^{j\omega t} \} + \Re \{ R I_m e^{j\beta} e^{j\omega t} \} = \Re \{ V_m e^{j\phi} e^{j\omega t} \}$$




$$\Re \{ (j\omega L + R) I_m e^{j\beta} e^{j\omega t} \} = \Re \{ V_m e^{j\phi} e^{j\omega t} \}$$



$$(j\omega L + R) I_m e^{j\beta} = V_m e^{j\phi}$$


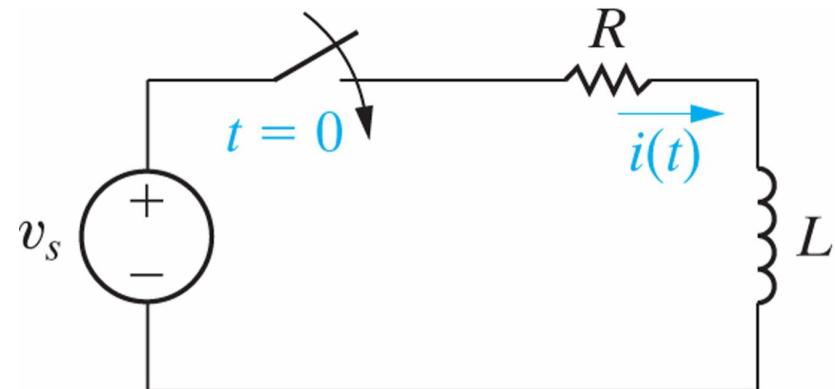
$$I_m e^{j\beta} = \frac{V_m e^{j\phi}}{R + j\omega L}$$



- The phasor transform, along with the inverse phasor transform, allows you to go back and forth between the time domain and the frequency domain. Therefore, when you obtain a solution, you are either in the time domain or the frequency domain. You cannot be in both domains simultaneously. Any solution that contains a mixture of time and phasor domain nomenclature is nonsensical.
- The phasor transform is also useful in circuit analysis because it applies directly to the sum of sinusoidal function, if

$$v = v_1 + v_2 + \dots + v_n$$

When all the voltages on the righthand side are sinusoidal voltages of the same frequency, then

$$\mathbf{V} = \mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n$$

# 9.12 Phasor Diagrams

- We can now apply our phasor concept to solve problems in the frequency domain.
- We do this by plotting our phasors in the complex plane.
- The benefit comes from the fact that we can simply **add phasors**.
- Before we do this we have to introduce the concept of **impedance**.
- We've already seen this in our development of inductive and capacitive reactance.
- Impedance follows from the V-I relations we just derived.

## Resistance Phasor


$$i = \frac{V_0}{R} \cos \omega t$$

$$\mathbf{i} = \frac{V_0}{R} \exp(j\omega t)$$

$$\mathbf{V} = V_0 \exp(j\omega t)$$

$$\mathbf{i} = \mathbf{V}/R$$

$$\boxed{\mathbf{V} = R\mathbf{i}}$$

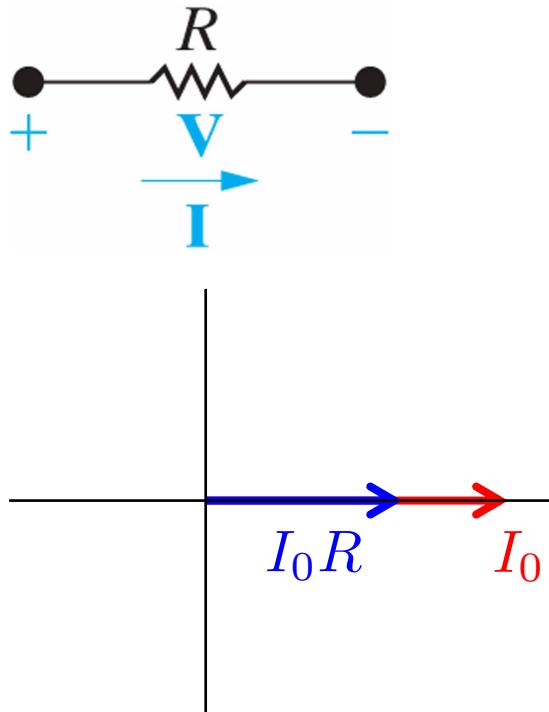

More generally

$$v = R[I_m \cos(\omega t + \theta_i)]$$

$$\mathbf{V} = RI_m e^{j\theta_i} = RI_m \angle \theta_i$$

## Inductive Phasor

$$i = \frac{V_0}{\omega L} \cos(\omega t - 90^\circ)$$

$$I = \frac{V_0}{\omega L} \exp \left[ j \left( \omega t - \frac{\pi}{2} \right) \right]$$


$$I = \frac{V_0}{\omega L} \exp(j\omega t) \exp \left( -j \frac{\pi}{2} \right) = \frac{\mathbf{V}}{\omega L} \exp \left( -j \frac{\pi}{2} \right)$$

$$\mathbf{V} = \underbrace{\omega L I \exp \left( j \frac{\pi}{2} \right)}_{=j} \quad \boxed{\mathbf{V} = j X_L I}$$

More generally


$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \theta_i)$$
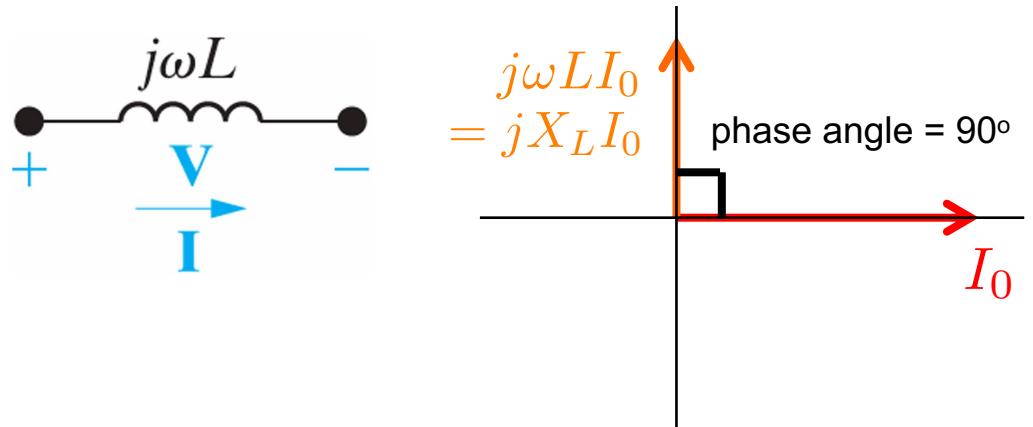
$$\mathbf{V} = (\underline{\omega L / 90^\circ}) \underline{I_m / \theta_i} = \underline{\omega L I_m / (\theta_i + 90^\circ)}$$



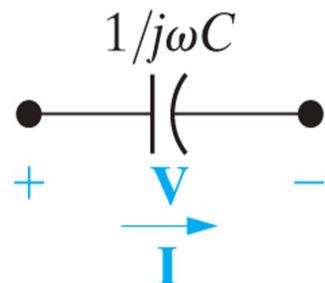
## Capacitive Phasor

$$i = \omega C V_0 \cos(\omega t + 90^\circ)$$



$$\mathbf{I} = \omega C V_0 \exp \left[ j \left( \omega t + \frac{\pi}{2} \right) \right]$$
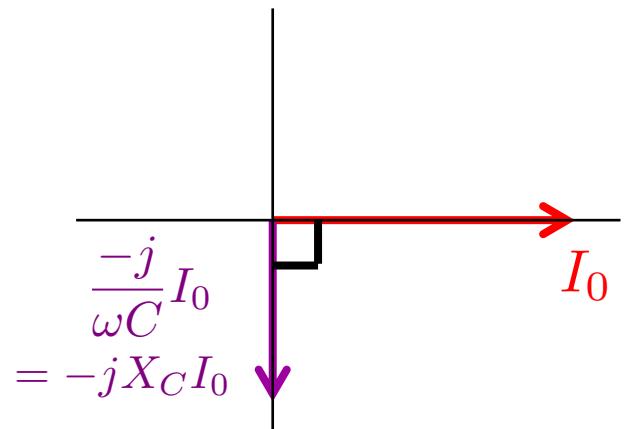
$$\mathbf{I} = \underbrace{\omega C \mathbf{V}}_{=j} \exp \left( j \frac{\pi}{2} \right)$$



$$\mathbf{V} = -j X_C \mathbf{I}$$

More generally

$$i = C \frac{dv}{dt} \quad v = V_m \cos(\omega t + \theta_v)$$

$$\mathbf{V} = \frac{1}{\omega C} \angle -90^\circ I_m \angle \theta_i = \frac{I_m}{\omega C} \angle (\theta_i - 90)^\circ$$

# Impedance and Reactance

Resistance

$$\mathbf{V} = R\mathbf{I}$$

Inductance

$$\mathbf{V} = jX_L \mathbf{I}$$

Capacitance

$$\mathbf{V} = -jX_C \mathbf{I}$$

All voltage-current relations look like Ohm's Law:

$$\mathbf{V} = Z\mathbf{I}$$

(complex) **Impedance**  $Z$  (units of ohms)

CIVIL

Circuit Element	Reactance $X$	Impedance $Z$	Phase $\theta$	Angle Notation
Resistor	-	R	in phase	$\mathbf{V} = RI_0 \angle 0^\circ$
Capacitor	$1/\omega C$	$-j/\omega C$	CIV Leads +90°	$\mathbf{V} = X_C I_0 \angle -90^\circ$
Inductor	$\omega L$	$j\omega L$	VIL Lags -90°	$\mathbf{V} = X_L I_0 \angle 90^\circ$



# Combining Impedances

$$\mathbf{V} = \mathbf{ZI}$$

- Impedance in ac circuits behaves like resistance in dc circuits.
- Use similar rules for combining impedances.
- Combining **impedances in series**:

$$\mathbf{V} = \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C \quad (\text{LCR circuit})$$


$$= \mathbf{Z}_R \mathbf{I} + \mathbf{Z}_L \mathbf{I} + \mathbf{Z}_C \mathbf{I} = (\mathbf{Z}_R + \mathbf{Z}_L + \mathbf{Z}_C) \mathbf{I} = \mathbf{ZI}$$

But remember impedance is a **complex** number...

# Analysis of the LRC series circuit using phasors


$$\mathbf{V} = \mathbf{V}_R + \mathbf{V}_L + \mathbf{V}_C$$

Example:  $X_L > X_C$

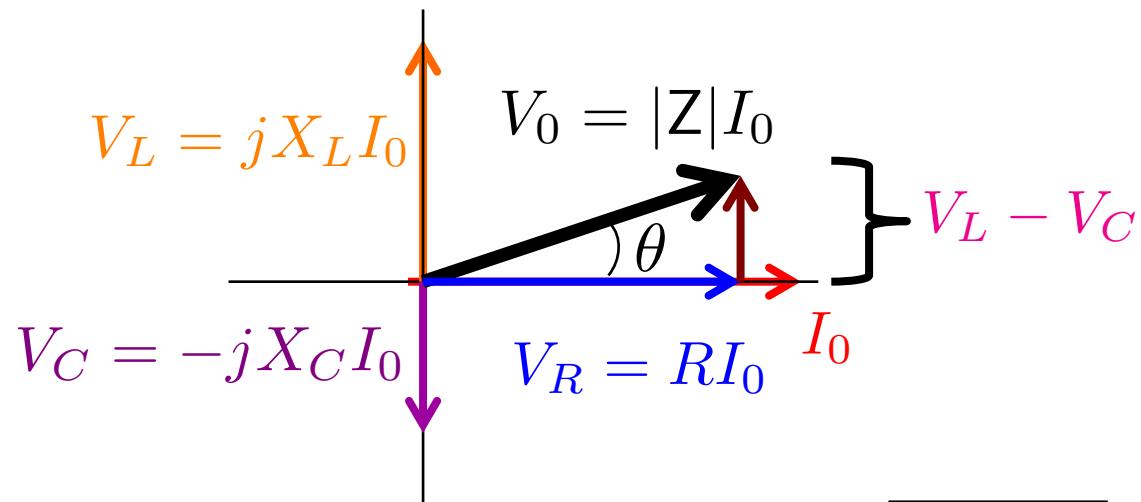

Recall:  $|z| = \sqrt{x^2 + y^2}$        $\theta = \tan^{-1} \left( \frac{y}{x} \right)$

$$x = V_R \qquad y = V_L - V_C$$

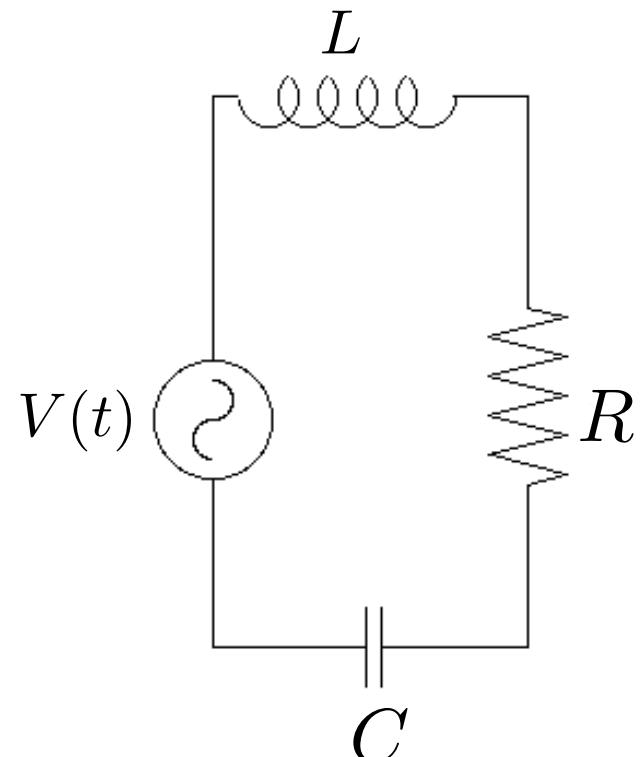


# Analysis of the LRC series circuit using phasors

$$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$= I_0 \sqrt{R^2 + (X_L - X_C)^2}$$

Example:  $X_L > X_C$

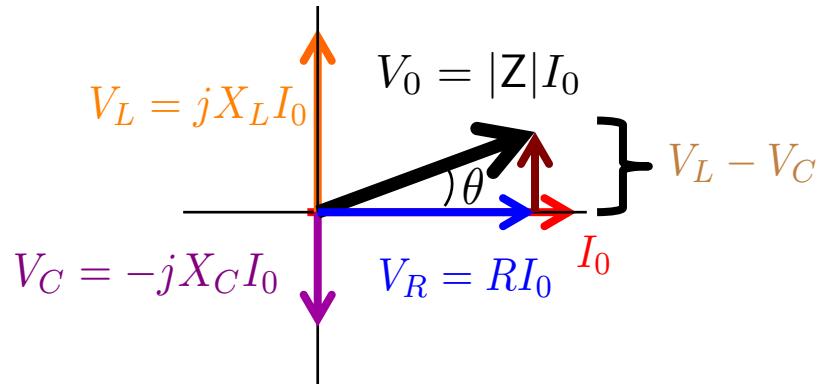

Impedance

$$V_0 = |Z|I_0 \quad \rightarrow \quad |Z| = \sqrt{R^2 + (\omega L - 1/\omega C)^2} \quad \text{impedance of LRC circuit}$$

Phase Angle:

$$\tan \theta = \frac{V_L - V_C}{V_R} = I_0 \frac{(X_L - X_C)}{I_0 R} = \frac{X_L - X_C}{R}$$

$$\rightarrow \quad \theta = \tan^{-1} \left( \frac{\omega L - 1/\omega C}{R} \right) \quad \text{phase angle of LRC circuit}$$

Angle Notation:  $\mathbf{V} = ZI_0/\theta^\circ$

## EXAMPLE: RESONANCE


### RLC CIRCUIT

- Notice from the expression for the impedance for the RLC circuit, the current can become very large for certain values of the inductance and capacitance:

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

- In particular, when  $X_L = X_C$
- This defines the resonant, or center, frequency  $\omega_0$ :

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

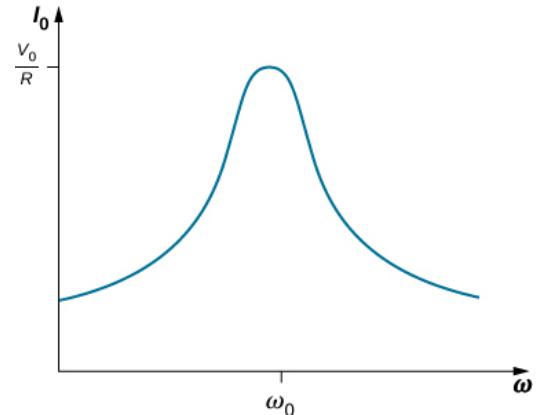

- RLC circuits were used in devices such as radios to pick out specific radio channels.

# 9.5 Kirchhoff's law in the Frequency Domain

$$v_1 + v_2 + \cdots + v_n = 0$$



$$V_{m_1} \cos(\omega t + \theta_1) + V_{m_2} \cos(\omega t + \theta_2) + \cdots + V_{m_n} \cos(\omega t + \theta_n) = 0$$



$$\Re\{V_{m_1} e^{j\theta_1} e^{j\omega t}\} + \Re\{V_{m_2} e^{j\theta_2} e^{j\omega t}\} + \cdots + \Re\{V_{m_n} e^{j\theta_n} e^{j\omega t}\}$$



$$\Re\{(V_{m_1} e^{j\theta_1} + V_{m_2} e^{j\theta_2} + \cdots + V_{m_n} e^{j\theta_n}) e^{j\omega t}\} = 0$$



$$\Re\{(\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n) e^{j\omega t}\} = 0$$




$$\text{KVL } \mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0 \quad \text{KCL } \mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_n = 0$$

# 9.6 Series, Parallel, and Delta-Wye Simplification

The rules for combining impedances in series or parallel and for making delta-to-wye transformations are the same as those for resistors. The only difference is that combining impedances involves the algebraic manipulation of complex numbers.
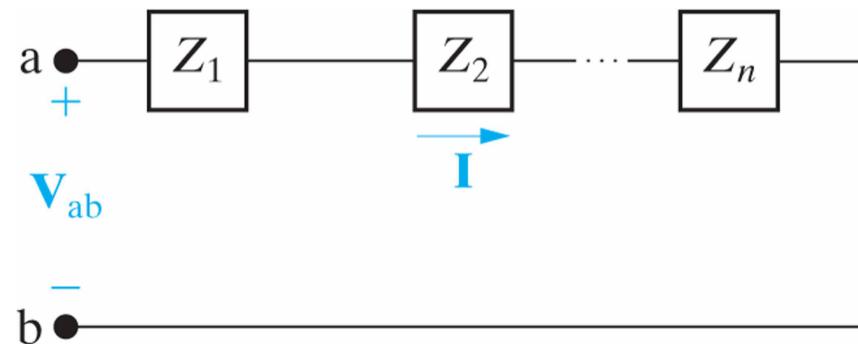
## Impedances in series:

$$\begin{aligned}\mathbf{V}_{ab} &= Z_1 \mathbf{I} + Z_2 \mathbf{I} + \dots + Z_n \mathbf{I} \\ &= (Z_1 + Z_2 + \dots + Z_n) \mathbf{I}\end{aligned}$$



$$Z_{ab} = \frac{\mathbf{V}_{ab}}{\mathbf{I}} = Z_1 + Z_2 + \dots + Z_n$$

## Impedances in parallel:

$$\mathbf{I} = \mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_n$$




$$\frac{\mathbf{V}}{Z_{ab}} = \frac{\mathbf{V}}{Z_1} + \frac{\mathbf{V}}{Z_2} + \cdots + \frac{\mathbf{V}}{Z_n}$$



$$\frac{1}{Z_{ab}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \cdots + \frac{1}{Z_n}$$

Two impedance

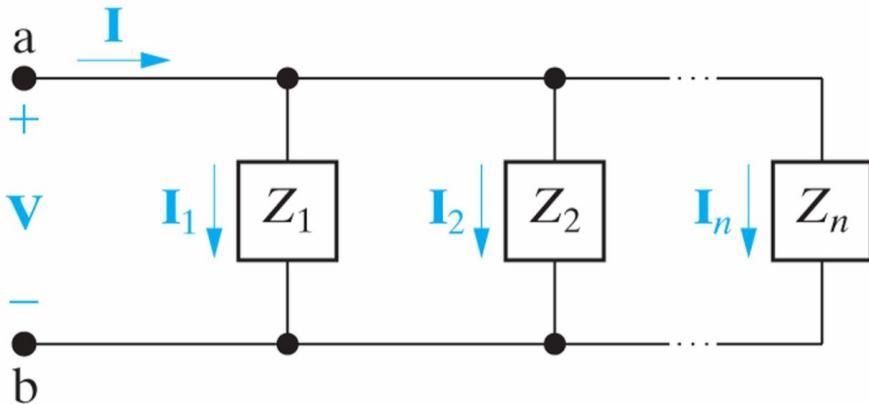

susceptance

$$Y = \frac{1}{Z} = G + jB \text{ (siemens)}$$


conductance

$$Y_{ab} = Y_1 + Y_2 + \cdots + Y_n$$

admittance

Circuit Element	Admittance ( $Y$ )	Susceptance
Resistor	$G$ (conductance)	—
Inductor	$j(-1/\omega L)$	$-1/\omega L$
Capacitor	$j\omega C$	$\omega C$

## Delta-To-Wye Transformations

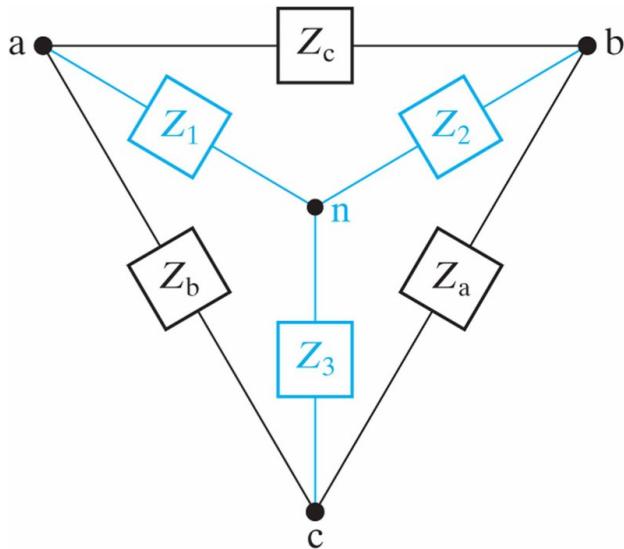

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$



$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$


$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

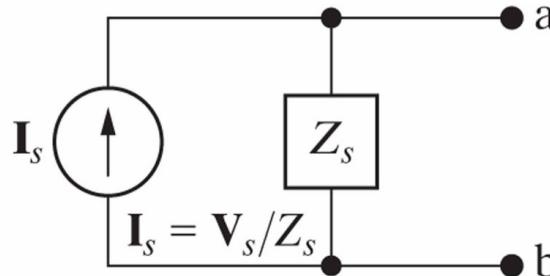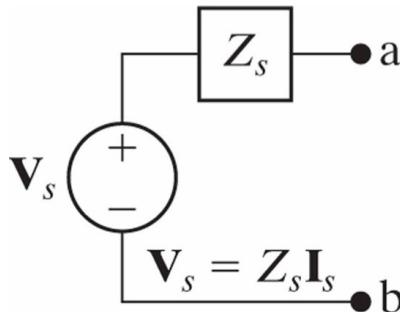
# 9.7 Source Transformations and Thévenin-Norton Equivalent Circuits



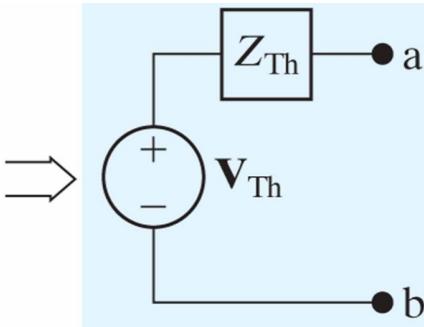● a  
Frequency-domain linear circuit; may contain both independent and dependent sources. ● b



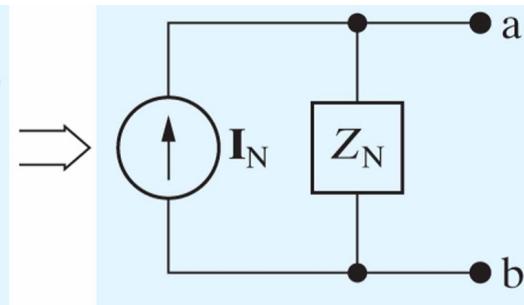● a  
Frequency-domain linear circuit; may contain both independent and dependent sources. ● b



# 9.8/9 Node-Voltage & Mesh-Current Methods

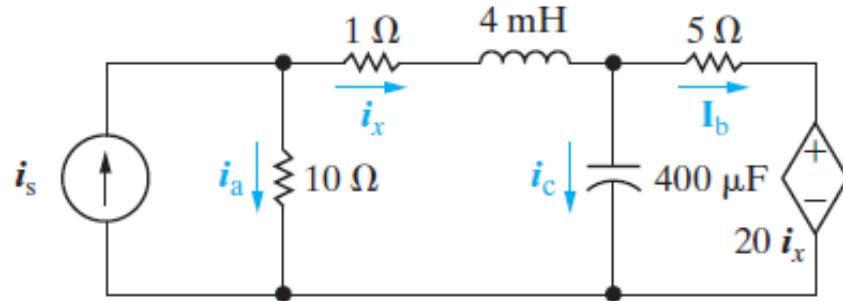


Figure 9.36: The circuit for Example 9.13.

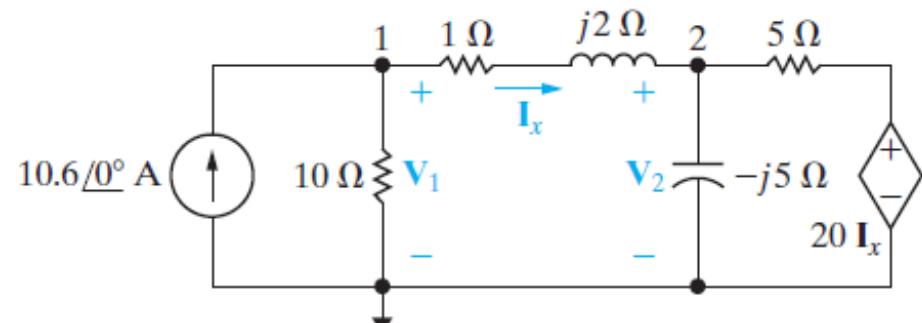


Figure 9.38: The circuit shown in Fig. 9.37, with the node voltages defined.

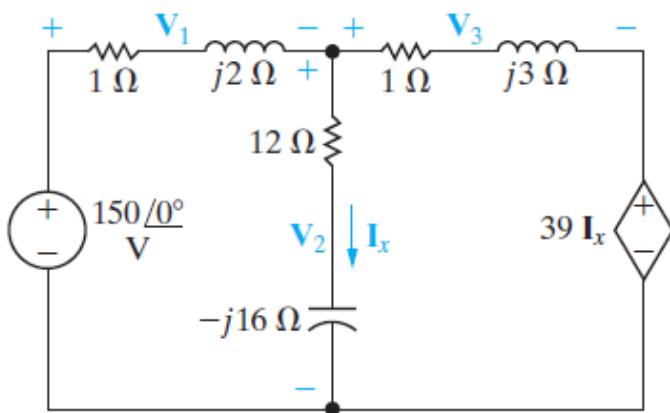


Figure 9.39: The circuit for Example 9.14.


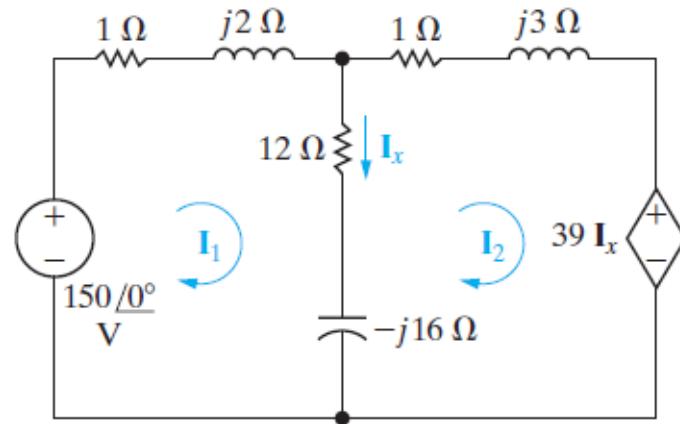


Figure 9.40: Mesh currents used to solve the circuit shown in Fig. 9.39.

# 9.10 The Transformer

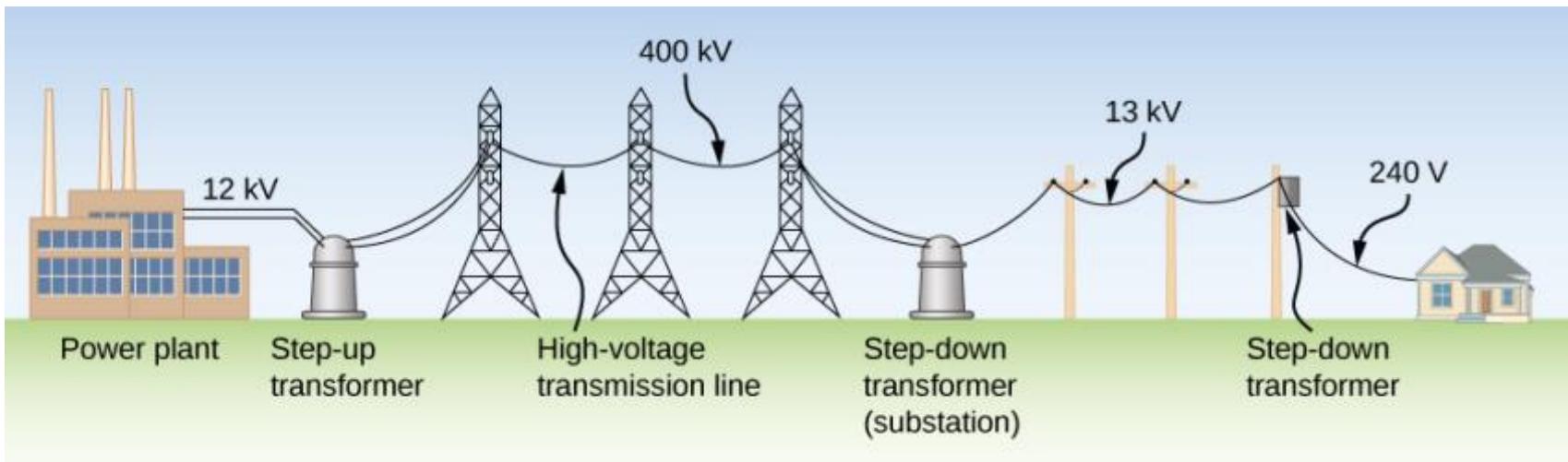

A **transformer** is a device that is based on magnetic coupling.

- Transformers are used in both communication and power circuits.
- **linear transformer:** is found primarily in communication circuits
- **Ideal transformer:** is used to model the ferromagnetic transformer found in power systems.

# TRANSFORMERS

- A **transformer** is a device for increasing or decreasing an ac voltage.
- The ac current in the primary coil creates a changing magnetic field that is fed by the iron core through the primary and secondary coils.
- The resulting changing flux generates an induced emf in both the primary (self-inductance) and secondary coils (mutual-inductance).

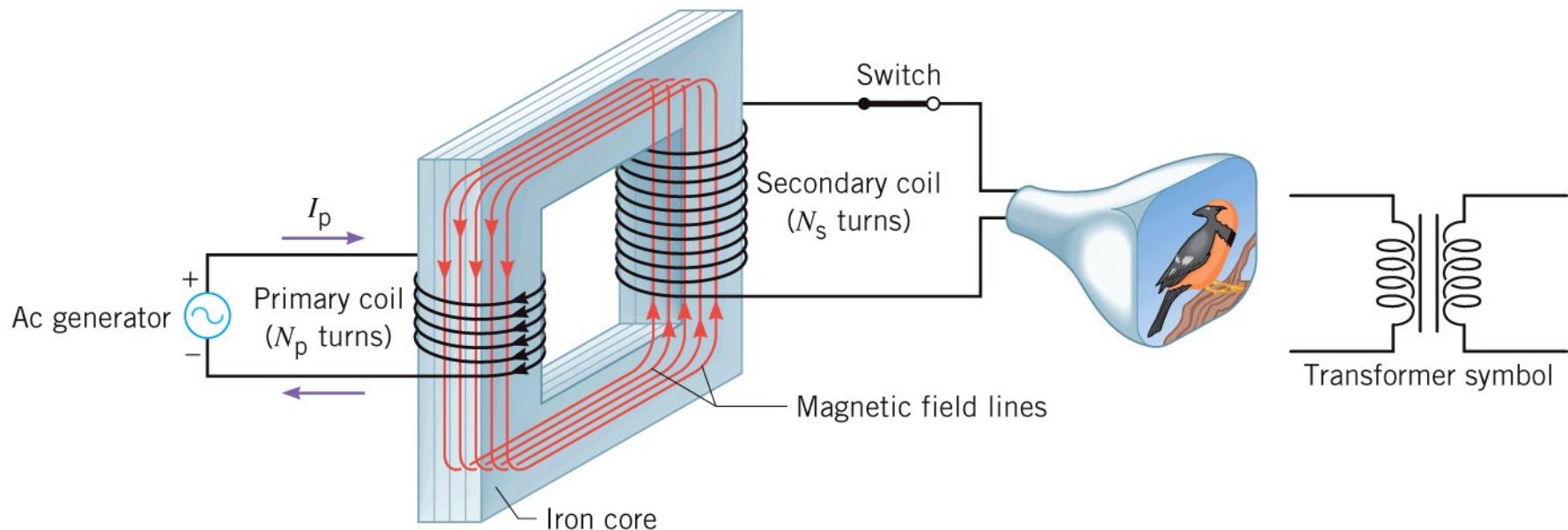


Figure 22.29

© John Wiley & Sons, Inc. All rights reserved.

# TRANSFORMER EQUATION

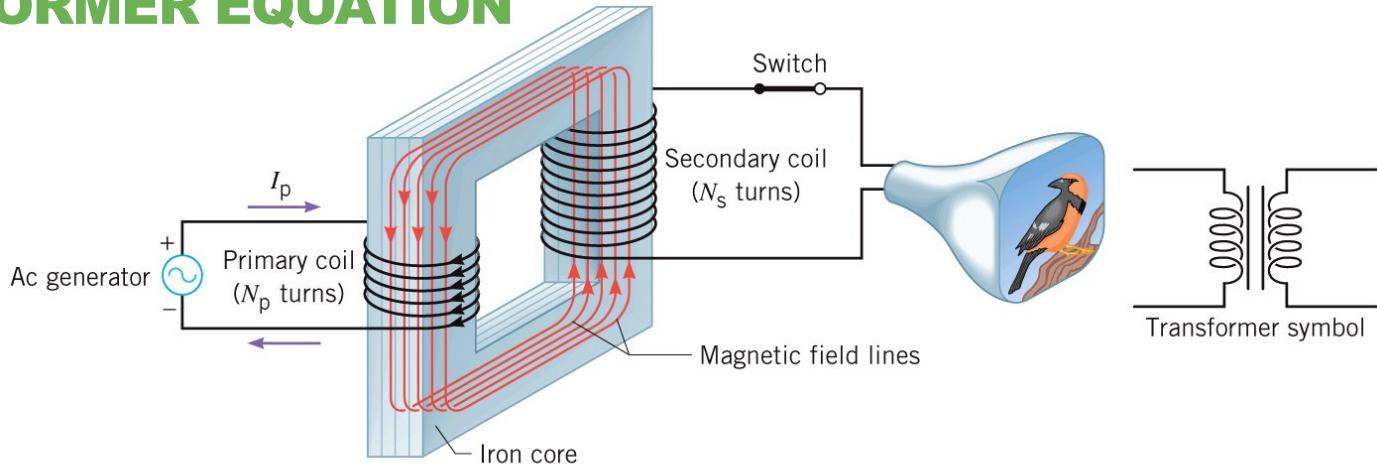


Figure 22.29  
© John Wiley & Sons, Inc. All rights reserved.

- Applying Faraday's law to both coils:
- Now using the fact that the flux is (approximately) the same in both coils:
- Finally, if the resistances in the coils are negligible, so the emfs are nearly equal to the terminal voltages, V:

$$\mathcal{E}_s = -N_s \frac{\Delta\Phi}{\Delta t} \quad \mathcal{E}_p = -N_p \frac{\Delta\Phi}{\Delta t}$$

$$\frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p}$$

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

**Transformer equation**

$N_s > N_p$ : larger secondary voltage  $\Leftrightarrow$  step-up transformer. Step-down transformer is opposite.

# POWER

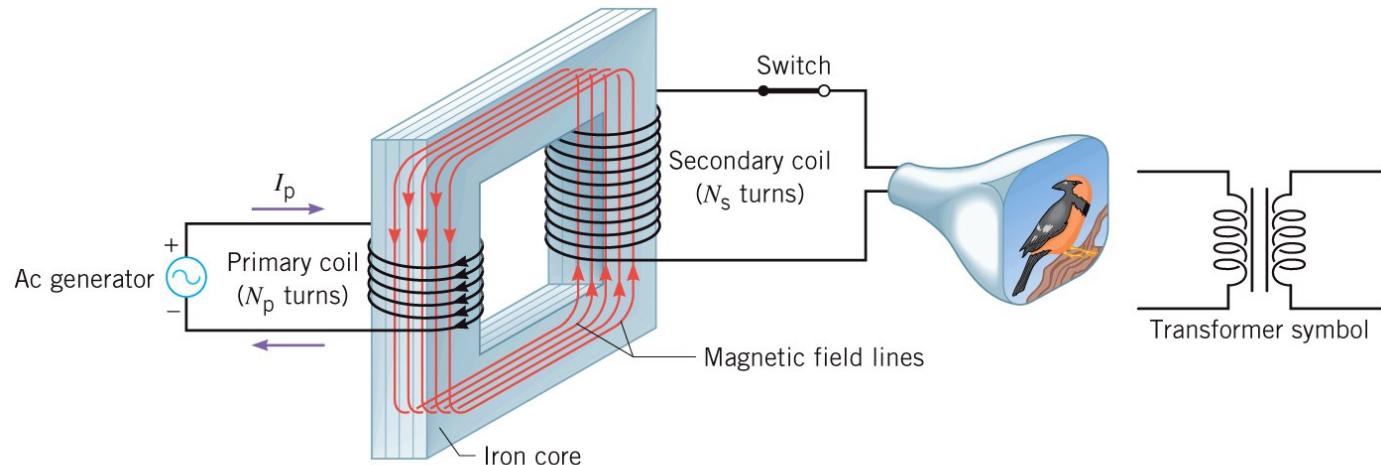


Figure 22.29  
© John Wiley & Sons, Inc. All rights reserved.

The average power delivered to each coil,  $P = IV$ , is (approximately) the same (conservation of energy):

$$\frac{I_s}{I_p} = \frac{V_p}{V_s} = \frac{N_p}{N_s}$$

Step-up transformer steps up the voltage & steps down the current.

Step-down transformer steps down the voltage & steps up the current.

# The Analysis of a Linear Transformer Circuit

A simple **transformer** is formed *when two coils are wound on a single core to ensure magnetic coupling.*

- **Primary winding:** the transformer winding connected to the source;
- **Secondary winding:** the winding connected to the load as the.


$R_1$  = the resistance of the primary winding

$R_2$  = the resistance of the secondary winding

$L_1$  = the self-inductance of the primary winding

$L_2$  = the self-inductance of the secondary winding

$M$  = the mutual inductance

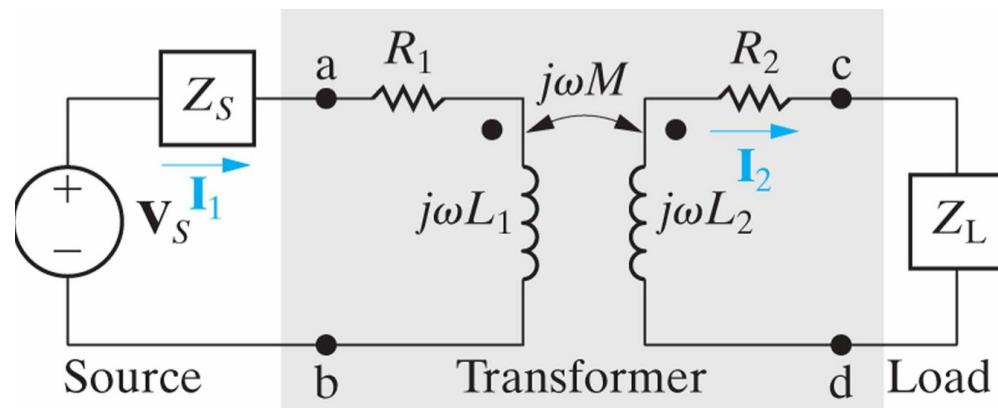


$$\mathbf{V}_s = (Z_s + R_1 + j\omega L_1)\mathbf{I}_1 - j\omega M\mathbf{I}_2$$

$$0 = -j\omega M\mathbf{I}_1 + (R_2 + j\omega L_2 + Z_L)\mathbf{I}_2$$



$$\boxed{Z_{11} = Z_s + R_1 + j\omega L_1}$$
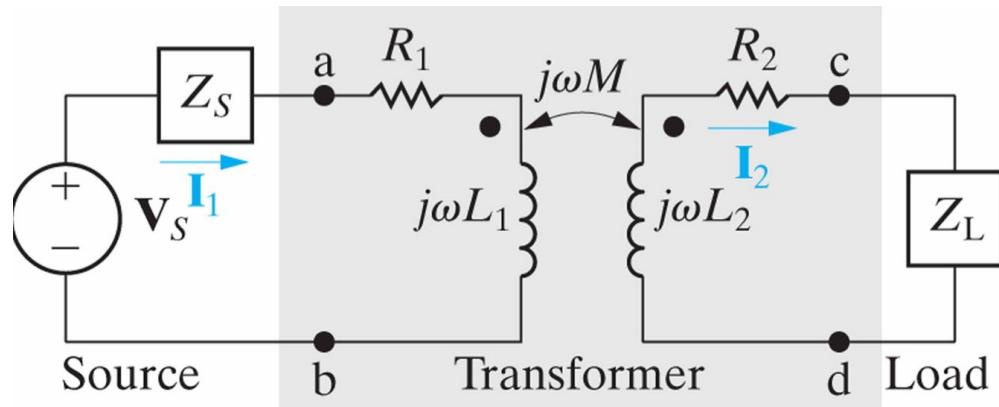
$$\boxed{Z_{22} = R_2 + j\omega L_2 + Z_L}$$



$$\mathbf{I}_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} \mathbf{V}_s \quad \mathbf{I}_2 = \frac{j\omega M}{Z_{11}Z_{22} + \omega^2 M^2} \mathbf{V}_s = \frac{j\omega M}{Z_{22}} \mathbf{I}_1$$


---



$$\frac{\mathbf{V}_s}{\mathbf{I}_1} = Z_{\text{int}} = \frac{Z_{11}Z_{22} + \omega^2 M^2}{Z_{22}} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$

$$\xrightarrow{\hspace{1cm}} Z_{ab} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$

*The impedance  $Z_{ab}$  is independent of the magnetic polarity of the transformer!*

# Reflected Impedance

$$Z_{ab} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = R_1 + j\omega L_1 + \boxed{\frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}}$$

Reflected impedance  $Z_r$

$$Z_L = R_L + jX_L$$

$$\begin{aligned} Z_r &= \frac{\omega^2 M^2}{R_2 + R_L + j(\omega L_2 + X_L)} = \frac{\omega^2 M^2 [(R_2 + R_L) - j(\omega L_2 + X_L)]}{(R_2 + R_L)^2 + (\omega L_2 + X_L)^2} \\ &= \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)] \end{aligned}$$

## 9.11 The Ideal Transformer

An **ideal transformer** consists of two magnetically coupled coils having  $N_1$  and  $N_2$  turns, respectively, and exhibiting these three properties:

1. The coefficient of coupling is unity ( $k = 1$ ).
2. The self-inductance of each coil is infinite ( $L_1 = L_2 = \infty$ ).
3. The coil losses, due to parasitic resistance, are negligible.

# Exploring Limiting Values

$$Z_{ab} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{(R_2 + j\omega L_2 + Z_L)}$$



$$Z_{22} = R_2 + R_L + j(\omega L_2 + X_L) = R_{22} + jX_{22}$$

$$Z_{ab} = R_1 + \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} + j \left( \omega L_1 - \frac{\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2} \right) = R_{ab} + jX_{ab}$$

$$X_{ab} = \omega L_1 - \frac{(\omega L_1)(\omega L_2)X_{22}}{R_{22}^2 + X_{22}^2} = \omega L_1 \left( 1 - \frac{\omega L_2 X_{22}}{R_{22}^2 + X_{22}^2} \right)$$

$$M^2 = L_1 L_2$$

$$X_{22} = \omega L_2 + X_L$$

$$X_{ab} = \omega L_1 \left( \frac{R_{22}^2 + \omega L_2 X_L + X_L^2}{R_{22}^2 + X_{22}^2} \right)$$

Factoring  $\omega L_2$  out of the numerator and denominator yields:

$$X_{ab} = \frac{L_1}{L_2} \frac{X_L + (R_{22}^2 + X_L^2)/\omega L_2}{(R_{22}/\omega L_2)^2 + [1 + (X_L/\omega L_2)]^2}$$



$$L_1 \rightarrow \infty, L_2 \rightarrow \infty, \text{ and } k \rightarrow 1.0 \quad L_1/L_2 = (N_1/N_2)^2$$

$$X_{ab} = \left(\frac{N_1}{N_2}\right)^2 X_L \quad \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} = \frac{L_1}{L_2} R_{22} = \left(\frac{N_1}{N_2}\right)^2 R_{22}$$



$$Z_{ab} = R_1 + \left(\frac{N_1}{N_2}\right)^2 R_2 + \left(\frac{N_1}{N_2}\right)^2 (R_L + jX_L)$$

Scaling factor

# Determining the Voltage and Current Ratios

(a)

$$\mathbf{I}_1 = \frac{\mathbf{V}_1}{j\omega L_1}$$

$$\mathbf{V}_2 = j\omega M \mathbf{I}_1$$


$$\rightarrow \mathbf{V}_2 = \frac{M}{L_1} \mathbf{V}_1$$

$$M^2 = L_1 L_2$$


$$\boxed{\frac{\mathbf{V}_1}{N_1} = \frac{\mathbf{V}_2}{N_2}}$$

$$L_1/L_2 = (N_1/N_2)^2$$
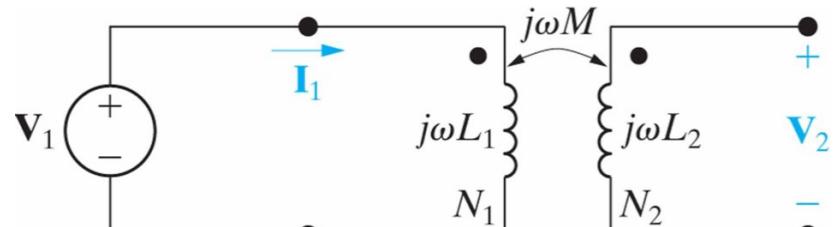
$$\leftarrow \mathbf{V}_2 = \sqrt{\frac{L_2}{L_1}} \mathbf{V}_1$$



(a)

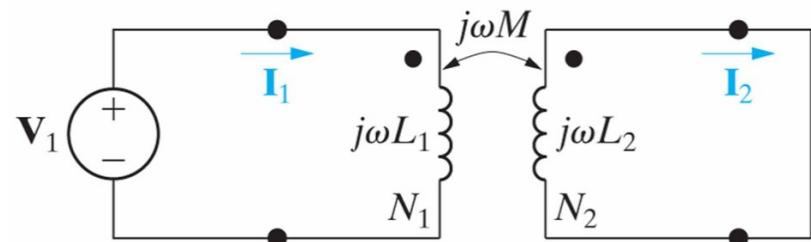


(b)

$$R_1 = R_2 = 0$$

$$0 = -j\omega M \mathbf{I}_1 + j\omega L_2 \mathbf{I}_2$$

$$\rightarrow \frac{\mathbf{I}_1}{\mathbf{I}_2} = \frac{L_2}{M} = \frac{L_2}{\sqrt{L_1 L_2}} = \sqrt{\frac{L_2}{L_1}} = \frac{N_2}{N_1}$$

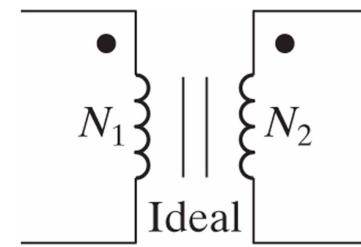
$$\rightarrow \mathbf{I}_1 N_1 = \mathbf{I}_2 N_2$$




(b)

## Determining the Polarity of the Voltage and Current Ratios

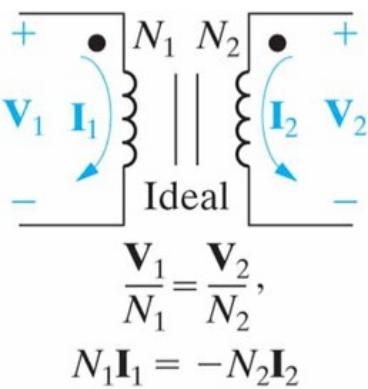
- a) If the coil voltages  $\mathbf{V}_1$  and  $\mathbf{V}_2$  are both positive or negative at the dot-marked terminal, *use a plus sign*, Otherwise, use a negative sign.
- b) If the coil currents  $\mathbf{I}_1$  and  $\mathbf{I}_2$  are both directed into or out of the dot-marked terminal, *use a minus sign*. Otherwise, use a plus sign.




(a)

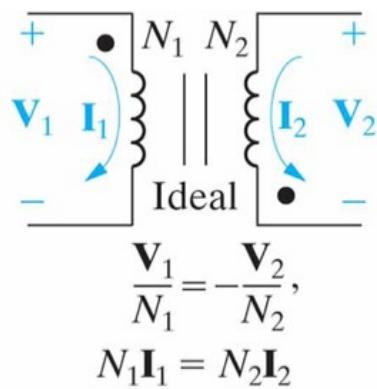

(b)

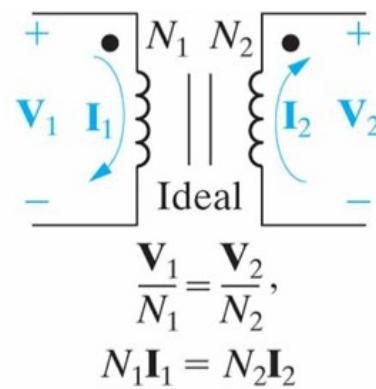

(c)

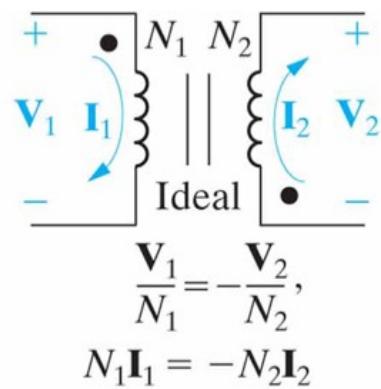


(d)


$$a = \frac{N_2}{N_1}$$

Important parameter for  
ideal transformer!


$$N_1 = 500 \quad N_2 = 2500$$

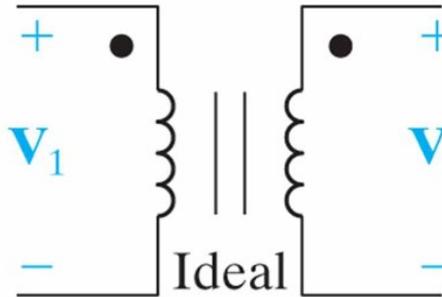

(a)

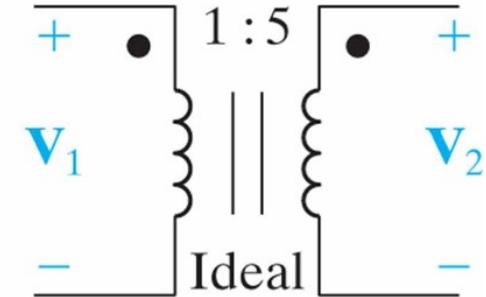

(b)

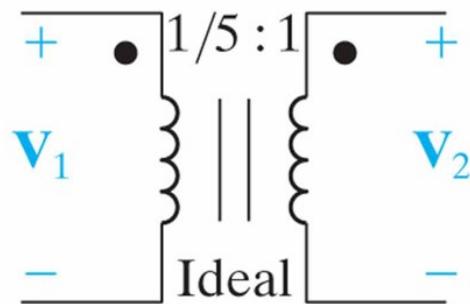


(c)
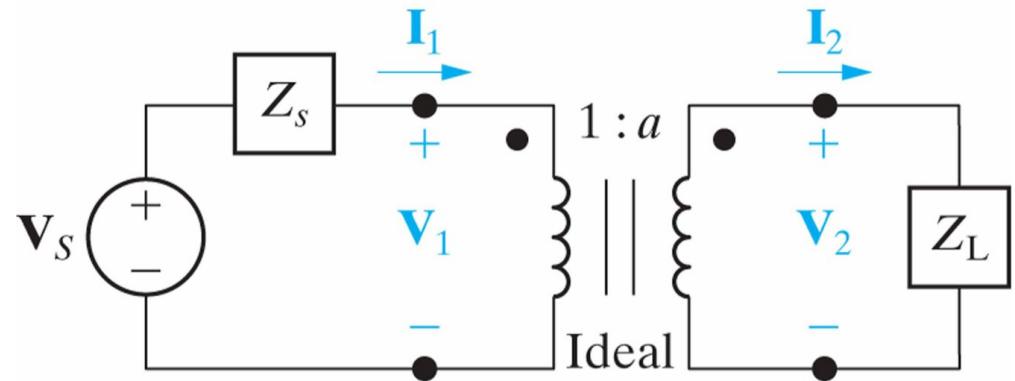
## Ideal Transformer Used for Impedance Matching

$$\mathbf{V}_1 = \frac{\mathbf{V}_2}{a} \quad \mathbf{I}_1 = a\mathbf{I}_2$$

$$Z_{IN} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{1}{a^2} \frac{\mathbf{V}_2}{\mathbf{I}_2} = \frac{1}{a^2} Z_L$$



Thus, the ideal transformer's secondary coil reflects the load impedance back to the primary coil, with the scaling factor  $1/a^2$ .

Note that the ideal transformer changes the magnitude of  $Z_L$  but does not affect its phase angle. Whether  $Z_{IN}$  is greater or less than  $Z_L$  depends on the turns ratio  $a$ .