

**ECE 203**

**Circuits I**

# **More 1st Order Transient Circuits**

**Lecture 10-2**

# 1<sup>st</sup> Order Circuits Continued


- We've already discussed one method for solving 1<sup>st</sup> order circuits, the “differential equation method”
- Now we will learn the “step-by-step method”

# ***The Step-by-Step Approach***


- 1. Assume that the form of the solution,  $x(t)$ , is known.**
- 2. Find  $v_C(0^-)$  or  $i_L(0^-)$ , prior to switch action.**
- 3. Considering that  $v_C(0^+) = v_C(0^-)$  or  $i_L(0^+) = i_L(0^-)$ , find  $x(0^+)$ . This can be done by replacing the capacitor with a voltage source of  $v_C(0^+)$  or the inductor with a current source of  $i_L(0^+)$  with the switch in the new position.**
- 4. Find  $x(\infty)$ , by replacing the capacitor with an open circuit or inductor with a short circuit.**
- 5. Find the time constant by obtaining the Thevenin equivalent circuit at the capacitor or inductor after switching.**
- 6. The solution will be:**

$$x(t) = x(\infty) + [x(0^+) - x(\infty)]e^{-t/\tau}$$

# Example 1: Step-by-Step Approach

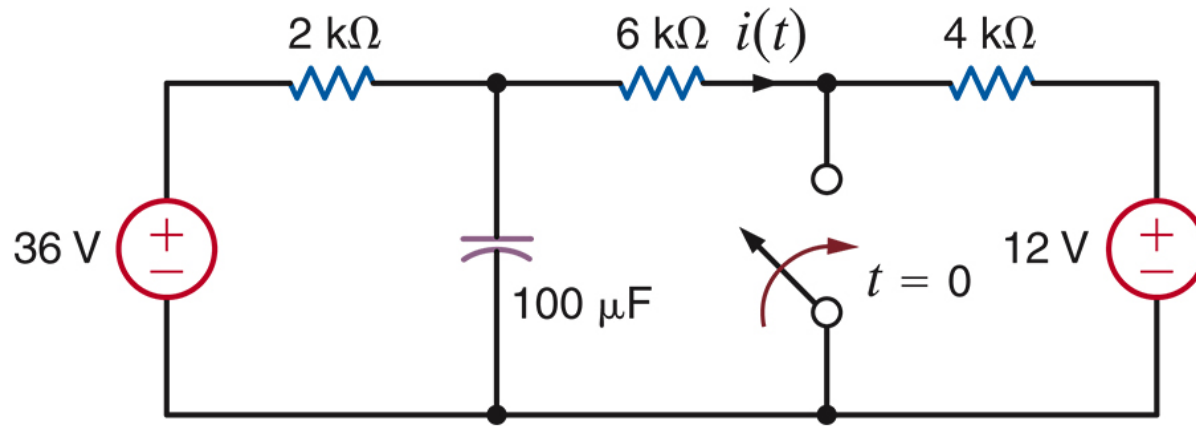


**Step 2 ( $t=0^-$ ):**

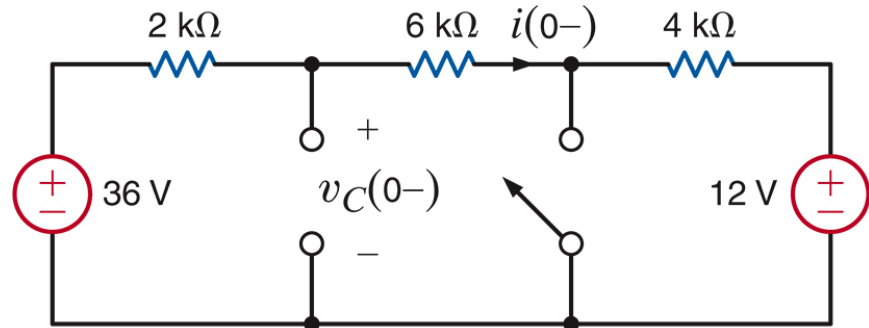


$$\begin{aligned} v_C(0^-) &= 36 - (2)(2) \\ &= 32 \text{ V} \end{aligned}$$

# Example 1: Step-by-Step Approach

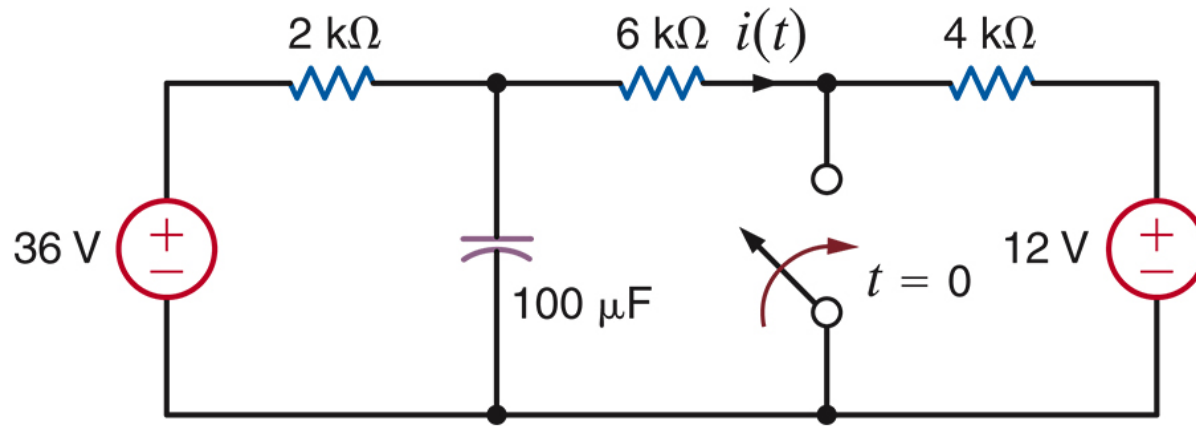


**Step 3 ( $t=0^+$ ):**

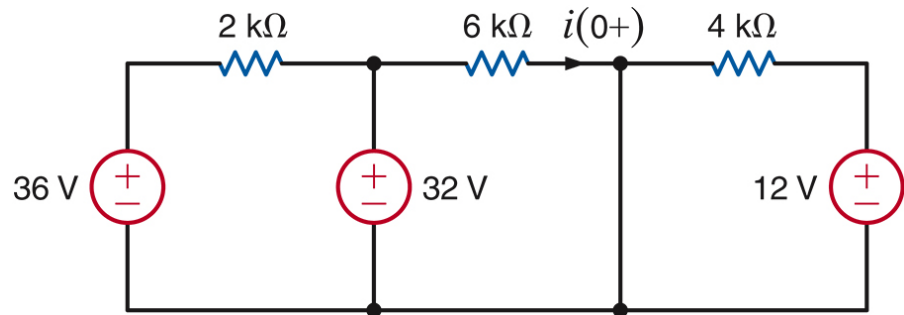


$$\begin{aligned} i(0^+) &= \frac{32}{6k} \\ &= \frac{16}{3} \text{ mA} \end{aligned}$$

# Example 1: Step-by-Step Approach

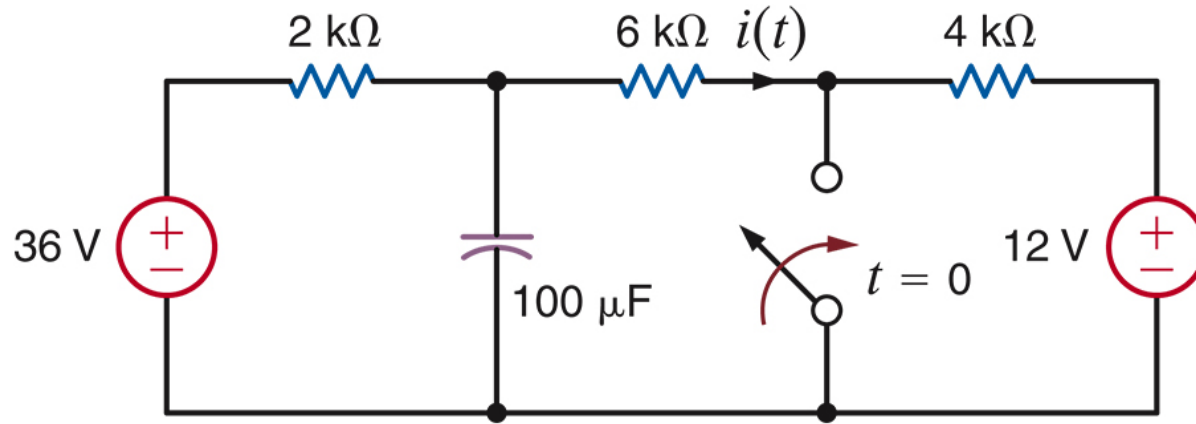


**Step 4 ( $t = \infty$ ):**

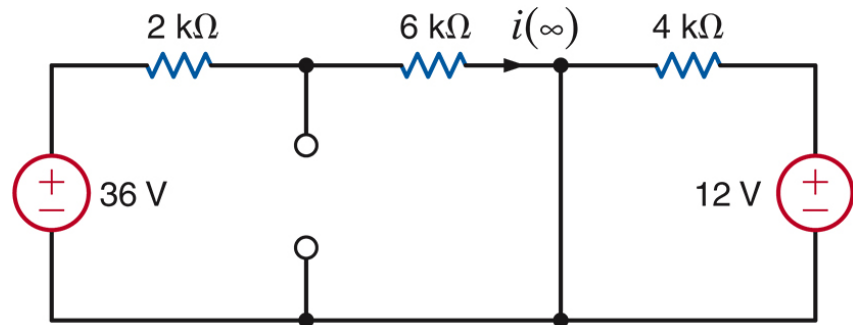


$$\begin{aligned} i(\infty) &= \frac{36}{2\text{k} + 6\text{k}} \\ &= \frac{9}{2} \text{ mA} \end{aligned}$$


# Example 1: Step-by-Step Approach

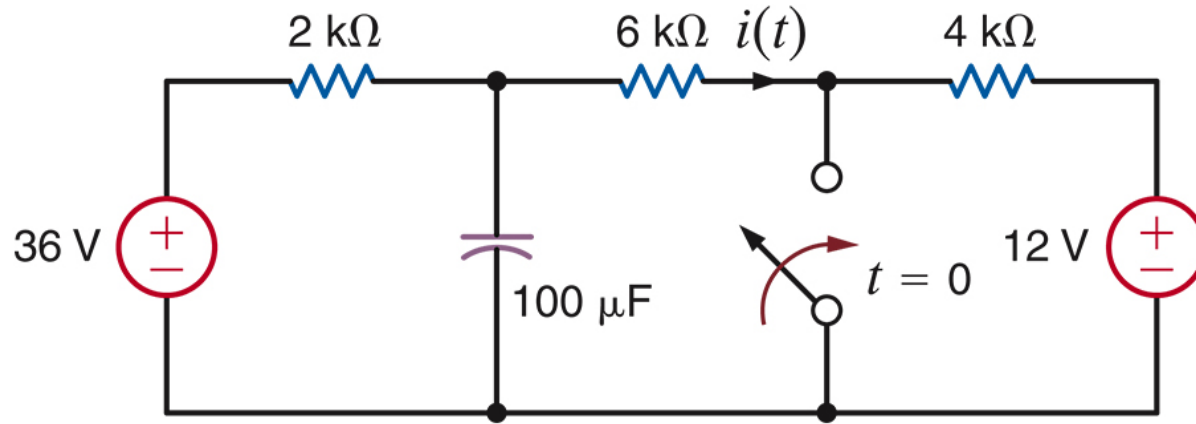

**Step 5 ( $R_{Th}$ ):**

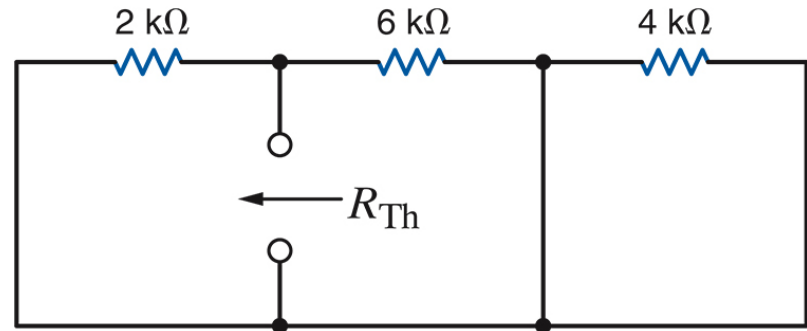

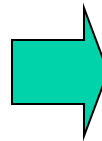
$$R_{Th} = \frac{(2k)(6k)}{2k + 6k} = \frac{3}{2} k\Omega$$



$$\begin{aligned}\tau &= R_{Th} C \\ &= \left(\frac{3}{2}\right)(10^3)(100)(10^{-6}) \\ &= 0.15 \text{ s}\end{aligned}$$


# Example 1: Step-by-Step Approach

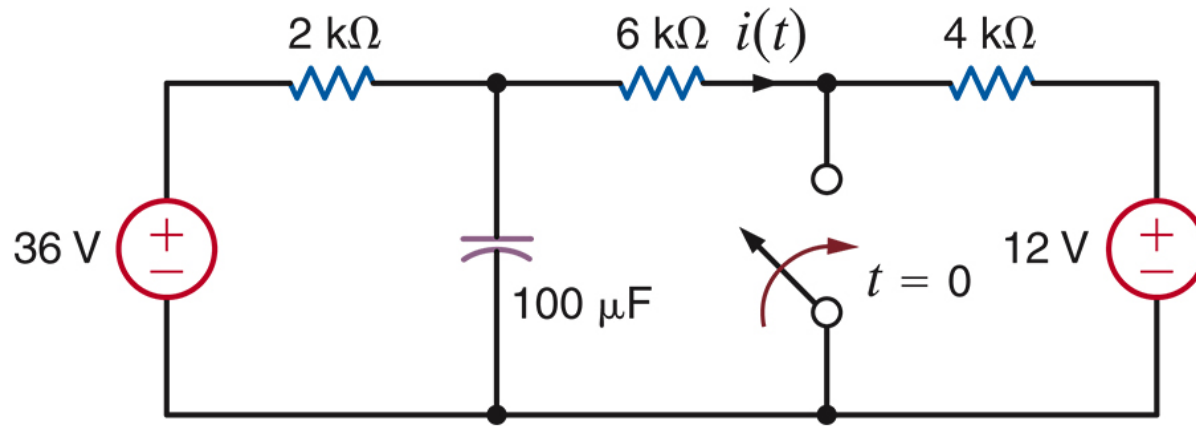

$$x(t) = x(\infty) + [x(0+) - x(\infty)]e^{-t/\tau}$$


$$i(t) = \frac{36}{8} + \frac{5}{6} e^{-t/0.15} \text{ mA}$$

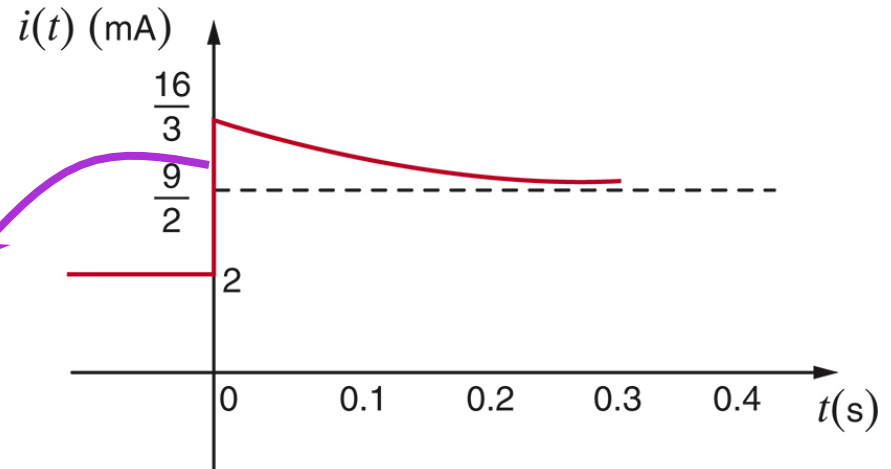*i(t)* is not a continuous function.  
Is it OK?





# Example 2: Step-by-Step Approach

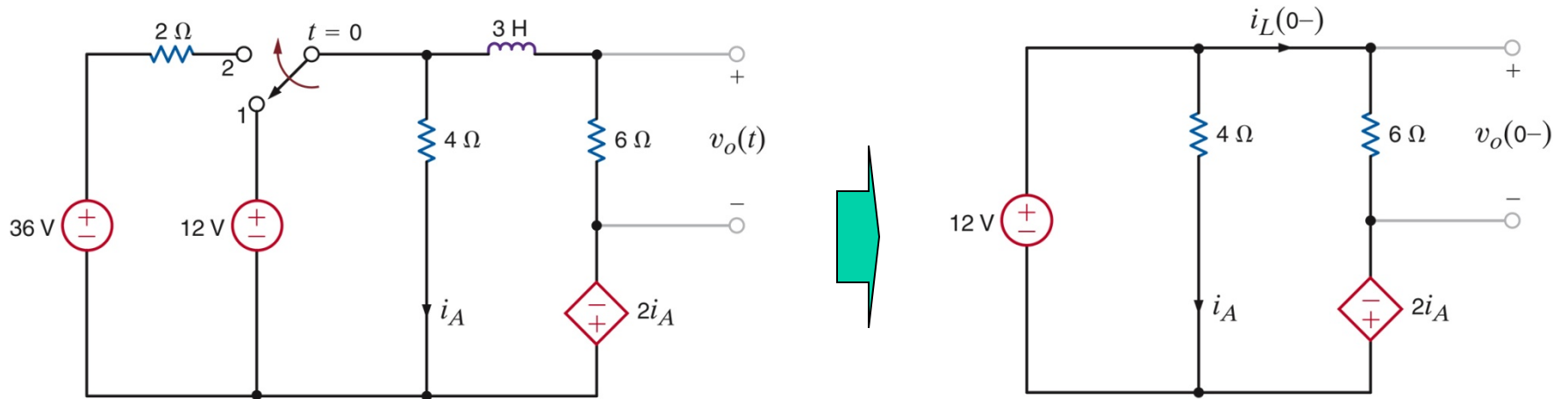


**Step 2 ( $t=0^-$ )**

$$i_A = \frac{12}{4} = 3\ \text{A}$$

$$i_L(0^-) = \frac{12 + 2i_A}{6} = \frac{18}{6} = 3\ \text{A}$$



## Example 2: Step-by-Step Approach

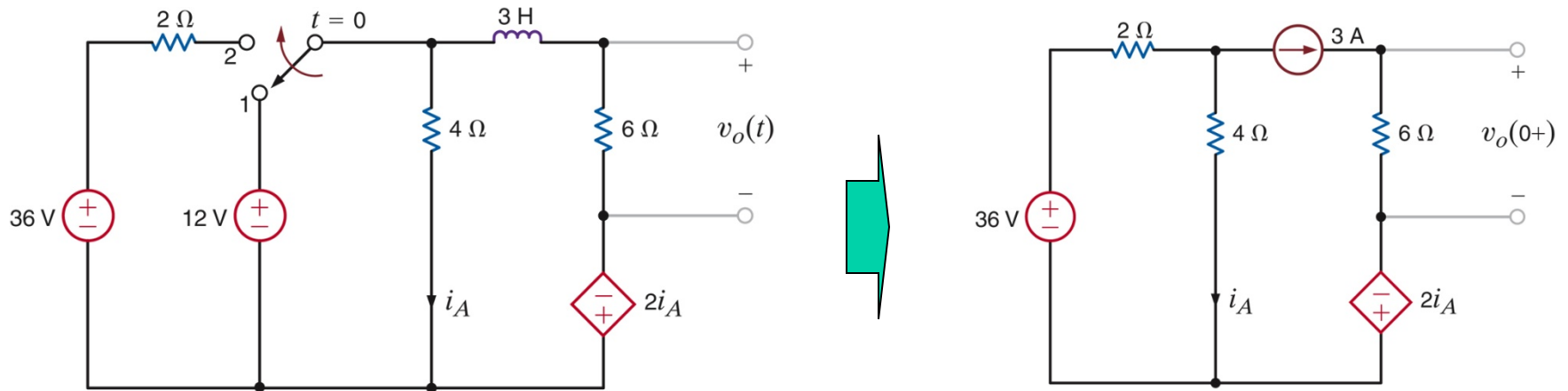

**Step 3 ( $t=0^+$ )**

$$v_o(0^+) = (3)(6) = 18 \text{ V}$$

# Example 2: Step-by-Step Approach

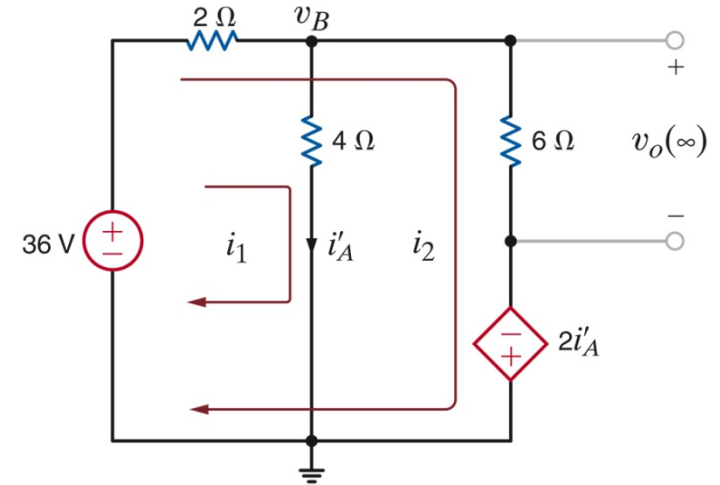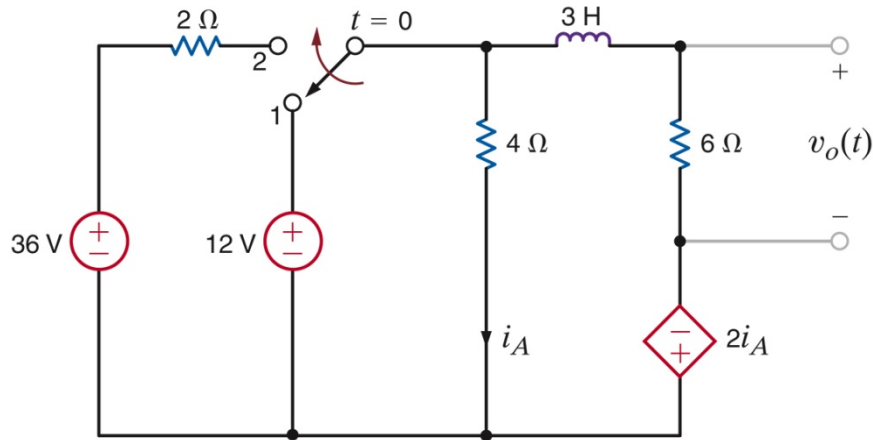

**Step 4 ( $t=\infty$ )**

$$\frac{v_B - 36}{2} + \frac{v_B}{4} + \frac{v_B + 2i'_A}{6} = 0$$


$$i'_A = \frac{v_B}{4}$$

$$v_o(\infty) = v_B + 2i'_A$$




$$v_o(\infty) = 27 \text{ V}$$

# Example 2: Step-by-Step Approach

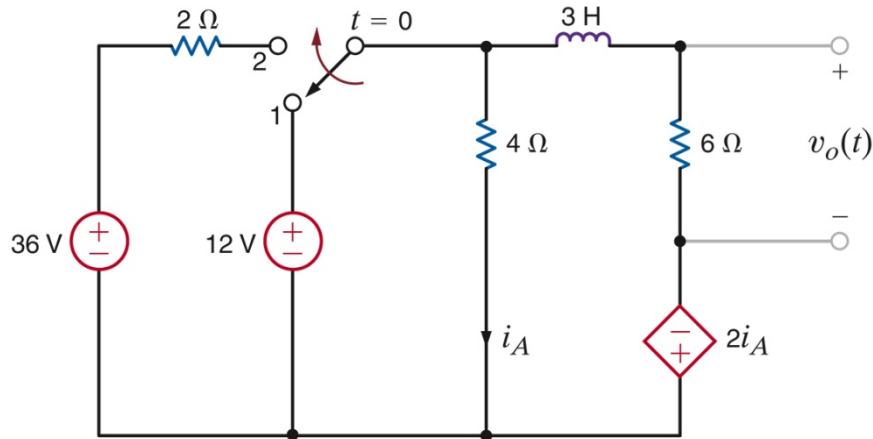


**Step 5 ( $R_{TH}$ )**

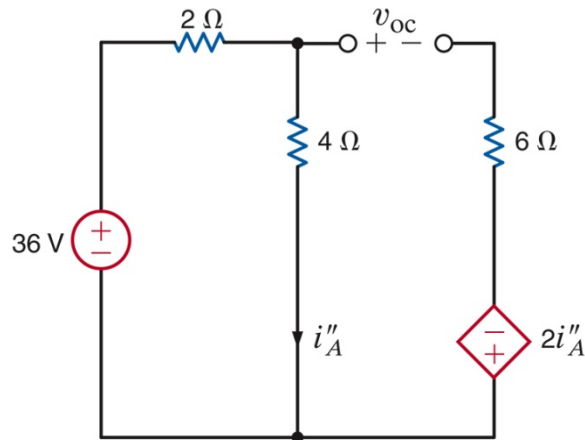

$$i''_A = \frac{36}{2 + 4} = 6 \text{ A}$$
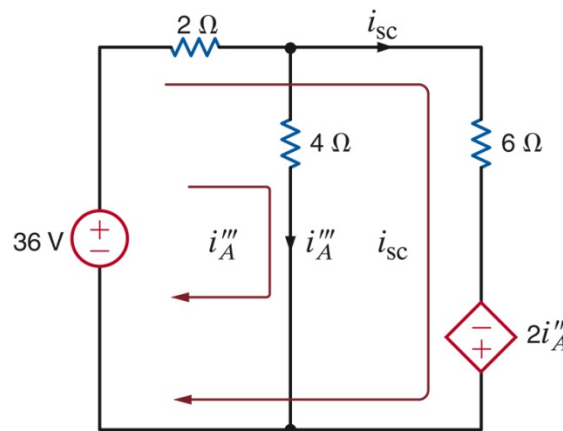
$$v_{oc} = (4)(6) + 2(6) = 36 \text{ V}$$



$$36 = 2(i'''_A + i_{sc}) + 4i'''_A$$


$$36 = 2(i'''_A + i_{sc}) + 6i_{sc} - 2i'''_A$$

$$i_{sc} = \frac{9}{2} \text{ A}$$

$$R_{Th} = \frac{v_{oc}}{i_{sc}} = \frac{36}{9/2} = 8 \Omega$$

$$\tau = L/R = 3/8 \text{ sec}$$

## Example 2: Step-by-Step Approach

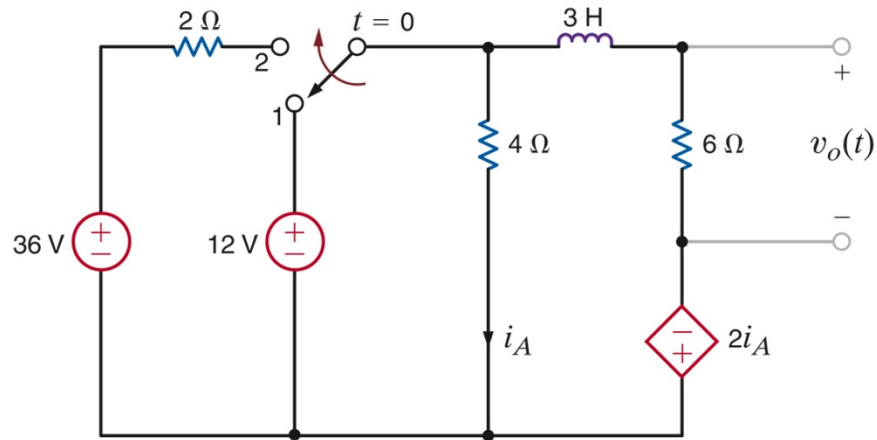

$$x(t) = x(\infty) + [x(0+) - x(\infty)]e^{-t/\tau}$$

$$v_o(t) = 27 - 9e^{-t/(3/8)} \text{ V}$$