


$$\#2 \quad c) \quad i = \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{6} = \frac{230 - 150}{1} + \frac{230 - 140}{6} = 95A$$

$$P = IV \Rightarrow P = (95)(230) = 21850W$$

$$\boxed{P = 21,850W}$$

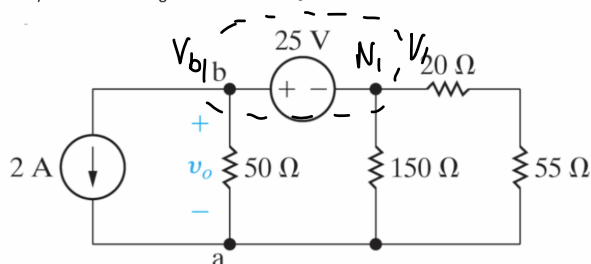Question 3 (15 points)

- Identify the super node.
- Use node-voltage method to find V_o .



a) the super node encompasses the 25V source between nodes b and N_1 . (I circled it)

b) ① $V_b - V_1 = 25$ (constraining super Node)

② $\frac{V_1}{150} + \frac{V_1}{20+55} + 2 + \frac{V_b}{50} = 0$

$$V_1 + 2V_1 + 300 + 3V_b = 0$$

$$3V_1 + 3V_b = -300$$

$$V_1 + V_b = -100$$

Solve w/ matrix

$$\begin{bmatrix} -1 & 1 & : 25 \\ 1 & 1 & : -100 \end{bmatrix} \Rightarrow \begin{matrix} V_1 = 37.5V \\ V_2 = 62.5V \end{matrix}$$


Given the circuit V_o would be equivalent to V_b

So: $V_o = V_b = 37.5V$

$$\boxed{V_o = 37.5V}$$

Question 4 (15 points)

- Use mesh-current method to find out how much power the 5A source delivers.
- Find total power delivered to the circuit by the current and voltage sources.
- Find total power dissipated in the circuit by the resistors.

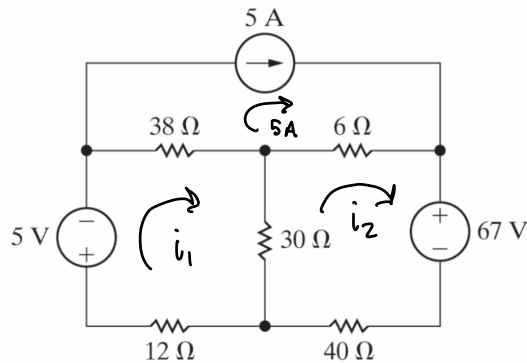

loop 1: $5V + 38(i_1 - 5) + 30(i_1 - i_2) + 12i_1 = 0$

$$38i_1 + 30i_1 + 12i_1 - 30i_2 - 185 = 0$$

$$80i_1 - 30i_2 = 185$$

loop 2: $67 + 40i_2 + 6(i_2 - 5) + 30(i_2 - i_1) = 0$

$$-30i_1 + 40i_2 + 6i_2 + 30i_2 + 37 = 0$$

$$-30i_1 + 76i_2 = -37$$

Solving w/ matrix:

$$\begin{bmatrix} 80 & -30 & 185 \\ -30 & 76 & -37 \end{bmatrix}$$

$$i_1 = 2.5A \quad i_2 = 0.5A$$

a) $V_{5A} = 38(2.5 - 5) + 6(0.5 - 5) = -122V$

$$P = IV = (5)(-122V) = -610W$$

$$P_{5A} = 610W$$

b) $P_{67V} = 0.5(67) = 33.5W$

$$P_{5V} = 2.5(5) = 12.5W$$

$$P_{5A} = 610W$$

c) $P_R = I^2 R$

$$P_{38\Omega} = (2.5)^2 38 = 237.5W$$

$$P_{30\Omega} = (2.5 - 0.5)^2 (30) = 120W$$

$$P_{6\Omega} = (5 - 0.5)^2 (6) = 121.5W$$

$$P_{40\Omega} = (0.5)^2 (40) = 10W$$

$$P_{12\Omega} = (2.5)^2 (12) = 75W$$

$$P_{resistors} = 237.5 + 120 + 121.5 + 10 + 75 = 564W$$

$$P_{resistors} = 564W$$