

ECE 203

Circuits I

Nodal Analysis

Chapter 3 Nodal and Loop Analysis

Will begin looking at two new analysis methods for your toolbox


Both are based on linear algebra techniques

Nodal Analysis


- ❑ The variables are node voltages**
- ❑ Node voltages are defined with respect to a common point (ground, *i.e.* zero potential)**
- ❑ Ground is usually the node with the largest number of branches**
- ❑ We select our variables as being positive with respect to ground (although they may turn out to be negative)**
- ❑ Once the node voltages are known, any circuit parameter can be calculated**

The Concept of Node Voltage

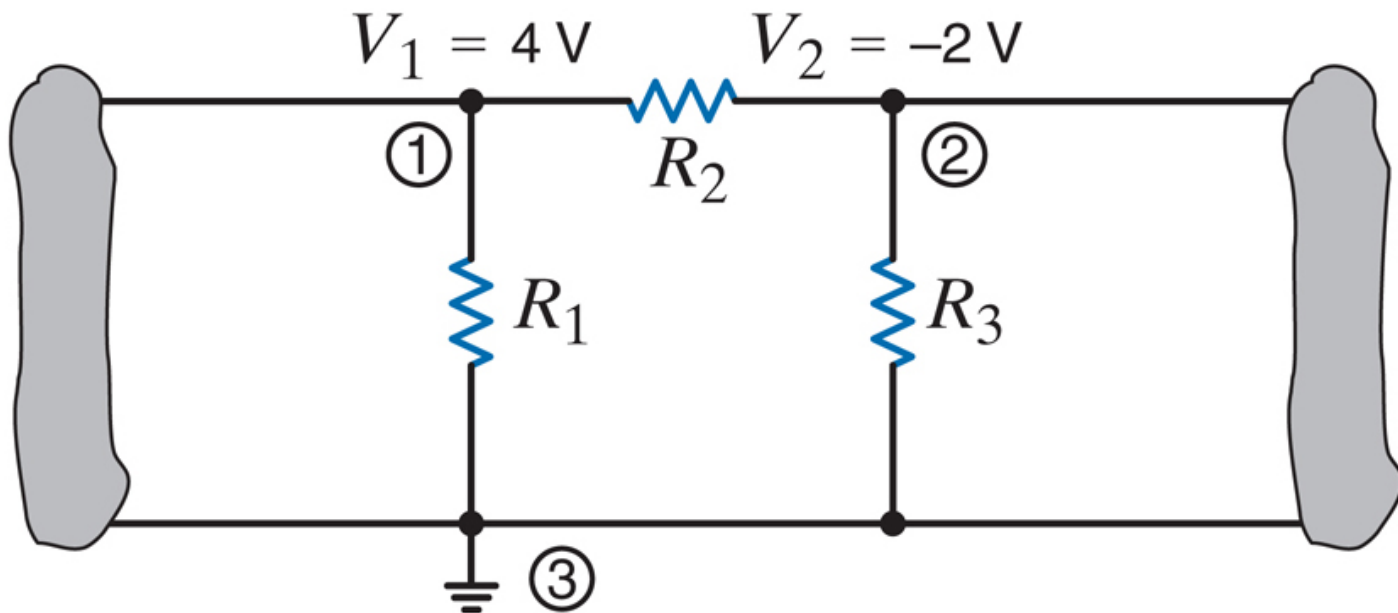- ❑ V_1 is 4V. What does this mean? With respect to what?
- ❑ V_2 is -2V. What does this mean? With respect to what?
- ❑ What is the voltage at node 1 with respect to node 2?
- ❑ What is the voltage at node 2 with respect to node 1?



General Rule

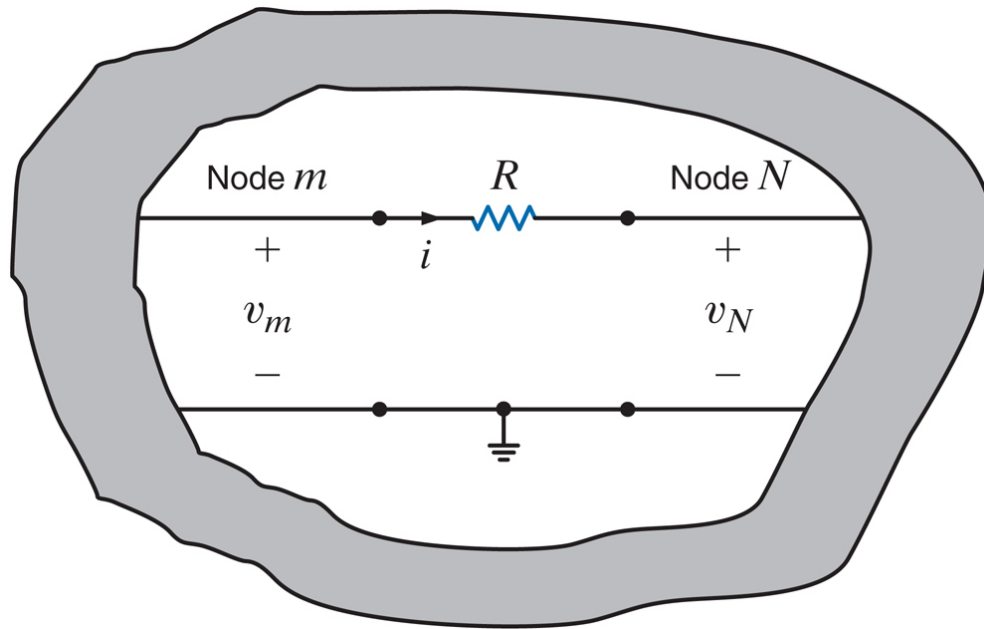

$$i = \frac{v_m - v_N}{R}$$

General Rules

- ❑ For nodal analysis, we employ KCL**
- ❑ One node is designated as GND**
- ❑ Therefore in an N node circuit, there will be $N-1$ unknown variables (node voltages)**
- ❑ KCL gives us $N-1$ linearly independent equations**
- ❑ Solution of KCL equations gives all node voltages with respect to GND (reference)**
- ❑ Any other circuit parameter can be determined by the node voltages**

Step-by-step

- 1) Establish where each node is; must have a reference node
- 2) Assign the voltage variables at each node; for example, V_1 , V_2 , ...
- 3) Write the equations for KCL at each node
- 4) Use Ohm's law to rewrite the equation in terms of voltages and resistances (You should have the same number of equations as unknowns)

Step-by-step continued

- 5) Solve for the unknown voltages (you have a few choices of how to do this)
- 6) Use Ohm's law to solve for unknown currents

Examples: