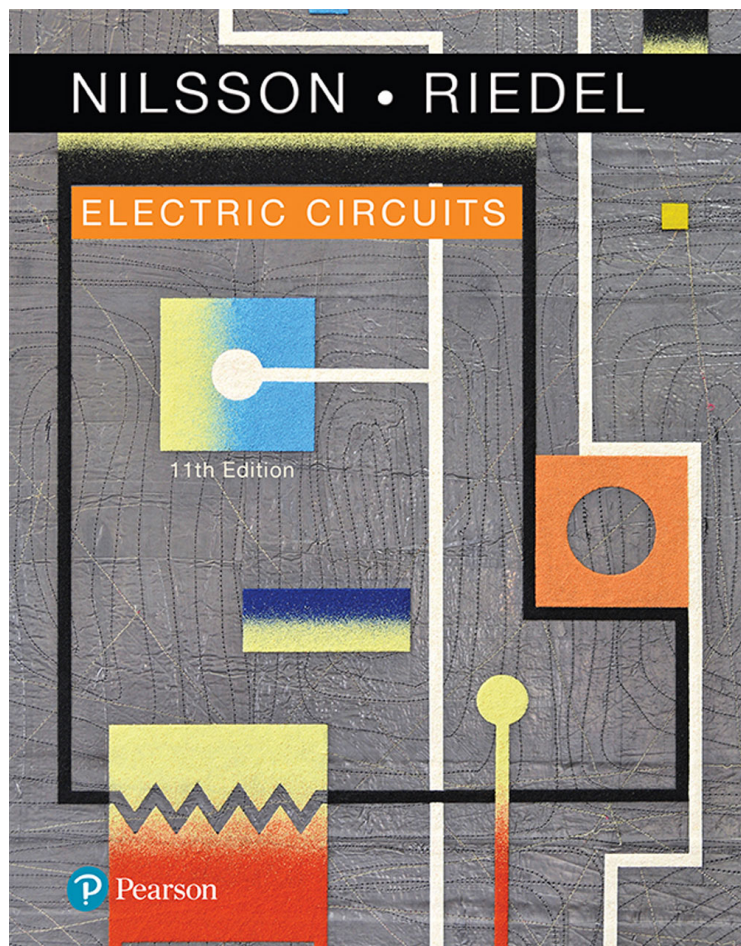


Electric Circuits

Eleventh Edition





Chapter 7

Response of
First-Order RL
and RC
Circuits



Learning Objectives

- The Natural Response of an RL Circuit
- The Natural Response of an RC Circuit
- The Step Response of RL and RC Circuits
- A General Solution for Step and Natural Responses
- Sequential Switching
- Unbounded Response
- The Integrating Amplifier*

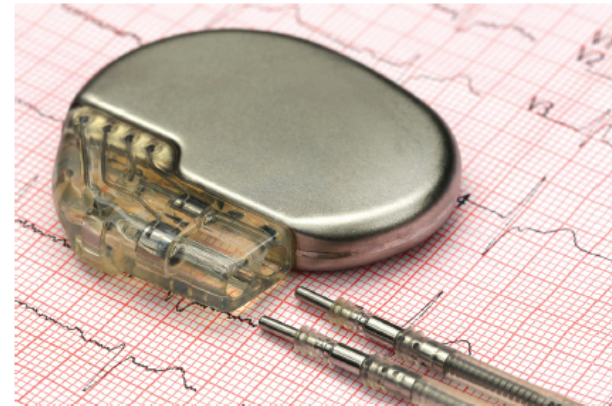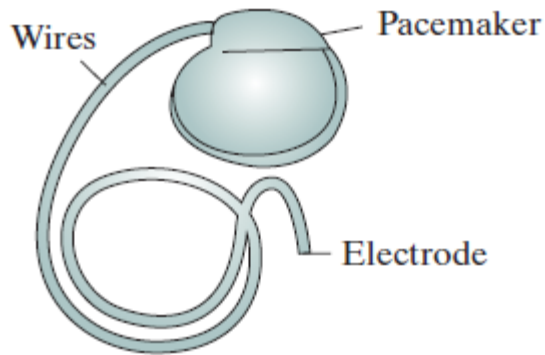Practical Perspective - Artificial Pacemaker




Swapan Photography/Shutterstock

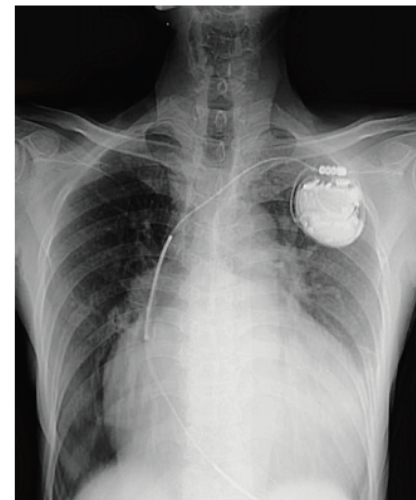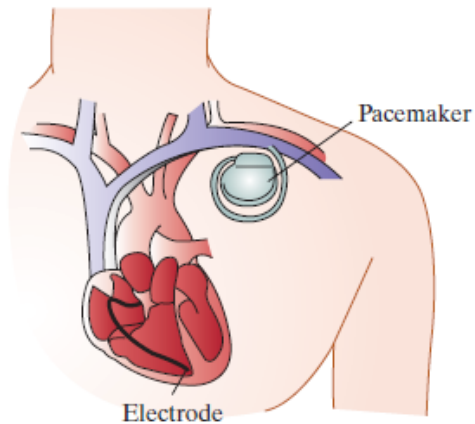


Tewan Banditrukkanka/Shutterstock

RL & RC Circuits

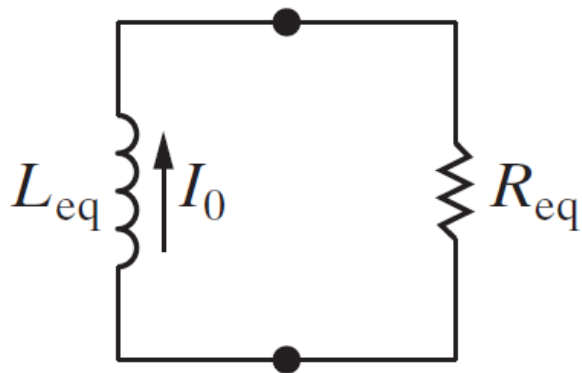


(a)

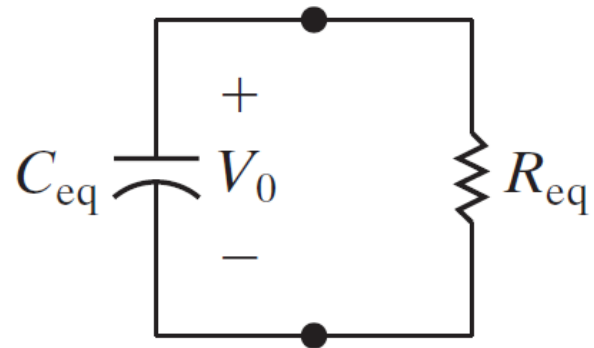


(b)


Figure 7.1: The two forms of the circuits for natural response. (a) RL circuit. (b) RC circuit.

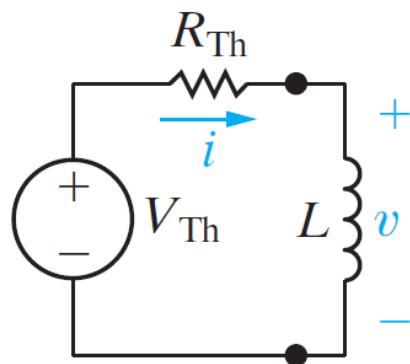


(a)

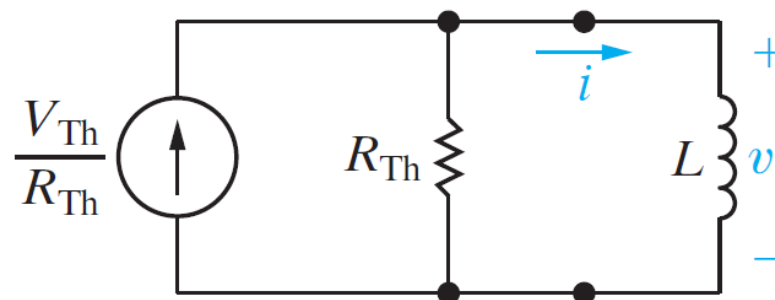

(b)

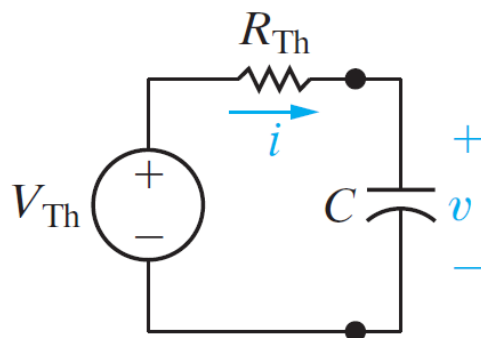

(c)

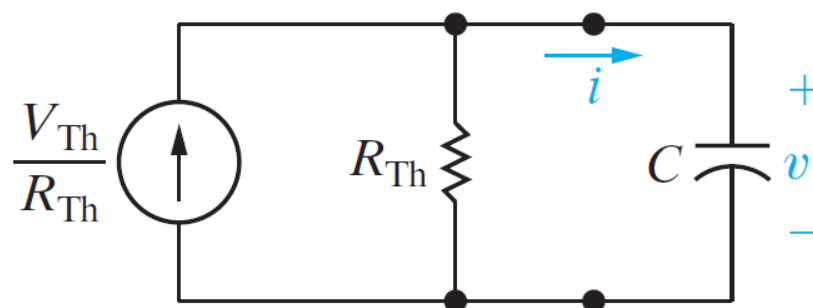

(d)

Figure 7.2: Four possible first-order circuits. (a) An inductor connected to a Thévenin equivalent. (b) An inductor connected to a Norton equivalent. (c) A capacitor connected to a Thévenin equivalent. (d) A capacitor connected to a Norton equivalent.

7.1 Natural Response of RL Circuit

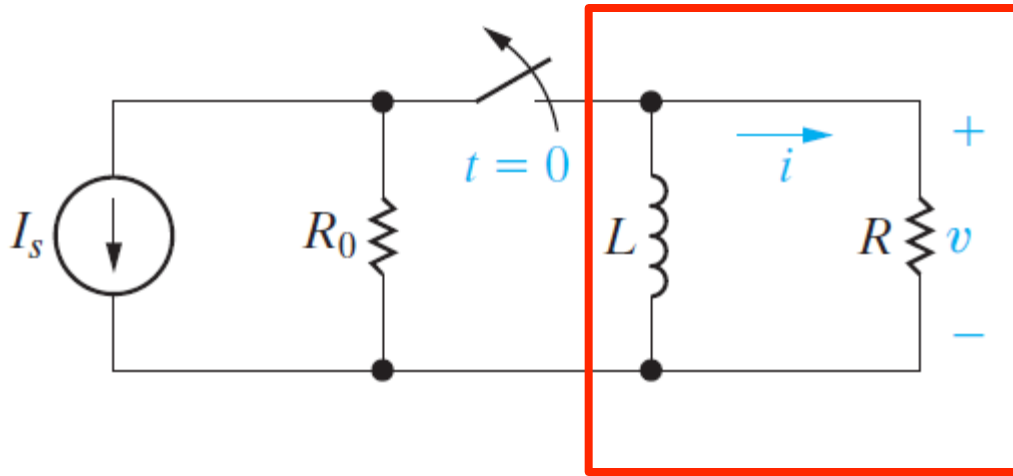


Figure 7.3: An RL circuit.

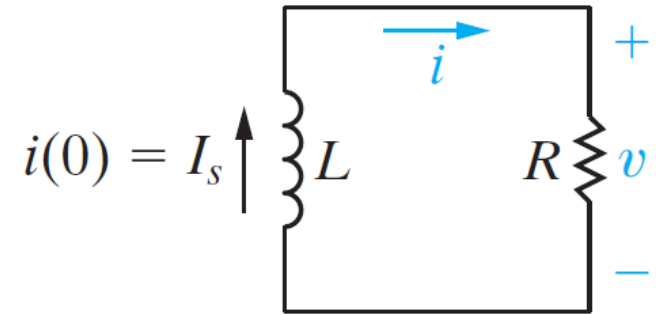


Figure 7.4: The circuit shown in Fig. 7.3, for $t \geq 0$.

- a) The switch has been in a closed position for a long time: *all currents and voltages have reached a constant value.*
- b) The inductor appears as a short circuit ($L di/dt = 0$) prior to the release of the stored energy.

Expression for the Current


$$L \frac{di}{dt} + Ri = 0$$




$$\frac{di}{i} = -\frac{R}{L} dt$$



$$\int_{i(t_0)}^{i(t)} \frac{dx}{x} = -\frac{R}{L} \int_{t_0}^t dy \quad \Rightarrow \quad \ln \frac{i(t)}{i(0)} = -\frac{R}{L} t$$


$$i(t) = i(0)e^{-(R/L)t}$$

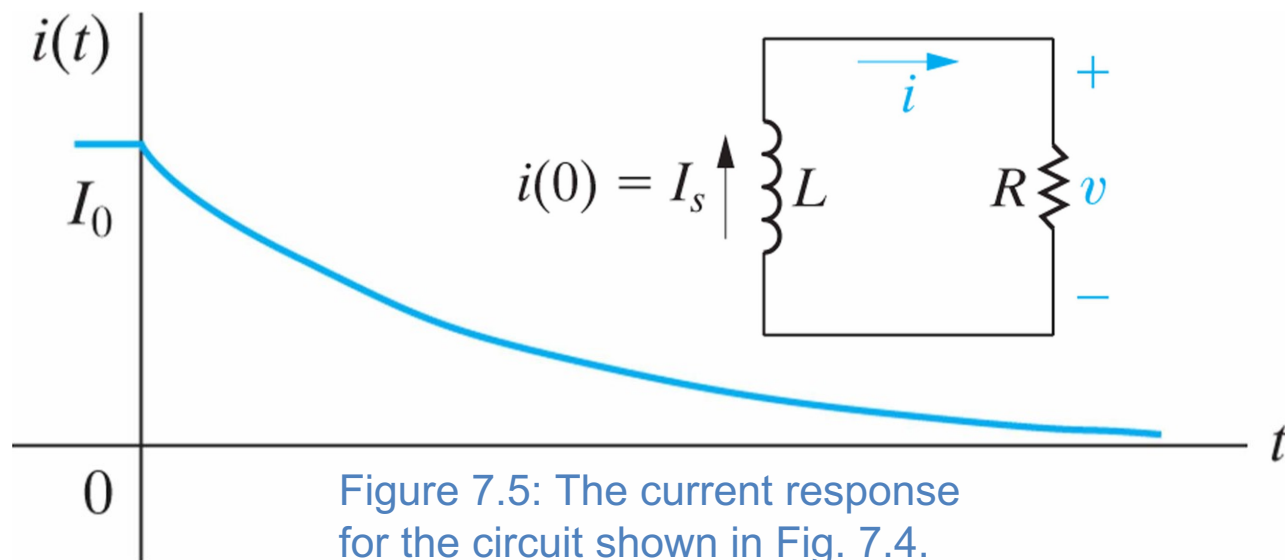

Expression for the Power and Energy

$$v = iR = I_0 R e^{-(R/L)t}, \quad t \geq 0^+$$

$$p = vi$$



$$p = I_0^2 R e^{-2(R/L)t}$$



$$w = \int_0^t p dx = \int_0^t I_0^2 R e^{-2(R/L)x} dx$$

$$= \frac{1}{2(R/L)} I_0^2 R (1 - e^{-2(R/L)t})$$

$$= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}), \quad t \geq 0.$$

The Significance of the Time Constant

$$i(t) = i(0)e^{-(R/L)t} \Rightarrow \tau = \text{time constant} = \frac{L}{R}$$

$$i(t) = I_0 e^{-t/\tau}, \quad t \geq 0,$$

$$v(t) = I_0 R e^{-t/\tau}, \quad t \geq 0^+,$$

$$p = I_0^2 R e^{-2t/\tau}, \quad t \geq 0^+,$$


$$w = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau}), \quad t \geq 0.$$

The time constant is an important parameter in first-order circuits, *it is convenient to think of the time elapsed after switching in terms of integral multiples of τ* : one time constant after the inductor starts to release its stored energy to the resistor, the current has been reduced to $e^{-1} \approx 0.37$ of its initial value.

Steady-State Response

TABLE 7.1 Value of $e^{-t/\tau}$
for t integral multiples of τ


t	$e^{-t/\tau}$	t	$e^{-t/\tau}$
τ	3.6788×10^{-1}	6τ	2.4788×10^{-3}
2τ	1.3534×10^{-1}	7τ	9.1188×10^{-4}
3τ	4.9787×10^{-2}	8τ	3.3546×10^{-4}
4τ	1.8316×10^{-2}	9τ	1.2341×10^{-4}
5τ	6.7379×10^{-3}	10τ	4.5400×10^{-5}

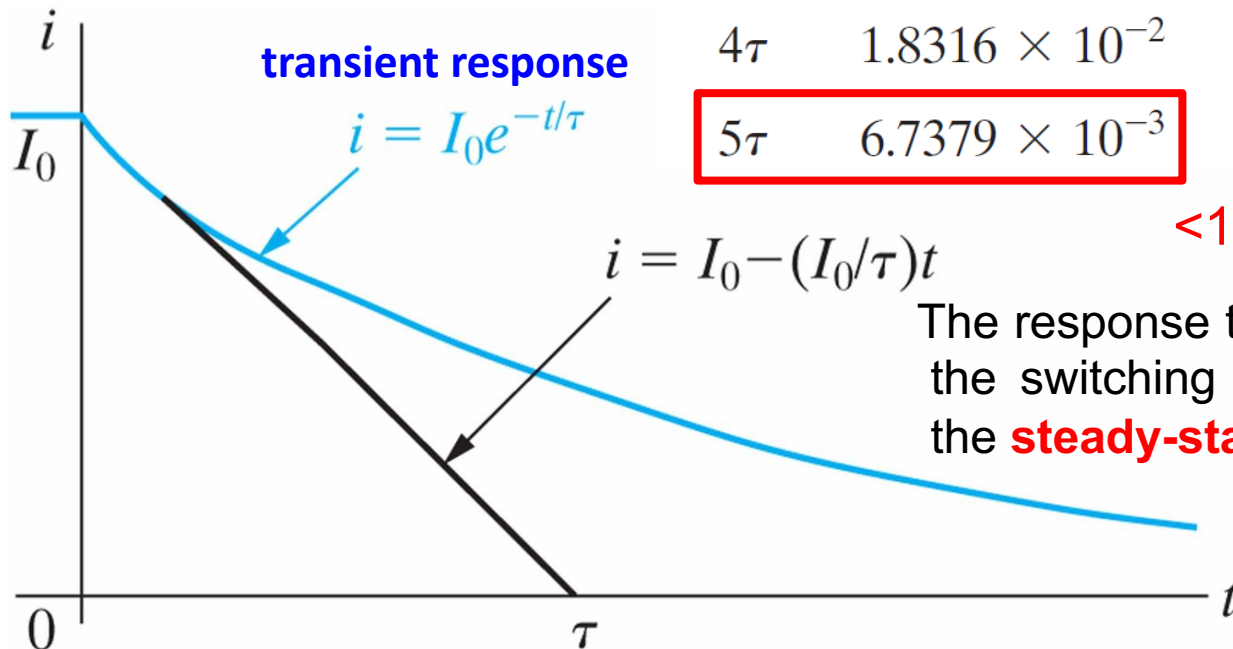

<1%

The response that exists *a long time* after the switching has taken place is called the **steady-state response**


Assessment Problems 7.1

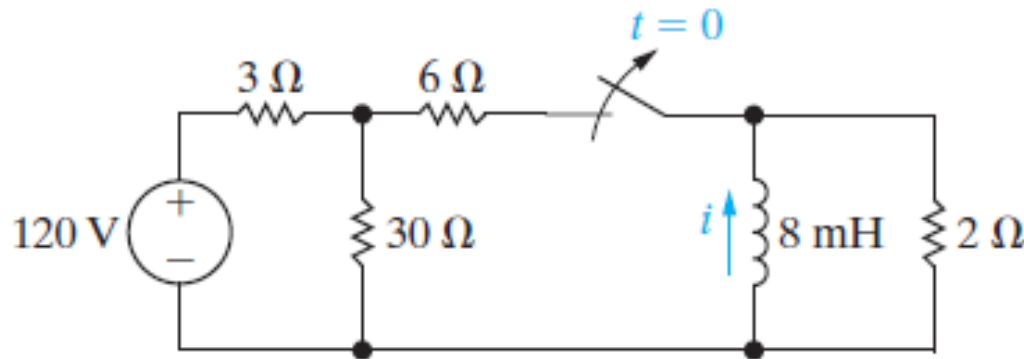

The switch in the circuit has been closed for a long time and is opened at $t = 0$.

- Calculate initial value of i .
- Calculate initial energy stored in inductor.
- What is τ ?
- What is the numerical expression for $i(t)$?
- What percentage of the initial energy stored has been dissipated in the $2\ \Omega$ resistor 5 ms after the switch is opened?

Assessment Problems 7.2

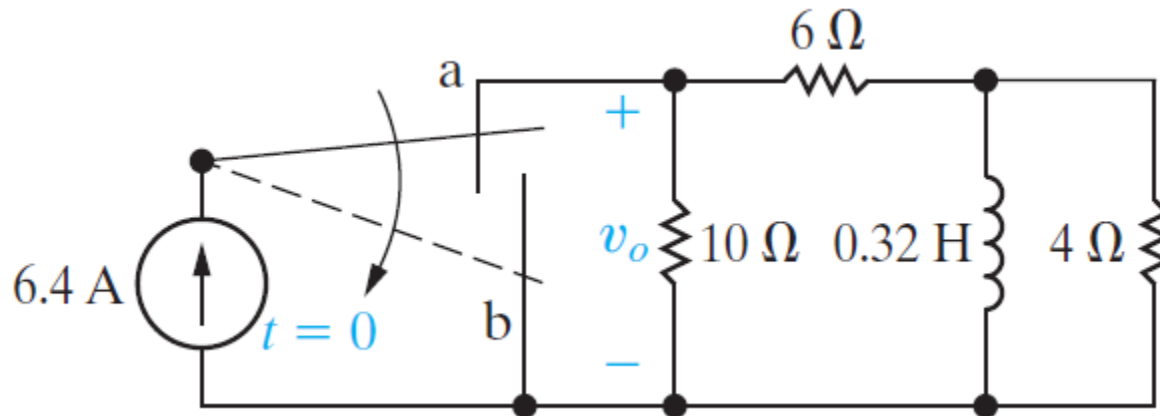

At $t = 0$, the switch is moved from a to b.

- Calculate v_o for $t \geq 0^+$.
- What percentage of the initial energy stored in the inductor is eventually dissipated in the 4 Ω resistor?

7.2 Natural Response of RC Circuit

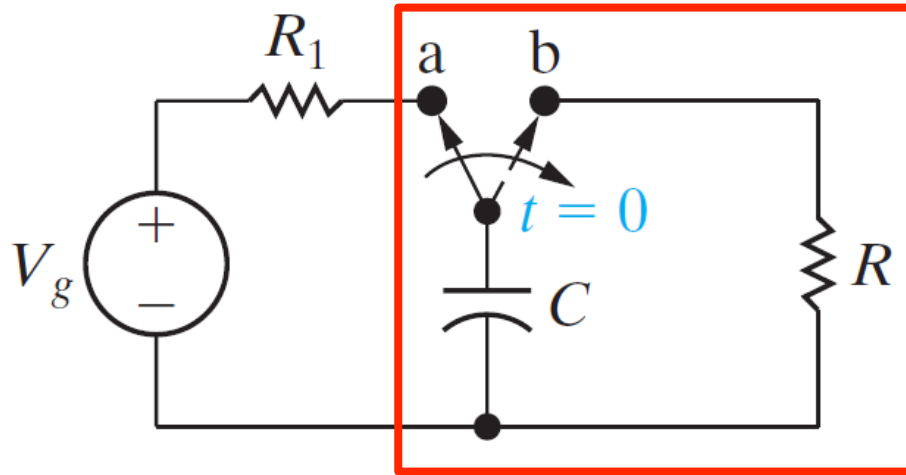


Figure 7.12: An RC circuit.

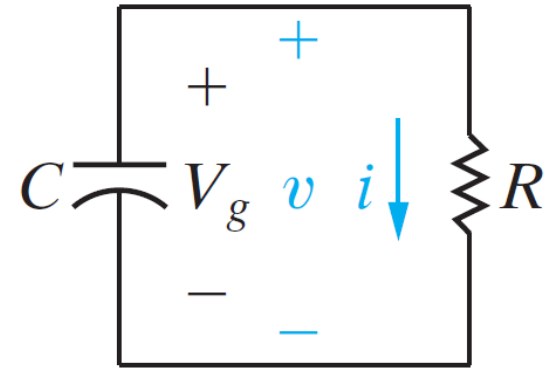


Figure 7.13: The circuit shown in Fig. 7.12, after switching.

- a) The switch has been in a closed position for a long time: *all currents and voltages have reached a constant value.*
- b) The capacitor appears as an open circuit ($Cdv/dt = 0$) prior to the release of the stored energy.

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$



$$v(t) = v(0)e^{-t/RC}, \quad t \geq 0$$



$$\tau = RC$$

$$v(t) = V_0 e^{-t/\tau}, \quad t \geq 0$$

$$i(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-\tau/t}, \quad t \geq 0^+$$

$$p(t) = vi = \frac{V_0^2}{R} e^{-2\tau/t}, \quad t \geq 0^+$$

$$w = \frac{1}{2} C V_0^2 \left(1 - e^{-2\tau/t} \right), \quad t \geq 0$$


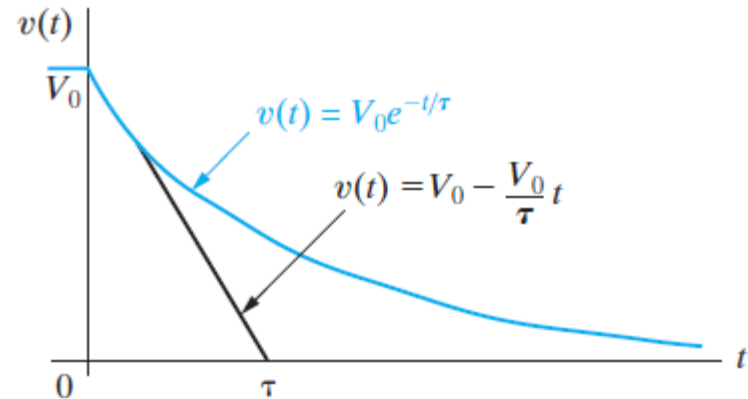


Figure 7.14: The natural response of an RC circuit.


Assessment Problems 7.3

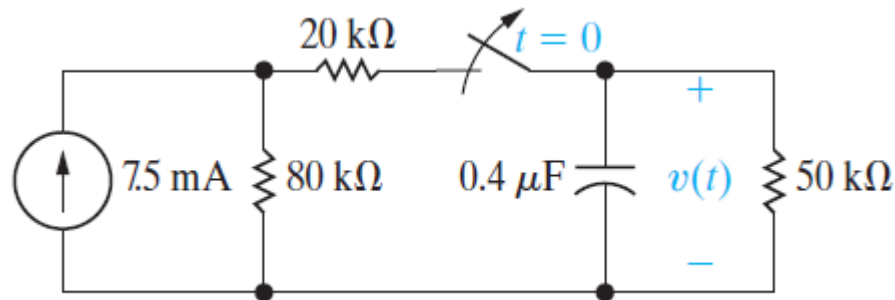

The switch in the circuit has been closed for a long time and is opened at $t = 0$. Find:

- a) the initial value of $v(t)$,
- b) the time constant for $t > 0$,
- c) $v(t)$ after the switch is opened
- d) the initial energy stored in the capacitor, and
- e) the time required to dissipate 75% of the initial energy.

Assessment Problems 7.4

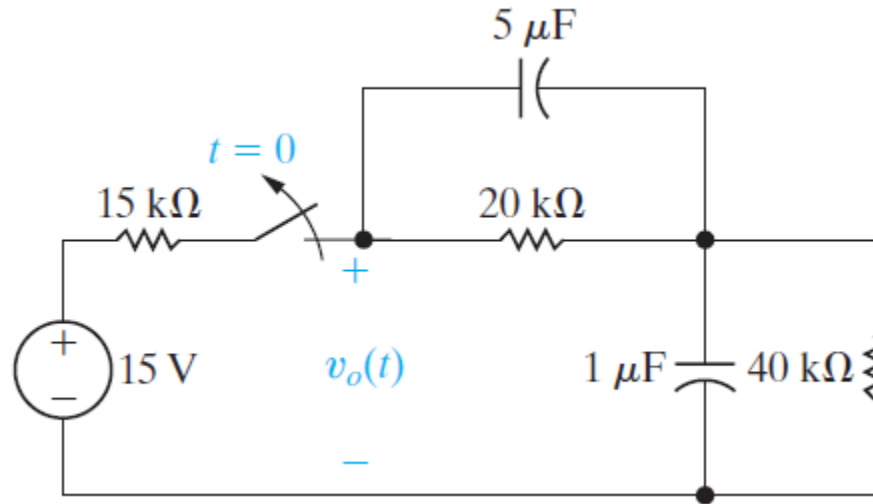

The switch in the circuit has been closed for a long time and is opened at $t = 0$.

- Find v_o for $t \geq 0$.
- What percentage of the initial energy stored in the circuit has been dissipated after 60 ms?

7.3 Step Response of RL & RC Circuits

Step Response of RL Circuit

KVL:

$$V_s = Ri + L \frac{di}{dt}$$



$$\frac{di}{dt} = \frac{-Ri + V_s}{L} = \frac{-R}{L} \left(i - \frac{V_s}{R} \right)$$

$$\frac{di}{i - (V_s/R)} = \frac{-R}{L} dt$$



$$\int_{I_0}^{i(t)} \frac{dx}{x - (V_s/R)} = \frac{-R}{L} \int_0^t dy$$

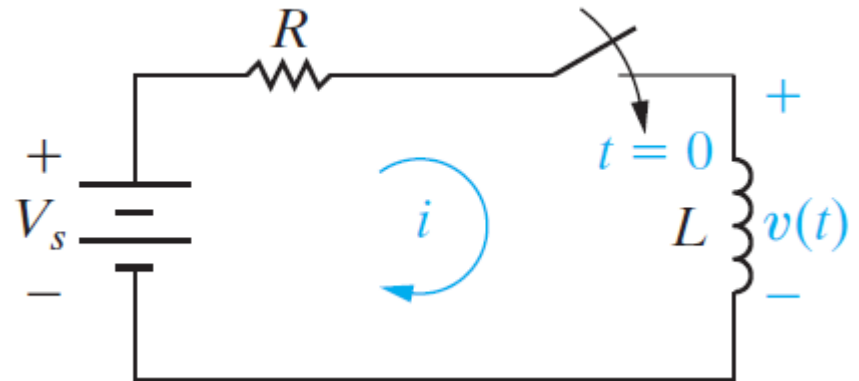






Figure 7.20: A circuit used to illustrate the step response of a first-order *RL* circuit.


$$\ln \frac{i(t) - (V_s/R)}{I_0 - (V_s/R)} = \frac{-R}{L}t$$


$$\frac{i(t) - (V_s/R)}{I_0 - (V_s/R)} = e^{-(R/L)t}$$


$$i(t) = \frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-(R/L)t}$$


$$i(t) = I_f + (I_0 - I_f)e^{-t/\tau}$$

Step Response Curve

$$I_0 = 0$$



$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-(R/L)t}$$




$$i(\tau) = \frac{V_s}{R} - \frac{V_s}{R} e^{-1} \approx 0.6321 \frac{V_s}{R}$$

$$\frac{di}{dt} = \frac{-V_s}{R} \left(\frac{-1}{\tau} \right) e^{-t/\tau} = \frac{V_s}{L} e^{-t/\tau}$$



$$\frac{di}{dt}(0) = \frac{V_s}{L}$$

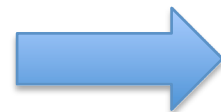

$$i(t = \tau) = \frac{V_s}{L} \boxed{\frac{L}{R}} = \frac{V_s}{R}$$

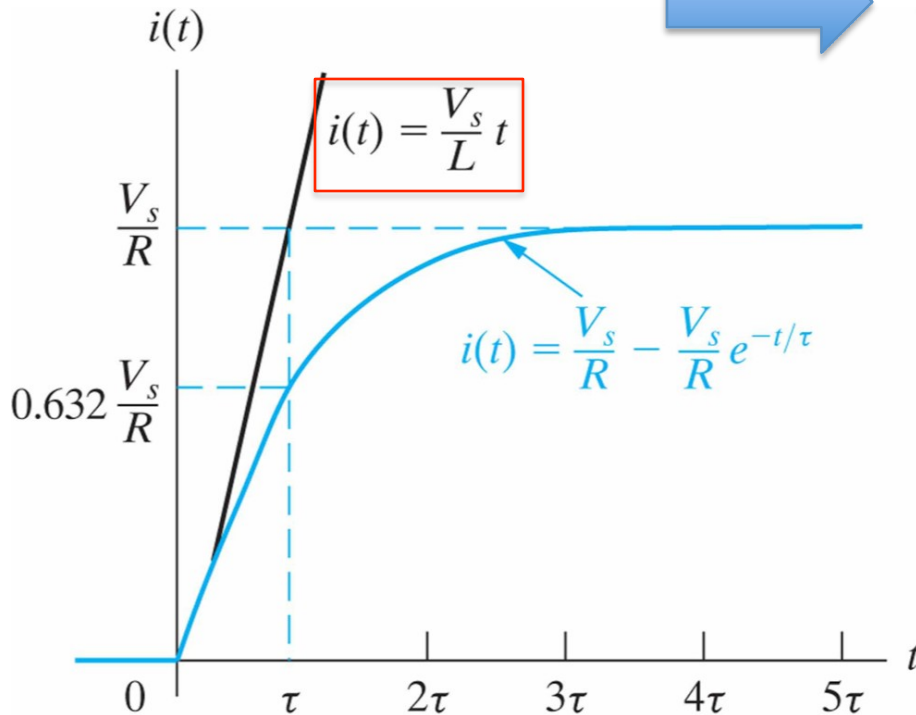


Figure 7.26: The step response of the RL circuit shown in Fig. 7.20 when $I_0 = 0$.

The voltage across an inductor is Ldi/dt , so for $t > 0^+$, we have:

$$v = L\left(\frac{-R}{L}\right)\left(I_0 - \frac{V_s}{R}\right)e^{-(R/L)t} = (V_s - I_0 R)e^{-(R/L)t}$$


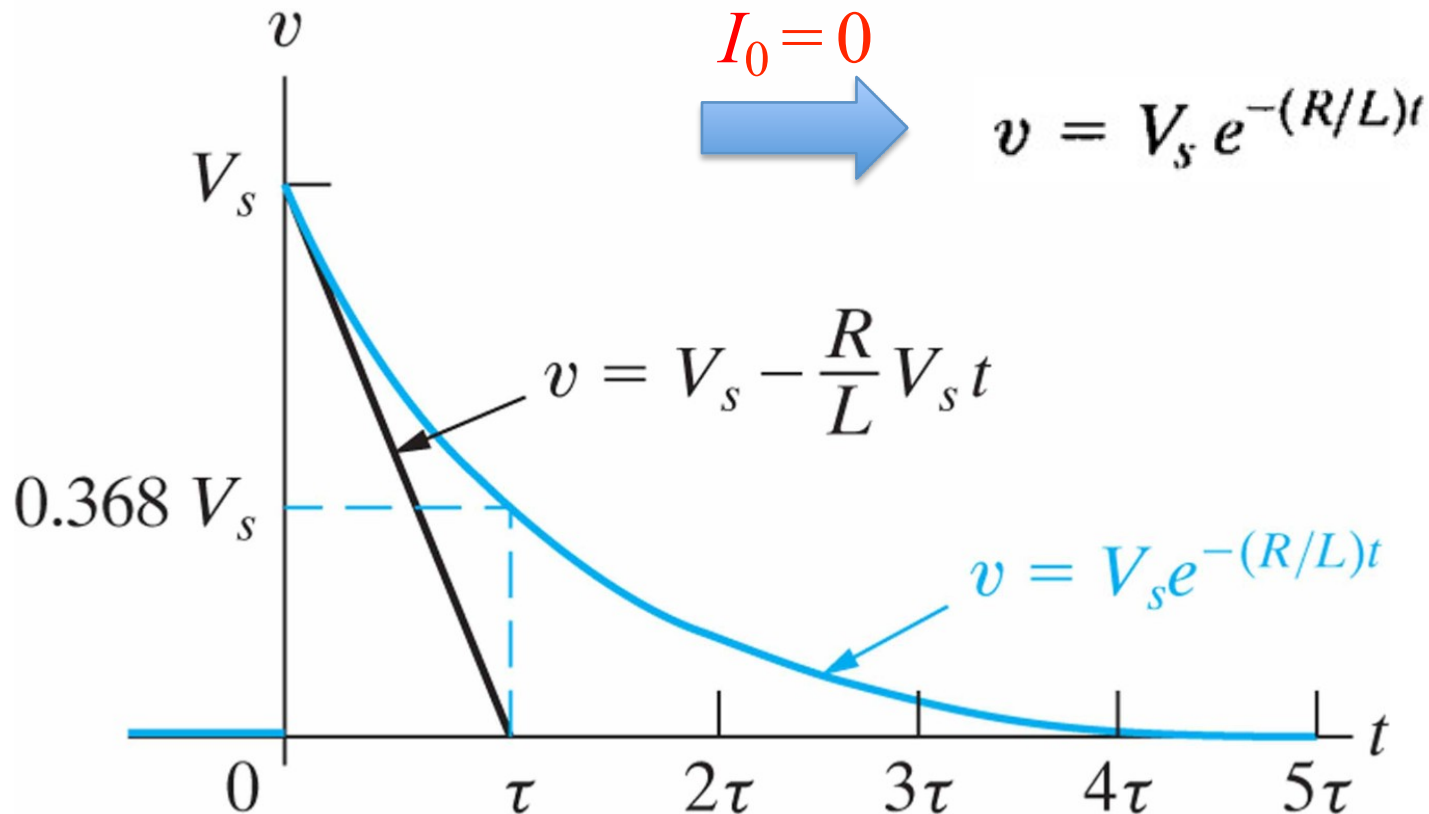


Figure 7.27: Inductor voltage versus time.

Assessment Problems 7.5

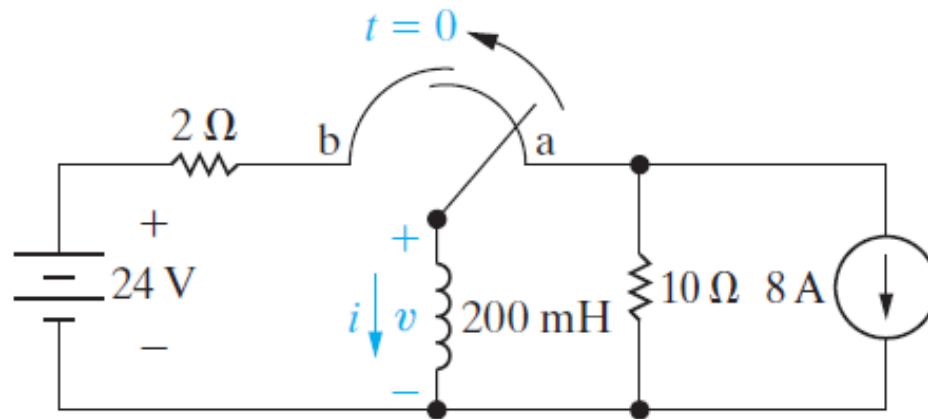

- a) Find $i(0+)$.
- b) Find $v(0+)$.
- c) What is τ ?
- d) Find $i(t)$.
- e) Find $v(t)$.

Step Response of RC Circuit

$$C \frac{dv_C}{dt} + \frac{v_C}{R} = I_s$$

↓

$$\frac{dv_C}{dt} + \frac{v_C}{RC} = \frac{I_s}{C}$$

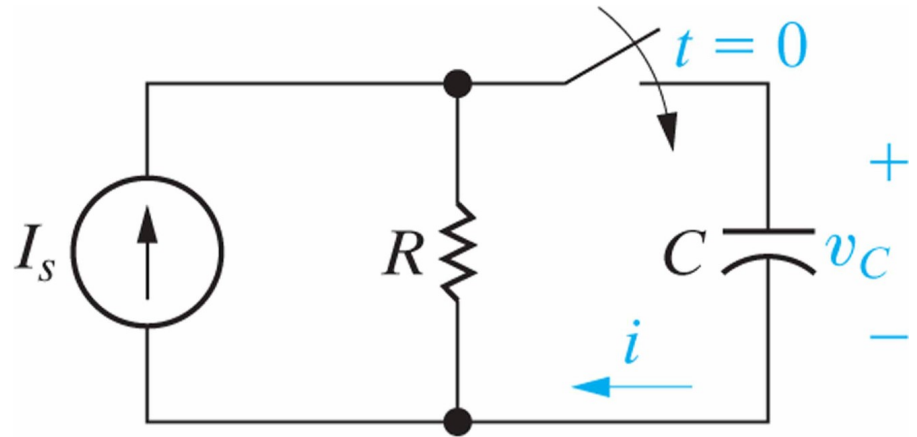


Figure 7.28: A circuit used to illustrate the step response of a first-order RC circuit.


By comparing with Eq. 7.17

→ $v_C = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0$

$$v(t) = V_f + (V_0 - V_f) e^{-t/\tau}$$

$$\frac{di}{dt} + \frac{1}{RC} i = 0 \quad \rightarrow \quad i = \left(I_s - \frac{V_0}{R} \right) e^{-t/RC}, \quad t \geq 0^+$$

Assessment Problems 7.6

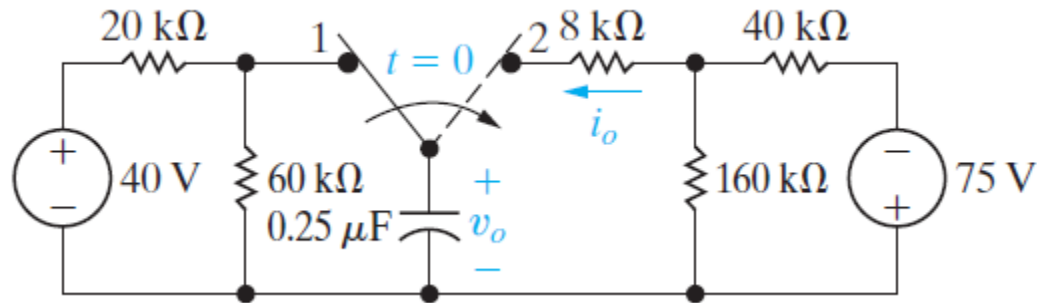

Find the expression for the voltage across the $160\text{ k}\Omega$ resistor. Call this voltage v_A , and assume that the reference polarity for the voltage is positive at the upper terminal of the $160\text{ k}\Omega$ resistor.

7.4 General Solution for Step and Natural Response





$$\frac{dx}{dt} + \frac{x}{\tau} = K \quad \Rightarrow \quad x_f = K\tau$$

$\tau = L/R$ for RL circuit
 $\tau = RC$ for RC circuit

$$\frac{dx}{dt} = \frac{-x}{\tau} + K = \frac{-(x - K\tau)}{\tau} = \frac{-(x - x_f)}{\tau}$$

$$\Rightarrow \frac{dx}{x - x_f} = \frac{-1}{\tau} dt$$
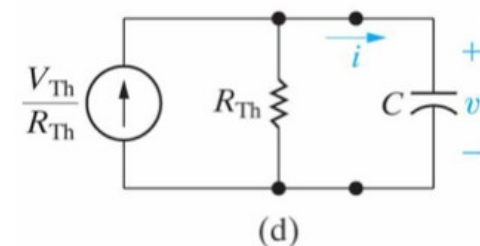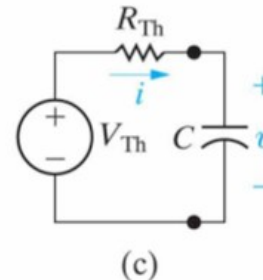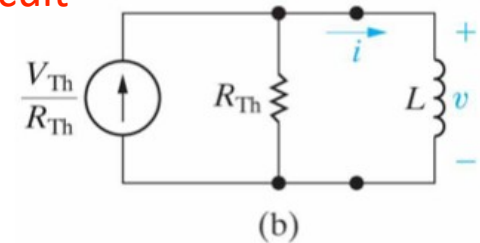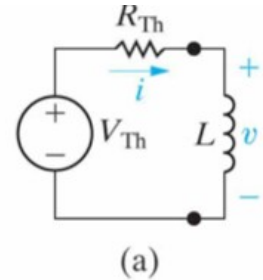
$$\int_{x(t_0)}^{x(t)} \frac{du}{u - x_f} = -\frac{1}{\tau} \int_{t_0}^t dv \quad \leftarrow$$





$$x(t) = x_f + [x(t_0) - x_f]e^{-(t-t_0)/\tau}$$


the unknown
variable as a function of time = the final
value of the
variable

$$+ \left[\begin{array}{cc} \text{the initial} & \text{the final} \\ \text{value of the} & \text{value of the} \\ \text{variable} & \text{variable} \end{array} \right] \times e^{-\frac{[t - (\text{time of switching})]}{(\text{time constant})}}$$

Helpful Notes


1. Identify the variable of interest for the circuit. For **RC circuits**, it is most convenient to choose the **capacitive voltage**; for **RL circuits**, it is best to choose the **inductive current**.
2. Determine the initial value of the variable, which is its value at t_0 . Note that if you choose capacitive voltage or inductive current as your variable of interest, it is not necessary to distinguish between $t = t_0^-$ and $t = t_0^+$. This is because **they both are continuous variables**. If you choose another variable, you need to remember that its initial value is defined at $t = t_0^+$.
3. Calculate the **final value** of the variable as $t \rightarrow \infty$.
4. Calculate the **time constant** for the circuit.

Assessment Problems 7.7

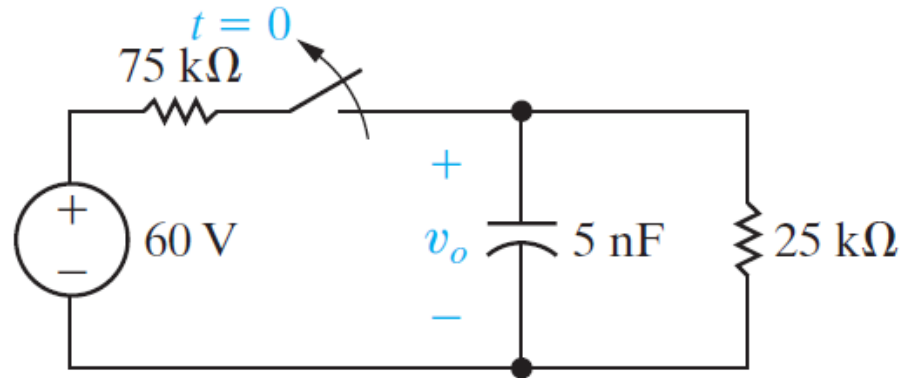

The switch in the circuit has been closed for a long time. At $t = 0$ the switch opens and stays open. Find the expression for $v_o(t)$ for $t \geq 0$.

Assessment Problems 7.8

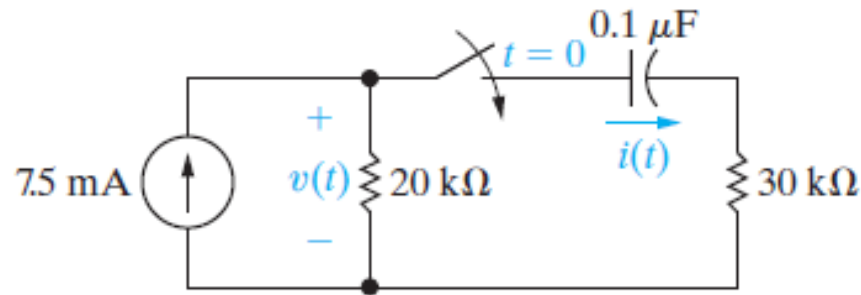


The switch in the circuit has been open for a long time. The initial charge on the capacitor is zero. At $t = 0$ the switch is closed. Find the expression for:

- a) $i(t)$ for $t \geq 0^+$ and
- b) $v(t)$ for $t \geq 0^+$.

7.5 Sequential Switching

- **Definition**: switching occurs **more than once** in a circuit.
- **Method**: derive the expressions for $v(t)$ and $i(t)$ for a given position of the switch or switches and then use these solutions to determine the initial conditions for the next position of the switch or switches.
- **Note**: anything but **inductive currents** and **capacitive voltages** can change instantaneously at the time of switching.

Assessment Problems 7.9

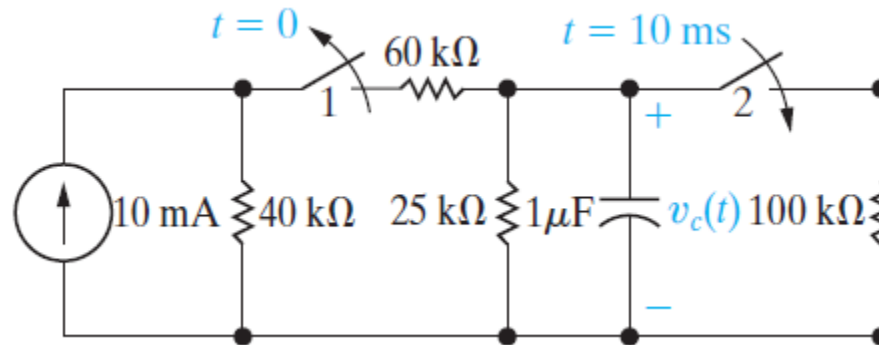


Switch 1 has been closed and switch 2 has been open for a long time. At $t = 0$, switch 1 is opened. Then, 10 ms later, switch 2 is closed. Find:

- $v_C(t)$ for $0 \leq t \leq 10$ ms,
- $v_C(t)$ for $t \geq 10$ ms,
- the total energy dissipated in the $25 \text{ k}\Omega$ resistor,
- the total energy dissipated in the $100 \text{ k}\Omega$ resistor.

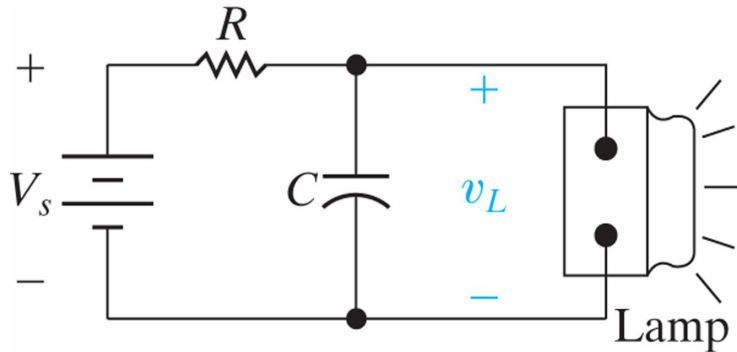7.6 Unbounded Response

- Under some conditions the circuit might grow, rather than decay, exponentially.
- This is known as **unbounded response**.
- In such circuits, the Thévenin equivalent resistance is **negative**.
- Generates a negative time constant.
- Hence, voltages and currents increase without limit.
- This ultimately leads to a breakdown of the circuit.

Practical Perspective - A Flashing Light Circuit



The lamp in this circuit starts to conduct whenever the lamp voltage reaches a value V_{\max} . During the time the lamp conducts, it can be modeled as a resistor whose resistance is R_L . The lamp will continue to conduct until the lamp voltage drops to the value V_{\min} . When the lamp is not conducting, it behaves as an open circuit.

