

# ECE 203 Circuits I

## Lecture 4

### Resistors and Ohm's Law

# **1<sup>st</sup> Circuit Element: Resistor**

Resistance: The ability of a material to resist the flow of current


Symbol: R

Units: Ohms ( $\Omega$ )


An insulator has infinite resistance

A conductor has very low resistance



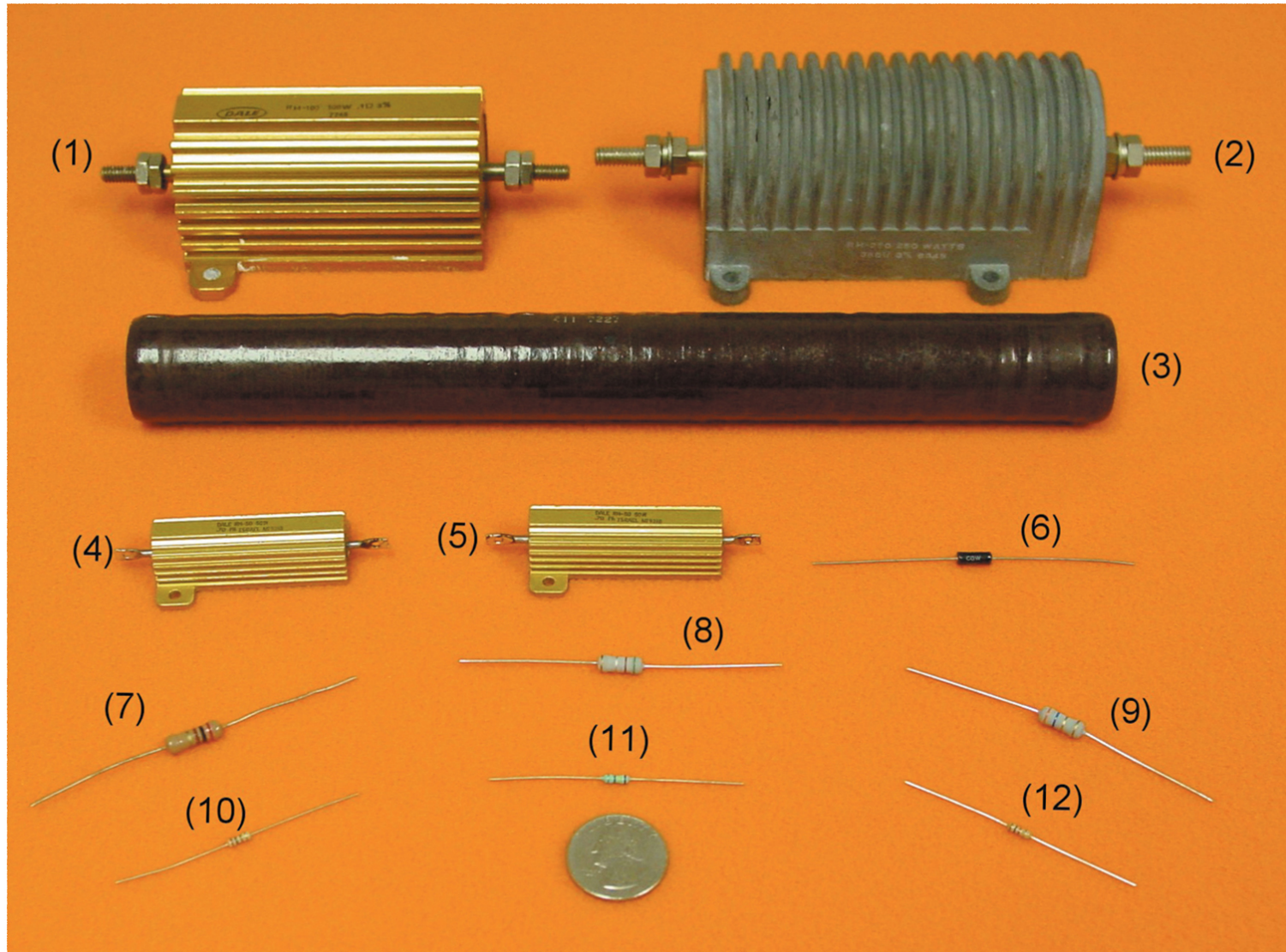

Resistors

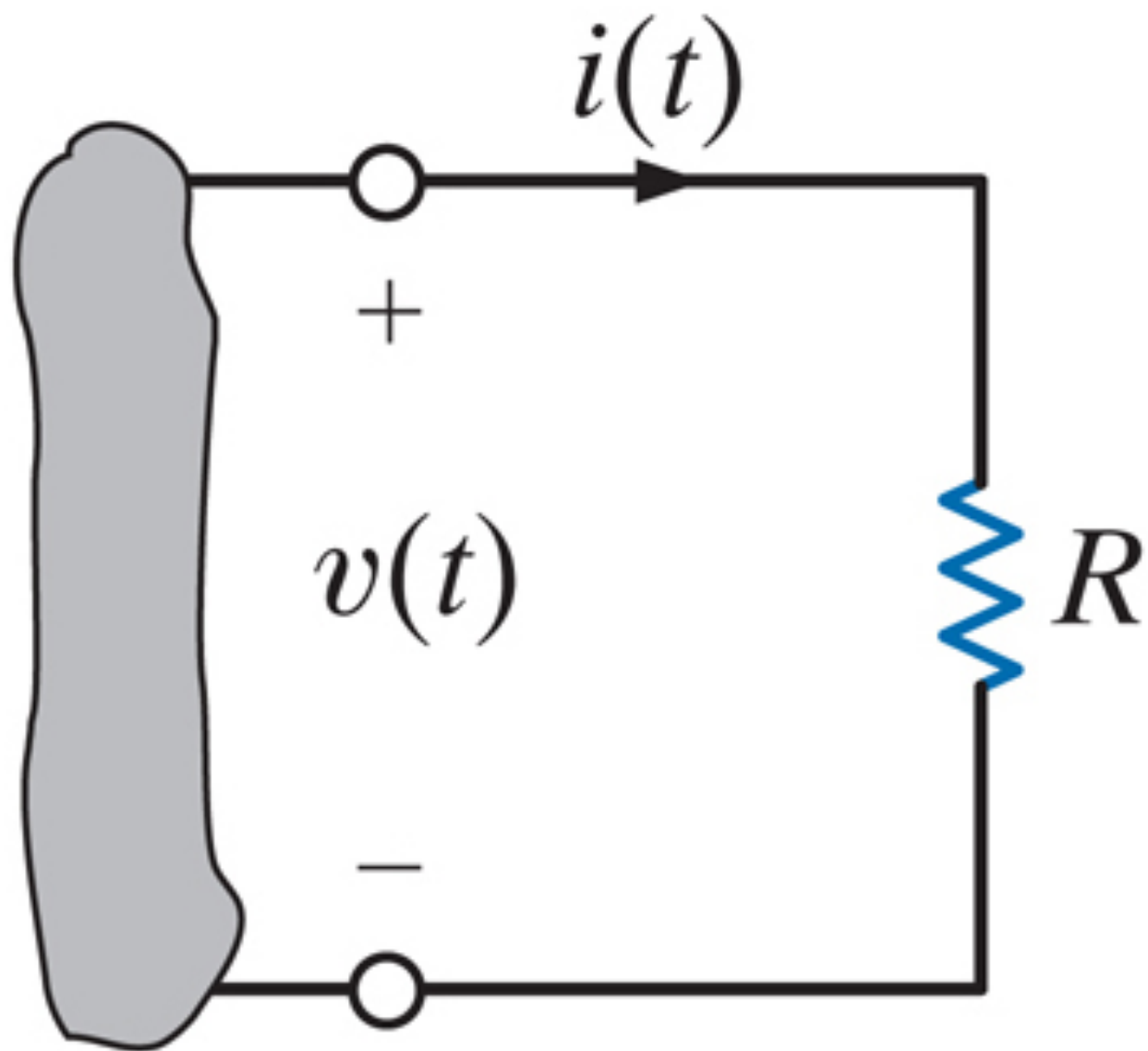


## Practical Perspective: Circuits with Realistic Resistors


Resistors are manufactured for a number of discrete values, and any resistor will vary from its stated value within some tolerance. Resistors with tighter tolerance, say 1%, are more expensive than resistors with greater tolerance, say 10%.

It is important to understand which resistor's value has the greatest impact on the expected performance of the circuit. In other words, we would like to predict the effect of varying each resistor's value on the output of the circuit.

If we know that a particular resistor must be very close to its stated value for the circuit to function correctly, we can decide to spend the extra money necessary to achieve a tighter tolerance on that particular resistor's value.

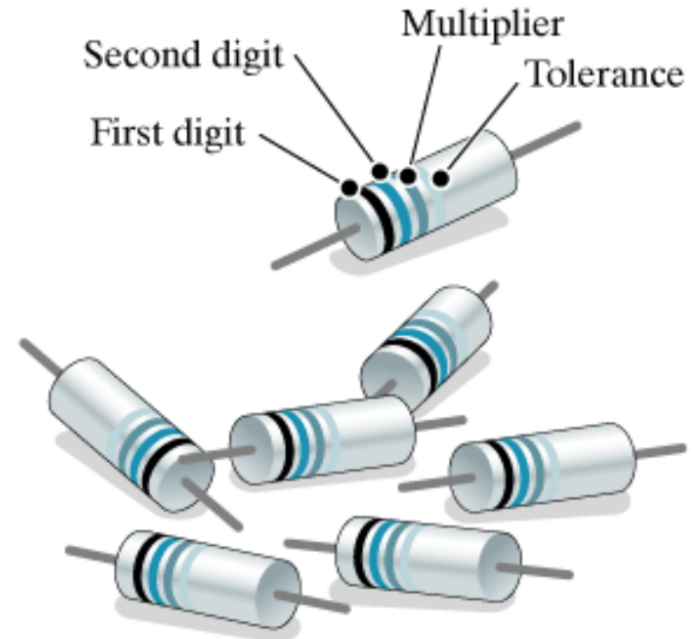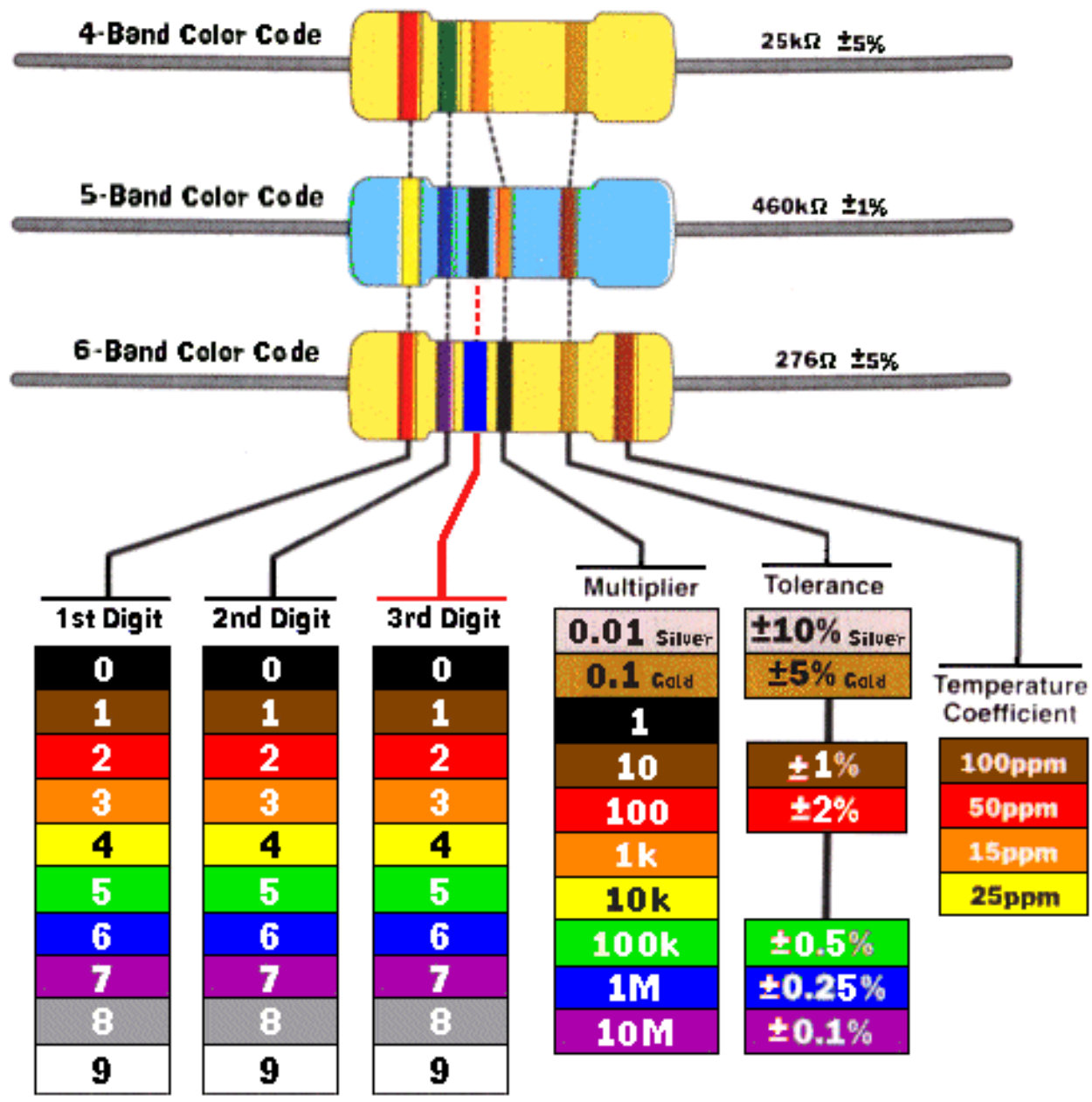Exploring the effect of a circuit component's value on the circuit's output is known as **sensitivity analysis**. We'll come back to this at the end of this chapter.

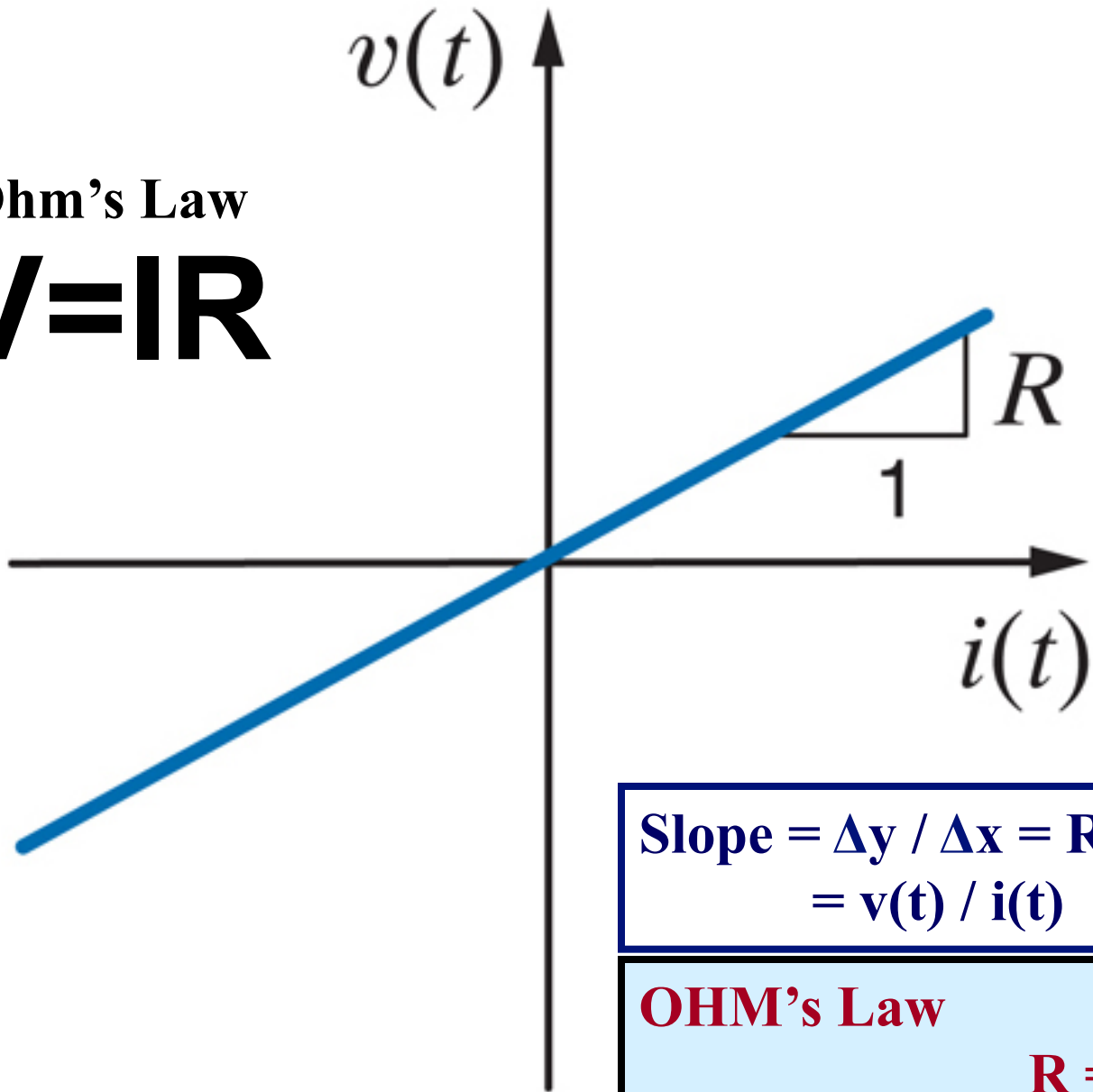




**TABLE 2.1** Standard resistor values for 5% and 10% tolerances (values available with a 10% tolerance shown in boldface)

<b>1.0</b>	<b>10</b>	<b>100</b>	<b>1.0k</b>	<b>10k</b>	<b>100k</b>	<b>1.0M</b>	<b>10M</b>
1.1	11	110	1.1k	11k	110k	<b>1.1M</b>	11M
<b>1.2</b>	<b>12</b>	<b>120</b>	<b>1.2k</b>	<b>12k</b>	<b>120k</b>	<b>1.2M</b>	<b>12M</b>
1.3	13	130	1.3k	13k	130k	1.3M	13M
<b>1.5</b>	<b>15</b>	<b>150</b>	<b>1.5k</b>	<b>15k</b>	<b>150k</b>	<b>1.5M</b>	<b>15M</b>
1.6	16	160	1.6k	16k	160k	1.6M	16M
<b>1.8</b>	<b>18</b>	<b>180</b>	<b>1.8k</b>	<b>18k</b>	<b>180k</b>	<b>1.8M</b>	<b>18M</b>
2.0	20	200	2.0k	20k	200k	2.0M	20M
<b>2.2</b>	<b>22</b>	<b>220</b>	<b>2.2k</b>	<b>22k</b>	<b>220k</b>	<b>2.2M</b>	<b>22M</b>
2.4	24	240	2.4k	24k	240k	2.4M	
<b>2.7</b>	<b>27</b>	<b>270</b>	<b>2.7k</b>	<b>27k</b>	<b>270k</b>	<b>2.7M</b>	
3.0	30	300	3.0k	30k	300k	3.0M	
<b>3.3</b>	<b>33</b>	<b>330</b>	<b>3.3k</b>	<b>33k</b>	<b>330k</b>	<b>3.3M</b>	
3.6	36	360	3.6k	36k	360k	3.6M	
<b>3.9</b>	<b>39</b>	<b>390</b>	<b>3.9k</b>	<b>39k</b>	<b>390k</b>	<b>3.9M</b>	
4.3	43	430	4.3k	43k	430k	4.3M	
<b>4.7</b>	<b>47</b>	<b>470</b>	<b>4.7k</b>	<b>47k</b>	<b>470k</b>	<b>4.7M</b>	
5.1	51	510	5.1k	51k	510k	5.1M	
<b>5.6</b>	<b>56</b>	<b>560</b>	<b>5.6k</b>	<b>56k</b>	<b>560k</b>	<b>5.6M</b>	
6.2	62	620	6.2k	62k	620k	6.2M	
<b>6.8</b>	<b>68</b>	<b>680</b>	<b>6.8k</b>	<b>68k</b>	<b>680k</b>	<b>6.8M</b>	
7.5	75	750	7.5k	75k	750k	7.5M	
<b>8.2</b>	<b>82</b>	<b>820</b>	<b>8.2k</b>	<b>82k</b>	<b>820k</b>	<b>8.2M</b>	
9.1	91	910	9.1k	91k	910k	9.1M	

Ohm's Law  
 **$V=IR$**




$$\begin{aligned}\text{Slope} &= \Delta y / \Delta x = R \\ &= v(t) / i(t)\end{aligned}$$

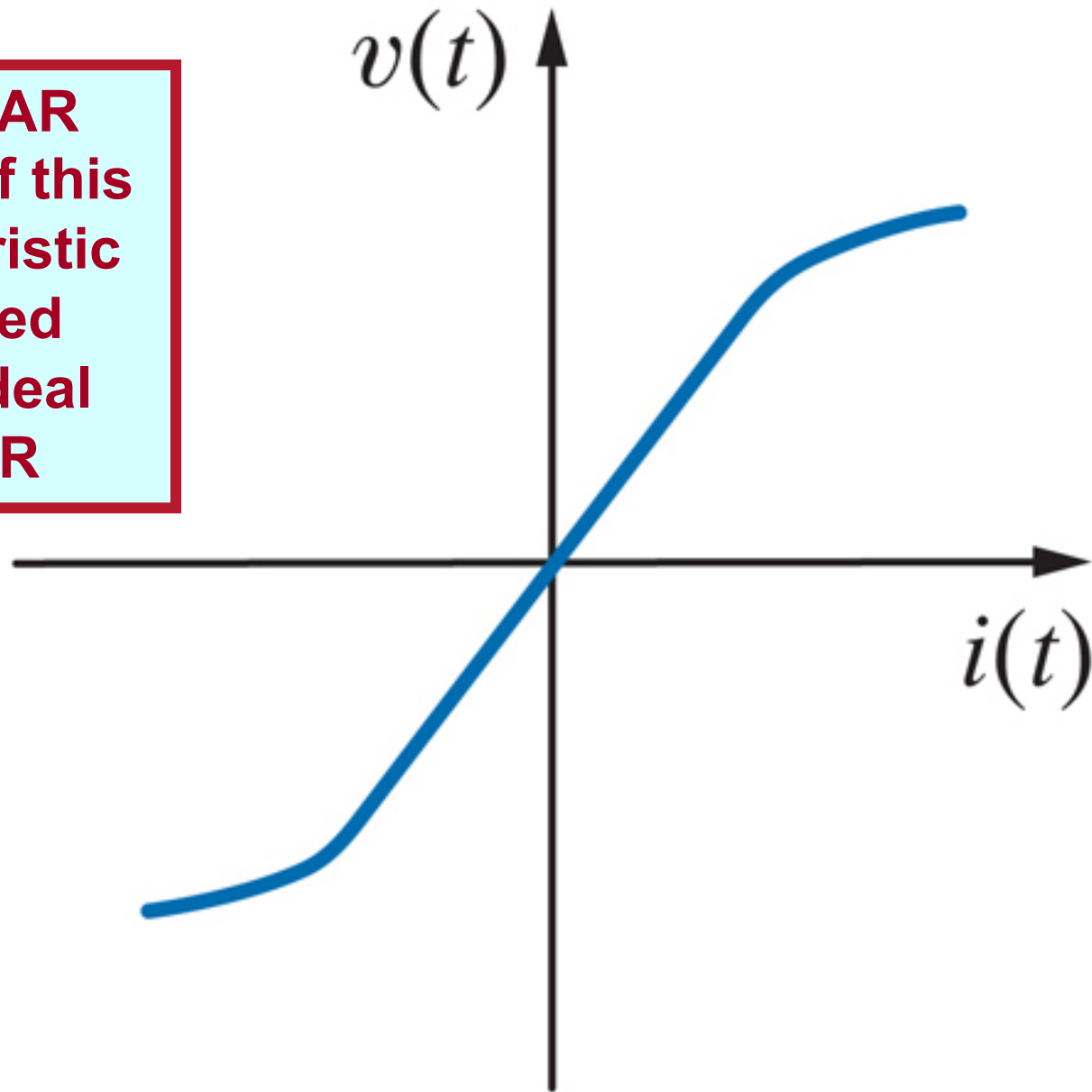**OHM's Law**

$$R = v(t) / i(t)$$



**The LINEAR  
portion of this  
characteristic  
is modelled  
with an ideal  
RESISTOR**



**Georg Simon Ohm** was a German physicist born in Erlangen, Bavaria, on March 16, 1787. As a high school teacher, Ohm started his research with the recently invented electrochemical cell, invented by Italian Count Alessandro Volta. Using equipment of his own creation, Ohm determined that the current that flows through a wire is proportional to its cross sectional area and inversely proportional to its length, or Ohm's law.

Using the results of his experiments, Georg Simon Ohm was able to define the fundamental relationship between voltage, current, and resistance. These fundamental relationships are of such great importance, that they represent the true beginning of electrical circuit analysis.


Unfortunately, when Ohm published his finding in 1827, his ideas were dismissed by his colleagues. Ohm was forced to resign from his high-school teaching position and he lived in poverty and shame until he accepted a position at Nuremberg in 1833 and although this gave him the title of professor, it was still not the university post for which he had strived all his life.


---

## **Georg Simon Ohm** (1787 – 1854)


---



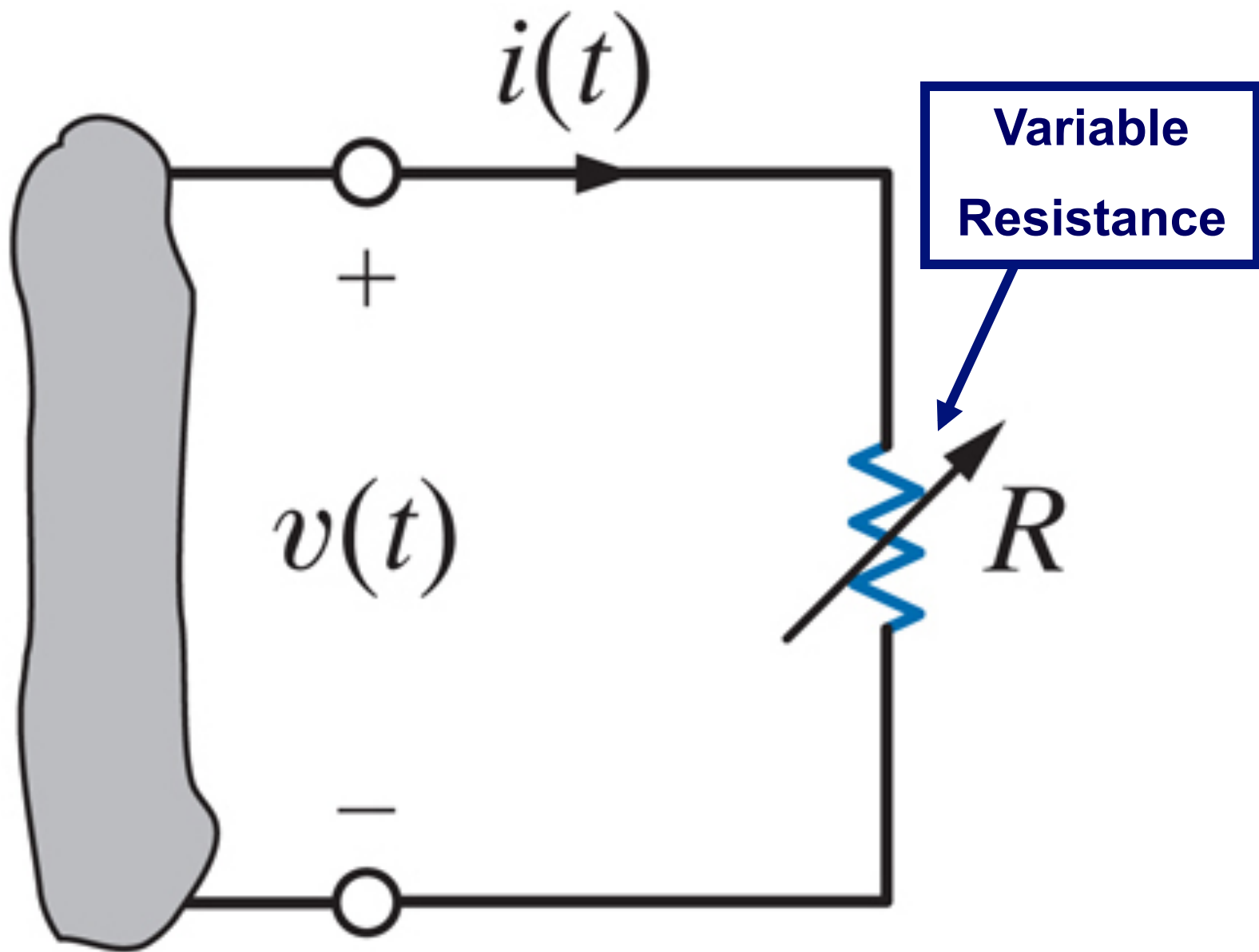

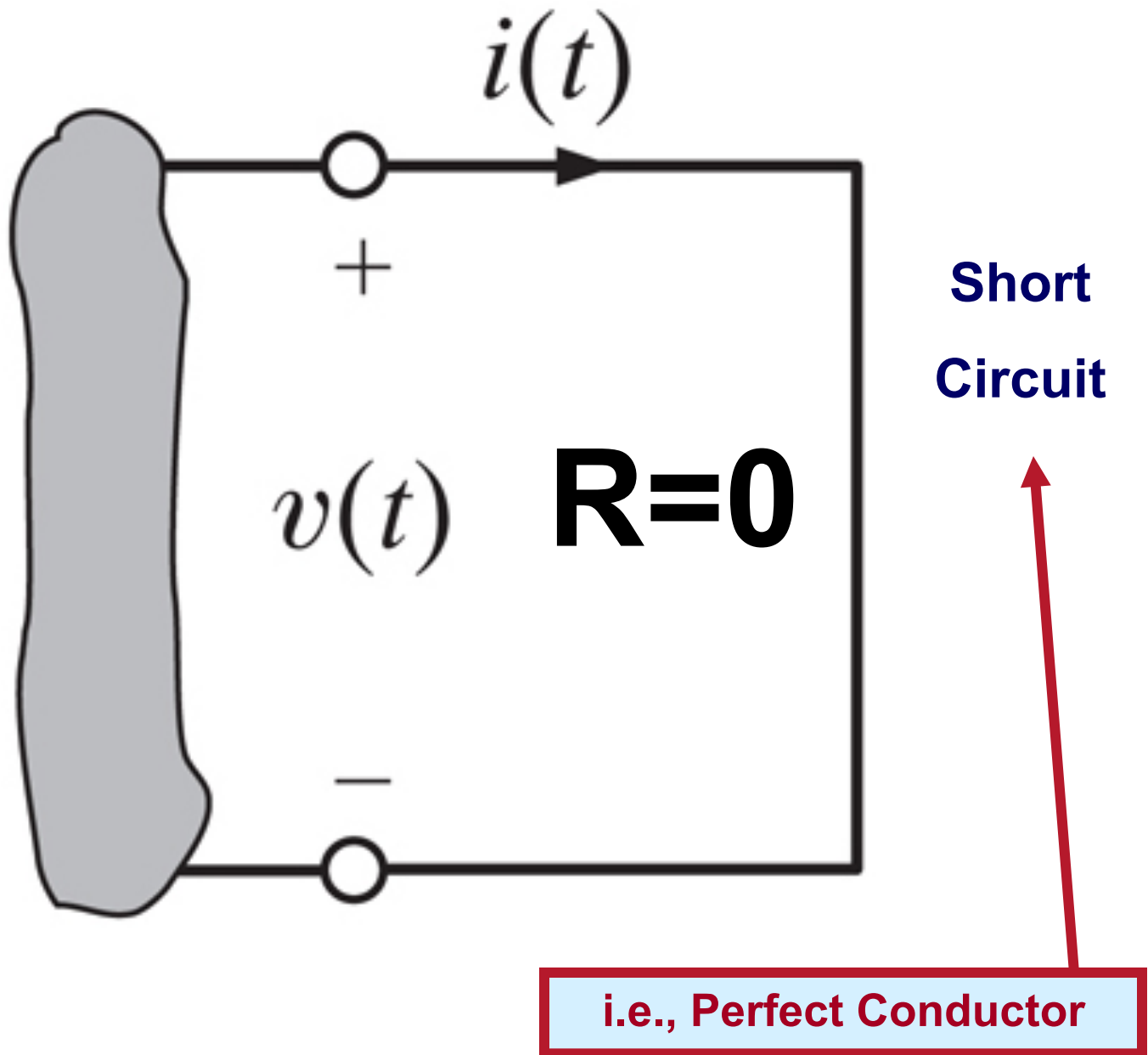



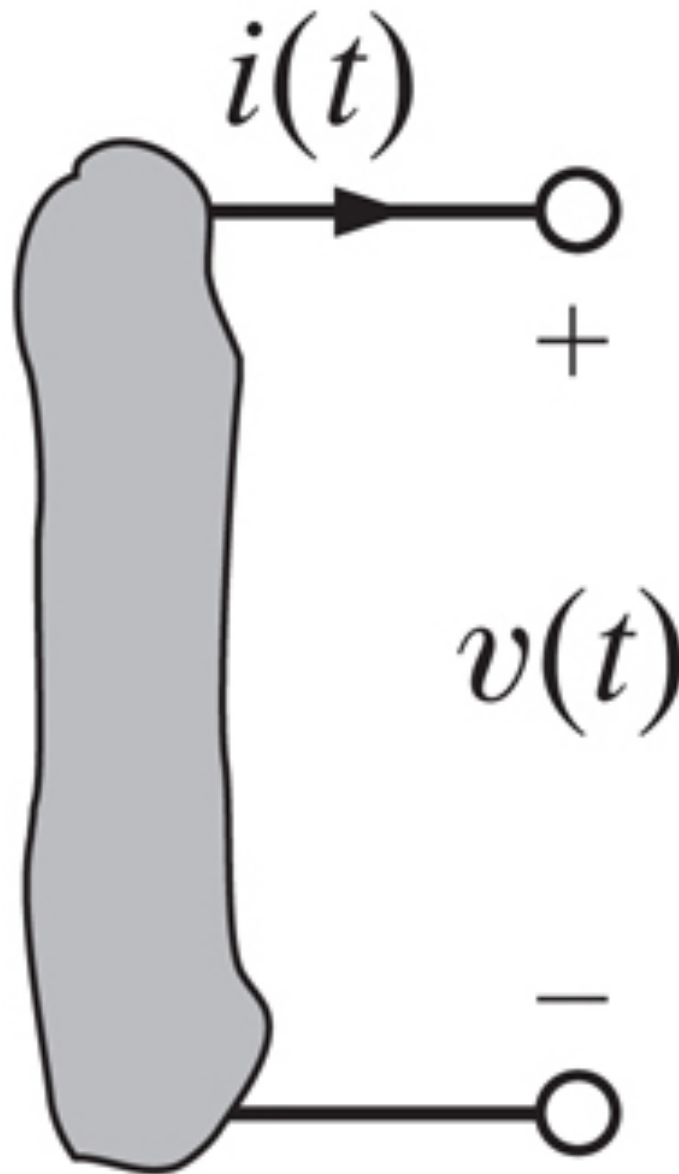

$$R = \infty$$

Open  
Circuit

# Conductance

A measure of the ability of a material to conduct current.

Notation:  $G$

$$G = 1/R$$

Unit: Siemens (S)

(Used to be Mhos  $\oslash$  or  $\Omega^{-1}$ )

# ***More Ohm's Law***


---

***Ohm's law:***  $V = IR$

***Power in resistors:***  $P = VI = RI^2 = \frac{V^2}{R}$

***Conductance (Siemens):***  $G = \frac{1}{R}$


Find  $I$

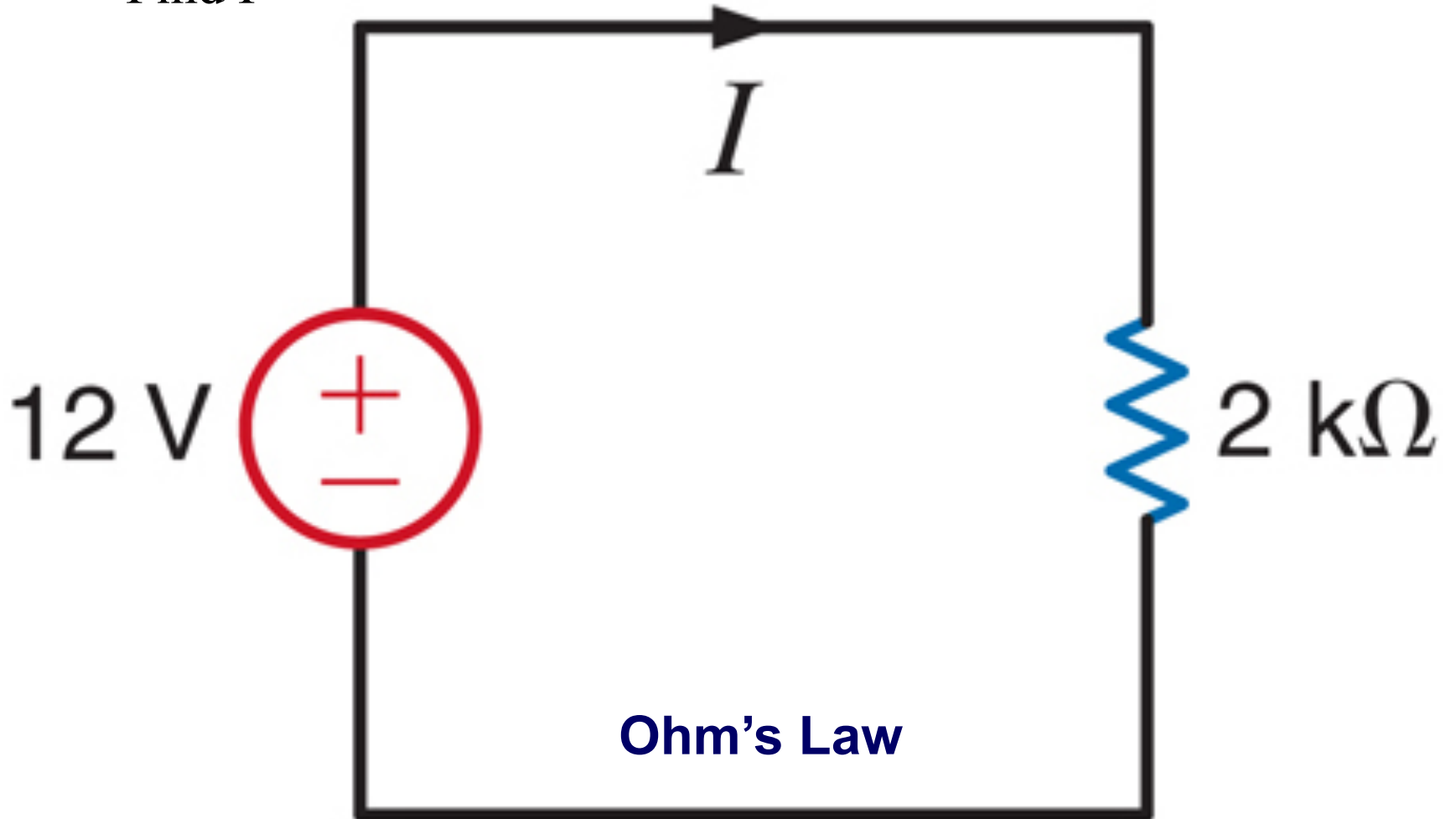

$$12\text{ volts} = I (2\text{k}\Omega) \text{ or } I = 6\text{ mA}$$



Find  $V_S$  and  $I$

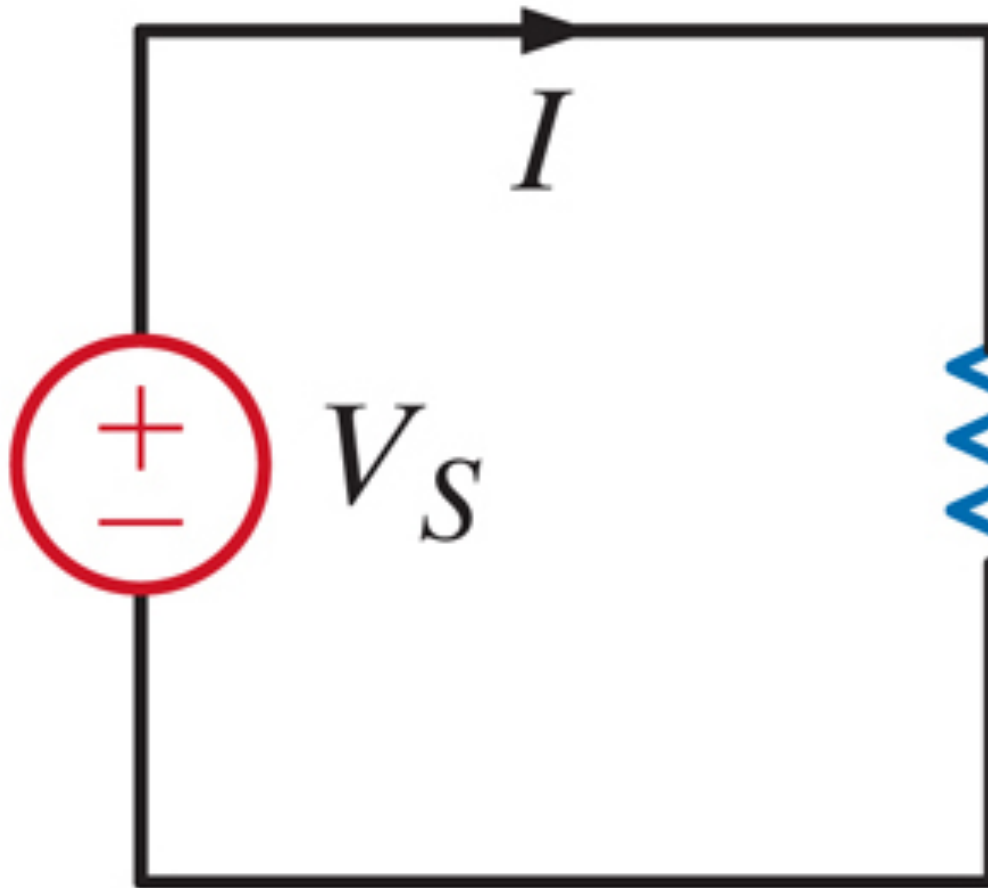

$$P = V^2 / R \text{ or}$$

$$V^2 = 3.6\text{ mW} \times 10\text{ k}\Omega$$

$$= 36 \times 10^{-0}$$

$$V = 6\text{ Volts}$$

$$10\text{ k}\Omega$$

$$P = 3.6\text{ mW}$$

$$P = I^2 R \text{ or}$$

$$I^2 = 3.6\text{ mW} / 10\text{ k}\Omega$$

$$= 0.36 \times 10^{-6}$$

$$I = 0.6\text{ mA}$$


## Ohm's Law

$$V_S = I R = I / G$$


$$= 0.5 \text{ mA} / 50 \text{ } \mu\text{S}$$

$$= 0.01 \times 10^3$$

$$= 10 \text{ Volts}$$

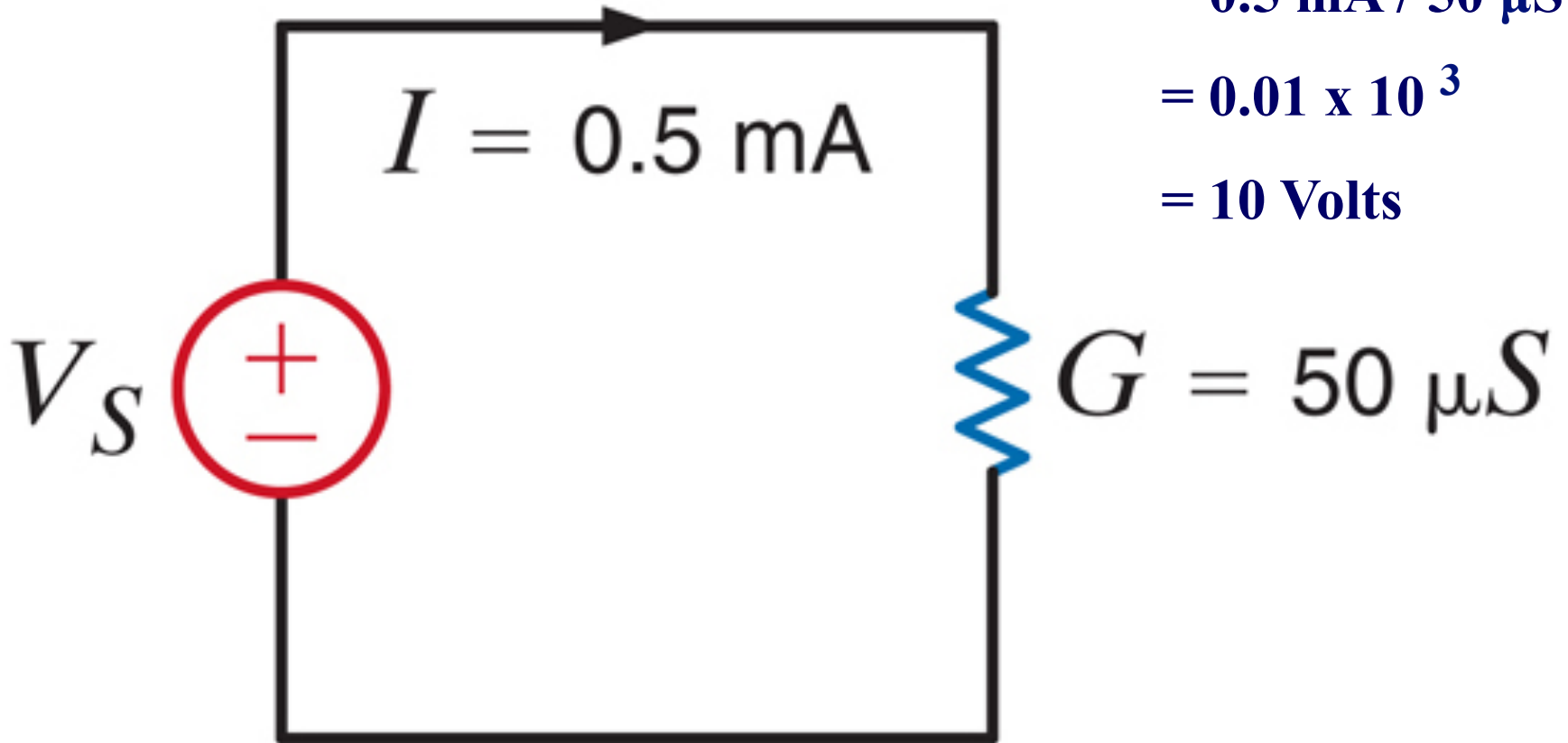

Find  $R$  and  $V_S$

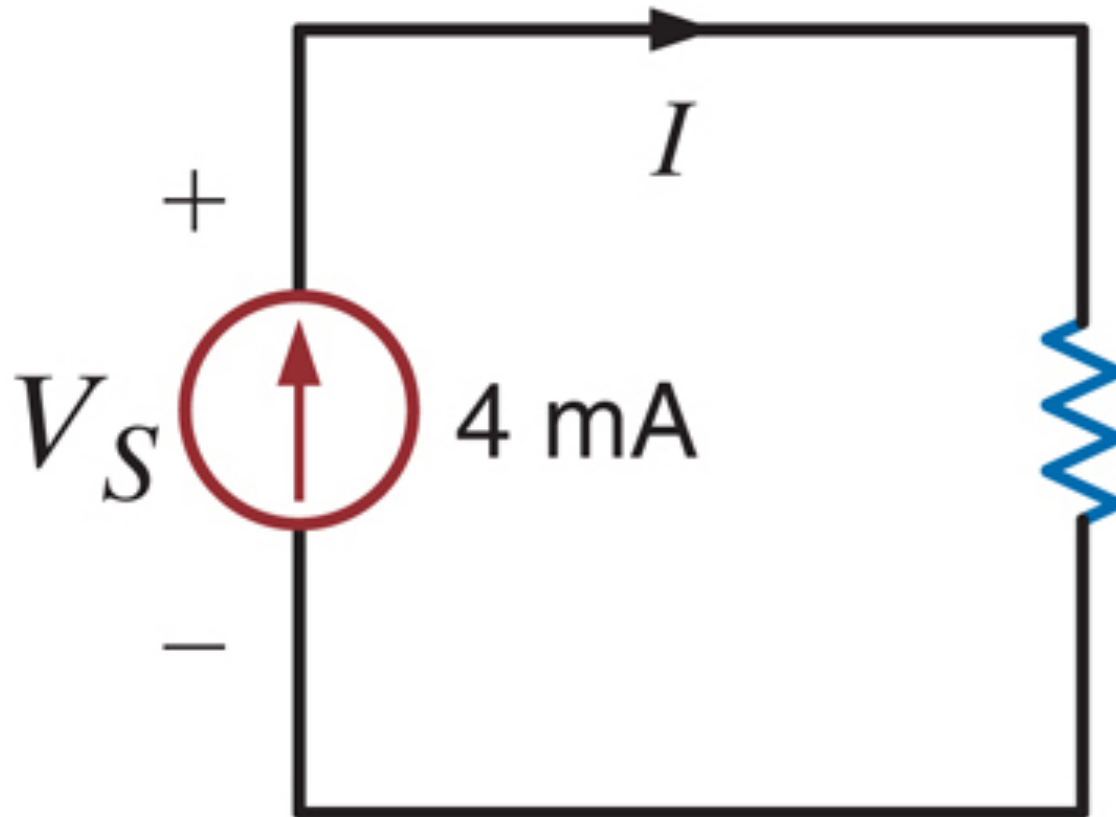

$$P = I^2 R$$

$$= (4\text{mA})^2 R$$

$$= 80 \text{ mW}$$

$$R = 80 \times 10^{-3} / 16 \times 10^{-6}$$

$$= 5 \times 10^3 = 5 \text{ k}\Omega$$

$$V_S = IR = 4\text{m} \times 5\text{k}$$

$$V_S = 20 \text{ V}$$

$$P = 80 \text{ mW}$$
$$R$$