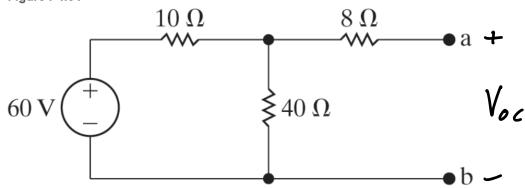



4.64 PSPICE MULTISIM Find the Thévenin equivalent with respect to the terminals a, b for the circuit in Fig. P4.64.

Figure P4.64




$$V_{oc} = \frac{40}{10+40} (60) = 48V$$
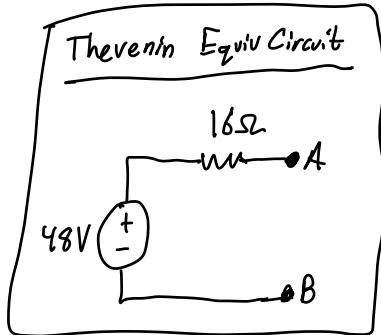
$$R_{th} = \frac{(10)(40)}{10+40} + 8 = 16\Omega$$



4.66 PSPICE MULTISIM Find the Norton equivalent with respect to the terminals a, b for the circuit in Fig. P4.66.

Figure P4.66

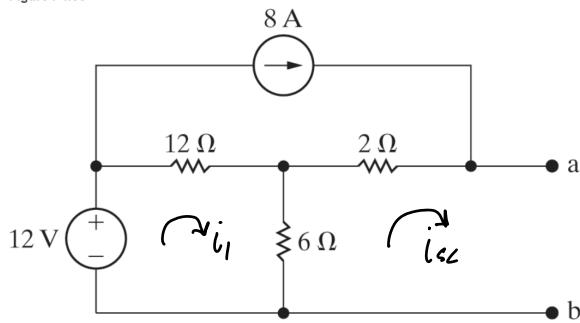

$$\textcircled{1} -12 + 12(i_1 - 8) + 6(i_1 - i_{sc}) = 0$$

$$-12 + 12i_1 - 96 + 6i_1 - 6i_{sc} = 0$$

$$18i_1 - 6i_{sc} = 108$$

$$\textcircled{2} 6(i_{sc} - i_1) + 2(i_{sc} - 8) = 0$$


$$6i_{sc} - 6i_1 + 2i_{sc} - 16 = 0$$

$$-6i_1 + 8i_{sc} = 16$$

Solve by matrix



$$\begin{bmatrix} 18 & -6 \\ -6 & 8 \end{bmatrix} \begin{bmatrix} i_1 \\ i_{sc} \end{bmatrix} = \begin{bmatrix} 108 \\ 16 \end{bmatrix} \Rightarrow \begin{array}{l} i_1 = 8.89A \\ i_{sc} = 8.67A \end{array}$$
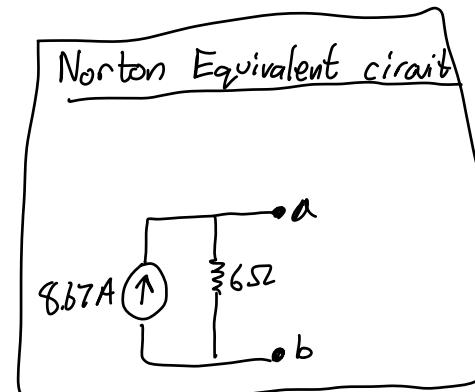
$$R_{th} = \frac{6(12)}{18} + 2 = 6\Omega$$



4.67 PSPICE MULTISIM Find the Thévenin equivalent with respect to the terminals a, b for the circuit in Fig. P4.67.

Figure P4.67

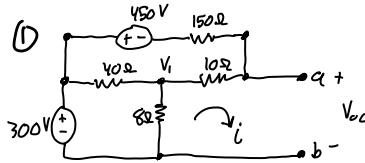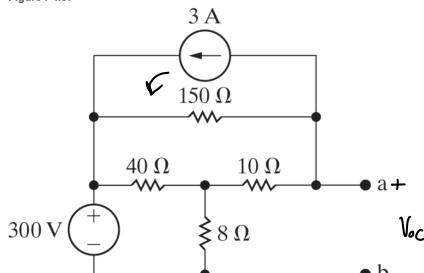

(1)

$$\frac{V_1 - 300}{40} + \frac{V_1}{8} + \frac{V_1 + (40-300)}{(150+10)} = 0$$

$$4V_1 - 1200 + 20V_1 + V_1 + 150 = 0$$

$$25V_1 = 1050$$

$$\therefore V_1 = 42V$$


$$i = \frac{V_1 + 150}{160} = \frac{42 + 150}{160}$$

$$\therefore i = 1.2A$$


$$V_1 - 10(i) - V_{oc} = 0$$

$$42 - 12 - V_{oc} = 0$$

$$V_{oc} = 30V$$

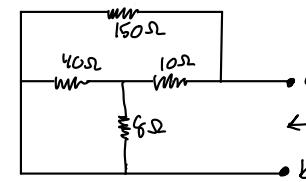


$$\frac{5(40)}{48} = 6.67\Omega$$

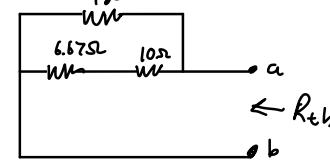

$$\frac{(6.67+10)(150)}{(6.67+10)+150} = 15\Omega$$

$$R_{th} = 15\Omega$$


Thevenin Equivalent circuit

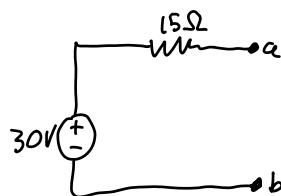

4.72 PSPICE MULTISIM A voltmeter with a resistance of 85.5 kΩ is used to measure the voltage V_{ab} in the circuit in Fig. P4.72.

- a) What is the voltmeter reading?
- b) What is the percentage of error in the voltmeter reading if the percentage of error is defined as $\frac{(\text{measured} - \text{actual})/\text{actual}}{\text{actual}} \times 100\%$?

Figure P4.72

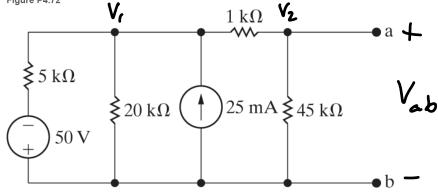

$$V_{actual} = V_2 = 54V$$

calculating error

$$\left(\frac{48.6 - 54}{54} \right) \times 100 = 10\%$$

b) The percent error in the voltmeter is 10%

$$\text{for } V_1: \frac{V_1 + 50}{5k} + \frac{V_1 - V_2}{20k} + \frac{V_1 - V_2}{1k} - 25mA = 0$$


$$V_1 \left[\frac{1}{5k} + \frac{1}{20k} + \frac{1}{1k} \right] - V_2 \left[\frac{1}{1k} \right] + \frac{50}{5k} = 25mA$$

$$V_1 (0.00125) - V_2 (0.001) = 0.015$$

$$\text{for } V_2: \frac{V_2 - V_1}{1k} + \frac{V_2}{45k} = 0$$

$$-45V_1 + 4.6V_2 = 0$$
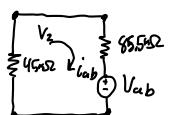
$$\text{Solve w/ matrix} \quad \begin{bmatrix} 0.00125 & -0.001 & 0.015 \\ -45 & 4.6 & 0 \end{bmatrix} \quad V_1 = 55.2V \quad V_2 = 54$$



$$i_{ab} = \frac{V_2}{4.6} = 1.2mA$$

measured

$$V_{ab} + I(85.5k\Omega) - V_2 = 0$$


$$V_{ab} = 54 - [1.2(85.5)]$$

$$V_{ab} = -48.6V$$

(a) The Voltmeter is reading
-48.6 Volts

4.75 PSPICE MULTISIM Find the Norton equivalent with respect to the terminals a, b for the circuit seen in Fig. P4.75.

Figure P4.75

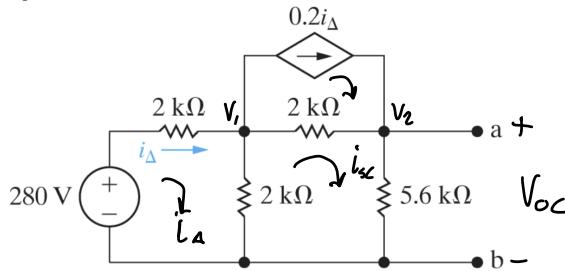

$$① \quad i_A = \frac{280 - V_1}{2k}$$

$$V_1 \left(\frac{1}{2k} \right) + i_A = \frac{280}{2k}$$

$$② \quad \frac{V_1 - 280}{2k} + \frac{V_1}{2k} + \frac{V_1 - V_2}{2k} + 0.2i_A = 0$$

$$V_1 \left(\frac{3}{2k} \right) - V_2 \left(\frac{1}{2k} \right) + 0.2i_A = \frac{280}{2k}$$

$$③ \quad \frac{V_2 - V_1}{2k} + \frac{V_2}{5.6k} - 0.2i_A = 0$$

$$-V_1 \left(\frac{1}{2k} \right) + V_2 \left(\frac{1}{2k} + \frac{1}{5.6k} \right) - 0.2i_A = 0$$

mesh current equations

$$④ \quad -280 + 2k i_A + 2k(i_A - i_{sc}) = 0$$

$$4k i_A - 2k i_{sc} = 280$$

$$⑤ \quad 2k(i_{sc} - 0.2i_A) + 2k(i_{sc} - i_A) = 0$$

$$-2.4k i_A + 4k i_{sc} = 0$$

$$\begin{bmatrix} 4k & -2k & 280 \\ -2.4k & 4k & 0 \end{bmatrix} \Rightarrow \begin{array}{l} i_A = 0.1A \\ i_{sc} = 0.06A \end{array}$$


Solving w/ matrix

$$\begin{bmatrix} 0.0005 & 0 & 1 & 1 & 0.14 \\ 0.0015 & 0.0005 & 0.2 & 1 & 0 \\ -0.0005 & 0.00068 & -0.2 & 1 & 0 \end{bmatrix} \rightarrow \begin{array}{l} V_1 = 120V \\ V_2 = 112V \\ i_A = 0.08A \end{array}$$

$$V_{oc} = V_2 = 112V$$



R_{th}
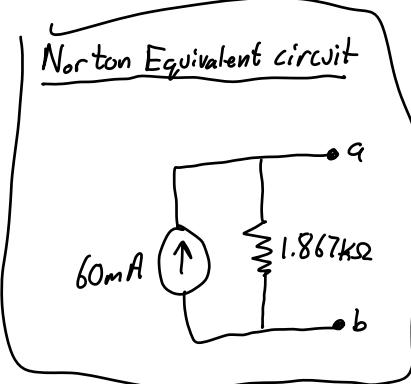
$$R_{th} = \frac{112}{0.06} = 1866.67\Omega$$



- a) Find the Thévenin equivalent with respect to the terminals a, b for the circuit in Fig. P4.78 by finding the open-circuit voltage and the short-circuit current.
- b) Solve for the Thévenin resistance by removing the independent sources. Compare your result to the Thévenin resistance found in (a).

Figure P4.78

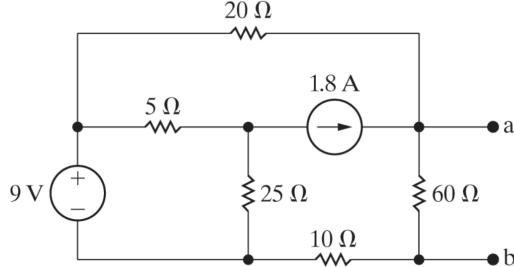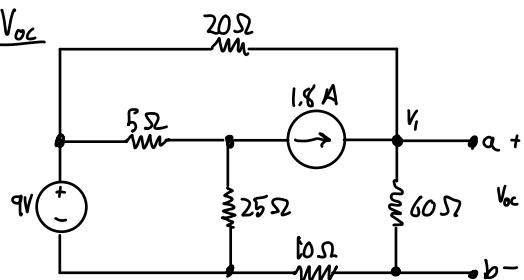a) V_{oc} 

$$\frac{V_i - 9}{20} + \frac{V_i}{60+10} - 1.8 = 0$$


$$V_i \left(\frac{1}{20} + \frac{1}{70} \right) - \frac{9}{20} - 1.8 = 0$$

$$\frac{9}{140} V_i = \frac{9}{4}$$

$$V_i = 35V$$

$$V_{oc} = \frac{60}{70} (35) = 30V$$

b)

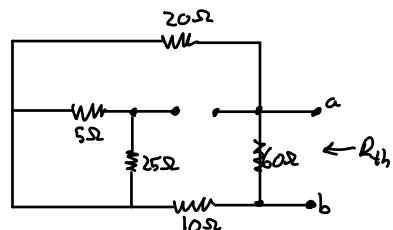


$$R_{th} = (20+10) \parallel 60$$

$$= \frac{(30)(60)}{90} = 20\Omega$$

$$R_{th} = 20\Omega$$

The Thévenin Resistances match

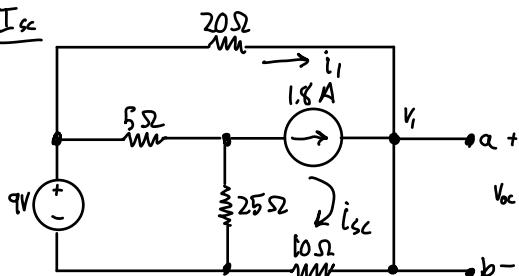 I_{sc} 

$$\frac{V_i - 9}{20} + \frac{V_i}{10} - 1.8 = 0$$

$$V_i \left(\frac{3}{20} \right) - \frac{9}{20} - 1.8 = 0$$

$$V_i = 15V$$

$$i_1 = \frac{9-15}{20} = 0.3A$$


$$i_{sc} = 1.8 - 0.3 = 1.5A$$

$$\therefore R_{th} = \frac{30}{1.5} = 20\Omega$$


4.82 PSPICE MULTISIM The variable resistor in the circuit in Fig. P4.82 is adjusted for maximum power transfer to R_o .

- Find the value of R_o .
- Find the maximum power that can be delivered to R_o .
- Find a resistor in Appendix H closest to the value in part (a). How much power is delivered to this resistor?

Figure P4.82

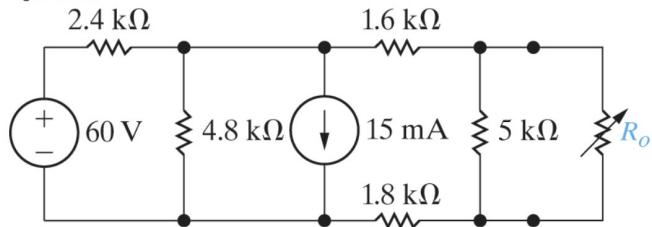


a)

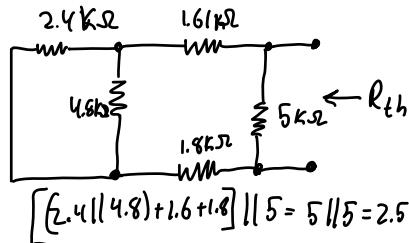

$$R_{th} = R_o = 2.5 \text{ k}\Omega$$

b)

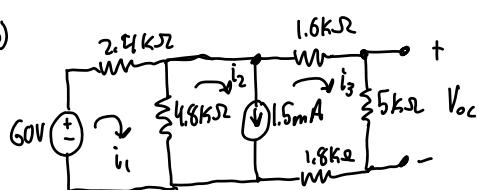

$$\textcircled{1} \quad -60 + 2.4k(i_1) + 4.8k(i_1 - i_2) = 0 \\ 7.2k i_1 - 4.8k i_2 = 60$$

$$\textcircled{2} \quad 4.8k(i_2 - i_1) + (1.6 + 1.8 + 5)k i_3 = 0 \\ -4.8k i_1 + 4.8k i_2 + 8.4k i_3 = 0$$

$$\textcircled{3} \quad i_2 - i_3 = 1.6 \text{ mA}$$

Solving w/ matrix

$$\begin{bmatrix} 7.2k & -4.8k & 0 & 60 \\ -4.8k & 4.8k & 8.4k & 0 \\ 0 & 1 & -1 & 0.015 \end{bmatrix} \Rightarrow \begin{aligned} i_1 &= 19.4 \text{ mA} \\ i_2 &= 16.6 \text{ mA} \\ i_3 &= 1.6 \text{ mA} \end{aligned}$$

$$P_{max} = i^2 R_o$$


i_3 is current across V_{oc}

$$\therefore P_{max} = (1.6 \text{ mA})^2 (2.5 \text{ k}\Omega) = 6.4 \text{ mW}$$

c)

by appendix H the closest value to my calculated value $R_o = 2.5 \text{ k}\Omega$ is $2.7 \text{ k}\Omega$
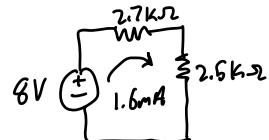
$$V_{oc} = 5 \text{ k}\Omega (1.6 \text{ mA}) = 8 \text{ V}$$







$$V_{2.7k\Omega} = \frac{2.7k}{2.7k + 2.5k} (8 \text{ V}) = 4.15 \text{ V}$$

$$P = \frac{V^2}{R} = \frac{(4.15 \text{ V})^2}{2.7k\Omega}$$

$$P_{2.7k\Omega} = 6.38 \text{ mW}$$

4.87 PSPICE MULTISIM The variable resistor (R_o) in the circuit in Fig. P4.87 is adjusted until the power dissipated in the resistor is 250 W. Find the values of R_o that satisfy this condition.

Figure P4.87

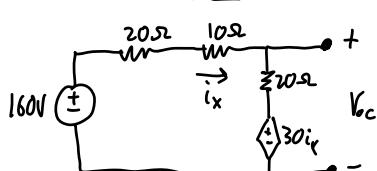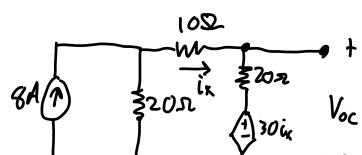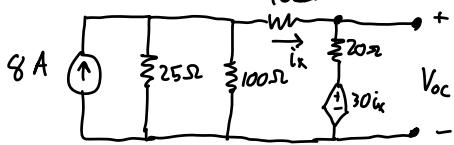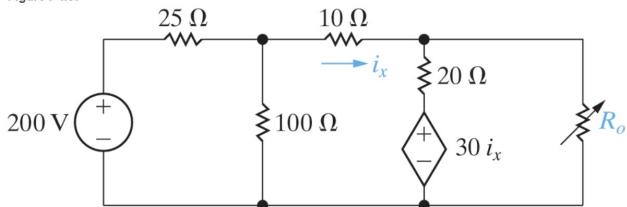


$$i_x = \frac{160 - 30i_x}{(20+10)+20}$$

$$50i_x + 30i_x = 160$$

$$i_x = 2 \text{ A}$$
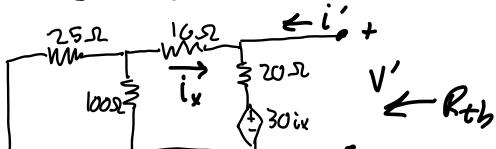
$$V_{oc} = 20(2) + 30(2) = 100 \text{ V}$$




$$i' = \frac{16}{30} + \frac{V' + V'}{20} = \frac{2V'}{60} + \frac{8V'}{60}$$

$$i' = \frac{8V'}{60} = \frac{2V'}{15}$$

$$\frac{i'}{V'} = \frac{2}{15}$$

$$R_{th} = \frac{V'}{i'} = \frac{15}{2} = 7.5 \Omega$$

Thevenin equiv circuit

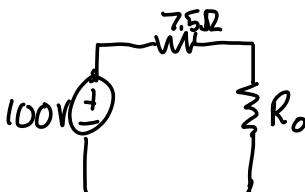

$$P = i^2 R_o = 250$$

$$P = \left(\frac{100}{7.5+R_o}\right)^2 R_o = 250$$

$$P = \frac{10000}{R_o^2 + 15R_o + 60.25} \cdot R_o = 250$$

$$\frac{10000R_o}{250} = R_o^2 + 15R_o + 60.25$$

$$40R_o = R_o^2 + 15R_o + 60.25$$

$$R_o^2 - 25R_o = -56.25 \Rightarrow R_o^2 - 25 + 56.25$$

$$R_o = \frac{+25 \pm \sqrt{(25)^2 - 4(1)(56.25)}}{2}$$

$$= \frac{25 \pm 20}{2} = 12.5 \pm 10$$

$$R_o = 22.5 \Omega \text{ or } R_o = 2.5 \Omega$$