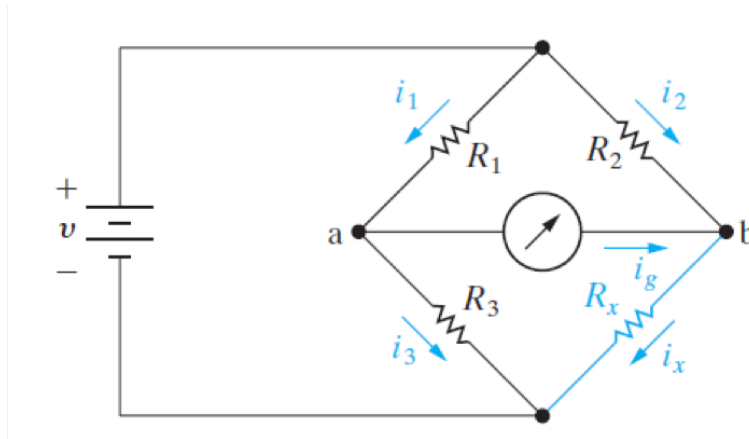


**Question 1** [6]

Consider the Wheatstone bridge circuit below with known resistors  $R_1$  and  $R_2$ . When measuring the unknown resistance  $R_x$ , one adjusts the adjustable resistor  $R_3$ , such that the bridge becomes balanced. When the bridge is balanced the current  $i_g = 0$ . Using the above



information, apply the KCL and KVL to the bridge circuit to derive the equation:

$$R_x = \frac{R_2}{R_1} R_3.$$

---

**Question 2** [2]

Consider a circuit with a power source and a resistor. If you want to measure the current flowing through the resistor how should you connect the ammeter and ideally what would its own resistance be?

**Question 3** [2]

Consider a circuit with a power source and a resistor. If you want to measure the voltage across the resistor how should you connect the voltmeter and ideally what would its own resistance be?