

P 5.2 [a] Let the value of the voltage source be v_s :

$$\frac{v_n - v_s}{10,000} + \frac{v_n - v_o}{40,000} = 0.$$

But $v_n = v_p = 0$. Therefore,

$$v_o = -\frac{40,000}{10,000}v_s = -4v_s.$$

When $v_s = -6$ V, $v_o = -4(-6) = 24$ V; saturates at $v_o = 15$ V.

When $v_s = -3.5$ V, $v_o = -4(-3.5) = 14$ V.

When $v_s = -1.25$ V, $v_o = -4(-1.25) = 5$ V.

When $v_s = 1$ V, $v_o = -4(1) = -4$ V.

When $v_s = 2.4$ V, $v_o = -4(2.4) = -9.6$ V.

When $v_s = 5.4$ V, $v_o = -4(5.4) = -21.6$ V; saturates at $v_o = -15$ V.

$$[b] \quad -4v_s = 15 \quad \text{so} \quad v_s = \frac{15}{-4} = -3.75 \text{ V};$$

$$-4v_s = -15 \quad \text{so} \quad v_s = \frac{-15}{-4} = 3.75 \text{ V}.$$

The range of source voltages that avoids saturation is
 $-3.75 \text{ V} \leq v_s \leq 3.75 \text{ V}$.

P 5.4 $\frac{v_b - v_a}{20} + \frac{v_b - v_o}{100} = 0$, therefore $v_o = 6v_b - 5v_a$.

[a] $v_a = 4 \text{ V}$, $v_b = 0 \text{ V}$, $v_o = -16 \text{ V}$ (sat).

[b] $v_a = 2 \text{ V}$, $v_b = 0 \text{ V}$, $v_o = -10 \text{ V}$.

[c] $v_a = 2 \text{ V}$, $v_b = 1 \text{ V}$, $v_o = -4 \text{ V}$.

[d] $v_a = 1 \text{ V}$, $v_b = 2 \text{ V}$, $v_o = 7 \text{ V}$.

[e] If $v_b = 1.6 \text{ V}$, $v_o = 9.6 - 5v_a = \pm 16$;

$\therefore -1.25 \leq v_a \leq 5.12 \text{ V}$.

P 5.5 [a] $i_a = \frac{240 \times 10^{-3}}{8000} = 30 \mu\text{A}$.

[b] $\frac{0 - v_a}{60,000} = i_a$ so $v_a = -60,000i_a = -1.8 \text{ V}$.

[c] $\frac{v_a}{60,000} + \frac{v_a}{40,000} + \frac{v_a - v_o}{30,000} = 0$;

$\therefore v_o = 2.25v_a = -4.05 \text{ V}$.

[d] $i_o = \frac{-v_o}{20,000} + \frac{v_a - v_o}{30,000} = 277.5 \mu\text{A}$.

P 5.6 $v_p = \frac{5000}{5000 + 10,000}(6) = 2 \text{ V} = v_n$;

$\frac{v_n + 5}{3000} + \frac{v_n - v_o}{6000} = 0$;

$2(2 + 5) + (2 - v_o) = 0$;

$v_o = 16 \text{ V}$.

$i_L = \frac{v_o}{8000} = \frac{16}{8000} = 2000 \times 10^{-6}$;

$i_L = 2 \text{ mA}$.

P 5.7 Since the current into the inverting input terminal of an ideal op-amp is zero, the voltage across the $3.3 \text{ M}\Omega$ resistor, positive on the left, is $(3.3 \times 10^6)(2.5 \times 10^{-6})$ or 8.25 V . Therefore the voltmeter reads -8.25 V .

P 5.12 [a] This circuit is an example of an inverting summing amplifier.

$$[b] \quad v_o = -\frac{220}{33}v_a - \frac{220}{22}v_b - \frac{220}{80}v_c = -8 + 15 - 11 = -4 \text{ V.}$$

$$[c] \quad v_o = -19 - 10v_b = \pm 6;$$

$$\therefore v_b = -1.3 \text{ V} \quad \text{when} \quad v_o = -6 \text{ V};$$

$$v_b = -2.5 \text{ V} \quad \text{when} \quad v_o = 6 \text{ V};$$

$$\therefore -2.5 \text{ V} \leq v_b \leq -1.3 \text{ V.}$$

$$P 5.17 \quad [a] \quad \frac{8-4}{40,000} + \frac{8-9}{22,000} + \frac{8-13}{100,000} + \frac{8}{352,000} + \frac{8-v_o}{R_f} = 0;$$

$$\frac{8-v_o}{R_f} = -2.7272 \times 10^{-5} \quad \text{so} \quad R_f = \frac{8-v_o}{-2.727 \times 10^{-5}}.$$

$$\text{For } v_o = 15 \text{ V}, \quad R_f = 256.7 \text{ k}\Omega;$$


$$\text{For } v_o = -15 \text{ V}, \quad R_f < 0 \quad \text{so this solution is not possible.}$$

$$[b] \quad i_o = -(i_f + i_{10k}) = -\left[\frac{15-8}{256.7 \times 10^3} + \frac{15}{10,000}\right] = -1527 \mu \text{ A.}$$

$$P 5.14 \quad v_o = -\left[\frac{R_f}{3000}(0.15) + \frac{R_f}{5000}(0.1) + \frac{R_f}{25,000}(0.25)\right];$$

$$-6 = -8 \times 10^{-5} R_f; \quad R_f = 75 \text{ k}\Omega; \quad \therefore 0 \leq R_f \leq 75 \text{ k}\Omega.$$

P 5.31 [a]

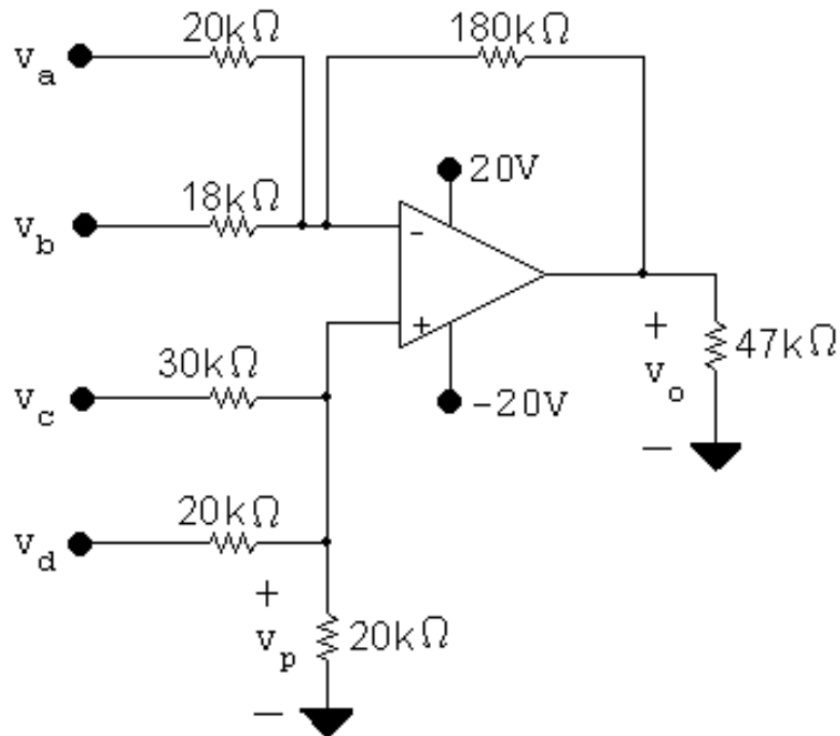

$$\frac{v_p}{20,000} + \frac{v_p - v_c}{30,000} + \frac{v_p - v_d}{20,000} = 0;$$

$$\therefore 8v_p = 2v_c + 3v_d = 8v_n.$$

$$\frac{v_n - v_a}{20,000} + \frac{v_n - v_b}{18,000} + \frac{v_n - v_o}{180,000} = 0;$$

$$\begin{aligned} \therefore v_o &= 20v_n - 9v_a - 10v_b \\ &= 20[(1/4)v_c + (3/8)v_d] - 9v_a - 10v_b \\ &= 20(0.75 + 1.5) - 9(1) - 10(2) = 16 \text{ V}. \end{aligned}$$

[b] $v_o = 5v_c + 30 - 9 - 20 = 5v_c + 1;$

$$\pm 20 = 5v_c + 1;$$

$$\therefore v_b = -4.2 \text{ V} \quad \text{and} \quad v_b = 3.8 \text{ V};$$

$$\therefore -4.2 \text{ V} \leq v_b \leq 3.8 \text{ V}.$$