

**ECE 203**

**Circuits I**

# **Maximum Power Transfer**


**Lecture 8-3**

# Maximum Power Transfer

---

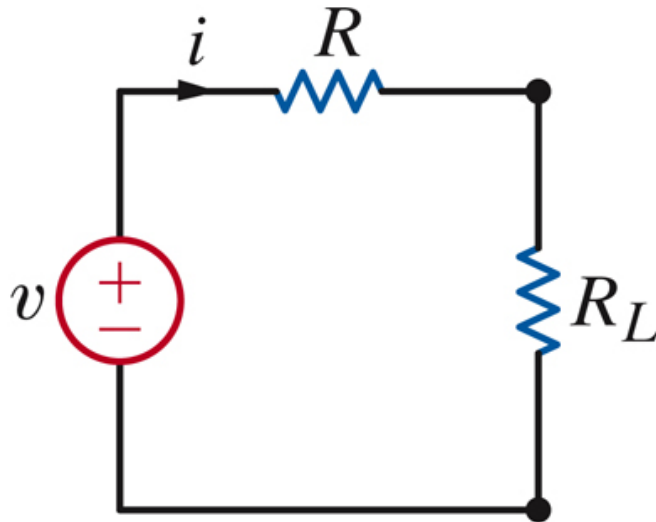**Question:** For what condition will the power transferred to the load be maximized?

**Note:**  $R$  and  $v$  can be the equivalent Thévenin circuit of any linear circuit!




$$P_{\text{load}} = i^2 R_L = \left( \frac{v}{R + R_L} \right)^2 R_L$$

# Maximum Power Transfer

---

$$P_{\text{load}} = i^2 R_L = \left( \frac{v}{R + R_L} \right)^2 R_L$$

$$\frac{dP_{\text{load}}}{dR_L} = \frac{(R + R_L)^2 v^2 - 2v^2 R_L (R + R_L)}{(R + R_L)^4} = 0$$

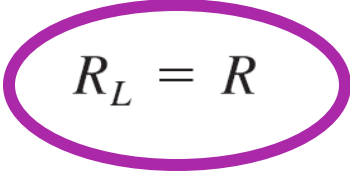
$$R_L = R$$

In other words, maximum power transfer takes place when the load resistance  $R_L = R$

Example: [Go to Example 8-3.1](#)

# Max power and Thévenin equivalent

This demonstrates an important application of the Thévenin equivalent circuit: You get maximum power transfer to a load when  $R_L = R_{Th}$

So, once you calculate  $R_{Th}$  of a circuit, you can either adjust the load to equal  $R_{Th}$ , or redesign the circuit so that  $R_{Th}$  is the same as the load your would like to drive.

# Max power example

Go to Example 8-3.2